

ECE 111 - Homework #9


Week #9: ECE 311 Circuits II - Due 11am Tuesday, November 2nd

Please submit as a Word or pdf file and email to Jacob_Glower@yahoo.com with header ECE 111 HW#9


1) Solve for Y

- $Y = \left(\frac{(7+j8)(6+j2)}{(6+j3)} \right)$
- $Y = \left(\left(\frac{9+j8}{6-j10} \right) + \left(\frac{2+j9}{5-j5} \right) \right) \left(\frac{6+j7}{9+j10} \right)$


2) Determine the impedance Z_{ab}

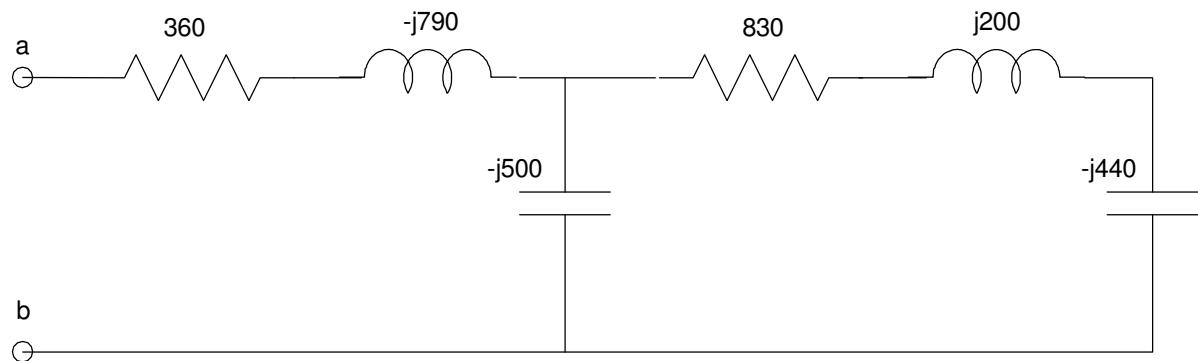

3) Determine the impedance Z_{ab}

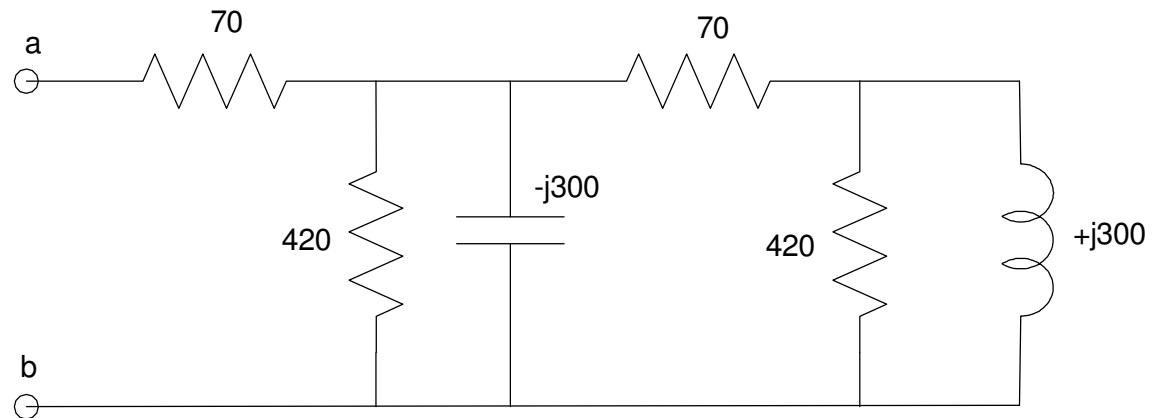

4) Assume $V_0 = 10$

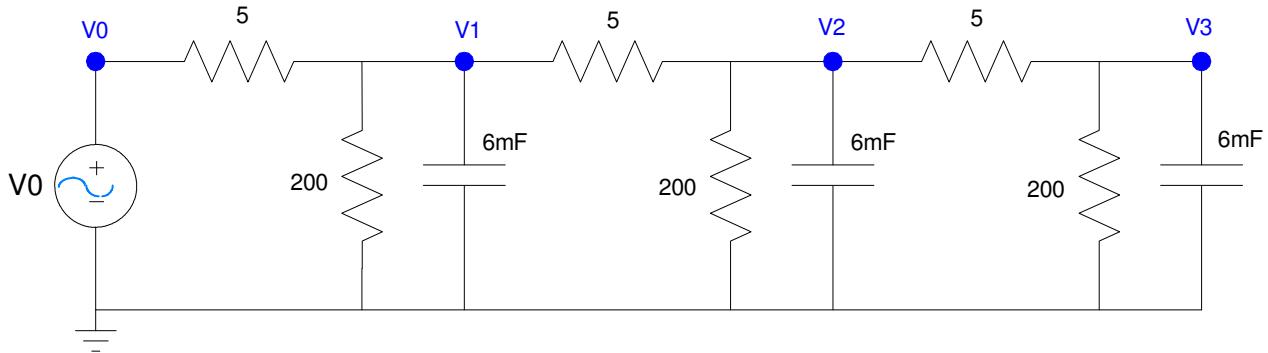

a) Determine the impedances of each element at 0 rad/sec

b) Write the voltage node equations

c) Solve for V_1 , V_2 , and V_3 .

5) Check your results in CircuitLab

6) Assume V_0 is a 10V, 3 rad/sec (0.477Hz)

$$V_0 = 10 \sin(3t)$$

a) Determine the impedances of each element at 3 rad/sec

b) Write the voltage node equations

c) Solve for V_1 , V_2 , and V_3 as complex numbers

d) Express V_1 , V_2 , and V_3 in terms of sine and cosine function:

- hint: $V_1 = a + jb$ (phasor representation) means $V_1(t) = a \cos(3t) - b \sin(3t)$

7) Check your results in CircuitLab using a transient simulation for 6 seconds