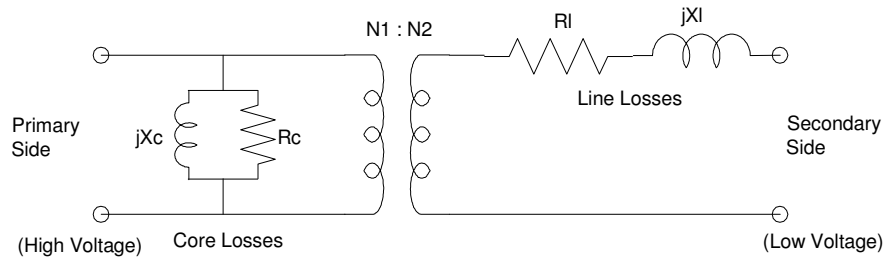


ECE 111: Homework 16

ECE 331 Energy Conversion - Due Monday, May 6th

1) Determine the circuit model for a 13.2kV : 240V transformer is tested with the following test results:



Transformer Model

| | V | Power | pf |
|--------------------|-------------|-------|------|
| Open-Circuit Test | V1 = 13.2kV | 60 W | 0.02 |
| Short-Circuit Test | V2 = 40V | 15 W | 0.99 |

For the utility grid on the back of the page....

- 2) Convert the voltages and impedances to the 120V node (right side)
- 3) Write the voltage node equations for this circuit (with transformers removed)
- 4) Determine the voltages at each node
- 5) Determine the efficiency of this system
 - Ignoring the core losses
 - Assumes a large number of customers share these losses
 - Including the core losses
 - Assumes a single customer

