

Voltage Nodes

Write the voltage node equations for the following circuits

