

SuperNodes

Write the voltage node equations for the following circuits



