

# Inductors

Determine the differential equations which describe the following RL circuit

