

Mutual Inductance

Determine the impedances and resistances as seen by the 20 Ω load to the right

Write the voltage node equations for V1, V2, and V3

