


EE 206: Homework #5

Thevenin Equivalents, Maximum Power Transfer. Due Monday, October 5th


Please make the subject "EE 206 HW#5" if submitting homework electronically to lauren.n.singelmann@ndsu.edu (or on blackboard)

Thevenin Equivalents

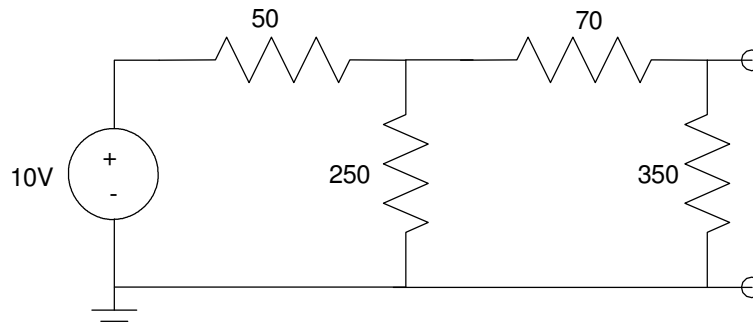
1) Find the Thevenin equivalent for the following circuit by transforming between Thevenin and Norton equivalents:



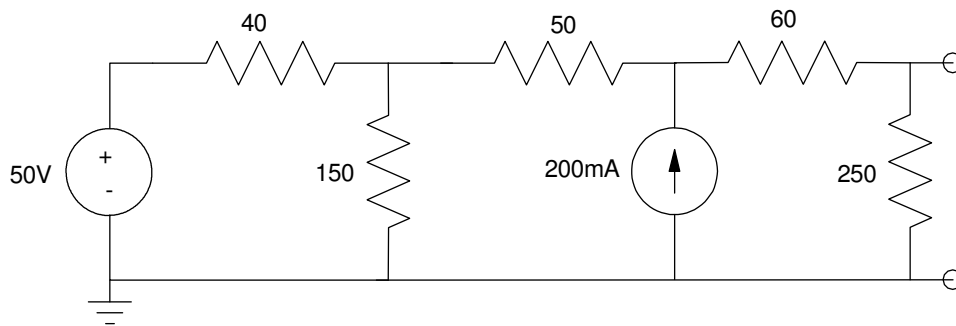
2) Find the Thevenin equivalent for the following circuit by transforming between Thevenin and Norton equivalents:



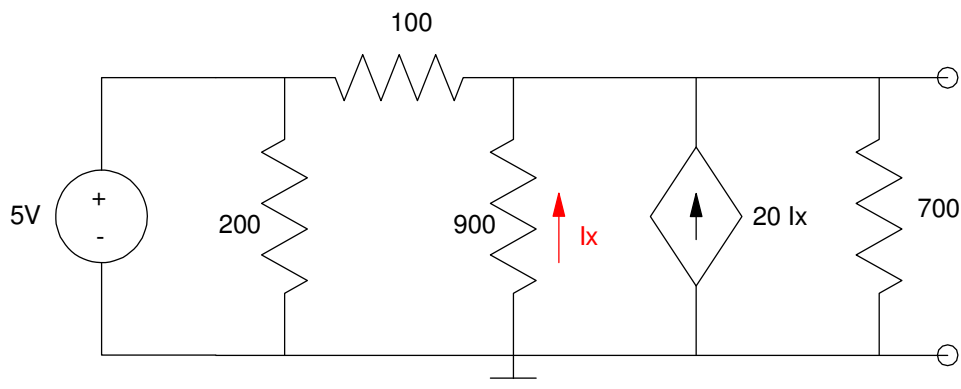3) Find the Thevenin equivalent for the following circuit:




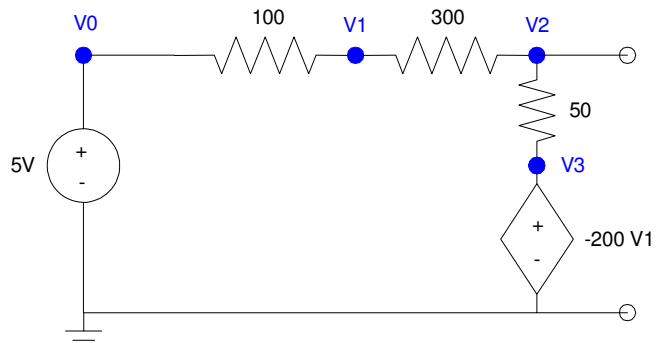4) Find the Thevenin equivalent for the following circuit:



Maximum Power Transfer

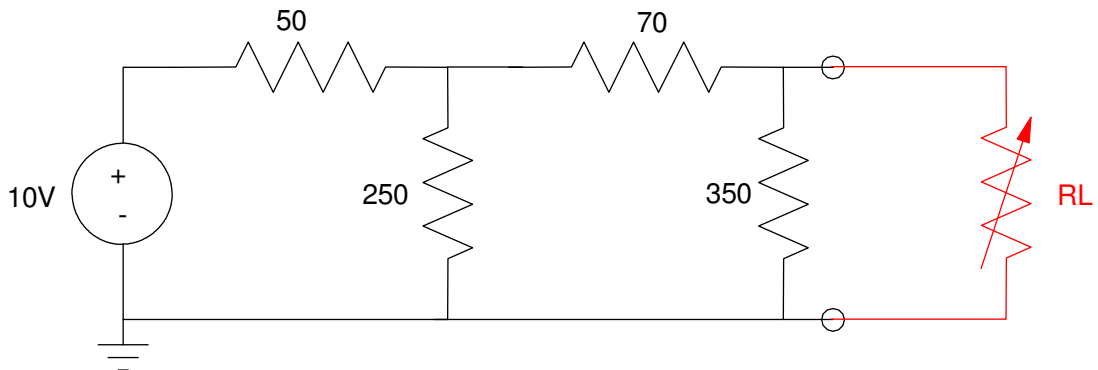5) Determine R_L so that the maximum power is delivered to the load (R_L)




CircuitLab

6) Simulate the circuit of problem 5. Determine the voltage and current at the load for

	V	I	Power
R = 0			
R = 10			
R = max power			
R = 50			
R = 100			
R = infinite			

Superposition

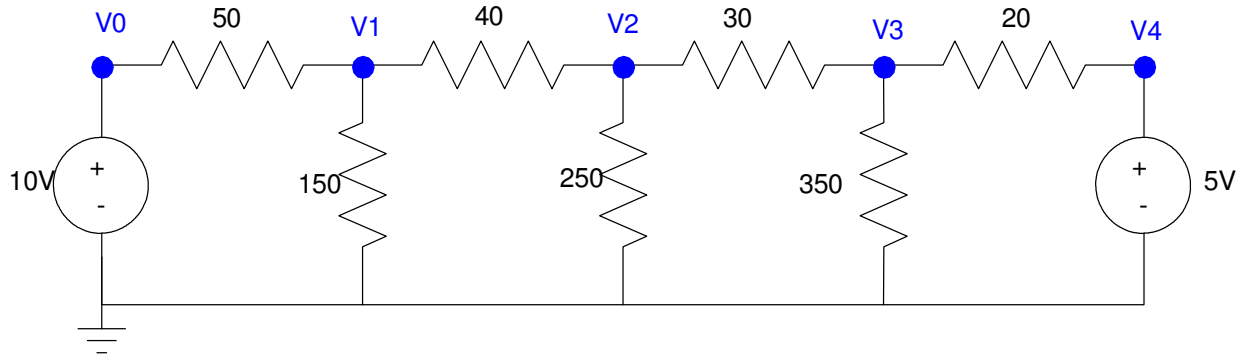- 7) Use Circuitlab to determine the voltage at Y assuming $V_a = 10V$, $V_b = 0V$.
- 8) Use Circuitlab to determine the voltage at Y assuming $V_a = 0V$, $V_b = 5V$.
- 9) Use Circuitlab to determine the voltage at Y assuming $V_1 = 10V$, $V_b = 5V$



Does problem 7 + problem 8 = problem 9?

	V_a	V_1	V_2	V_3	V_b
$V_a = 10V$ $V_b = 0V$	10.00 V				0.00 V
$V_a = 0V$ $V_b = 5V$	0.00 V				5.00 V
$V_a = 10V$ $V_b = 5V$	10.00 V				5.00 V