

EE 206: Homework #11

Superposition with Phasors. Due Monday, November 23rd

Please make the subject "EE 206 HW#11" if submitting homework electronically to lauren.n.singelmann@ndsu.edu (or on blackboard)

Problem 1) Assume V_{in} is a 0V / 10V square wave at 500 rad/sec.

$$V_{in} = \begin{cases} 10V & \sin(500t) > 0 \\ 0V & \text{otherwise} \end{cases}$$

Determine V1 using CircuitLab

- DC value (average)
- AC value (peak-to-peak)


Problem 2) Assume V_{in} is

$$V_{in} \approx 5 + 5 \cos(500t)$$

Determine $V_1(t)$ using phasor analysis and superposition.

- How does your answer for problem #2 compare to the simulation results for problem #1?

note: this is similar to problem #1. This V_{in} has the same DC value, the same V_{pp} , and the same frequency as problem #1

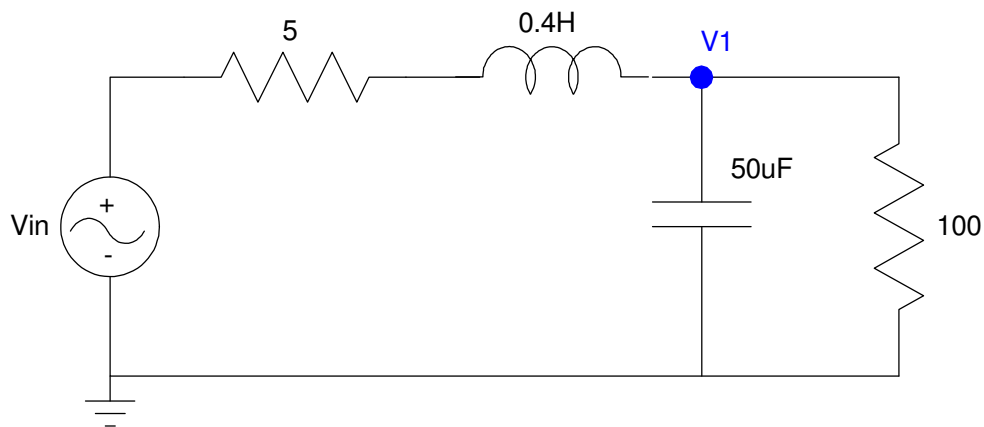

Problem 1-2

Problem 3) Assume V_{in} is a 0V / 10V square wave at 500 rad/sec.

$$V_{in} = \begin{cases} 10V & \sin(500t) > 0 \\ 0V & \text{otherwise} \end{cases}$$

Determine V_1 using CircuitLab


- DC value (average)
- AC value (peak-to-peak)

Problem 4) Assume V_{in} is

$$V_{in} \approx 5 + 5 \cos(500t)$$

Determine $V_1(t)$ using phasor analysis and superposition.

- How does your answer for problem #4 compare to the simulation results for problem #3?

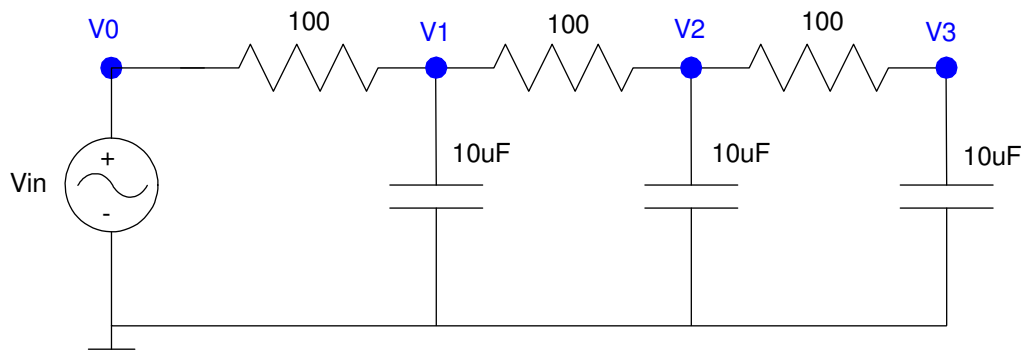

Problem 3 - 4

Fourier Transform

Problem 5) Let

$$x(t) = 7 \sin(t)$$

Let $y(t)$ be $x(t)$, clipped at $\pm 5V$

$$y(t) = \begin{cases} +5 & x(t) > +5 \\ x(t) & -5 < x(t) < +5 \\ -5 & x(t) < -5 \end{cases}$$

Find the Fourier Transform for $x(t)$ and out to its 3rd harmonic

$$x(t) \approx a_0 + a_1 \cos(t) + b_1 \sin(t) + a_2 \cos(2t) + b_2 \sin(2t) + a_3 \cos(3t) + b_3 \sin(3t)$$

$$y(t) \approx a_0 + a_1 \cos(t) + b_1 \sin(t) + a_2 \cos(2t) + b_2 \sin(2t) + a_3 \cos(3t) + b_3 \sin(3t)$$