
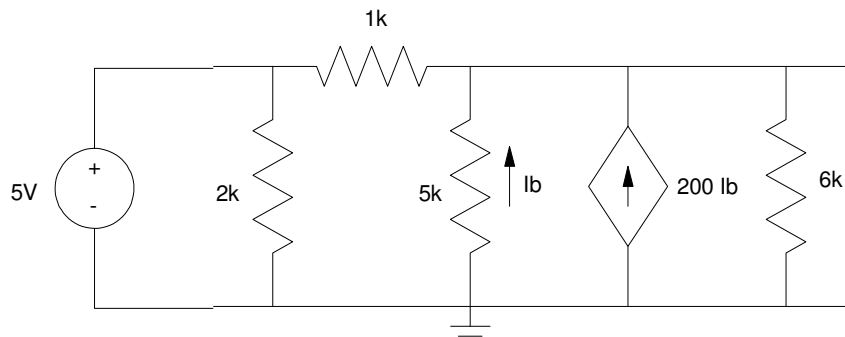
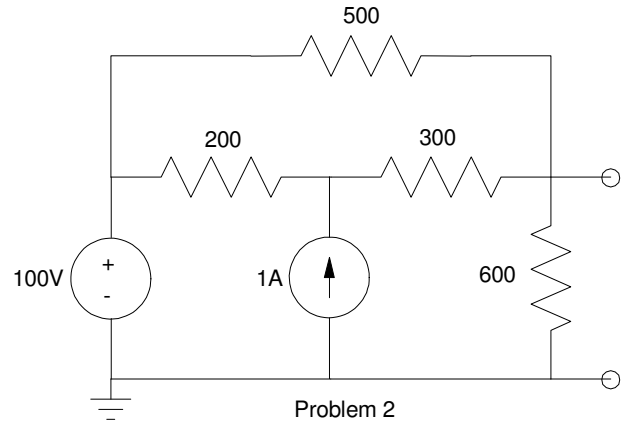



Thevenin Equivalents (Harder problems)

EE 206 Practice Problems


Find the Thevenin equivalent for the following circuits

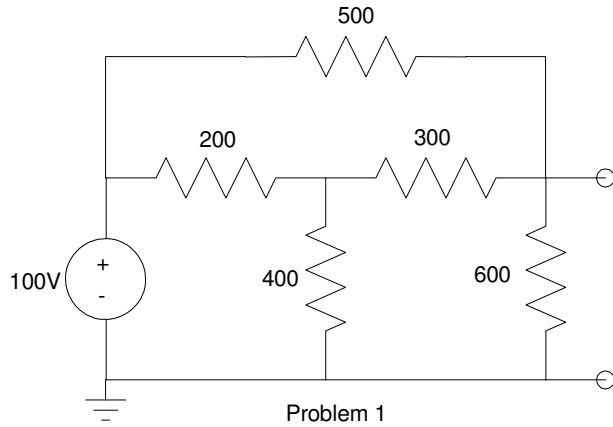


Problem 3: Assume V_{in} is connected to a +1.00V source

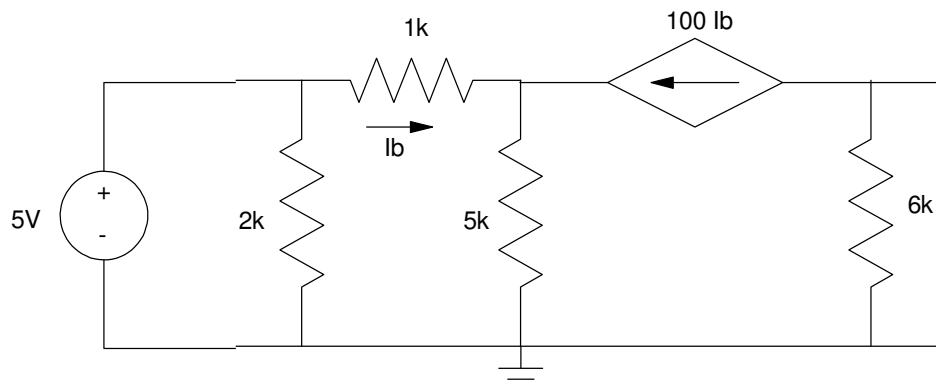

Problem 4: Assume V_{in} is connected to a +1.00V source

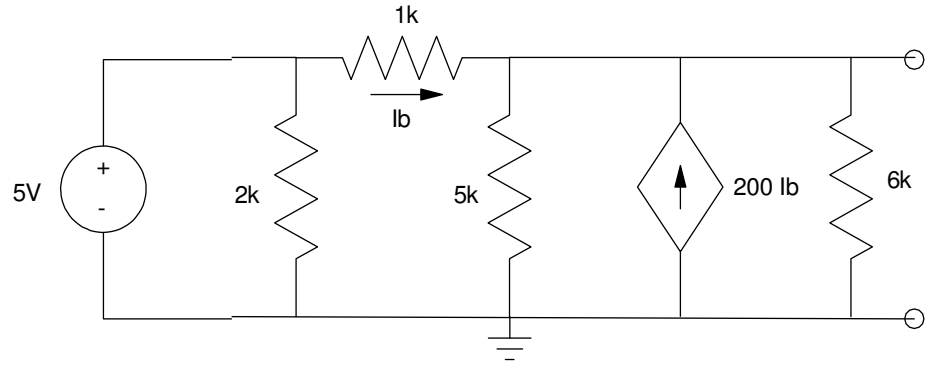


Problem 5: Assume V_{in} is connected to a +1.00V source

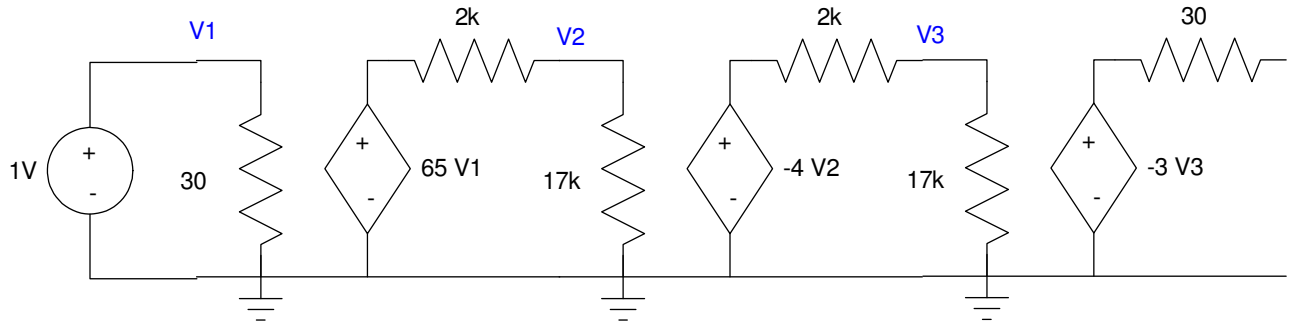

Problem 6

Solution - Problem 1:

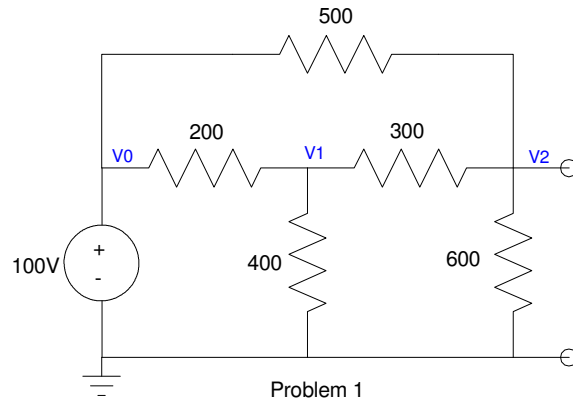

Open Circuit Voltage: Write the voltage node equations

$$V_0 = 10V$$

$$\left(\frac{V_1 - V_0}{200}\right) + \left(\frac{V_1}{400}\right) + \left(\frac{V_1 - V_2}{300}\right) = 0$$

$$\left(\frac{V_2 - V_0}{500}\right) + \left(\frac{V_2 - V_1}{300}\right) + \left(\frac{V_2}{600}\right) = 0$$

Solve


- $V_0 = 10$
- $V_1 = 64.377682$
- $V_2 = V_{th} = 59.227468 \text{ V}$

Thevenin Resistance: Turn off the power supply. Compute the resistance looking in:


$$R = ((200 \parallel 400) + 300) \parallel 600 \parallel 500$$

$$R_{th} = (133.333 + 300) \parallel 600 \parallel 500$$

$$R_{th} = 167.38$$

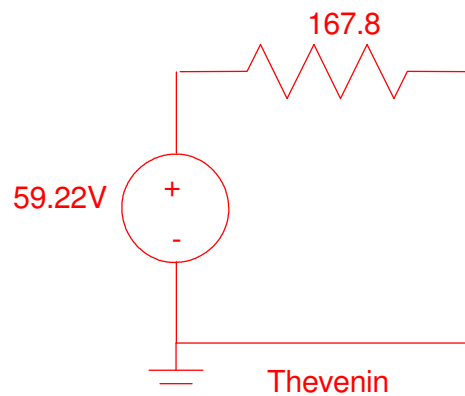

Solution - Problem 2:

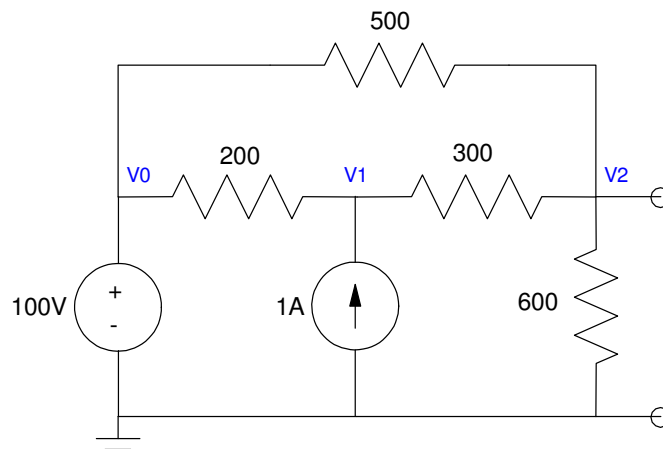

Open Circuit Voltage: Write the voltage node equations

$$V_0 = 10V$$

$$\left(\frac{V_1 - V_0}{200}\right) - 1 + \left(\frac{V_1 - V_2}{300}\right) = 0$$


$$\left(\frac{V_2 - V_0}{500}\right) + \left(\frac{V_2 - V_1}{300}\right) + \left(\frac{V_2}{600}\right) = 0$$

Solve


- $V_0 = 10V$
- $V_1 = 155.78824$
- $V_2 = V_{th} = 74.470588$

Rth: Turn off the sources ($V = 0V = \text{short}$, $I = 0A = \text{open}$). Compute the resistance looking in
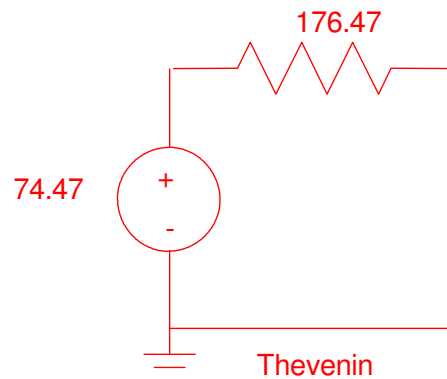
$$R_{th} = 600 \parallel 500 \parallel 500 = 176.47\Omega$$



Solution - Problem 3

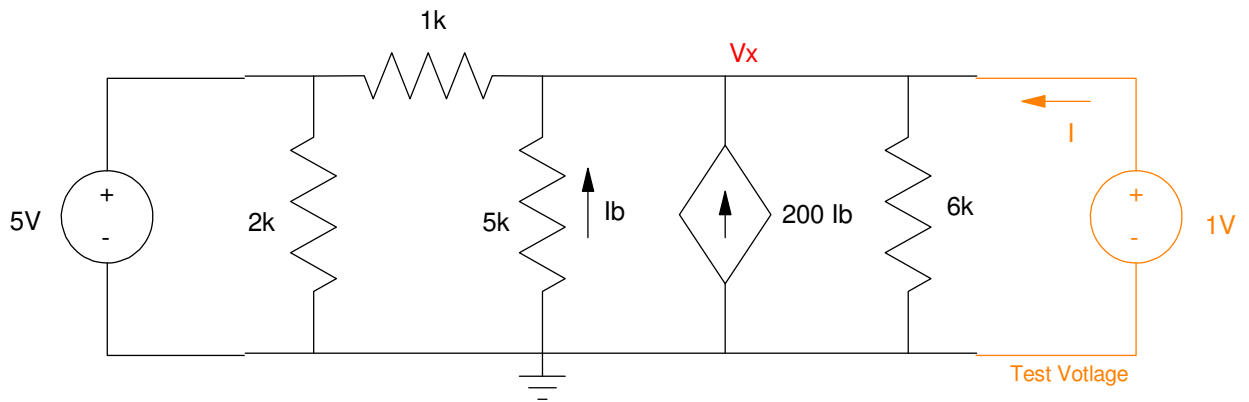

V_{th}: Compute the open circuit voltage. To do this, write the voltage node equation at V_x

$$I_b = \left(\frac{0 - V_x}{5k} \right)$$

$$\left(\frac{V_x - 5}{1k} \right) + \left(\frac{V_x}{5k} \right) - 200I_b + \left(\frac{V_x}{6k} \right) = 0$$

Solving


$$V_{th} = V_x = 0.1209V$$

R_{th}: Turn off the power supplies (5V becomes 0V or a short). Compute R_{in}.


This isn't obvious, so apply a 1V test voltage and compute the current

$$I = \left(\frac{1V}{6k\Omega} \right) + \left(\frac{1V}{1k\Omega} \right) + \left(\frac{1V}{5k\Omega} \right) + 200 \left(\frac{1V}{5k\Omega} \right) = 41.367mA$$
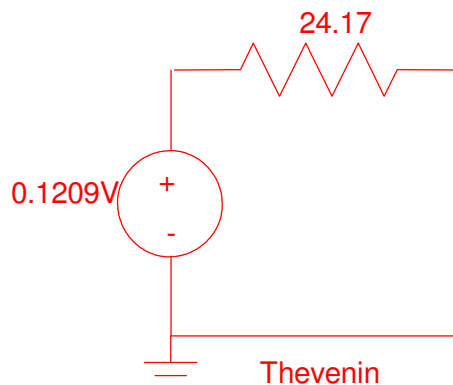
$$R_{th} = \left(\frac{1V}{41.37mA} \right) = 24.17\Omega$$



Solution - Problem 4

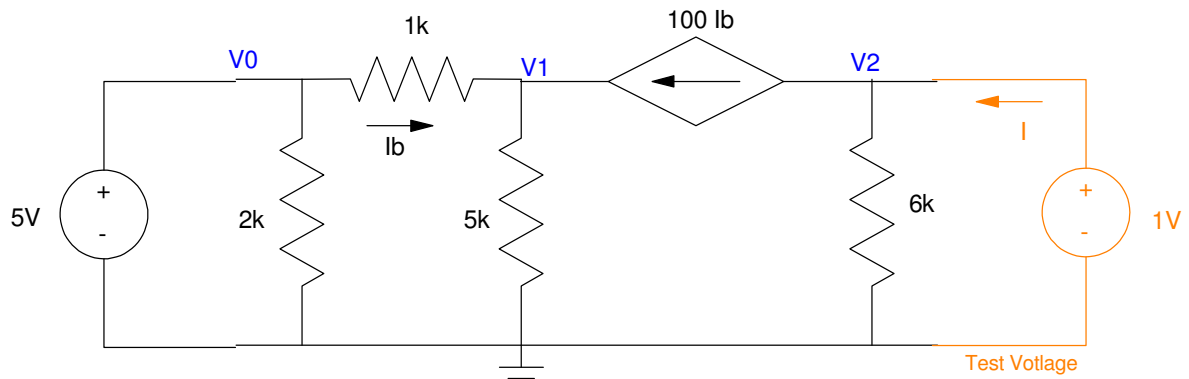

V_{th}: Compute the open-circuit voltage. To do this, compute V₁

$$I_b = \left(\frac{5 - V_1}{1k} \right)$$

$$\left(\frac{V_1 - 5}{1k} \right) + \left(\frac{V_1}{5k} \right) - 100I_b = 0$$

Solve

$$V_1 = 4.9901V$$

$$I_b = \left(\frac{5 - V_1}{1k} \right) = 9.881\mu A$$

$$V_{th} = V_2 = -6000 \cdot 100I_b = -5.929V$$


R_{th}: Turn off the source (5V becomes 0V or a short). Apply a 1V test voltage and compute the current. To do that, solve for V₁ (with V₀ = 0V)

$$\left(\frac{V_1 - 0}{1k} \right) + \left(\frac{V_1}{5k} \right) - 100 \left(\frac{0 - V_1}{1k} \right) = 0$$


$$V_1 = 0, \quad I_b = 0$$

$$I = \frac{1V}{6k} = 166.7\mu A$$
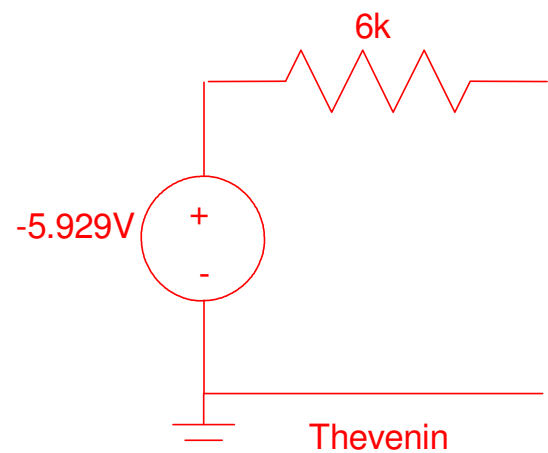
$$R_{th} = \frac{1V}{166.7\mu A} = 6k\Omega$$



Solution - Problem 5

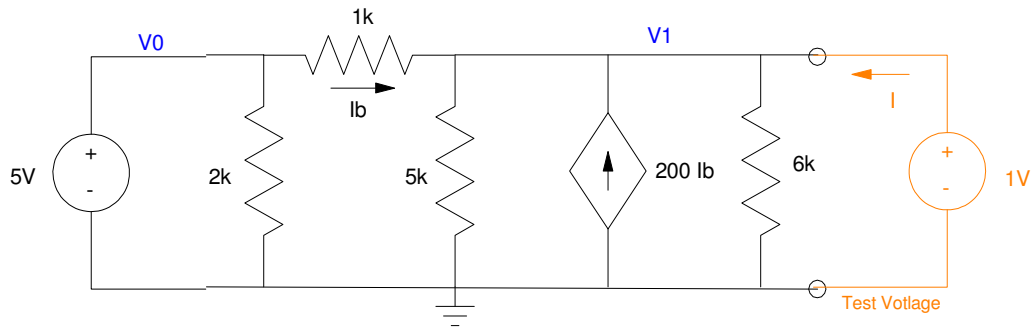

V_{th} : Measure the open-circuit voltage. To do this, write the voltage node equation at V_1

$$I_b = \left(\frac{5 - V_1}{1k} \right)$$

$$-I_b + \left(\frac{V_1}{5k} \right) - 200I_b + \left(\frac{V_1}{6k} \right) = 0$$

Solving


$$V_{th} = V_1 = 4.991V$$

R_{th} : Turn off the sources ($V_0 = 0V = \text{short}$). Apply a 1V test voltage and compute the resulting current


$$I_b = -\frac{1V}{1k} = -1mA$$

$$I = -I_b + \left(\frac{1}{5k} \right) - 200I_b + \left(\frac{1}{6k} \right) = 201.4mA$$
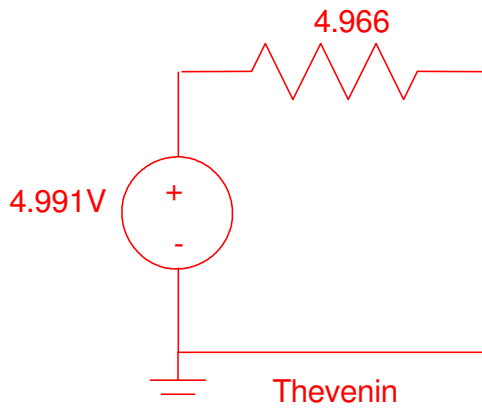
$$R_{th} = \frac{1V}{201.4mA} = 4.966\Omega$$



Solution - Problem 6

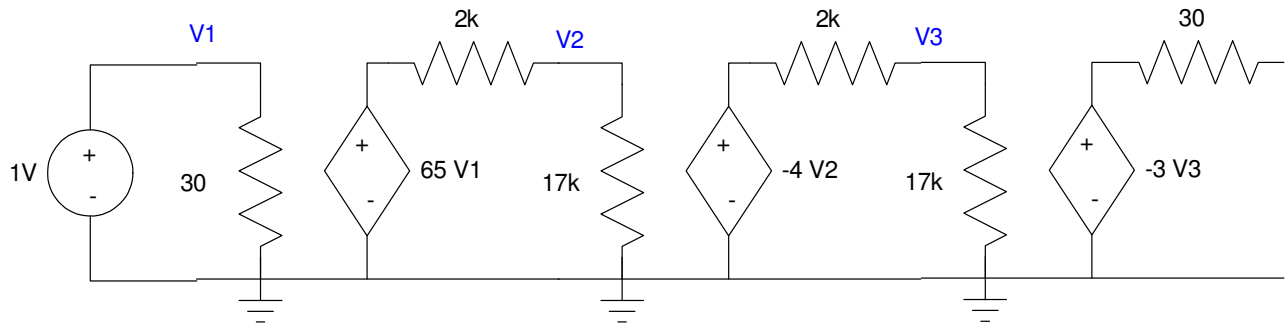

Rth: Set the sources to zero (1V becomes 0V or a short). This results in

- $V_1 = 0$ $65 V_1 = 0$
- $V_2 = 0$ $-4 V_2 = 0$
- $V_3 = 0$ $-3 V_3 = 0$

Rth = 30 Ohms

Vth: Compute the open-circuit voltage

$$V_1 = 1V$$

$$65V_1 = 65V$$

$$V_2 = \left(\frac{17k}{17k+2k} \right) \cdot 65V = 56.16V$$

$$-4V_2 = -232.632V$$

$$V_3 = \left(\frac{17k}{17k+2k} \right) \cdot (-232.632V) = -208.144V$$

$$V_{th} = -3V_3 = 624.432$$

