

Voltage Nodes with Phasors


EE 206 Practice Problems

- 1) Write the voltage node equations for the following circuit. Assume

$$V_{in} = 20 \cos(500t) + 5 \sin(500t)$$

- 2) Write the voltage node equations for the following circuit. Assume

$$V_{in} = 30 \cos(2000t - 50^\circ)$$

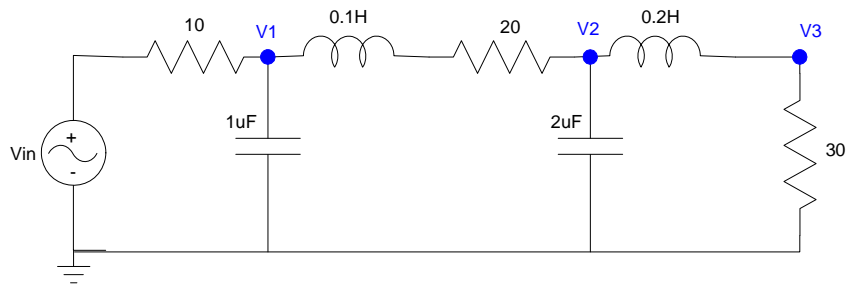


Problem 1 & 2

- 3) Write the voltage node equations for the following circuit. Assume

$$V_{in} = 20 \cos(500t) + 5 \sin(500t)$$

- 4) Write the voltage node equations for the following circuit. Assume

$$V_{in} = 30 \cos(2000t - 50^\circ)$$

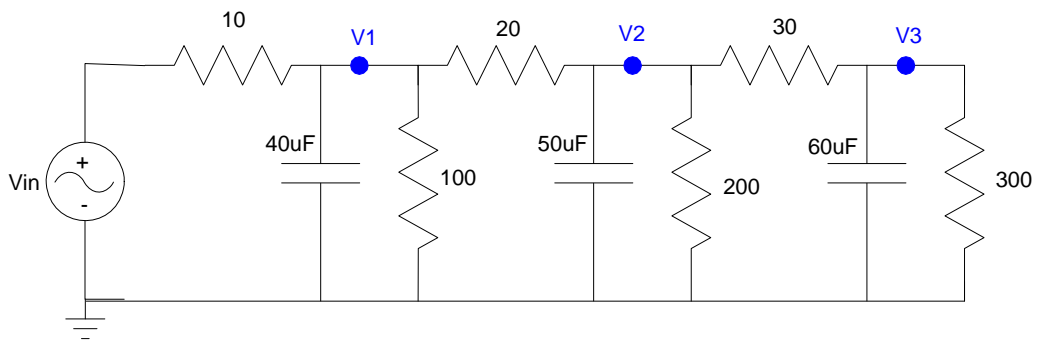


Solutions

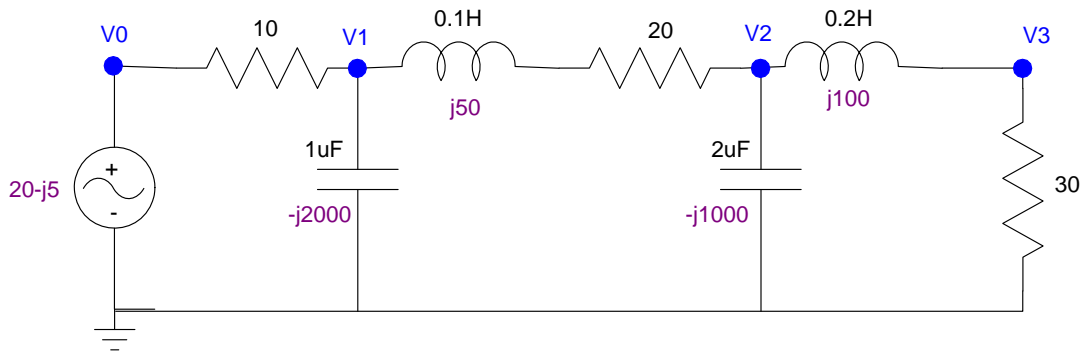1) Write the voltage node equations for the following circuit. Assume

$$V_{in} = 20 \cos(500t) + 5 \sin(500t)$$

Step 1) Convert to phasors (shown in figure below)



Now write the voltage node equations

$$V_0 = 20 - j5$$

$$\left(\frac{V_1 - V_0}{10} \right) + \left(\frac{V_1}{-j2000} \right) + \left(\frac{V_1 - V_2}{20 + j50} \right) = 0$$

$$\left(\frac{V_2 - V_1}{20 + j50} \right) + \left(\frac{V_2}{-j1000} \right) + \left(\frac{V_2 - V_3}{j100} \right) = 0$$

$$\left(\frac{V_3 - V_2}{j100} \right) + \left(\frac{V_3}{30} \right) = 0$$


Note that it's the same as we did at DC, only now with complex numbers

2) Write the voltage node equations for the following circuit. Assume

$$V_{in} = 30 \cos(2000t - 50^\circ)$$

First, convert to phasor notation. My circuit diagram software doesn't do greek letters well so V_{in} is expressed in rectangular form
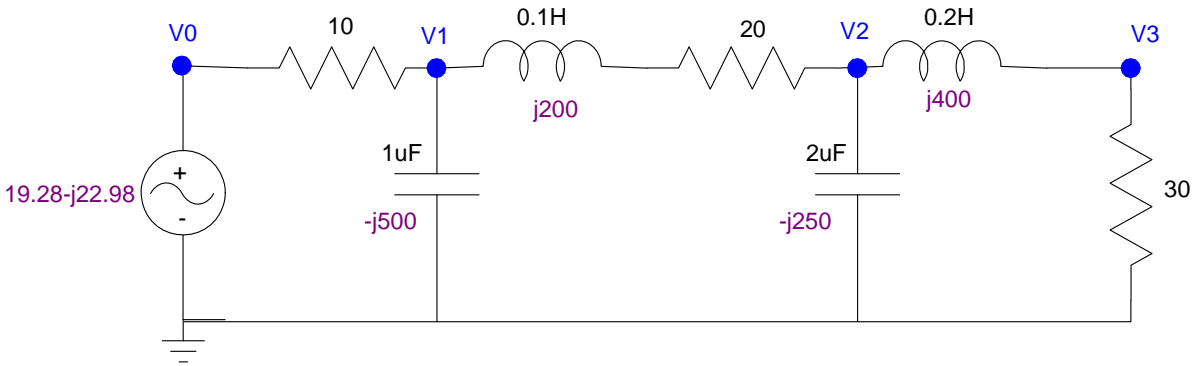
$$V_{in} = 19.28 \cos(2000t) + 22.98 \sin(2000t)$$



Now write the voltage node equations

$$V_0 = 30 \angle -50^\circ$$

$$\left(\frac{V_1 - V_0}{10} \right) + \left(\frac{V_1}{-j500} \right) + \left(\frac{V_1 - V_2}{20 + j200} \right) = 0$$

$$\left(\frac{V_2 - V_1}{20 + j200} \right) + \left(\frac{V_2}{-j250} \right) + \left(\frac{V_2 - V_3}{j400} \right) = 0$$

$$\left(\frac{V_3 - V_2}{j400} \right) + \left(\frac{V_3}{30} \right) = 0$$


Problem 3) Write the voltage node equations for the following circuit. Assume

$$V_{in} = 20 \cos(500t) + 5 \sin(500t)$$

Start by converting to phasors

$$\omega = 500$$

$$V_{in} = 20 - j5$$

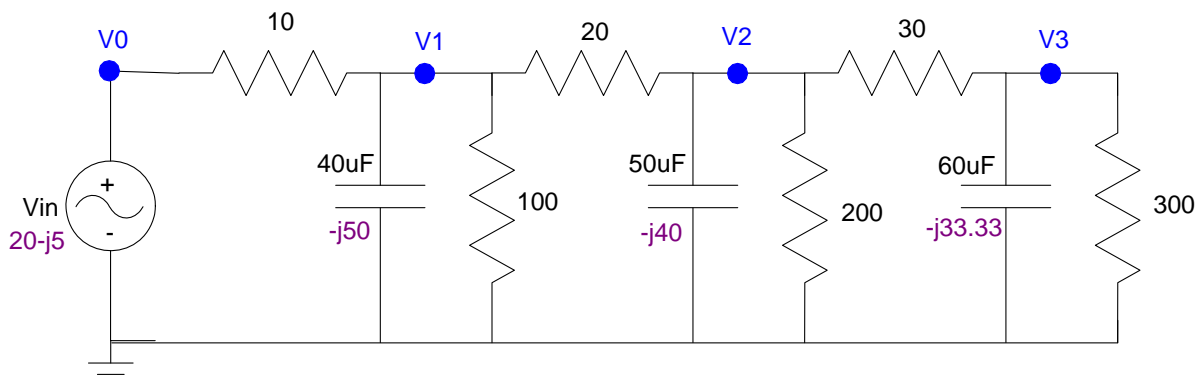

Now write the voltage node equations

$$V_0 = 20 - j5$$

$$\left(\frac{V_1 - V_0}{10} \right) + \left(\frac{V_1}{-j50} \right) + \left(\frac{V_1}{100} \right) + \left(\frac{V_1 - V_2}{20} \right) = 0$$

$$\left(\frac{V_2 - V_1}{20} \right) + \left(\frac{V_2}{-j40} \right) + \left(\frac{V_2}{200} \right) + \left(\frac{V_2 - V_3}{30} \right) = 0$$


$$\left(\frac{V_3 - V_2}{30} \right) + \left(\frac{V_3}{-j33.33} \right) + \left(\frac{V_3}{300} \right) = 0$$

Problem 4) Write the voltage node equations for the following circuit. Assume

$$V_{in} = 30 \cos(2000t - 50^\circ)$$

Start by converting to phasors
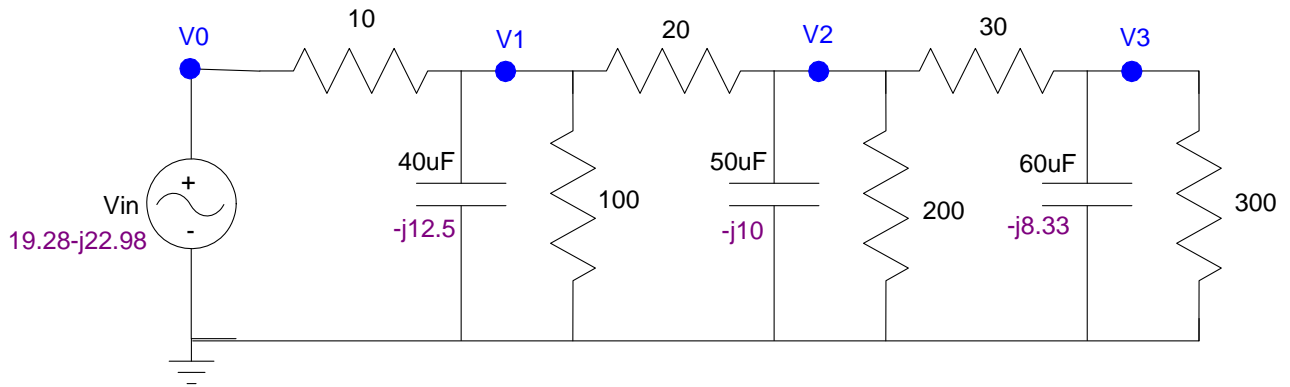
$$V_{in} = 30 \angle -50^\circ = 19.28 - j22.98$$



Now write the voltage node equations

$$V_0 = 30 \angle -50^\circ$$

$$\left(\frac{V_1 - V_0}{10} \right) + \left(\frac{V_1}{-j12.5} \right) + \left(\frac{V_1}{100} \right) + \left(\frac{V_1 - V_2}{20} \right) = 0$$

$$\left(\frac{V_2 - V_1}{20} \right) + \left(\frac{V_2}{-j10} \right) + \left(\frac{V_2}{200} \right) + \left(\frac{V_2 - V_3}{30} \right) = 0$$

$$\left(\frac{V_3 - V_2}{30} \right) + \left(\frac{V_3}{-j8.33} \right) + \left(\frac{V_3}{300} \right) = 0$$