

# Resistors in Series and Parallel

## EE 206 Practice Problems

1) Determine the resistance  $R_{ab}$ . Assume

- $R_1 = 100$
- $R_2 = 150$
- $R_3 = 200$

2) Determine the resistance  $R_{ab}$ . Assume

- $R_1 = 500$
- $R_2 = 400$
- $R_3 = 300$

3) Determine the resistance  $R_{ab}$ . Assume

- $R_1 = 600$
- $R_2 = 800$
- $R_3 = 700$


4) Assume  $R_{ab} = 100$  Ohms and

- $R_2 = 200$
- $R_3 = 300$


Find  $R_1$  (note: the answer might be negative)



a)

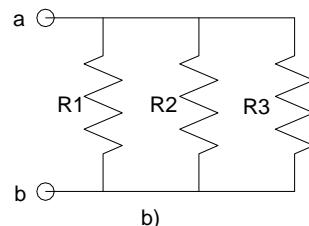


b)

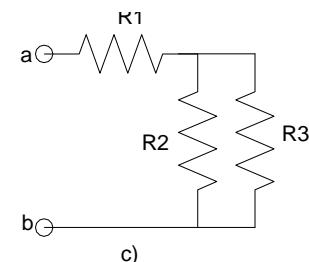

c)


5) Find the resistance  $R_{AB}$

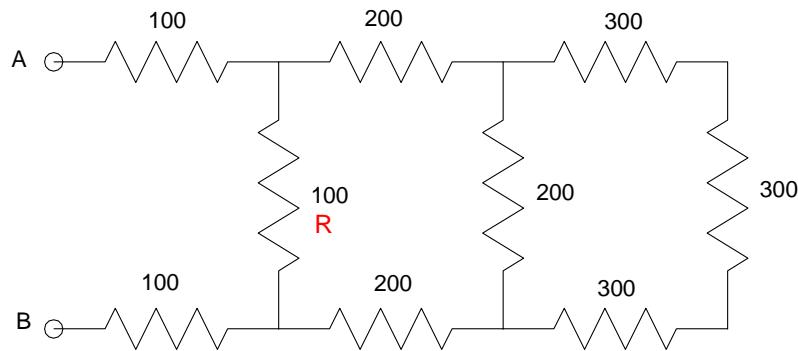6) Find  $R$  so that the resistance  $R_{AB} = 300$  Ohms



7) Find the resistance  $R_{AB}$

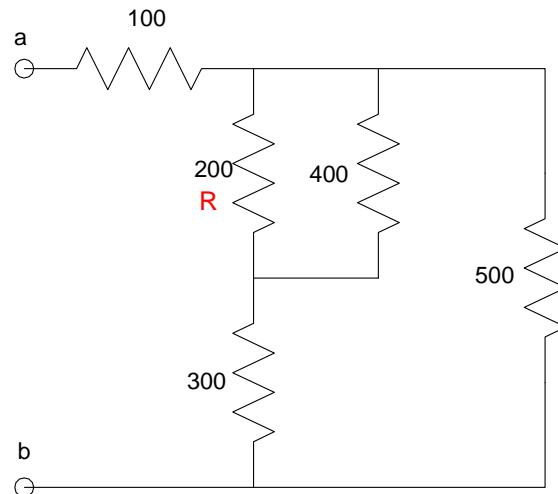8) Find  $R$  so that the total resistance  $R_{AB}$  is 300 Ohms



## **Solutions:**

Problem 1)

- 1a)  $R_{ab} = 450$
- 1b)  $R_{ab} = 46.154$
- 1c)  $R_{ab} = 185/714$

Problem 2)

- 2a)  $R_{ab} = 1200$
- 2c)  $R_{ab} = 127.660$
- 2c)  $R_{ab} = 671.429$

Problem 3)

- a)  $R_{ab} = 2100$
- b)  $R_{ab} = 230.137$
- c)  $R_{ab} = 973.333$

Problem 4)

- a)  $R_1 = -400$
- b)  $R_1 = 600 \text{ Ohms}$
- c)  $R_1 = -20 \text{ Ohms}$

5)  $R_{ab} = 284.932$

6)  $R_1 = 137.931$

7)  $R_{ab} = 332.143$

8)  $R_1 = 36.364$