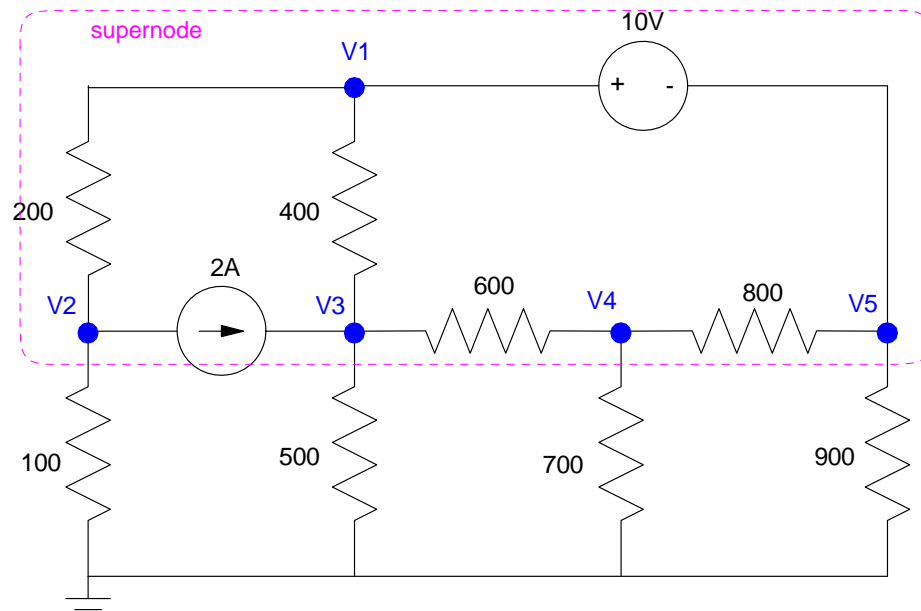


EE 206 Final - Name _____

Closed-Book, Closed Notes, Calculators Permitted. - Spring 2019

1) Write N equations which allow you to solve for the N unknown voltages



Voltage Source

$$\bullet V_1 - V_5 = 0$$

Node V2

$$\bullet \left(\frac{V_2 - V_1}{200} \right) + \left(\frac{V_2}{100} \right) + 2 = 0$$

Node V3

$$\bullet -2 + \left(\frac{V_3}{500} \right) + \left(\frac{V_3 - V_1}{400} \right) + \left(\frac{V_3 - V_4}{600} \right) = 0$$


Node V4

$$\bullet \left(\frac{V_4 - V_3}{600} \right) + \left(\frac{V_4}{700} \right) + \left(\frac{V_4 - V_5}{800} \right) = 0$$

Supernode

$$\bullet \left(\frac{V_2}{100} \right) + \left(\frac{V_3}{500} \right) + \left(\frac{V_4}{700} \right) + \left(\frac{V_5}{900} \right) = 0$$

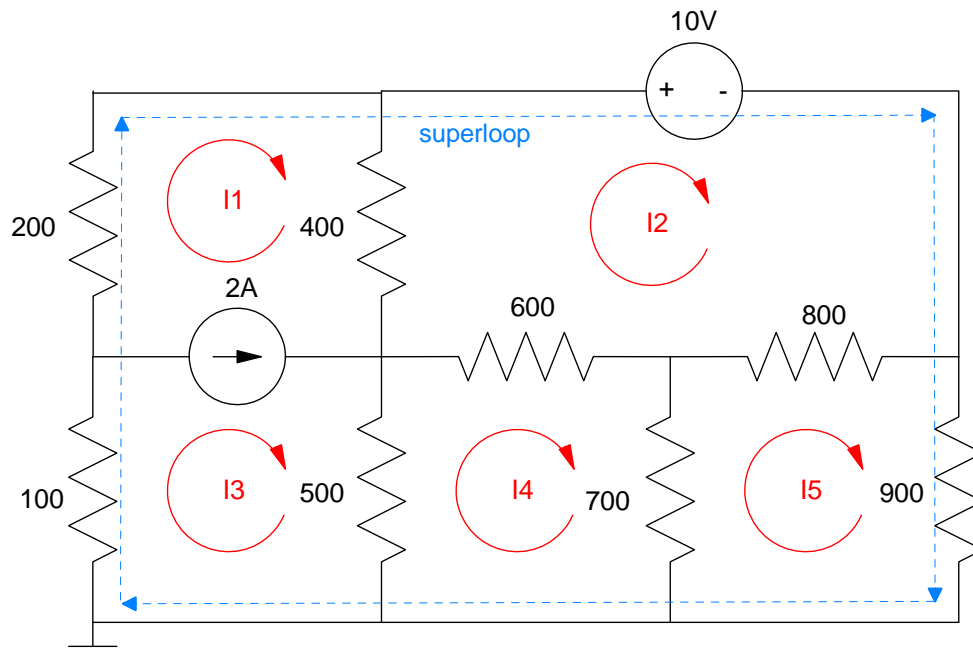2) Write N equations which allow you to solve for the N unknown currents



Current Source

- $I_3 - I_1 = 2$

Loop I2

- $10 + 800(I_2 - I_5) + 600(I_2 - I_4) + 400(I_2 - I_1) = 0$

Loop I4

- $500(I_4 - I_3) + 600(I_4 - I_2) + 700(I_4 - I_5) = 0$

Loop I5


- $700(I_5 - I_4) + 800(I_5 - I_2) + 900I_5 = 0$

Super Loop

- $100I_3 + 200I_1 + 10 + 900I_5 = 0$

3) Find the voltages V_0 , V_1 , V_2 given that $V_3 = 10.0V$

V_0	V_1	V_2	V_3
25.39	20.40	14.50	10.0V

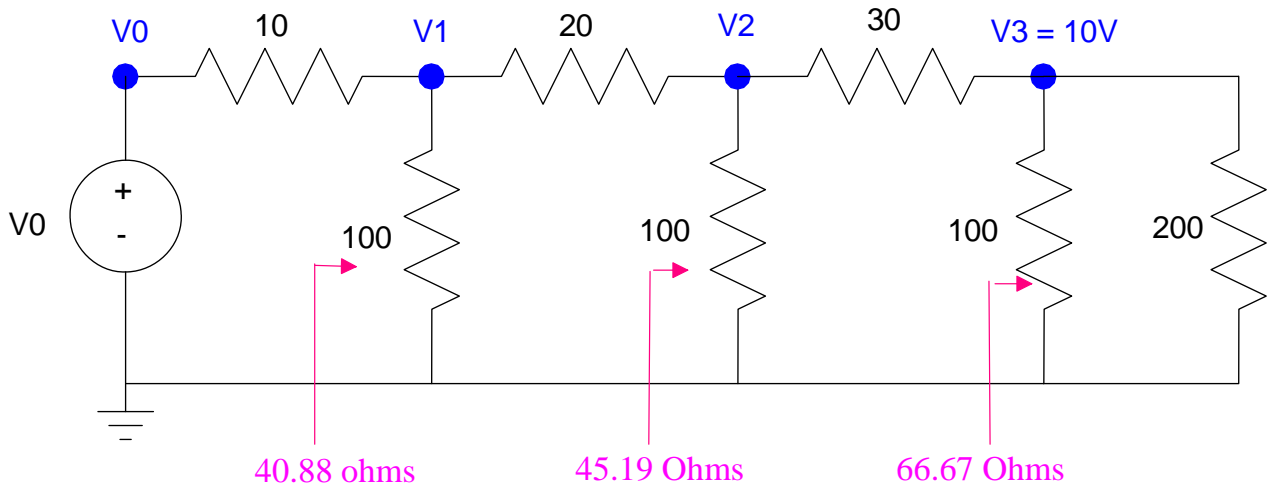

By voltage division


$$V_3 = \left(\frac{66.67}{66.67+30} \right) V_2 \quad \Rightarrow V_2 = 14.5V$$

$$V_2 = \left(\frac{49.15}{49.15+20} \right) V_1 \quad \Rightarrow V_1 = 20.4V$$


$$V_1 = \left(\frac{40.88}{40.88+10} \right) V_0 \quad \Rightarrow V_0 = 25.39V$$

4) Find the Thevenin equivalent for the following circuit:


Vth	Rth
41.7 V	19.13 Ohms

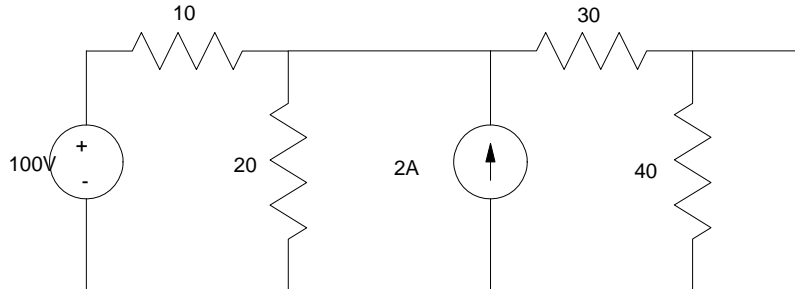

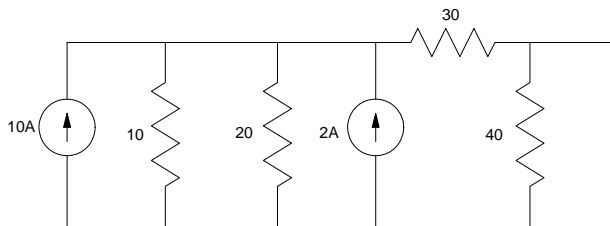
Convert the 100V / 10 Ohm to a Norton equivalent



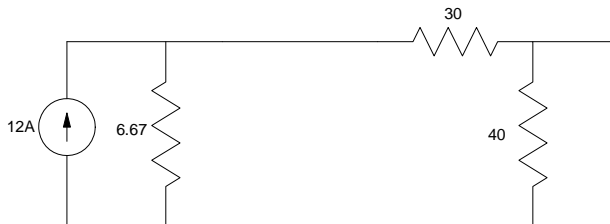Add current sources and resistors in parallel




Convert back to a Thevenin

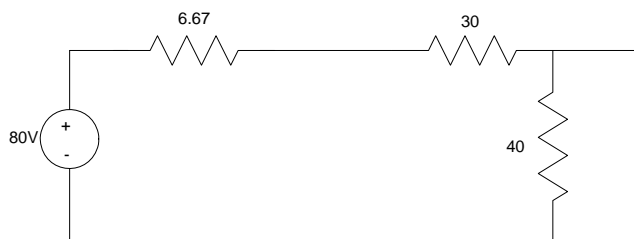

Now find Vopen (Vth) and R when V = 0

5) Find the voltages V1 .. V7

V1	V2	V3	V4
7 V	6 V	2 V	1 V
V5	V6	V7	
4.67 V	4.67 V	12 V	

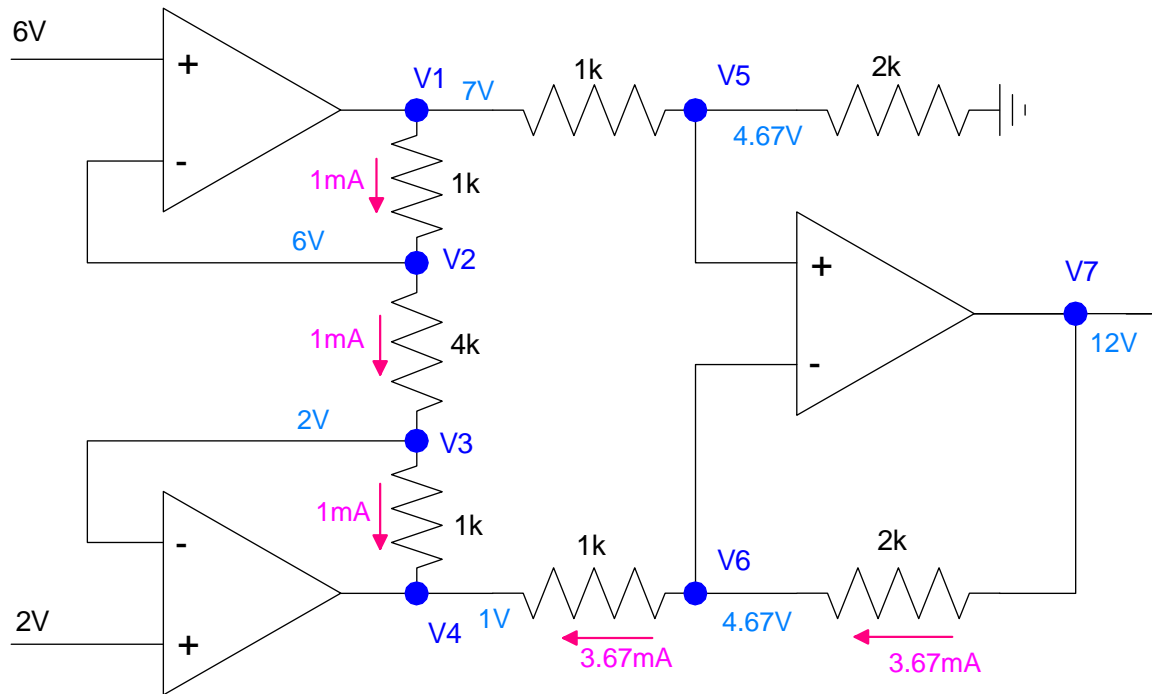

For an op-amp with negative feedback, $V_p = V_m$

- $V_2 = 6V$
- $V_3 = 2V$

4V across the 4k resistor produces 1mA. This 1mA also flows through the 1k resistors

- $V_1 - V_2 = 1mA \cdot 1k = 1V \quad \Rightarrow V_1 = 7V$
- $V_3 - V_4 = 1mA \cdot 1k = 1V \quad \Rightarrow V_4 = 1V$

By voltage division

$$V_5 = \left(\frac{2k}{2k+1k} \right) 7V \quad \Rightarrow V_5 = 4.67V$$


$V_p = V_m$

$$\Rightarrow V_6 = 4.67V$$

$$V_7 = 2(V_1 - V_4) = 12V$$

6) Determine the impedance between a and b

$$Z_{ab} = 64 - j42$$

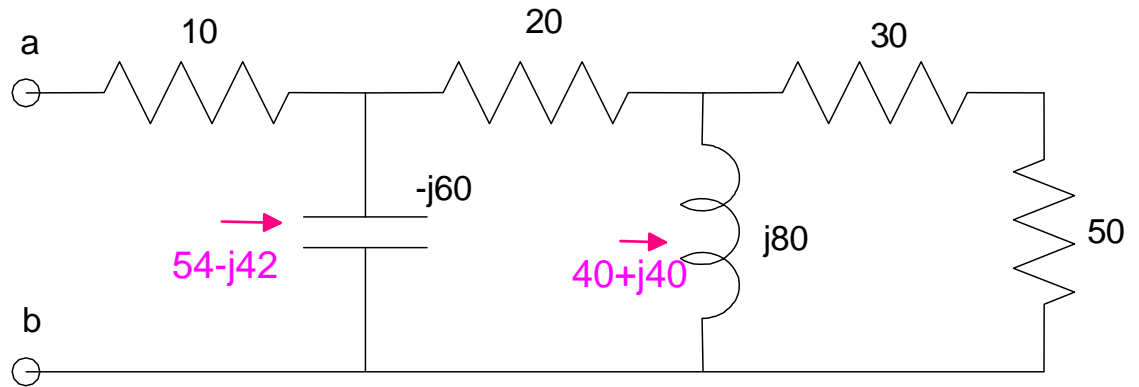

$$50 + 30 = 80$$

$$80 \parallel j80 = 40 + j40$$


$$(40 + j40) + (20) = 60 + j40$$

$$(60 + j40) \parallel (-j60) = 54 - j42$$

$$(54 - j42) + (10) = 64 - j42$$

7) Determine the voltages V1 and V2

Frequency (Hz)	V1		V2	
	Amplitude (Vp)	Phase (degrees)	Amplitude (Vp)	Phase (degrees)
4.38 Hz	23 Vp	-101 deg	17 Vp	-250 deg

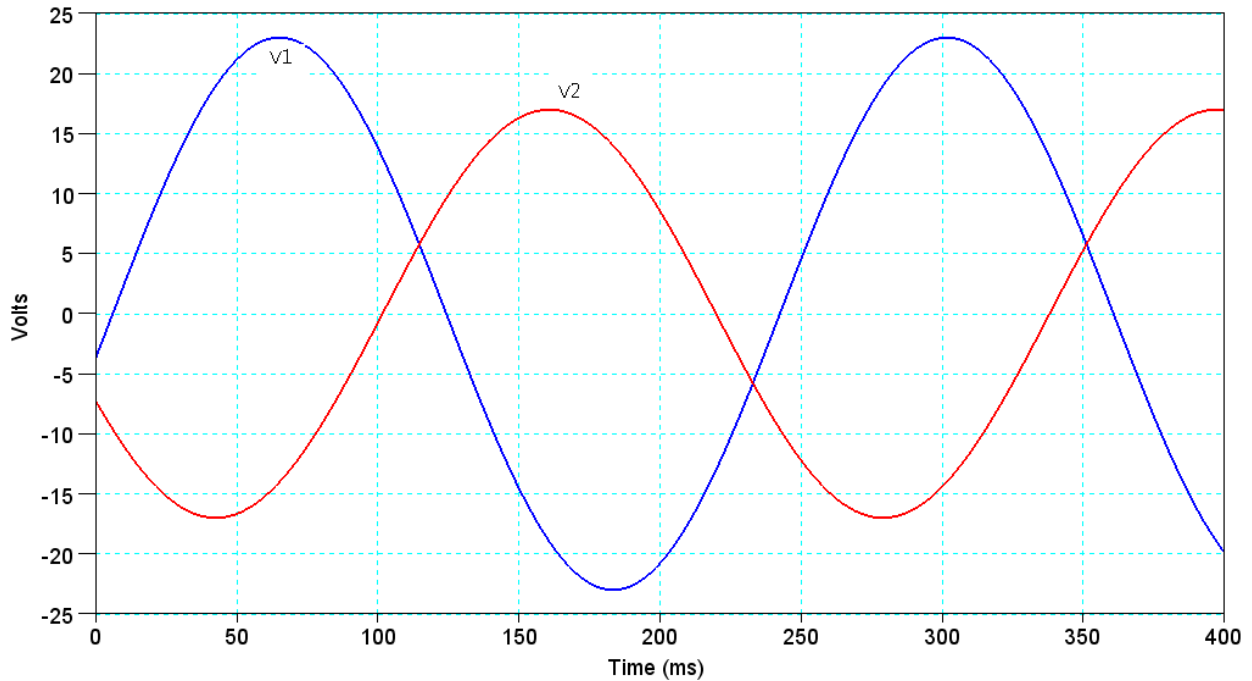

The period is 230ms

$$f = \frac{1}{T} = 4.38\text{Hz}$$

The delay tells you the phase shift. V1 is delayed by 65ms

$$\theta = -\left(\frac{\text{delay}}{\text{period}}\right) \cdot 360^\circ$$


$$\theta_1 = -\left(\frac{65\text{ms}}{230\text{ms}}\right) 360^\circ = -101^\circ$$

$$\theta_2 = -\left(\frac{160\text{ms}}{230\text{ms}}\right) 360^\circ = -250^\circ$$

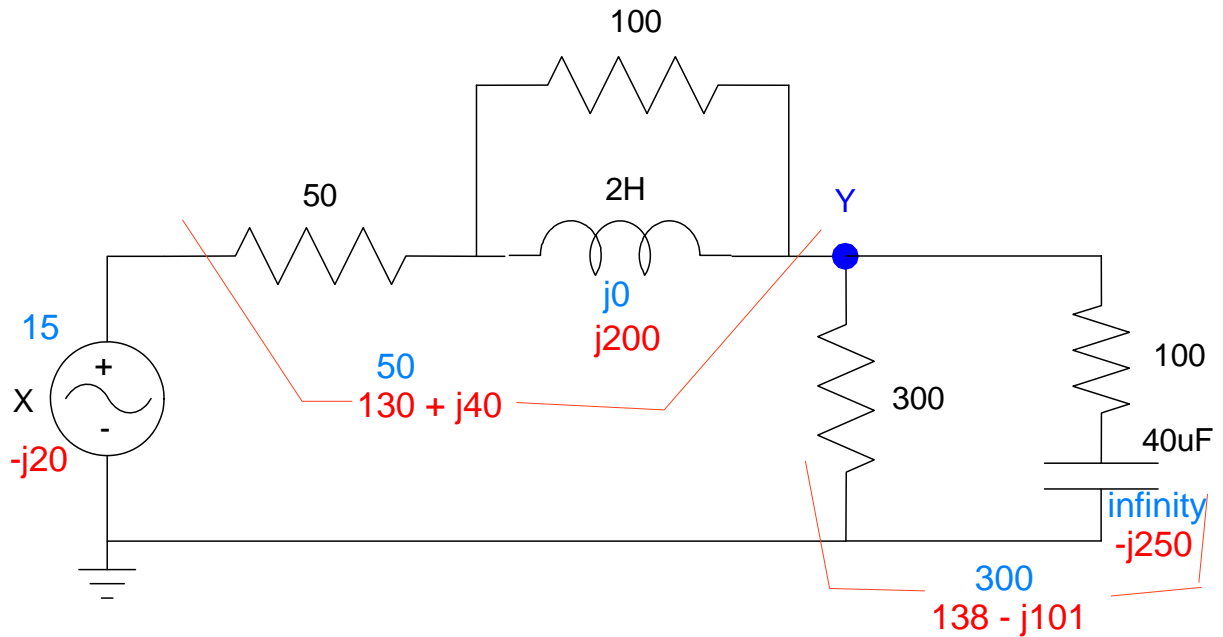8) Determine the voltage at Y. Assume

$$x(t) = 15 + 20 \sin(100t)$$

$$y(t) = 12.85 - 4.93 \cos(100t) + 11.43 \sin(100t)$$



DC Analysis: (Blue)

$$X = 15$$

$$L = 0$$

C = infinity (open)

$$Y = \left(\frac{300}{300+50} \right) 15 = 12.85$$

AC Analysis (red)

$$X = 0 - j20$$

$$L = j200$$

$$C = -j250$$

$$Y = \left(\frac{138-j101}{(138-j101)+(130+j40)} \right) (-j20)$$

$$Y = -4.93 - j11.43$$

real means cosine

complex means minus sine