

EE 206: Homework #8

Sinusoidal Source, Complex Numbers, Complex Impedance
Due Monday, March 25th

1) Convert to V_p , V_{pp} , V_{rms}

| V_p (peak) | V_{pp} (peak-to-peak) | V_{rms} |
|--------------|-------------------------|-----------|
| 10V | | |
| | 10V | |
| | | 10V |

2) Find Y

$$2a) \quad Y = \left(\frac{2+j3}{5+j7} \right) + \left(\frac{10-j3}{8+j5} \right)$$

$$2b) \quad Y = \left(\frac{100(s+3)}{s(s+5)(s+10)} \right)_{s=j2}$$

$$2c) \quad Y = \left(\frac{5s^2+10s+20}{s^3+6s^2+11s+6} \right)_{s=j3}$$

3) Express V in phasor form.



$$3a) \quad V = 3 \cos(10t) + 7 \sin(10t)$$

$$3b) \quad V = 3 \cos(20t - 30^\circ) + 7 \cos(20t + 5^\circ)$$

$$3c) \quad V = 6 \cos(5t - 50^\circ) + 8 \sin(5t)$$

4) Determine the impedance of the following circuits assuming the frequency is 50 rad/sec

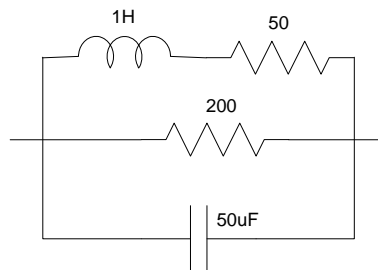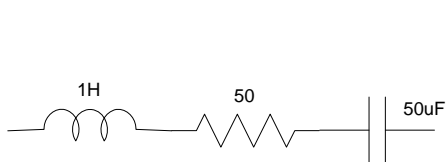5) Determine the impedance of the following circuits assuming the frequency is 300 rad/sec



Problem 4 & 5

