


EE 206: Solution #4

Super Nodes, Current Loops. Due Mon, Feb 4th

Note: In this assignment just write N equations for N unknowns.

Super Nodes

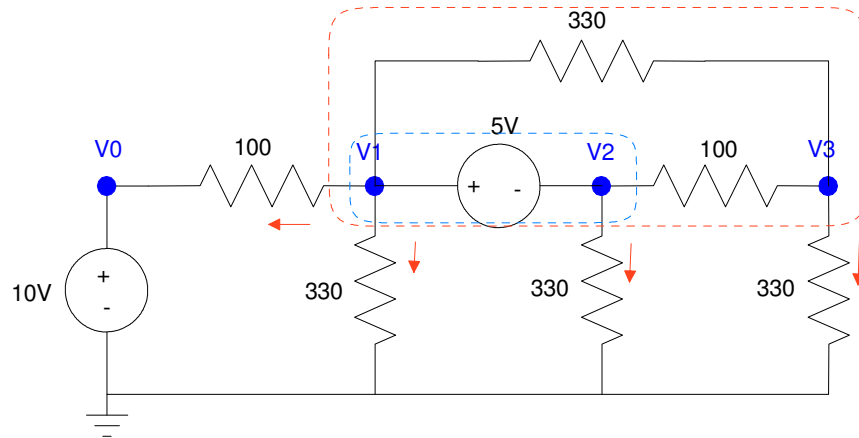1) Write the voltage node equations for the following circuit (N equations for N unknowns)



There are 4 voltage nodes. We need to write 4 equations to solve for 4 unknowns. Start with the easy ones

$$(1) \quad V_0 = 10$$

$$(2) \quad V_1 - V_2 = 5$$

Sum the currents from node V3 to zero

$$(3) \quad \left(\frac{V_3 - V_1}{330} \right) + \left(\frac{V_3 - V_2}{100} \right) + \left(\frac{V_3}{330} \right) = 0$$


We need one more equation. Define a super node (red dotted line). The sum of the currents from the super node must be zero

$$(4) \quad \left(\frac{V_1 - V_0}{100} \right) + \left(\frac{V_1}{330} \right) + \left(\frac{V_2}{330} \right) + \left(\frac{V_3}{330} \right) = 0$$

Note that other super nodes are also valid. If you use the blue dotted line, the 4th equation becomes

$$(4) \quad \left(\frac{V_1 - V_0}{100} \right) + \left(\frac{V_1 - V_3}{330} \right) + \left(\frac{V_1}{330} \right) + \left(\frac{V_2}{330} \right) + \left(\frac{V_2 - V_3}{100} \right) = 0$$

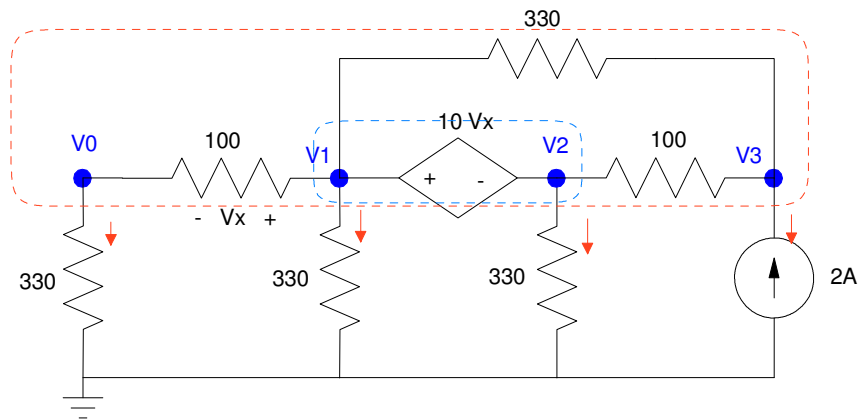2) Write the voltage node equations for the following circuit (N equations for N unknowns)



There are 4 voltage nodes plus V_x . That makes 5 unknowns. Write 5 equations for 5 unknowns.

Start with the easy ones

$$(1) \quad V_x = V_0 - V_1$$

$$(2) \quad V_1 - V_2 = 10V_x$$

Sum the current from node 0 to zero

$$(3) \quad \left(\frac{V_0}{330}\right) + \left(\frac{V_0 - V_1}{100}\right) = 0$$

Sum the current from node 3 to zero

$$(4) \quad \left(\frac{V_3 - V_1}{330}\right) + \left(\frac{V_3 - V_2}{100}\right) - 2 = 0$$

We need one more equation. Define a super-node (red dotted line)

$$(5) \quad \left(\frac{V_0}{330}\right) + \left(\frac{V_1}{330}\right) + \left(\frac{V_2}{330}\right) - 2 = 0$$


This gives 5 equations for 5 unknowns.

Note that you could use a different super node (blue dotted line). This makes the 5th equation:

$$(5) \quad \left(\frac{V_1 - V_0}{100}\right) + \left(\frac{V_1 - V_3}{330}\right) + \left(\frac{V_1}{330}\right) + \left(\frac{V_2}{330}\right) + \left(\frac{V_2 - V_3}{100}\right) = 0$$

Current Loops

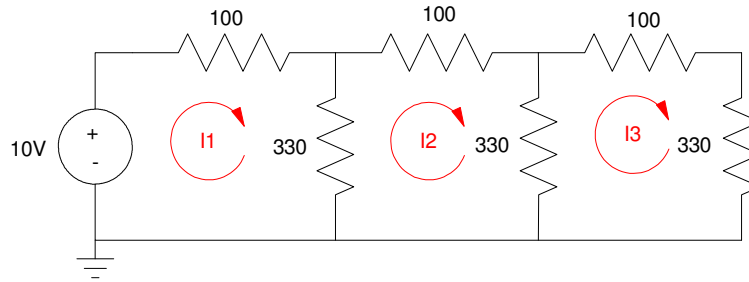3) Write the current loop equations for the following circuit



With 3 unknown currents, we need to write 3 equations to solve for 3 unknowns

$$(1) \quad -10 + 100I_1 + 330(I_1 - I_2) = 0$$


$$(2) \quad 330(I_2 - I_1) + 100I_2 + 330(I_2 - I_3) = 0$$

$$(3) \quad 330(I_3 - I_2) + 100I_3 + 330I_3 = 0$$

Note that around any loop I_x

- The sign is positive for I_x
- The sign is negative for all other currents

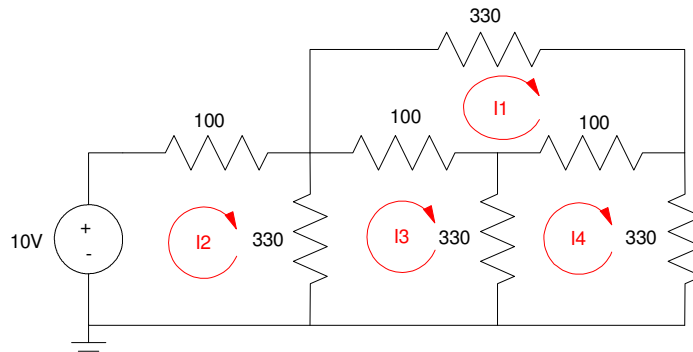4) Write the current loop equations for the following circuit



With 4 unknown currents, we need to write 4 equations to solve for 4 unknowns

$$(1) \quad 330I_1 + 100(I_1 - I_4) + 100(I_1 - I_3) = 0$$


$$(2) \quad -10 + 100I_2 + 330(I_2 - I_3) = 0$$

$$(3) \quad 330(I_3 - I_2) + 100(I_3 - I_1) + 330(I_3 - I_4) = 0$$

$$(4) \quad 330(I_4 - I_3) + 100(I_4 - I_1) + 330I_4 = 0$$

Super Loops

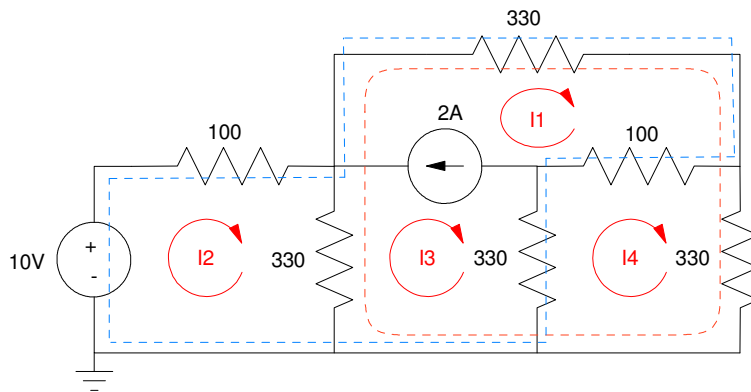5) Write the current loop equations for the following circuit



With 4 unknown currents, we need to write 4 equations to solve for 4 unknowns. Start with the easy one (the current source)

$$(1) \quad I_1 - I_3 = 0$$

Sum the voltages to zero around loop I2

$$(2) \quad -10 + 100I_2 + 330(I_2 - I_3) = 0$$

Sum the voltages around loop I4

$$(3) \quad 330(I_4 - I_3) + 100(I_4 - I_1) + 330I_4 = 0$$


We need one more equation. Define a super-loop (shown in the red dotted line)

$$(4) \quad 330(I_3 - I_2) + 330I_1 + 330I_4 = 0$$

Other super loops are also valid. If you prefer the blue dotted line

$$(4) \quad -10 + 100I_2 + 330I_1 + 100(I_1 - I_4) + 330(I_3 - I_4) = 0$$

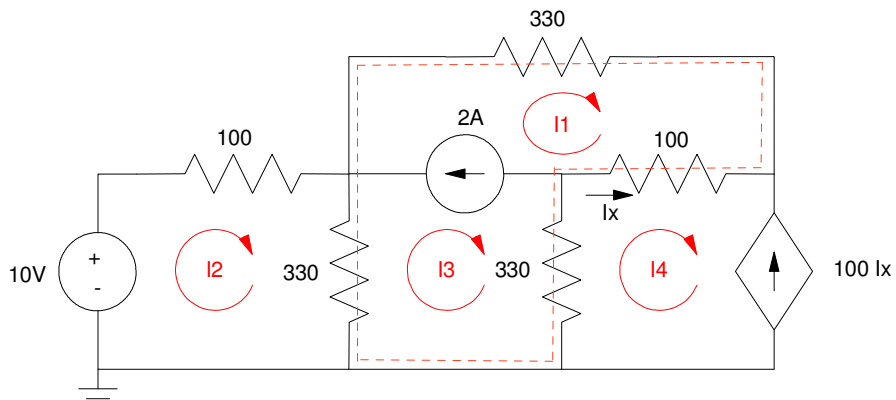6) Write the current loop equations for the following circuit



With 4 unknown current loops and I_x , we need to write 5 equations to solve for 5 unknowns. Start with the easy one (the current source)

$$(1) \quad I_x = I_4 - I_1$$

$$(2) \quad I_1 - I_3 = 2$$

$$(3) \quad I_4 = -100I_x$$


Sum the voltages around loop I2 to zero

$$(4) \quad -10 + 100I_2 + 330(I_2 - I_3) = 0$$

We need one more equation. Pick a closed path which has known voltages (i.e. avoids current sources)

$$(5) \quad 330(I_3 - I_2) + 330I_1 + 100(I_1 - I_4) + 330(I_3 - I_4) = 0$$

For the circuit of problem #4:

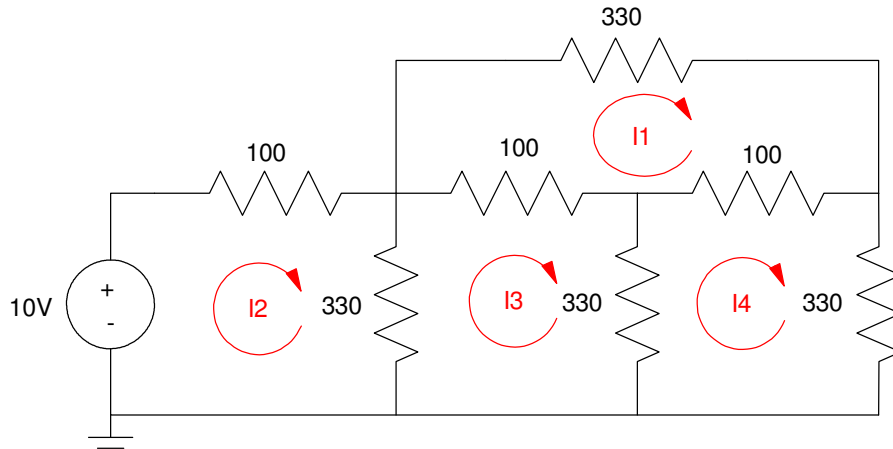

7) Solve your sets of equations to find the currents. Recall from problem #4:

$$330I_1 + 100(I_1 - I_4) + 100(I_1 - I_3) = 0$$

$$-10 + 100I_2 + 330(I_2 - I_3) = 0$$

$$330(I_3 - I_2) + 100(I_3 - I_1) + 330(I_3 - I_4) = 0$$

$$330(I_4 - I_3) + 100(I_4 - I_1) + 330I_4 = 0$$

Grouping terms

$$530I_1 - 100I_3 - 100I_4 = 0$$

$$430I_2 - 330I_3 = 10$$

$$-100I_1 - 330I_2 + 760I_3 - 330I_4 = 0$$

$$-100I_1 - 330I_3 + 760I_4 = 0$$

Place in matrix form

$$\begin{bmatrix} 530 & 0 & -100 & -100 \\ 0 & 430 & -330 & 0 \\ -100 & -330 & 760 & -330 \\ -100 & 0 & -330 & 760 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} 0 \\ 10 \\ 0 \\ 0 \end{bmatrix}$$

Solve in Matlab

$A = [530, 0, -100, -100 ; 0, 430, -330, 0 ; -100, -330, 760, -330 ; -100, 0, -330, 760]$

530 0 -100 -100
 0 430 -330 0
 -100 -330 760 -330
 -100 0 -330 760


$B = [0; 10; 0; 0]$

0
 10
 0
 0

$I = \text{inv}(A) * B$

I1 0.0066
I2 0.0415
I3 0.0237
I4 0.0112

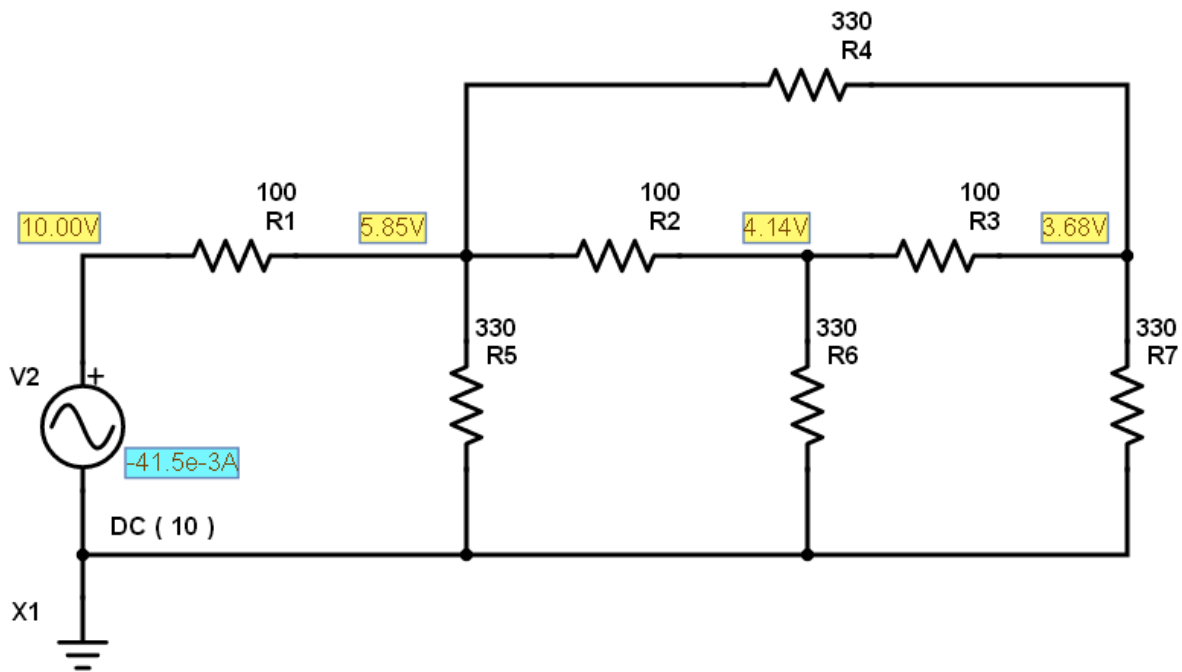8) Simulate the circuit in PartSim. Check that the simulation results match your calculations.



This gives

- $I_2 = 41.5\text{mA}$ (the voltage source)

To find I_1

$$I_1 = \left(\frac{5.85\text{V} - 3.68\text{V}}{330\Omega} \right) = 6.6\text{mA}$$

To find I4:

$$I_4 = \left(\frac{3.68V}{330\Omega} \right) = 11.2mA$$

To find I3,

$$I_2 - I_3 = \left(\frac{5.85V}{330\Omega} \right) = 17.7mA$$

$$I_3 = 23.8mA$$

	Calculated problem 7	Simulated problem 8
I1	0.0066	6.6 mA
I2	0.0415	41.5 mA
I3	0.0237	23.8 mA
I4	0.0112	11.2 mA