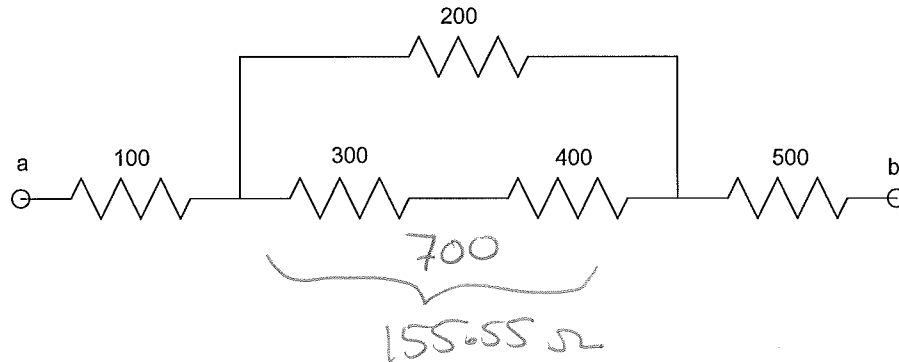


EE 206 Test #1 - Name $\bar{X} = 66\%$ $S = 18.7\%$

February 8, 2019


1a) Determine the resistance R_{ab}

$R_{ab} = 755.55$




1b) Determine R so that $R_{ab} = 700$ Ohms

$R = 116.67$

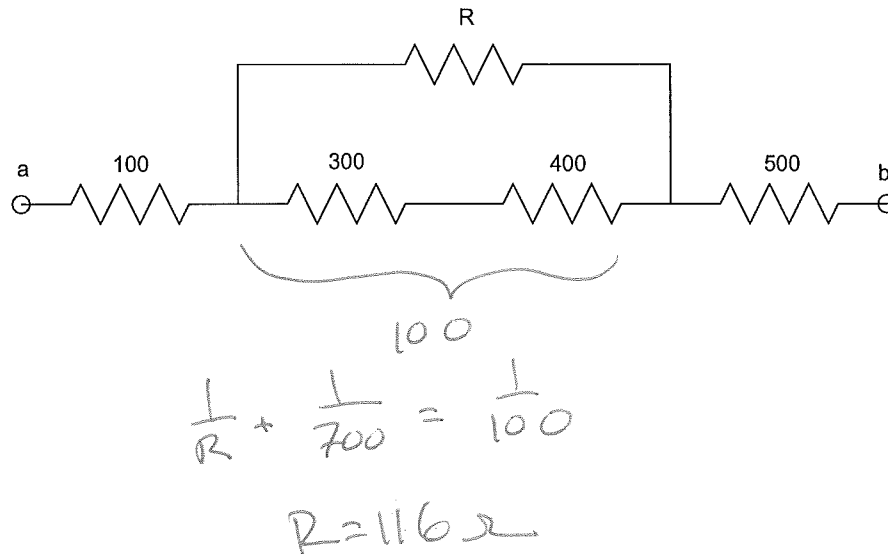

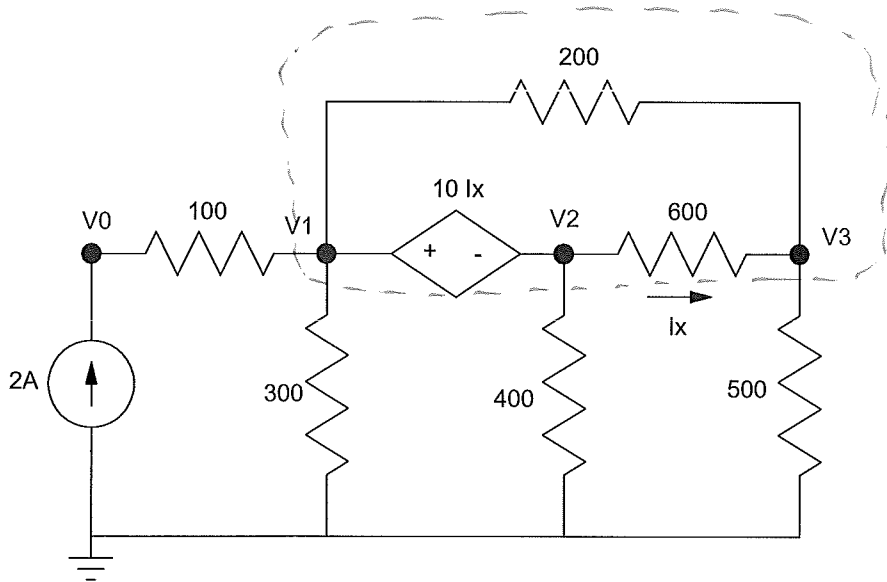2) Write N equations to allow you to solve for the N unknown voltages



$$I_x = \frac{V_2 - V_3}{600}$$

$$V_1 - V_2 = 10 I_x$$

$$-2 + \frac{V_0 - V_1}{100} = 0$$


$$\frac{V_3 - V_1}{200} + \frac{V_3 - V_2}{600} + \frac{V_3}{500} = 0$$

$$\frac{V_1 - V_0}{100} + \frac{V_1}{300} + \frac{V_2}{400} + \frac{V_3}{500} = 0$$

supernode

4pt each
20pt total

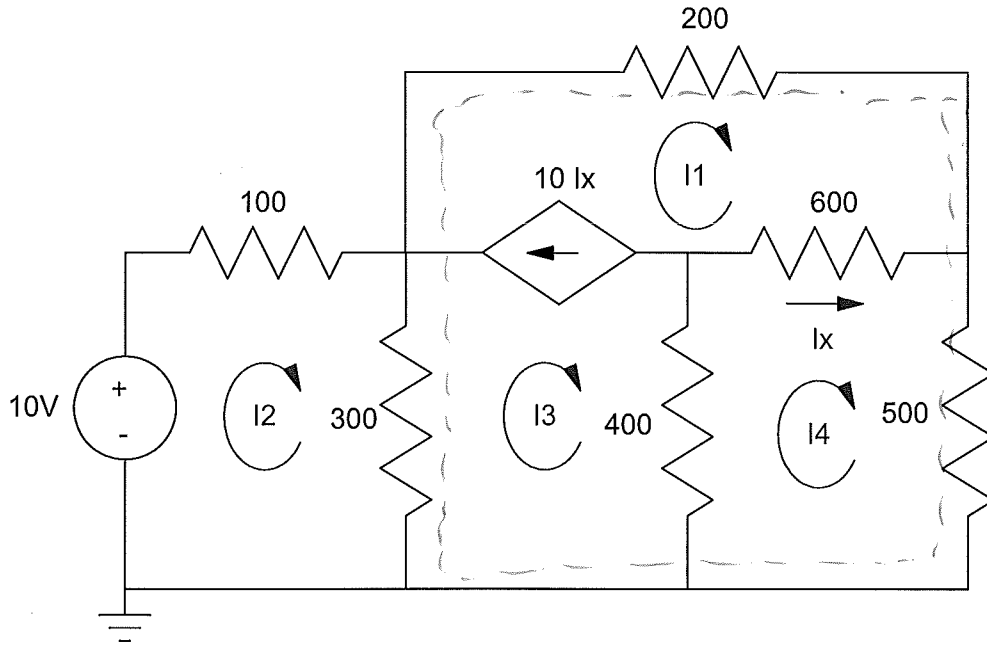3) Write N equations to allow you to solve for the N unknown currents



$$I_x = I_4 - I_1$$

$$I_1 - I_3 = 10 I_x$$

$$-10 + 100 I_2 + 300 (I_2 - I_3) = 0$$


$$400 (I_4 - I_3) + 600 (I_4 - I_1) + 500 I_4 = 0$$

$$300 (I_3 - I_2) + 200 I_1 + 500 I_4 = 0$$

4) For the following circuit, the voltage at V3 is measured as 10V. Determine the voltages V0, V1, V2

(hint: use voltage division)

V0	V1	V2	V3
35.92V	21.11V	13.33V	10.0V

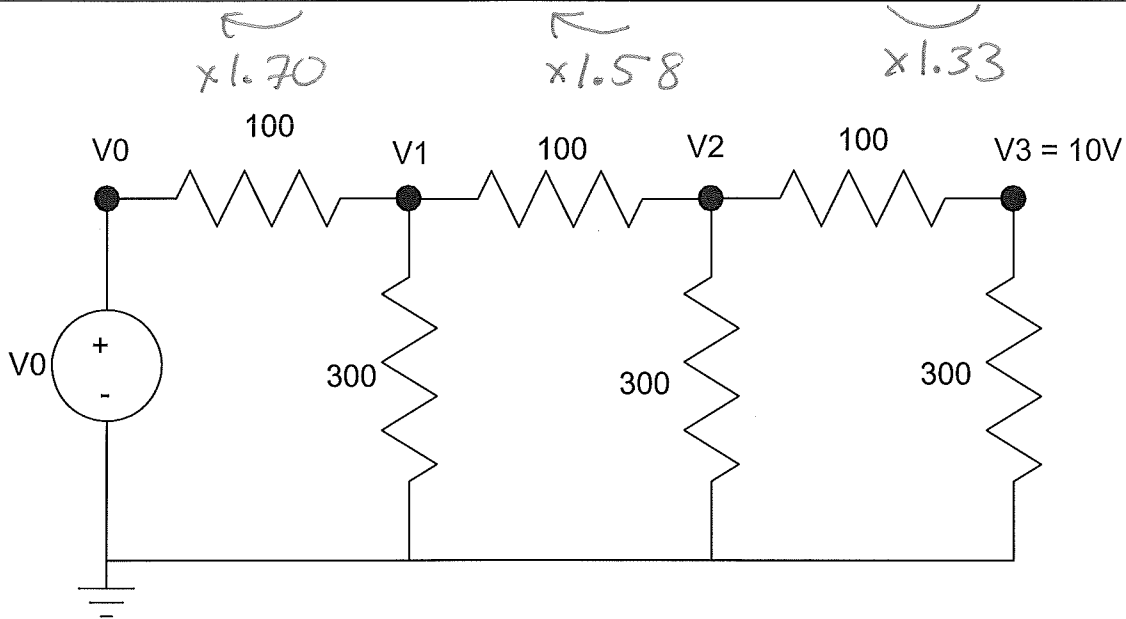

$$V_3 = \left(\frac{300}{300+100} \right) V_2 \Rightarrow V_2 = 13.33V$$

$$V_2 = \left(\frac{400 \parallel 300}{400 \parallel 300 + 100} \right) V_1$$

$$= \left(\frac{171}{171+100} \right) V_1 \Rightarrow V_1 = 21.11V$$

$$V_1 = \left(\frac{271 \parallel 300}{271 \parallel 300 + 100} \right) V_0$$

$$V_1 = \left(\frac{142}{142+100} \right) V_0 \Rightarrow V_0 = 35.92V$$

5) Given the voltages, determine the loop currents


I1	I2	I3	I4
34.6mA 18mA	34.6mA	21.3mA	11.7mA

17.97

34.579

21.226

11.7186

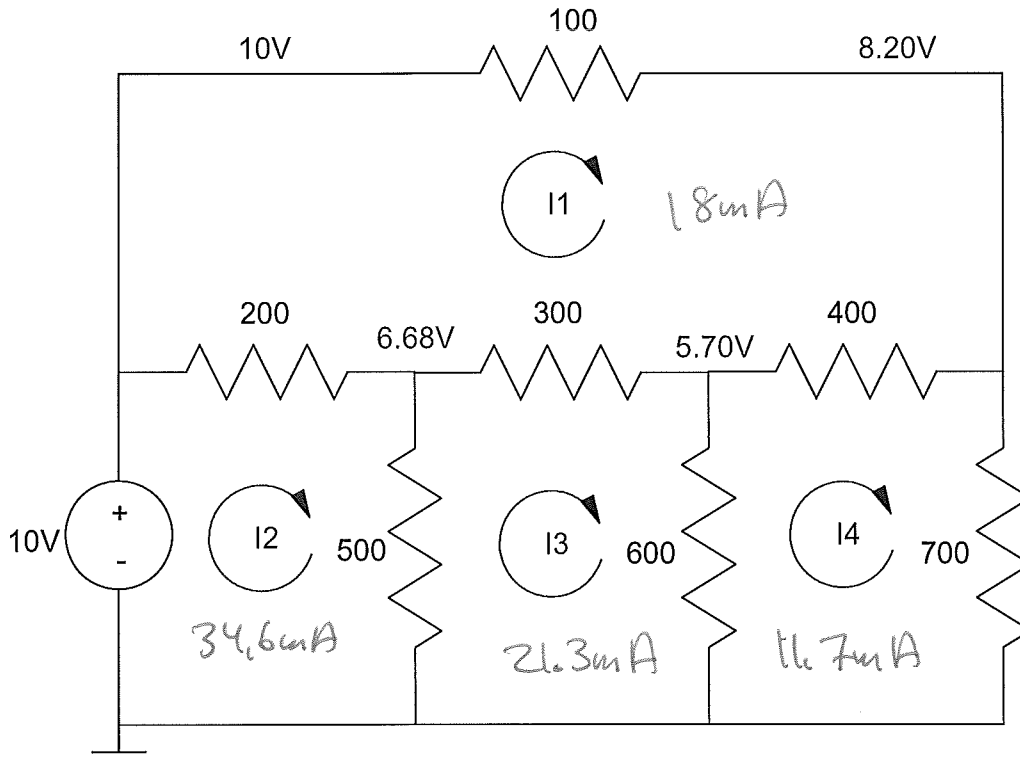

$$I_1 = \frac{10 - 8.2}{100} = 18 \text{ mA}$$

$$I_4 = \frac{8.2}{700} = 11.7 \text{ mA}$$

$$\frac{6.68 - 5.70}{300} = I_3 - I_1 = 3.3 \text{ mA}$$

$$I_3 = I_1 + 3.3 \text{ mA} = 21.3 \text{ mA}$$

Reich: 400
Forbes: 3

Bonus: There are 300 million people in the United States. How many people does it take for their total wealth to equal the total wealth of the poorest 150 million?

$$\frac{10 - 6.68}{200} = I_2 - I_1 = 16.6 \text{ mA}$$

$$I_2 = I_1 + 16.6 \text{ mA} = 34.6 \text{ mA}$$

(Handwritten scribbles)