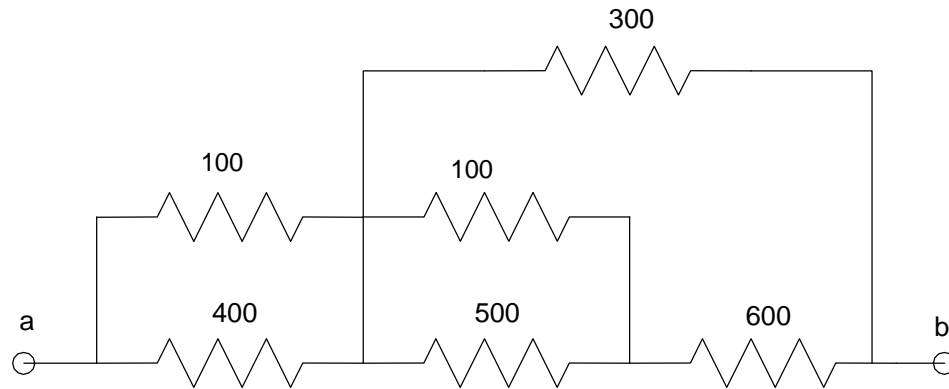


# EE 206 Test #1b - Name \_\_\_\_\_

March 8, 2019

1a) Determine the resistance  $R_{ab}$

$R_{ab} = 288.47$



$$100 \parallel 400 = 80$$


$$100 \parallel 500 = 83.33$$

$$83.33 + 600 = 683.33$$

$$683.33 \parallel 300 = 208.47$$

$$80 + 208.47 = 288.47$$

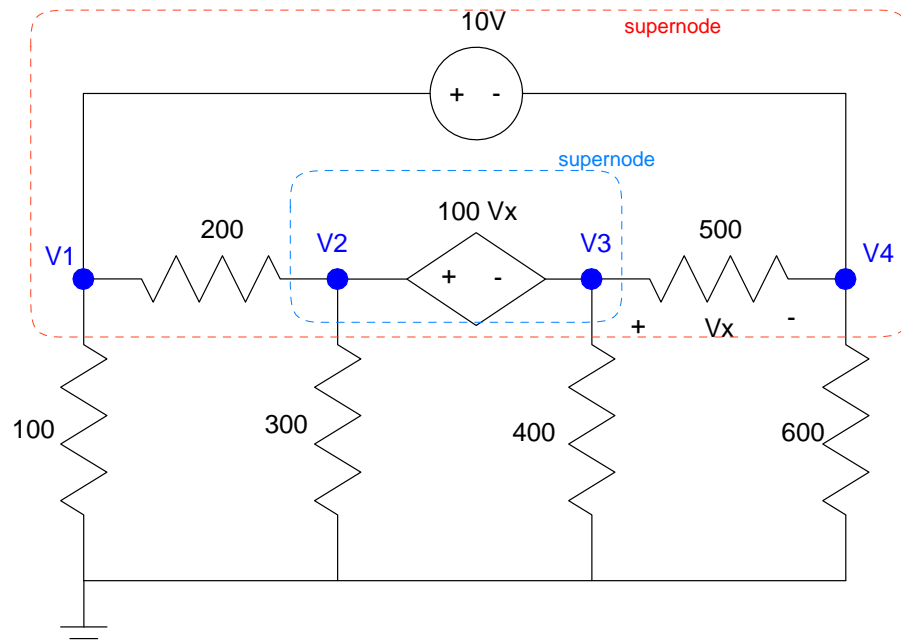2) Write N equations to allow you to solve for the N unknown voltages



$$V_1 - V_4 = 10$$


$$V_2 - V_3 = 100V_x$$

$$V_x = V_3 - V_4$$

$$\left(\frac{V_1}{100}\right) + \left(\frac{V_2}{300}\right) + \left(\frac{V_3}{400}\right) + \left(\frac{V_4}{600}\right) = 0$$

$$\left(\frac{V_2 - V_1}{200}\right) + \left(\frac{V_2}{300}\right) + \left(\frac{V_3}{400}\right) + \left(\frac{V_3 - V_4}{500}\right) = 0$$

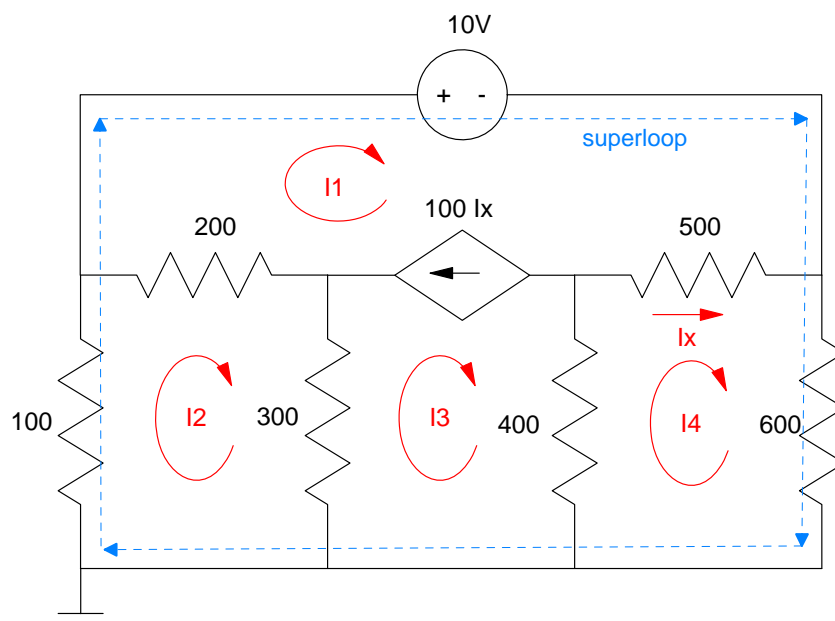3) Write N equations to allow you to solve for the N unknown currents



$$I_x = I_4 - I_1$$

$$100I_x = I_1 - I_3$$

$$100I_2 + 200(I_2 - I_1) + 300(I_2 - I_3) = 0$$


$$400(I_4 - I_3) + 500(I_4 - I_1) + 600I_4 = 0$$

$$100I_2 + 10 + 600I_4 = 0$$

4) For the following circuit, the voltage at V3 is measured as 10V. Determine the voltages V0, V1, V2

(hint: use voltage division)

V0	V1	V2	V3
<b>25.4 V</b>	<b>17.5 V</b>	<b>12.5 V</b>	10.0V

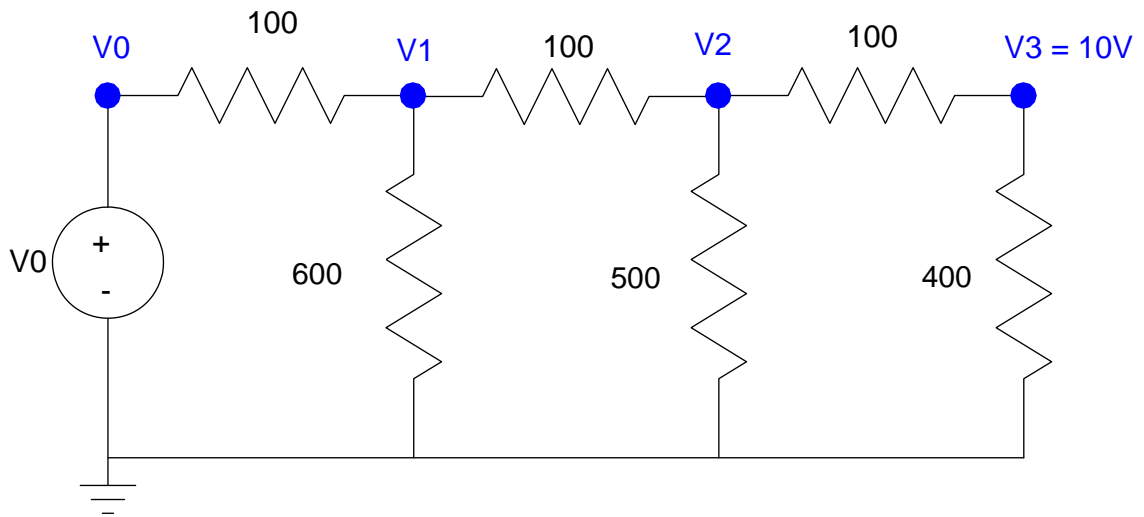

$$V_3 = 10V = \left( \frac{400}{400+100} \right) V_2$$

$$V_2 = \left( \frac{400+100}{400} \right) 10V = 12.5V$$

$$500 \parallel 500 = 250$$

$$V_2 = 12.5V = \left( \frac{250}{250+100} \right) V_1$$

$$V_1 = 17.5V$$


$$350 \parallel 600 = 221$$

$$V_1 = 17.5V = \left( \frac{221}{221+100} \right) V_0$$

$$V_0 = 25.4V$$

5) Given the voltages, determine the loop currents

I1	I2	I3	I4	I5
<b>97mA</b>	<b>97mA</b>	<b>194mA</b>	<b>71mA</b>	<b>53mA</b>

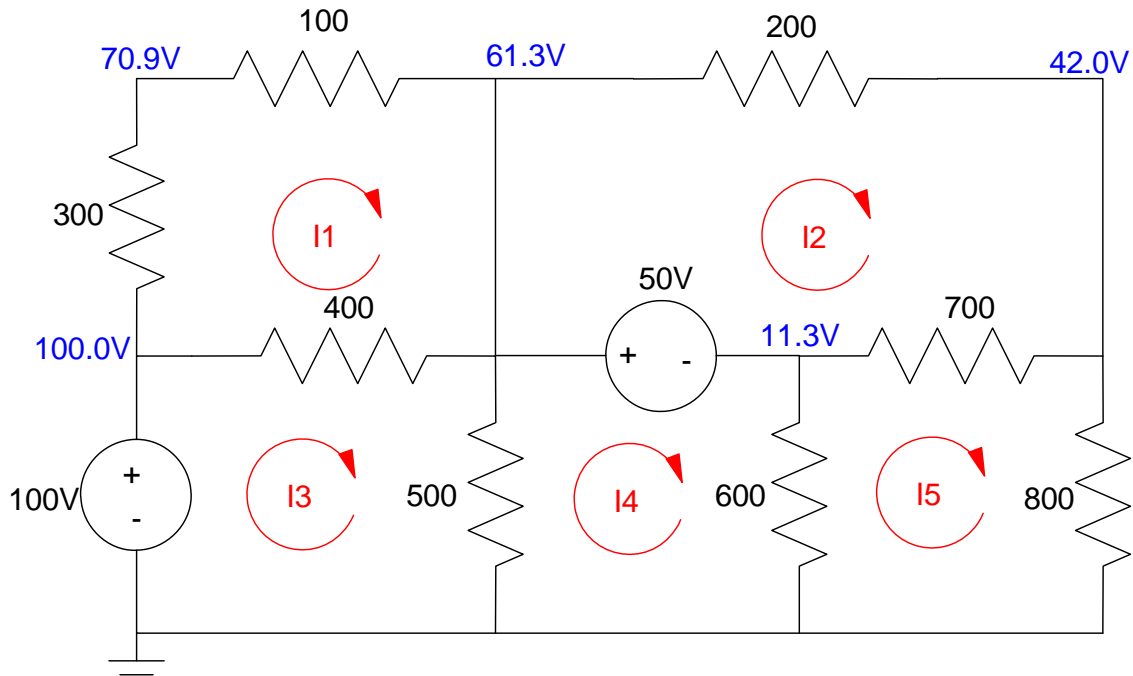

$$I_1 = \left( \frac{100V - 70.9V}{300\Omega} \right) = 97mA$$

$$I_2 = \left( \frac{61.3V - 42.0V}{200\Omega} \right) = 97mA$$

$$I_5 = \left( \frac{42.0V - 0V}{800\Omega} \right) = 53mA$$

$$I_4 - I_5 = \left( \frac{11.3V}{600\Omega} \right) = 19mA$$

$$I_4 = 19mA + I_5 = 71mA$$

$$I_3 - I_1 = \left( \frac{100V - 63.3V}{400\Omega} \right) = 97mA$$

$$I_3 = I_1 + 97mA = 194mA$$