
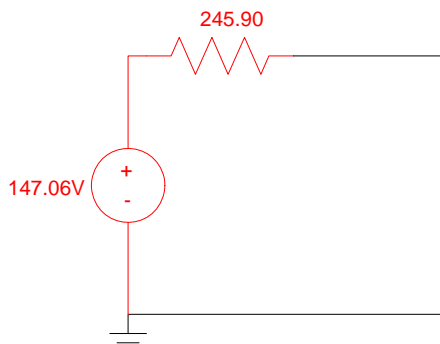
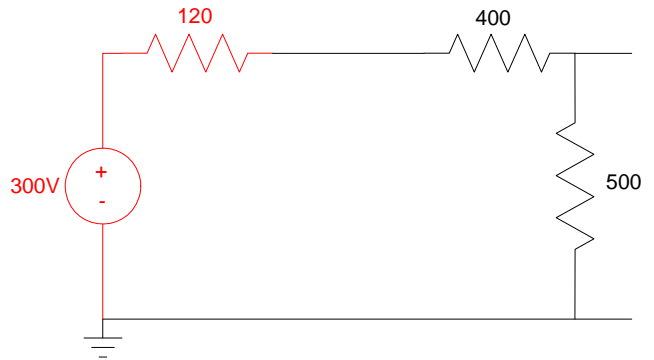
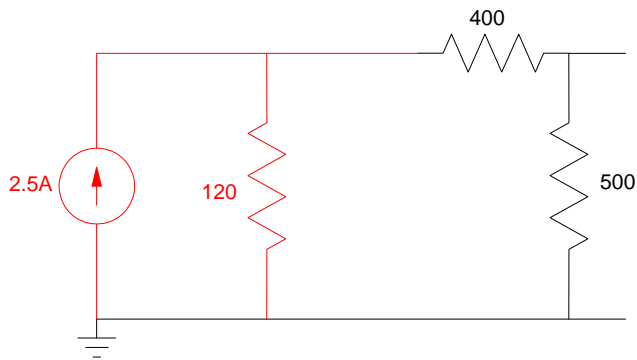
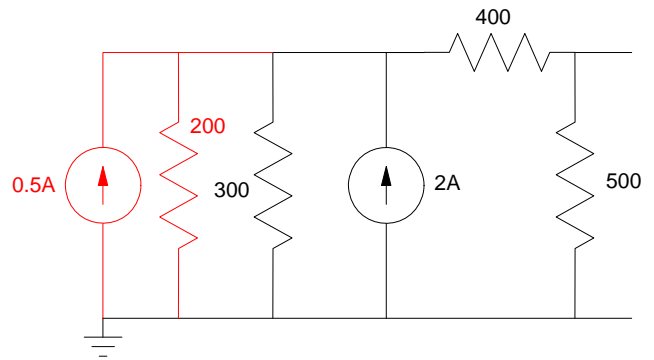


EE 206 Test #2 - Name _____

Thevenin Equivalents - Max Power Transfer - Superposition - Operational Amplifiers. March 8, 2019


1) Determine the Thevenin equivalent for the following circuit.

Vth	Rth
147.06 V	245.90 Ohms

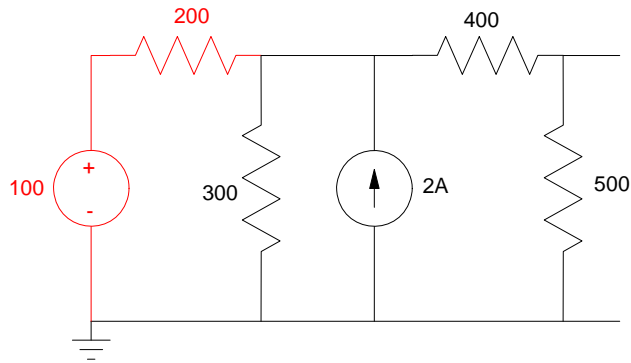

2) Determine the Thevenin equivalent for the following circuit

Vth	Rth
11.45 V	22.9 Ohms

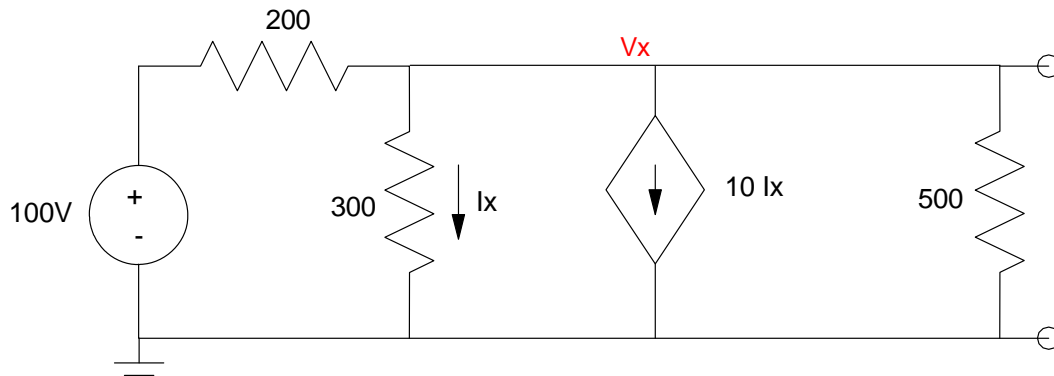


Vth: (red) Measure the open-circuit voltage (V_x)

$$I_x = \left(\frac{V_x}{300} \right)$$

$$\left(\frac{V_x - 100}{200} \right) + \left(\frac{V_x}{300} \right) + 10 \left(\frac{V_x}{300} \right) + \left(\frac{V_x}{500} \right) = 0$$

$$V_x = 11.45V$$

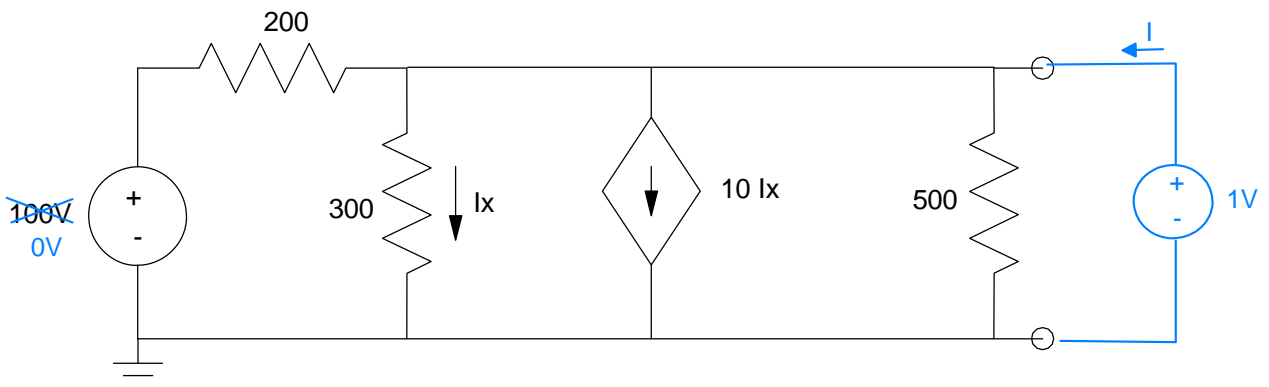


Rth: (blue) Set the voltages and currents to zero. Apply a 1V test voltage and compute the current it draws

$$I = \left(\frac{1V}{200\Omega} \right) + \left(\frac{1V}{300\Omega} \right) + 10 \left(\frac{1V}{300\Omega} \right) + \left(\frac{1V}{500\Omega} \right) = 44mA$$

$$R_{th} = \left(\frac{V}{I} \right) = \left(\frac{1V}{44mA} \right) = 22.9\Omega$$

3) The voltage and current for a circuit is measured as the resistance changes.

R	infinity	100 Ohms	25 Ohms	0 Ohms
V	15V	10V	5V	0V
I	0mA	100mA	200mA	300mA

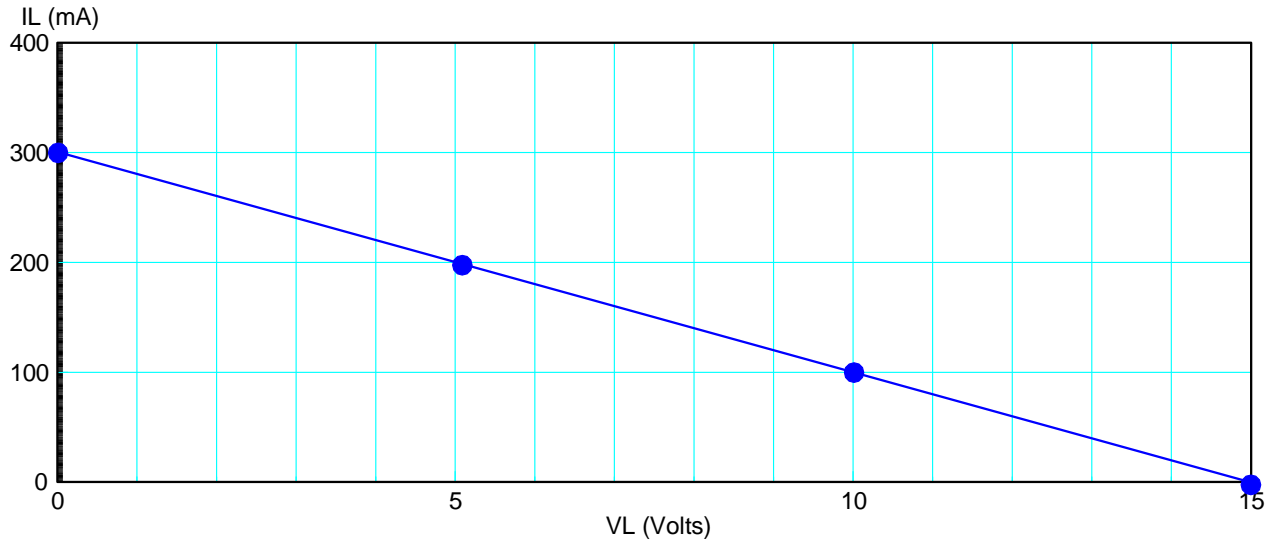

From this data, determine the Thevenin equivalent and the maximum power you can get out of this circuit.

V _{th}	R _{th}	R for maximum power transfer	Max power to R
15 V	50 Ohms	50 Ohms	1.125 W

The voltage is

$$V = \left(\frac{R}{R+R_{th}} \right) V_{th}$$

When R = infinity, V = V_{th} = 15V

When R = 0

$$I = \left(\frac{V_{th}}{R_{th}} \right) = 300mA$$


$$R_{th} = 50\Omega$$

max power transfer is when R = R_{th}

At R = R_{th}

$$V = 7.5V$$

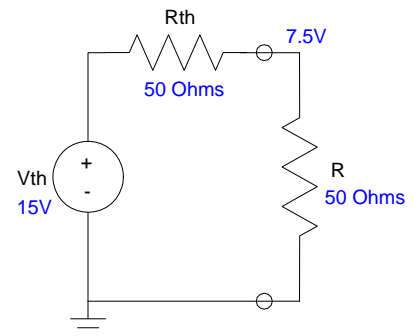
$$P = \left(\frac{V^2}{R} \right) = \left(\frac{7.5^2}{50} \right) = 1.125W$$



4) Find the voltage at Y as a function of A and B

$$Y = aA + bB + c$$

a	b	c
0.48	0.24	1.6

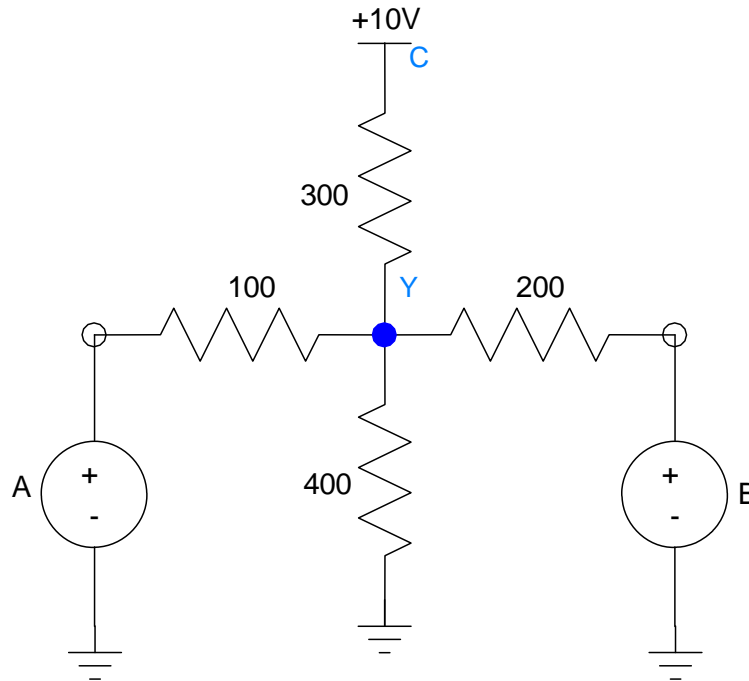

Using superposition

$$A = A, B = C = 0$$

$$Y = \left(\frac{300 \parallel 200 \parallel 400}{300 \parallel 200 \parallel 400 + 100} \right) A$$

$$Y = \left(\frac{92.31}{92.31 + 100} \right) A$$

$$Y = 0.48A$$

$$B = B, A = C = 0$$

$$Y = \left(\frac{100 \parallel 300 \parallel 400}{100 \parallel 300 \parallel 400 + 200} \right) B$$

$$Y = \left(\frac{63.15}{63.15 + 200} \right) B$$

$$Y = 0.24B$$

$$C = 10, A = B = 0.$$

$$Y = \left(\frac{100 \parallel 200 \parallel 400}{100 \parallel 200 \parallel 400 + 300} \right) 10$$

$$Y = \left(\frac{57.14}{57.14 + 300} \right) 10$$

$$Y = 1.6$$

Method #2: Voltage Nodes


$$\left(\frac{Y-A}{100} \right) + \left(\frac{Y}{400} \right) + \left(\frac{Y-B}{200} \right) + \left(\frac{Y-10}{300} \right) = 0$$

$$\left(\frac{1}{100} + \frac{1}{400} + \frac{1}{200} + \frac{1}{300} \right) Y = \left(\frac{1}{100} \right) A + \left(\frac{1}{200} \right) B + \left(\frac{10}{300} \right)$$

$$Y = 0.48A + 0.24B + 1.6$$

5) Determine the voltages V1, V2, V3, V4. Assume ideal op-amps.

V1	V2	V3	V4
3.14V	2.86V	2.86V	-8.57V

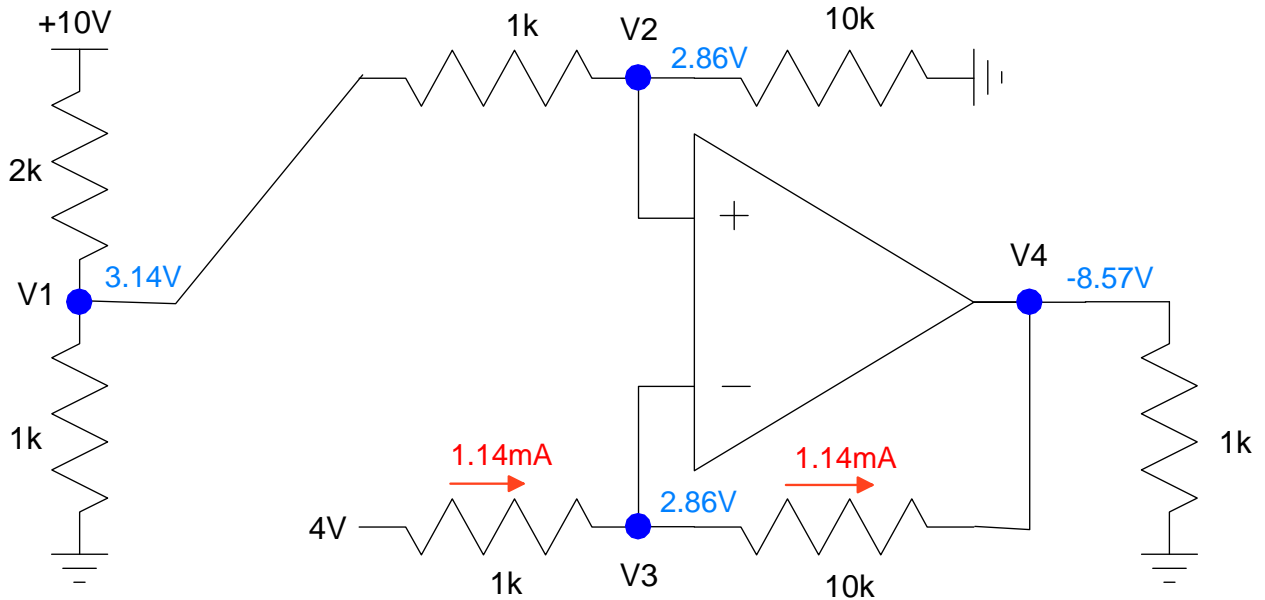

Use voltage division for V1

$$1k \parallel 11k = 916.67$$

$$V_1 = \left(\frac{916.67}{916.67 + 2000} \right) 10V = 3.14V$$

$$V_2 = \left(\frac{10k}{10k + 1k} \right) V_1 = 2.86V$$

$$V_3 = V_2 = 2.86V$$

$$I = \left(\frac{4V - 2.86V}{1k} \right) = 1.14mA$$

$$V_4 = V_3 - 10k \cdot 1.14mA$$

$$V_4 = -8.57V$$

or

$$V_4 = \left(\frac{10k}{1k} \right) (V_1 - 4V)$$

Bonus! Wealth inequality exists in the United State: presently, 3 families own over half of the wealth of the country.

Is wealth inequality a good thing or a bad thing? Explain.

Good:

- People need incentives to work
- If you want to start a company, it's much easier to go to a few people with lots of extra money than it is to go to a lot of people with a few extra dollars.
- To make progress, you *need* to have a surplus. Concentrating the wealth makes sure someone has more than they need.

Bad

- If you concentrate the wealth, public policy will favor the few rather than the many.
- If you concentrate the wealth, you also concentrate opportunities. The country is no longer a meritocracy.
- Too much inequality is harmful to the economy. 70% of our economy is based upon consumption. For our economy to work, people have to have money to buy things.

Example: Which has a greater impact on the economy

- One person making \$50 million per year
- 1000 people making \$50,000 per year?

1000 People will

- Buy 1000 houses, employing construction workers
- Buy 1000 cars, employing workers in the auto industry
- Have 1000 kids who go to school, employing teachers
- Make 1000 meals each day, employing farmers, grocers, truckers,
- etc

The ultra-rich are actually job killers, not job creators.