

EE 206: Homework #7

Op Amp Amplifiers. Due Monday, March 9th

Please make the subject "EE 206 HW#7" if submitting homework electronically to Jacob_Glower@yahoo.com (or on blackboard)

1) Design an op-amp circuit to implement

$$Y = 4X$$

Simulate this circuit in PartSim with

- $x(t) = 1V_p, 1kHz$ sine wave

Is Y four times X?

2) Design an op-amp circuit to implement

$$Y = -4X$$

Simulate this circuit in PartSim with

- $x(t) = 1V_p, 1kHz$ sine wave

Is Y four times X and 180 degrees out of phase?

3) Design an op-amp circuit to implement

$$Y = 4X - 10$$

4) Design an op-amp circuit which outputs

- $-10V$ when $R = 1000$ Ohms
- $+10V$ when $R = 1200$ Ohms

5) Simulate the circuit for problem #4. Plot the output voltage for $1000 < R < 1200$ Ohms

R	Vout		
	Calculated prob 4 - ignoring loading	Calculated including loading	Simulated prob 5
1000			
1050			
1100			
1150			
1200			