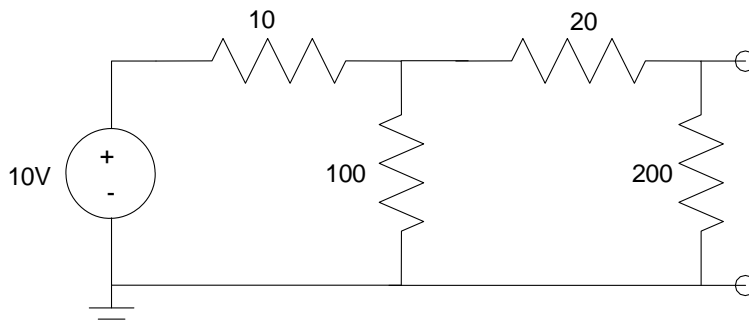


EE 206: Homework #5 Solution

Thevenin Equivalents, Maximum Power Transfer. Due Wed, Feb 24th

Thevenin Equivalents





1) Find the Thevenin equivalent for the following circuit by transforming between Thevenin and Norton equivalents:



Switch back and forth between Thevenin and Norton equivalents

$$I_n R_n = V_{th}$$


$$R_{th} = R_n$$

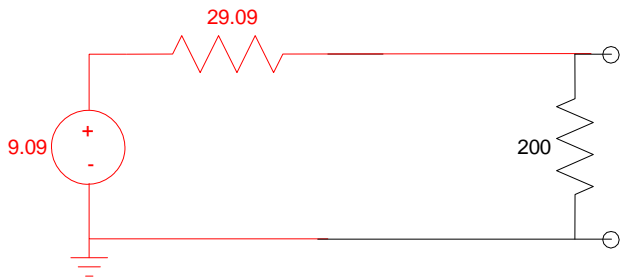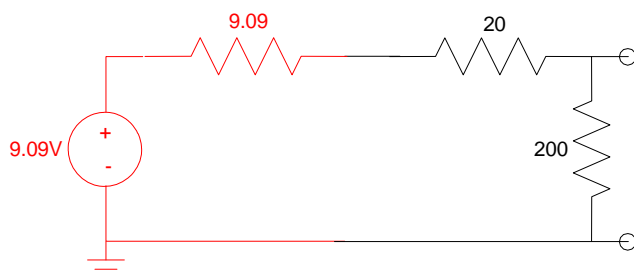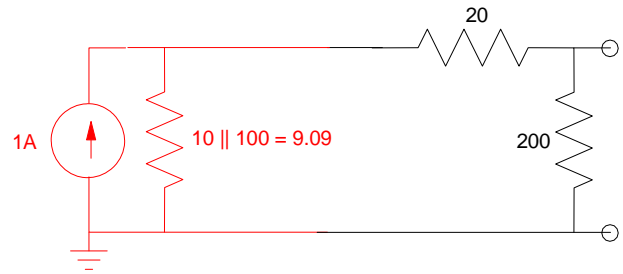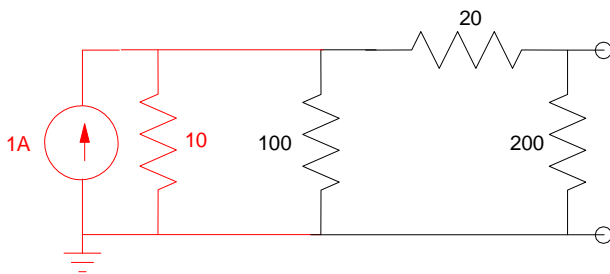





At this point we know the answer:





$$R_{th} = 200 \parallel 29.09 = 25.39\Omega$$
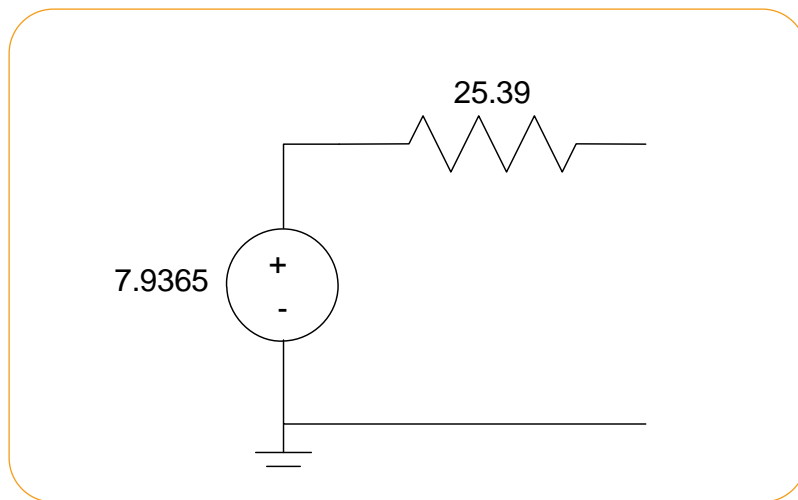
$$V_{th} = \left(\frac{200}{200+29.09} \right) \cdot 9.09V = 7.9365V$$




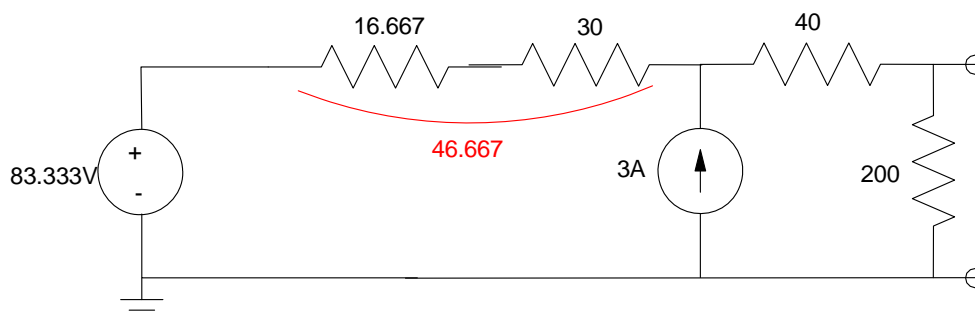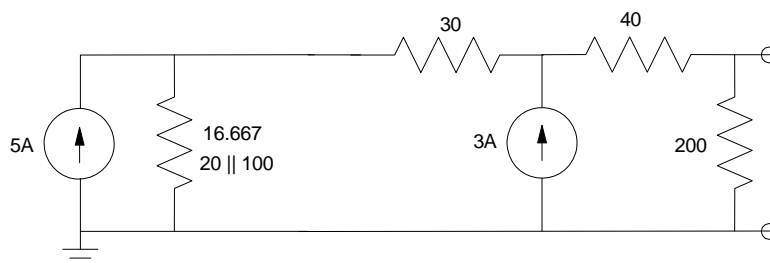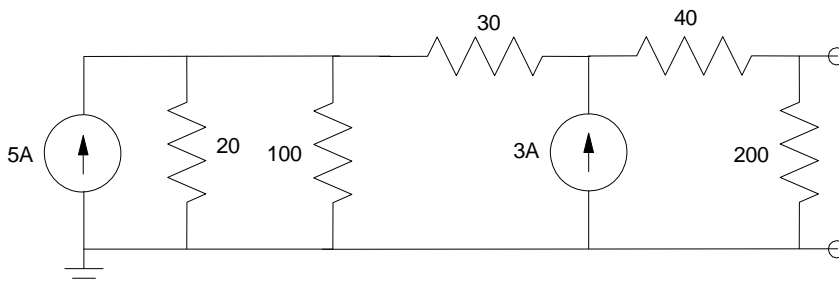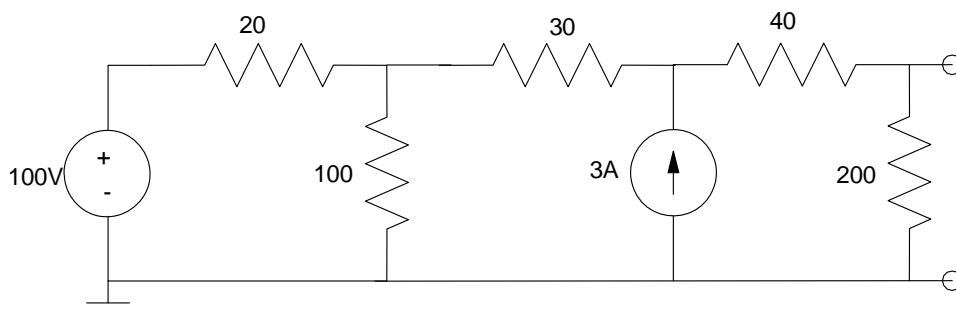2) Find the Thevenin equivalent for the following circuit by transforming between Thevenin and Norton equivalents:



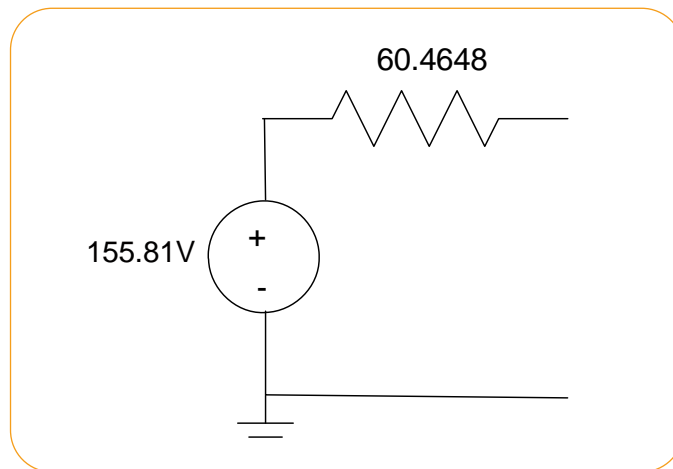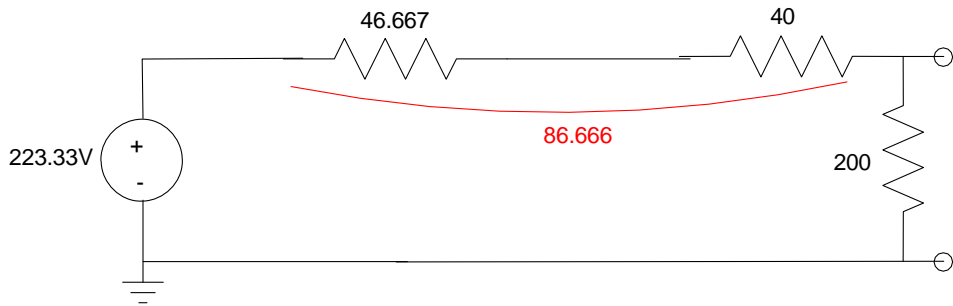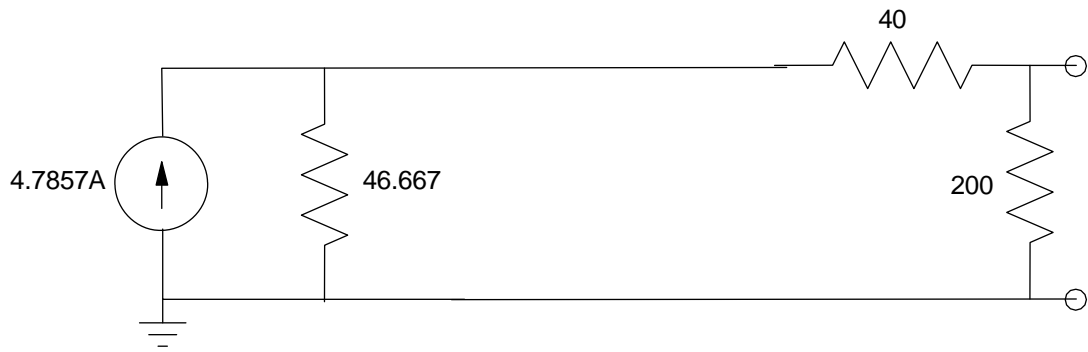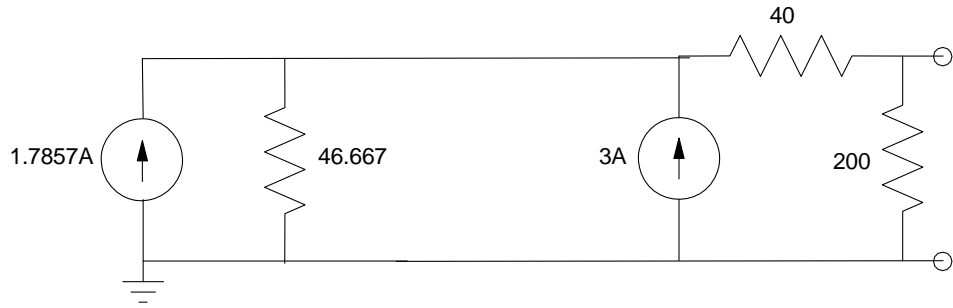

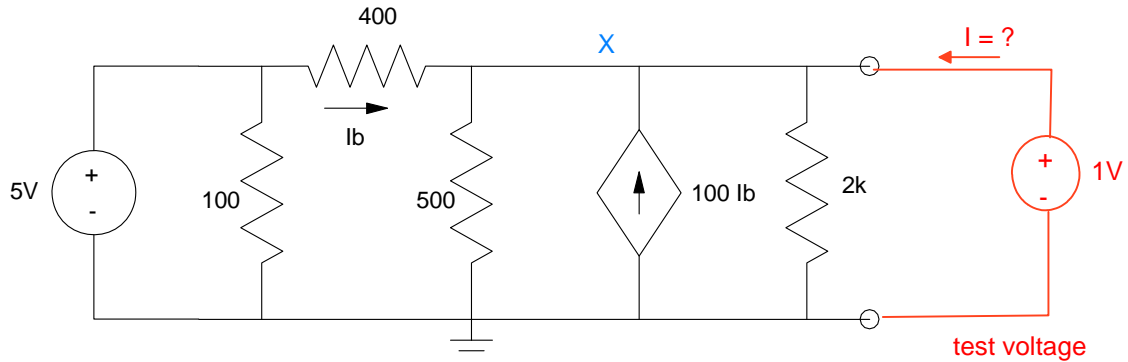3) Find the Thevenin equivalent for the following circuit:



Find the open-circuit voltage

$$\left(\frac{X-5}{400}\right) + \left(\frac{X}{500}\right) - 100\left(\frac{5-X}{400}\right) + \left(\frac{X}{2000}\right) = 0$$


$$X = 4.951V$$

Turn off the power supplies (5V goes to 0V). Measure the resistance at the output.


This isn't obvious, so add a 1V test voltage and compute the current

$$I = \left(\frac{1V}{400\Omega}\right) + \left(\frac{1V}{500\Omega}\right) + 100\left(\frac{1V}{400\Omega}\right) + \left(\frac{1V}{2000\Omega}\right) = 255mA$$
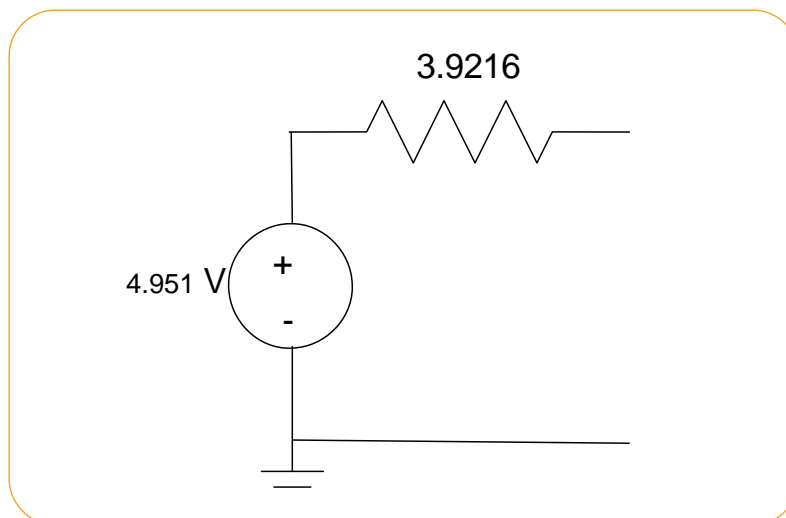
$$R_{th} = \frac{1V}{255mA} = 3.9216\Omega$$



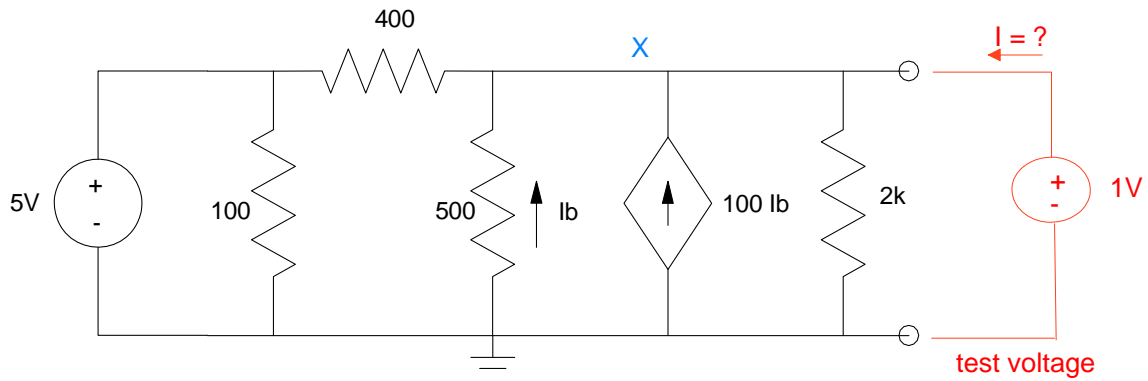4) Find the Thevenin equivalent for the following circuit:



Compute the open-circuit voltage (write the voltage node equation at X)

$$\left(\frac{X-5}{400}\right) + \left(\frac{X}{500}\right) - 100\left(\frac{0-X}{500}\right) + \left(\frac{X}{2000}\right) = 0$$

$$X = 0.06097V$$


Turn off the power supply (5V becomes 0V). Compute the resistance looking in.

This isn't obvious, so add a test voltage and compute the current

$$I = \left(\frac{1}{400}\right) + \left(\frac{1}{500}\right) - 100\left(\frac{0-1}{500}\right) + \left(\frac{1}{2000}\right)$$


$$I = 205mA$$

$$R = \frac{1V}{205mA} = 4.878\Omega$$

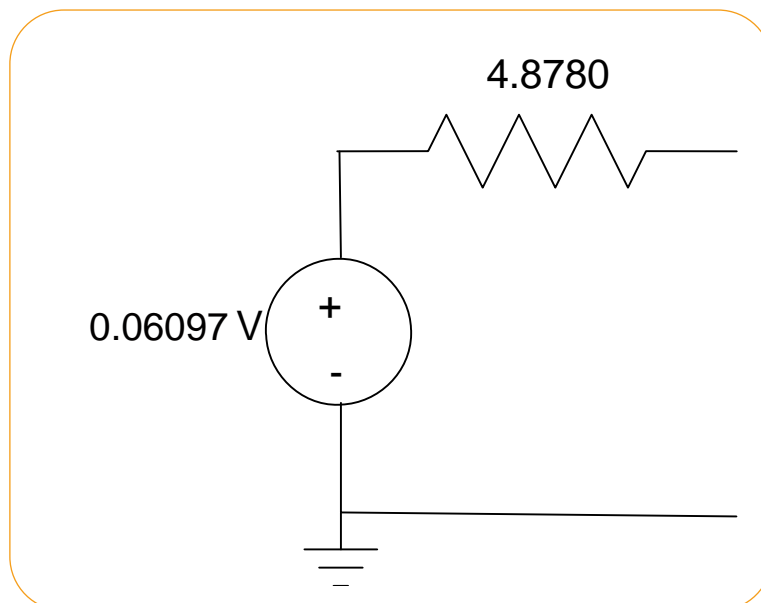


Maximum Power Transfer

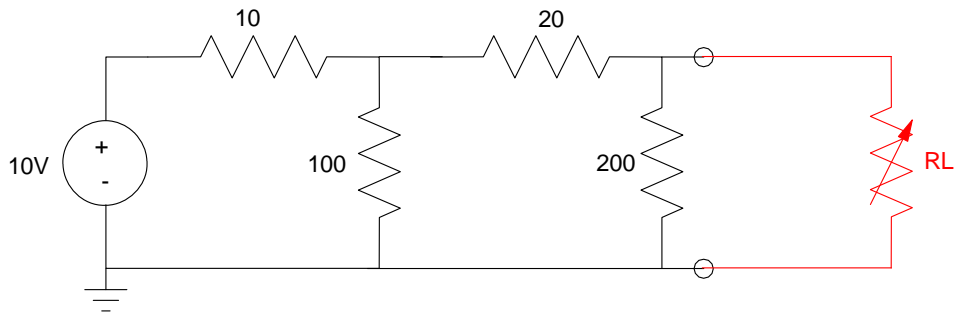5) Determine R_L so that the maximum power is delivered to the load (R_L)



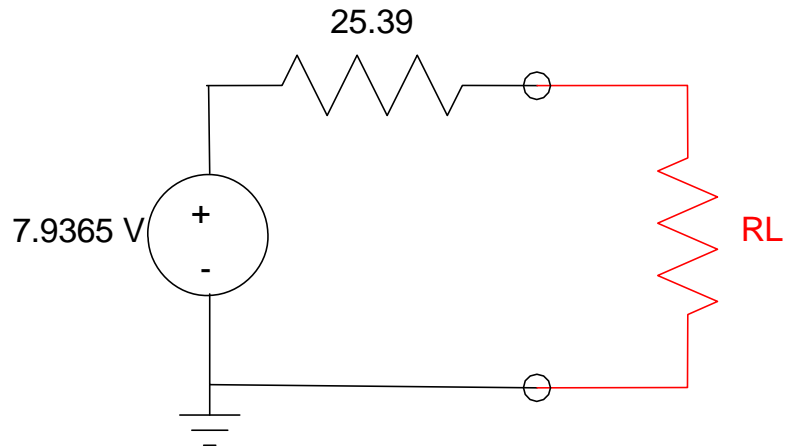Take the Thevenin equivalent of this circuit (problem #1)



Maximum power transfer is when $R_L = R_{th}$

answer: **$R_L = 25.39$ Ohms**

PartSim

6) Simulate the circuit of problem 5. Determine the voltage and current at the load

You can also use the Thevenin equivalent from problem #5:

| | V | I | Power |
|------------------------|---------|--------|--------|
| R = 0 | 0 V | 313mA | 0 mW |
| R = 10 | 2.243 V | 224mA | 503mW |
| R = 25.39 max power | 3.968 V | 156 mA | 620 mW |
| R = 50 | 5.264 V | 105 mA | 554 mW |
| R = 100 | 6.329 V | 63 mA | 401 mW |
| R = infinite | 7.936 V | 0 mA | 0 mW |

Note:

$$V = \left(\frac{R_L}{R_L + 25.39\Omega} \right) 7.9365V$$

$$I = \left(\frac{7.9365V}{R_L + 25.39\Omega} \right)$$

$$P = VI$$

7) Plot V vs. I on a graph and draw a line between these points. How does this line relate to the Thevenin equivalent for circuit #5?

- The y-axis intercept is $I(Norton)$
- The x axis intercept is $V(Thevenin)$
- The slope is $-1/R$ (25.39 Volts / Amp)

