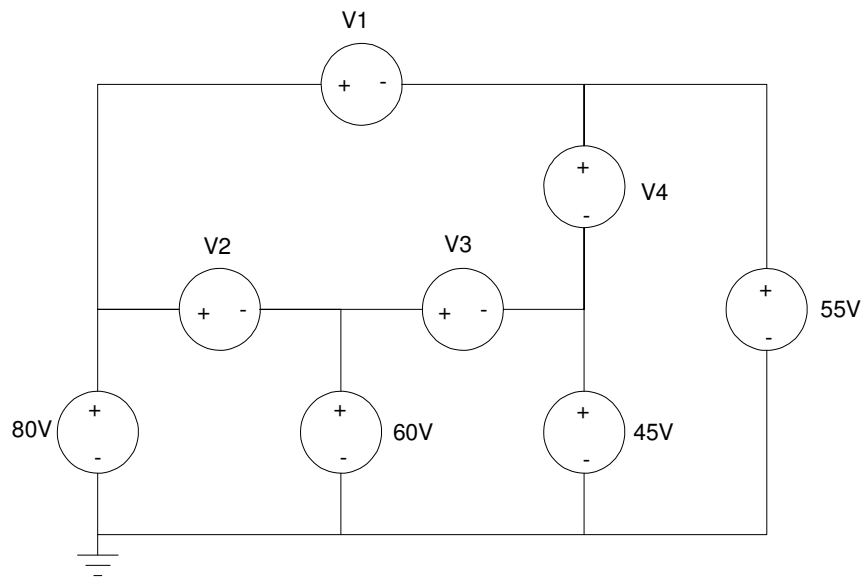


EE 206 Test #1 - Name _____

February 19, 2020


1) Kirchoff's Laws. Determine the unknown voltages

V1	V2	V3	V4




Determine the unknown currents

I1	I2	I3	I4

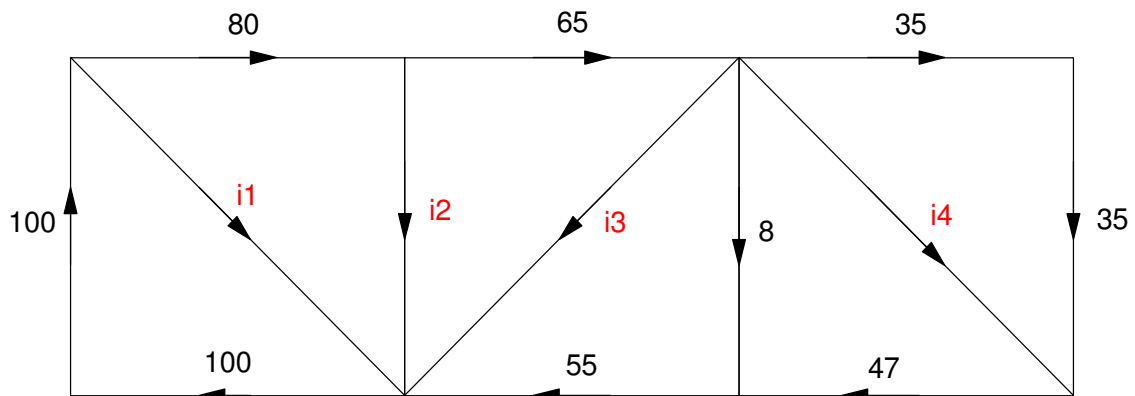


2) Determine the resistance R_{ab}

$R_{ab} =$

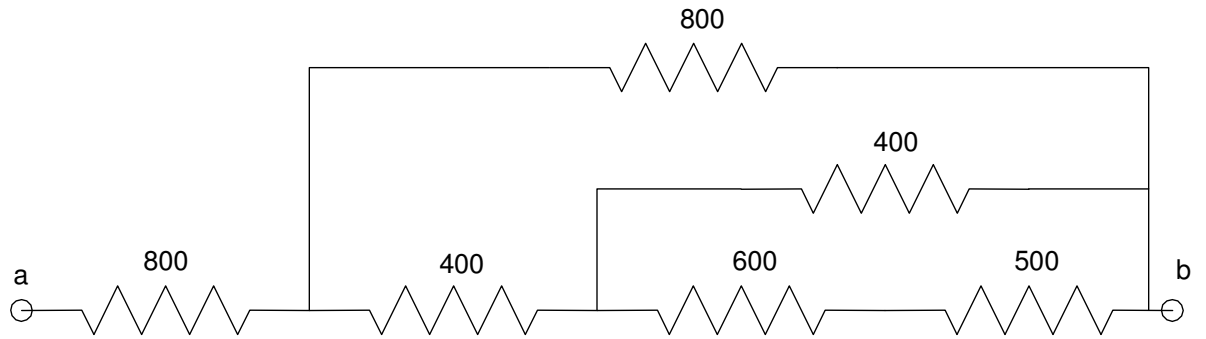


3) Voltage Division. Use voltage division to determine the voltages V_1 .. V_3

V_0	V_1	V_2	V_3

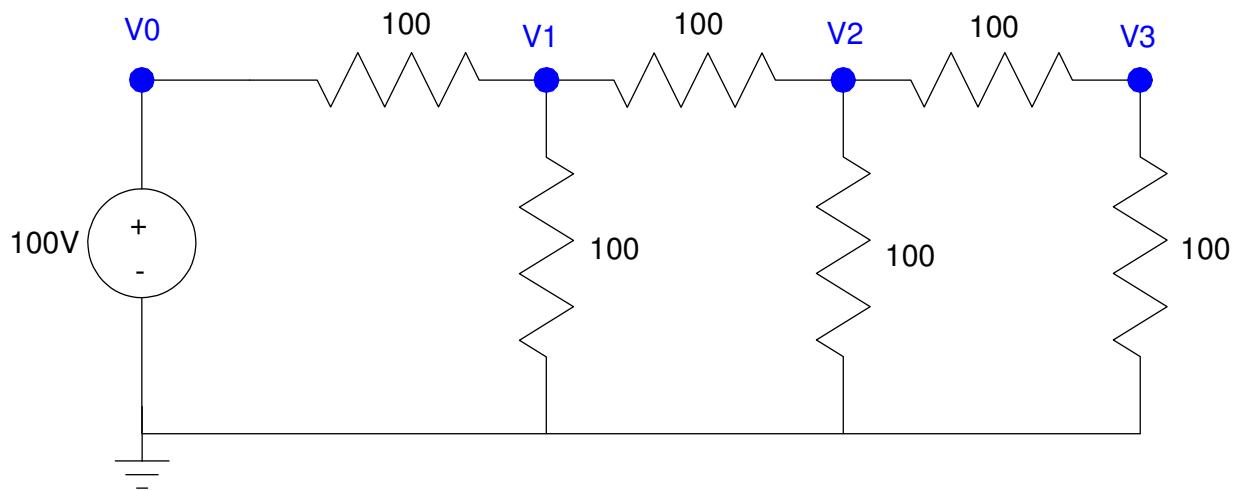


4) Current Division. Determine the currents $I_1 .. I_4$


I_1	I_2	I_3	I_4

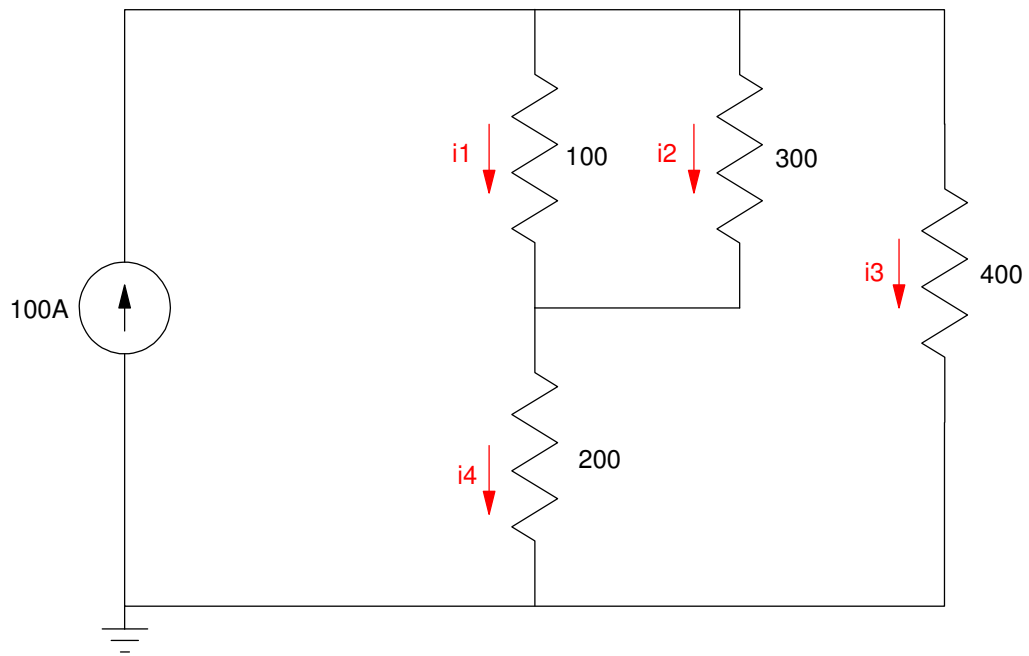

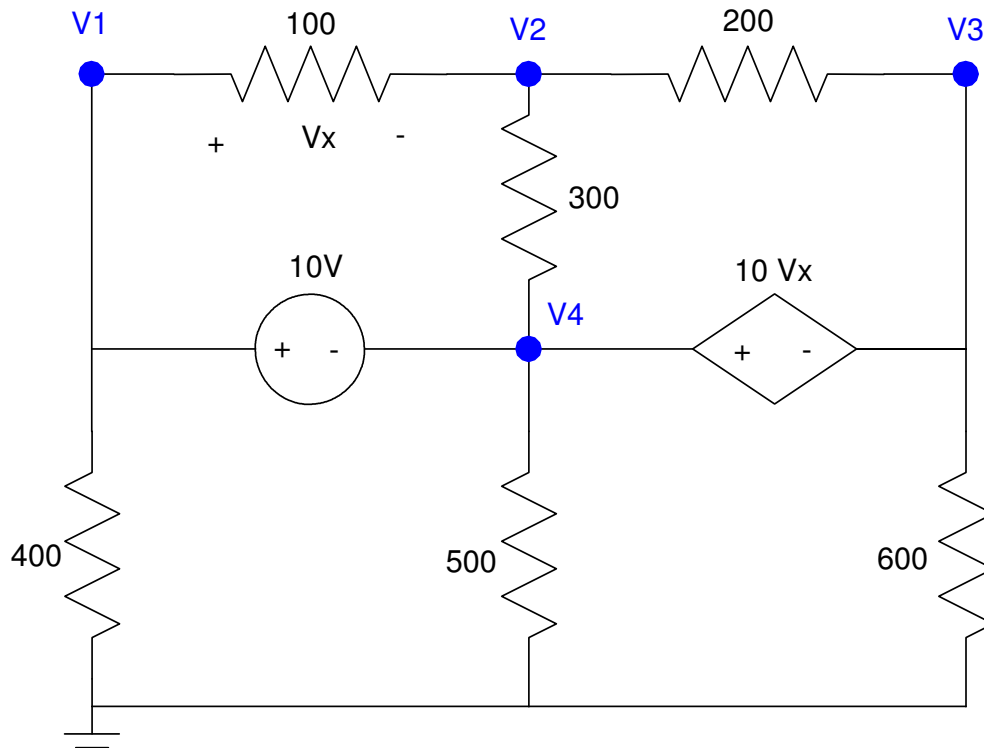5) Voltage Nodes: Write 5 equations to solve for the 5 unknowns.




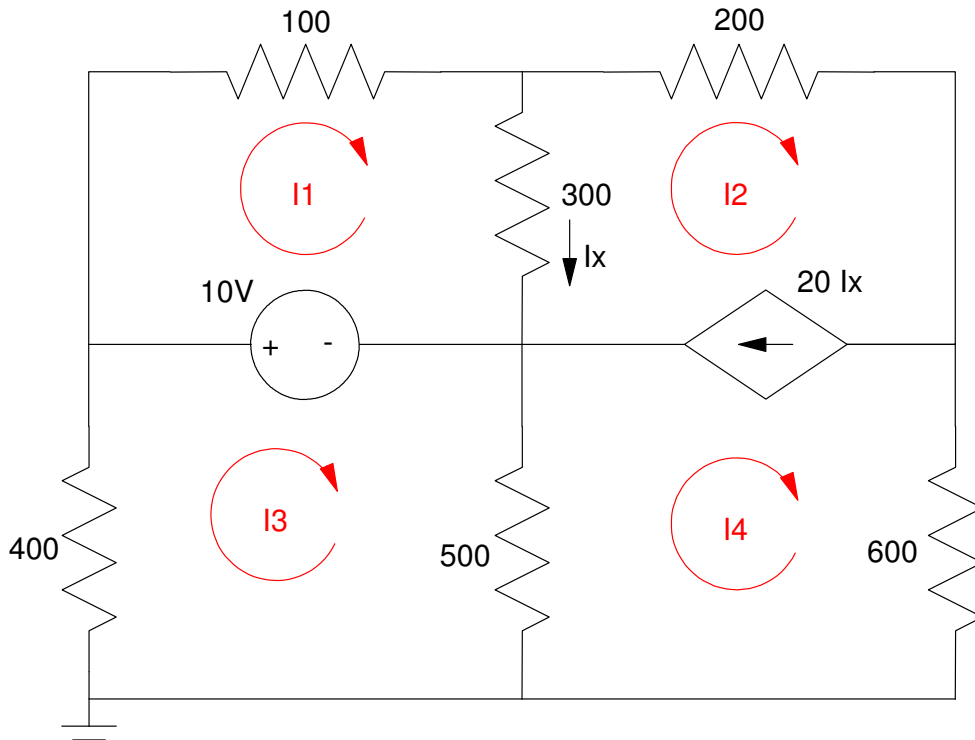6) Current Loops. Write 5 equations to solve for 5 unknowns




Green New Deal Bonus! Project Tundra is a \$75 million project to capture the CO₂ emissions from a coal plant and store it underground. How much CO₂ does a 100MW coal plant produce in one year? (in cubic meters)

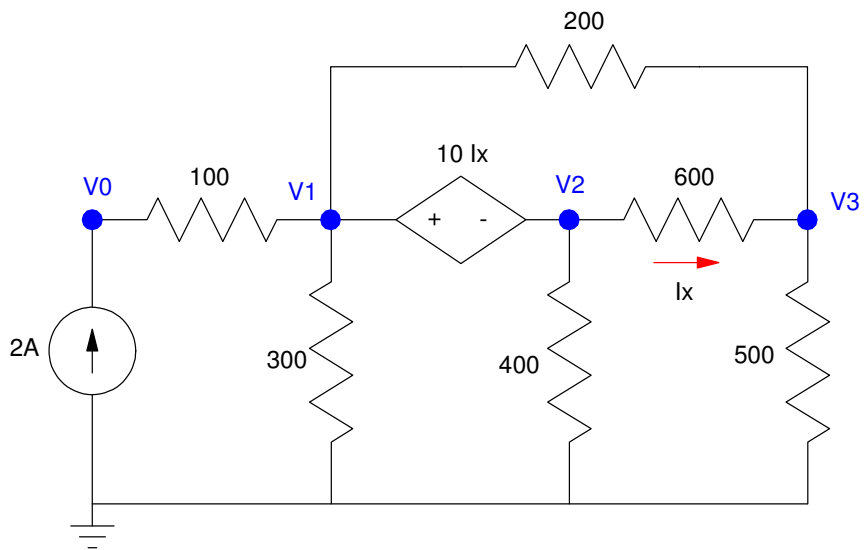2) Write N equations to allow you to solve for the N unknown voltages



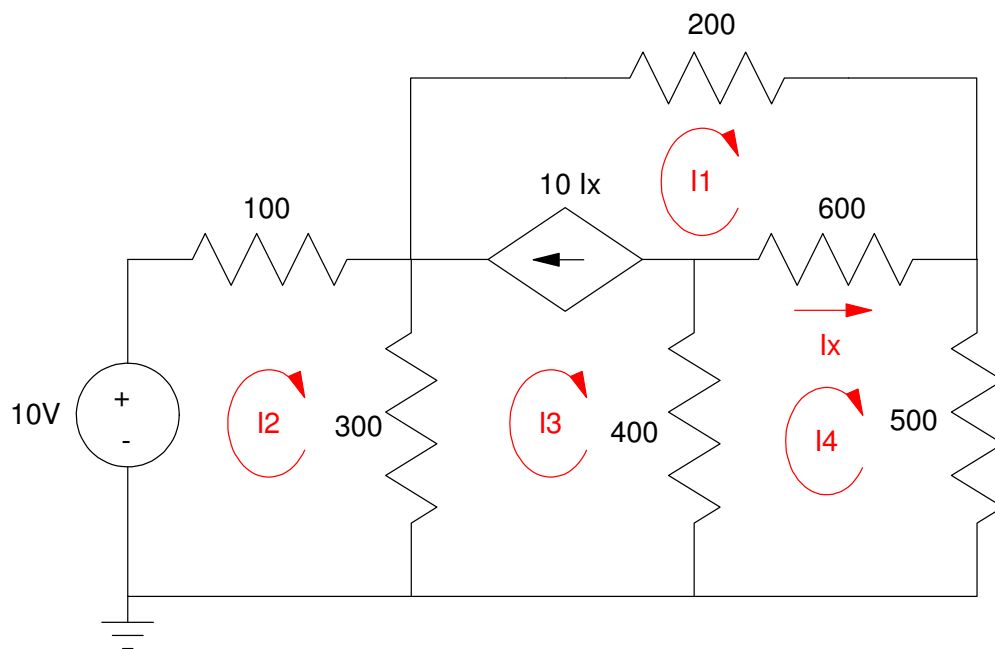
3) Write N equations to allow you to solve for the N unknown currents



4) For the following circuit, the voltage at V3 is measured as 10V. Determine the voltages V0, V1, V2


(hint: use voltage division)

V0	V1	V2	V3
			10.0V

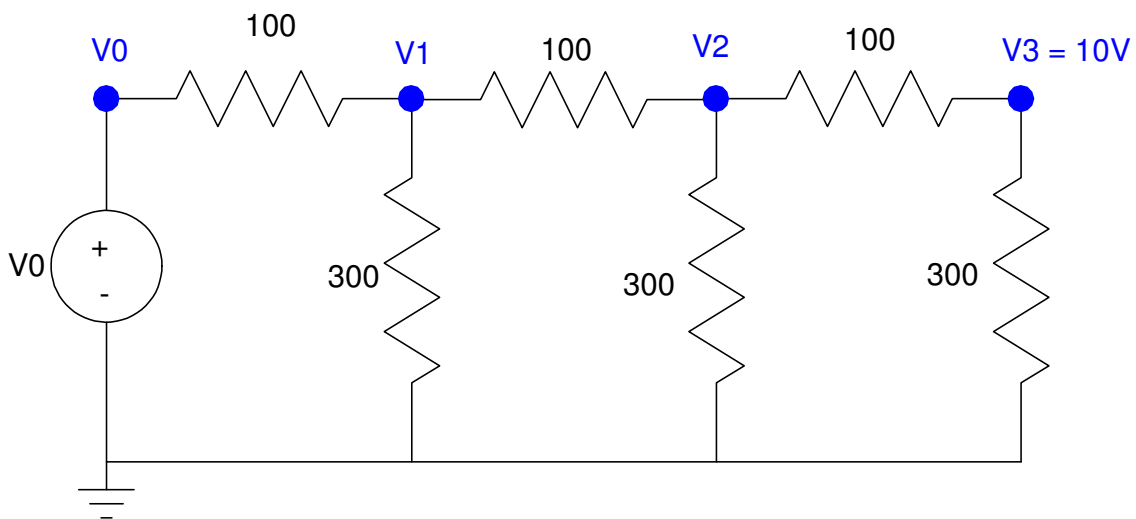

5) Given the voltages, determine the loop currents

I1	I2	I3	I4

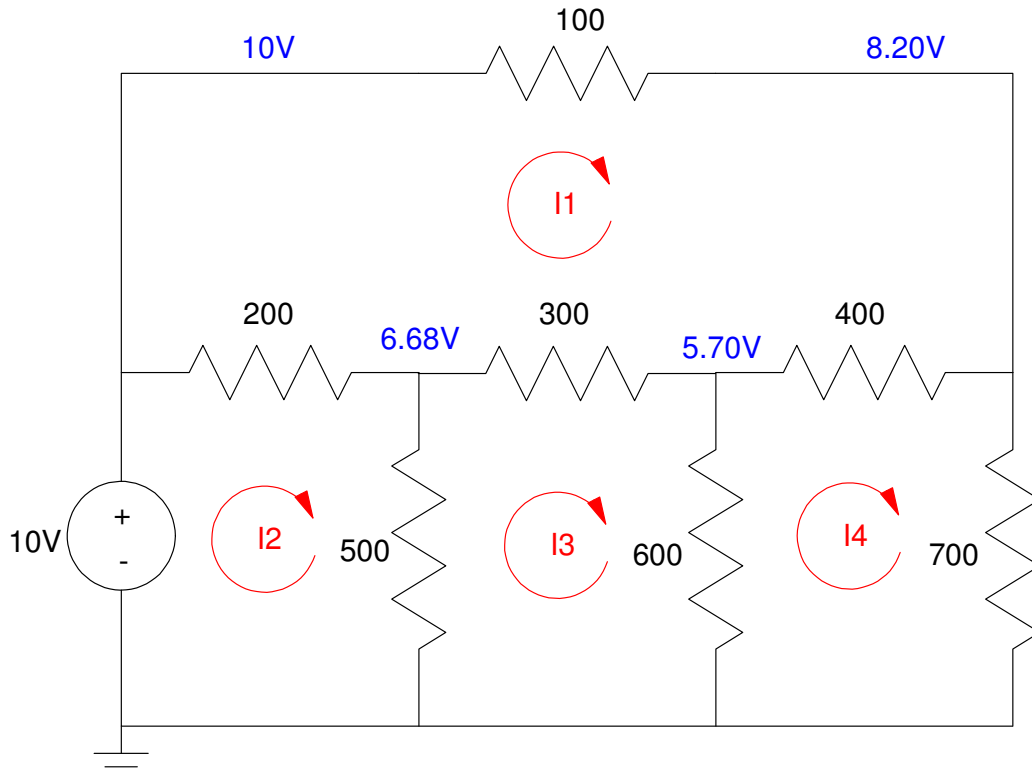

Bonus: There are 300 million people in the United States. How many people does it take for their total wealth to equal the total wealth of the poorest 150 million?