

# EE 206 Test #3d - Name \_\_\_\_\_


AC Analysis of Circuits. Due Thursday, May 7th at midnight

Open book, open notes, internet, calculators, matlab permitted. Individual effort only.


No aid given, received, or observed: (signature) \_\_\_\_\_

1) Determine the frequency and the phasor representation for X and Y.


Frequency (Hz)	X		Y	
	Amplitude	Phase	Amplitude	Phase

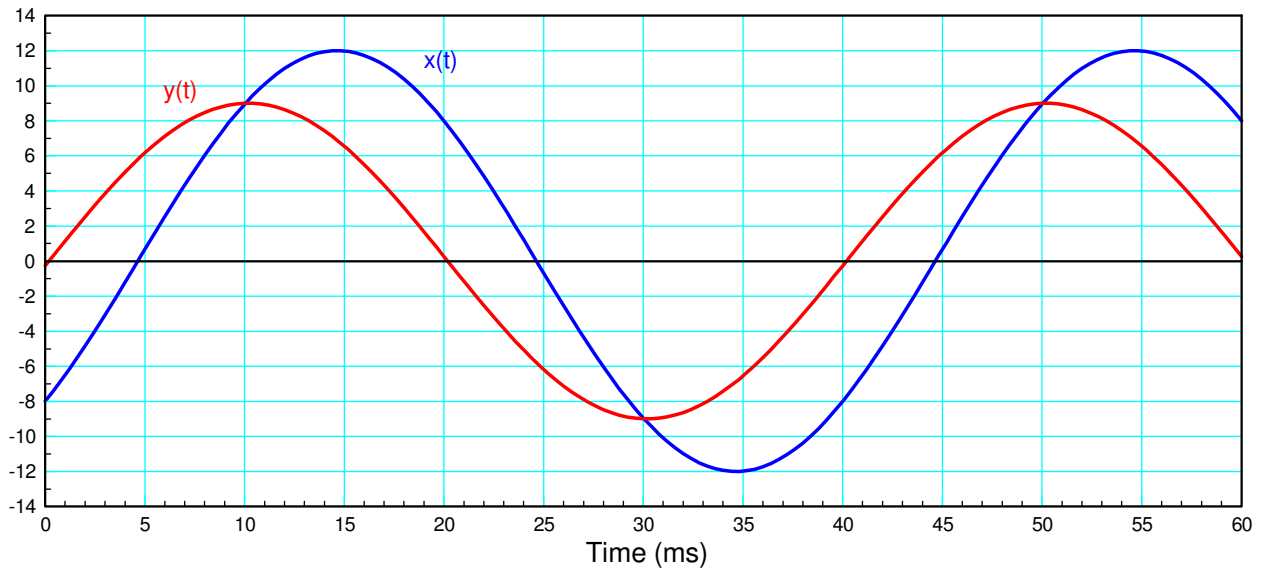

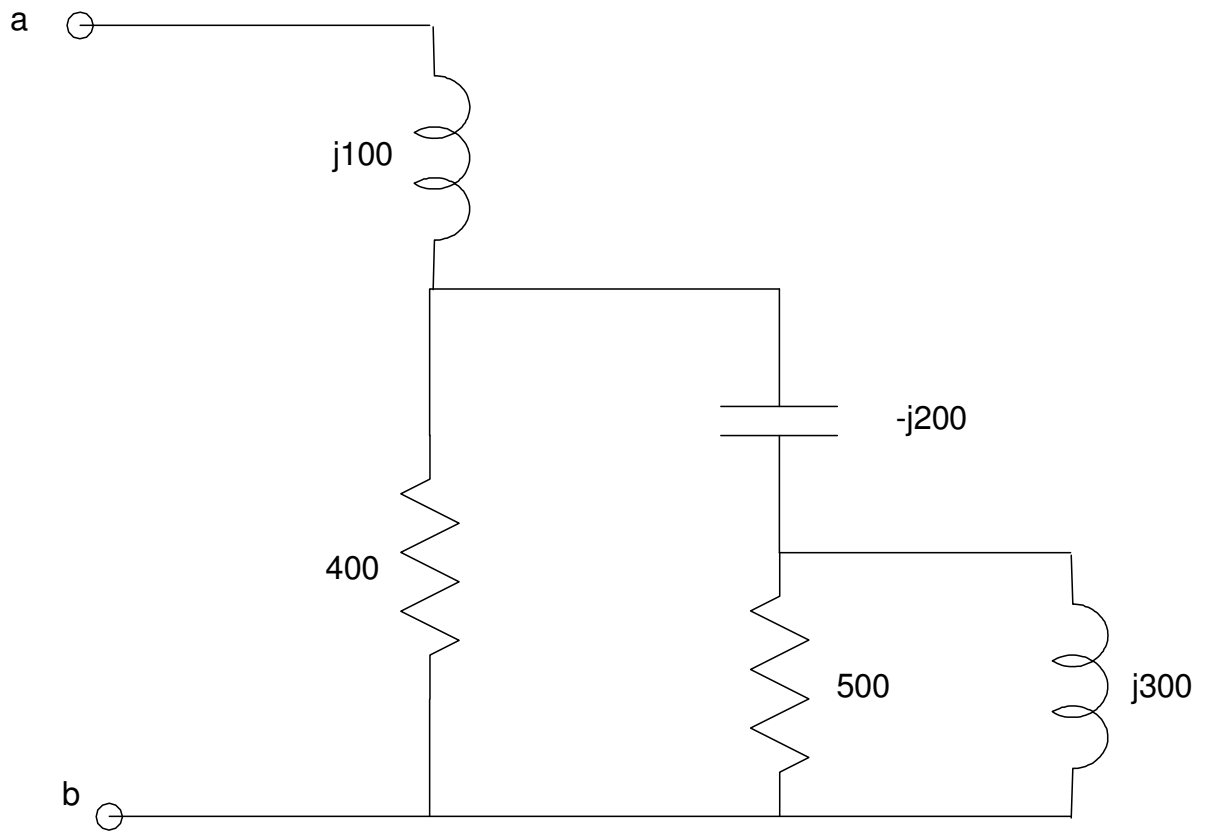2) Determine the resistance  $R_{ab}$  (it will be a complex number)



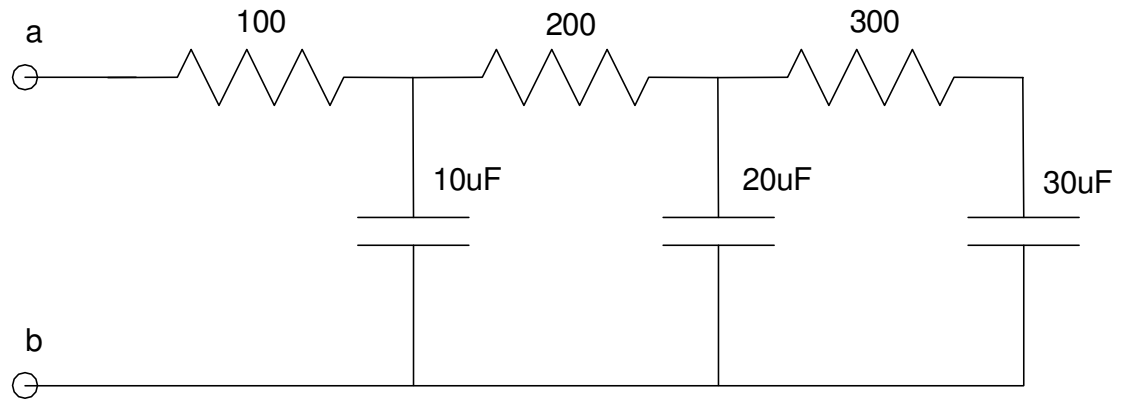3) Determine the impedance from a to b. Assume  $\omega = 100 \text{ rad/sec}$  (15.9Hz)




4) Assume

$$V_{in} = 3 \cos(5t) + 5 \sin(5t)$$

Determine the voltage  $Y(t)$

y(t) =

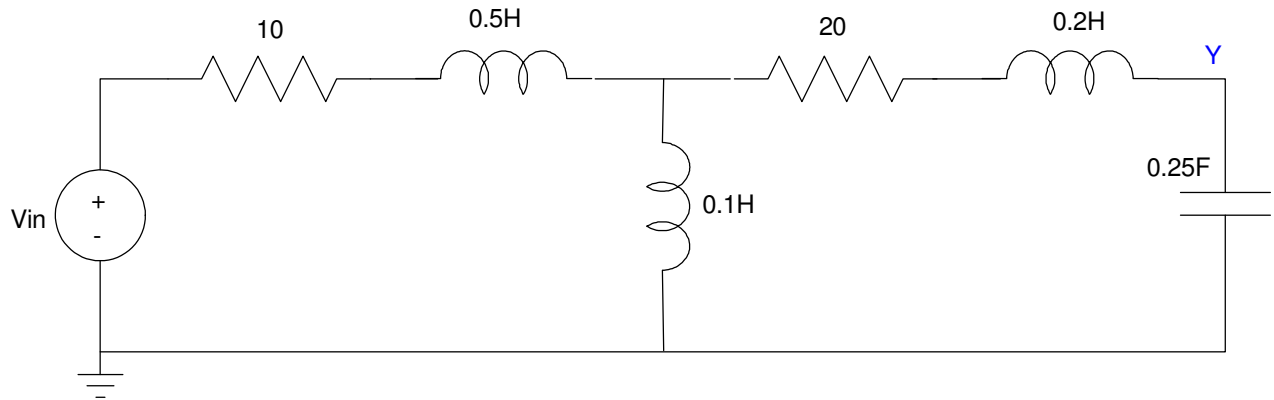


5) Assume

$$V_{in} = 3\cos(5t) + 7\sin(10t)$$

Determine the voltage  $y(t)$

$y(t) =$

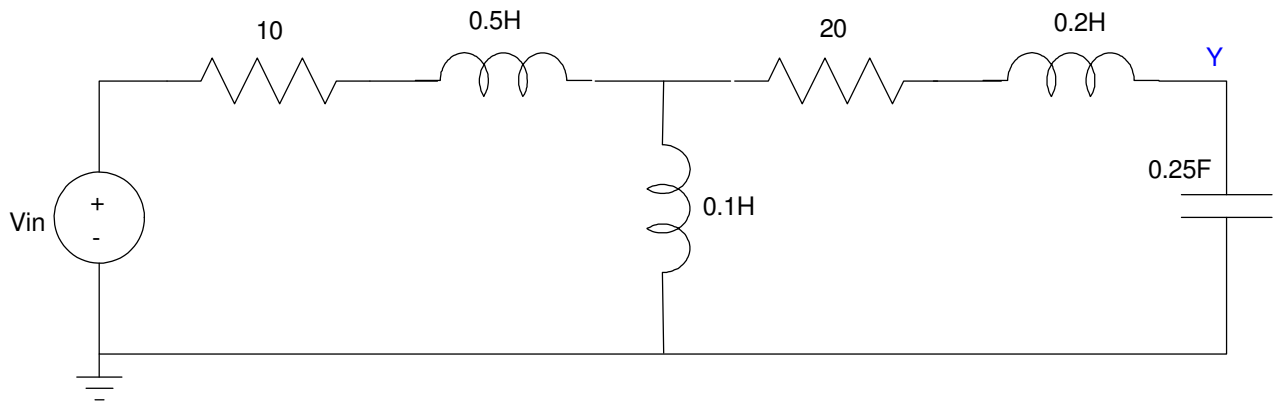

6) Determine the first 5 terms of the Fourier series approximation to  $x(t)$

$$T = 2\pi$$

$$x(t) = \begin{cases} 0 & 0 < t < 2 \\ 5 \sin(t/2) & 2 < t < 2\pi \end{cases}$$

$$x(t) \approx a_0 + a_1 \cos(t) + b_1 \sin(t) + a_2 \cos(2t) + b_2 \sin(2t)$$

a0	a1	b1	a2	b2

