

---

# **Circuit Elements and Kirchoff's Laws**



## **EE 206 Circuits I**

### **Jake Glower - Lecture #2**



Please visit [Bison Academy](#) for corresponding  
lecture notes, homework sets, and solutions

---




# Circuit Elements: Voltage Sources

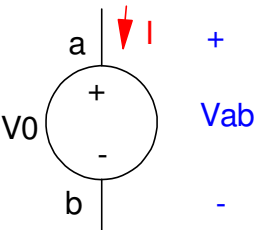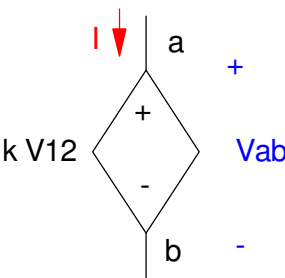Element	Symbol	VI Relationship
Voltage Source (battery)		$V_{ab} = V_0$ $I = \text{any}$
Voltage Controlled Voltage Source (amplifier)		$V_{ab} = kV_{12}$ $I = \text{any}$

# Circuit Elements: Current Sources

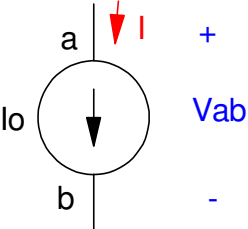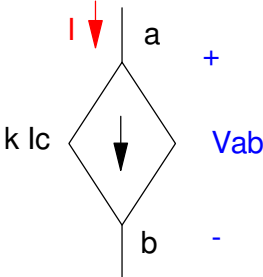Element	Symbol	VI Relationship
Current Source (LED driver)		$I = I_0$ $V_{ab} = \text{any}$
Current Controlled Current Source (transistor)		$I = kI_c$ $V_{ab} = \text{any}$

# Passive Circuit Elements

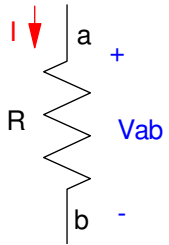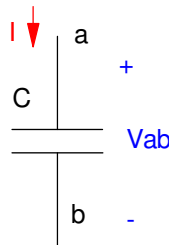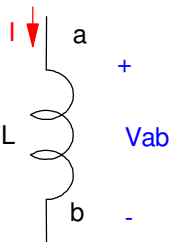
Element	Symbol	VI Relationship
Resistor (basic circuit element)		$V_{ab} = IR$
Capacitor (basis circuit element)		$I = C \frac{dV_{ab}}{dt}$
Inductor (basic circuit element)		$V_{ab} = L \frac{dI}{dt}$

---

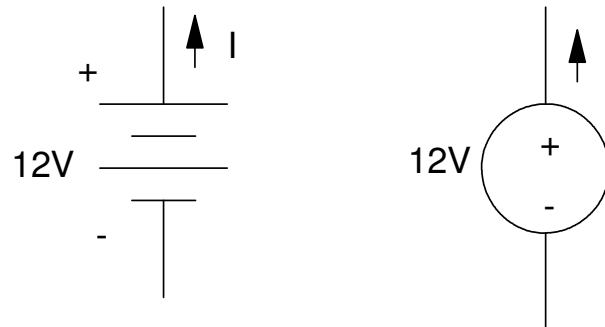
# Independent Sources

Voltage Source: Like a battery: the voltage is fixed

- Current depends upon the load (can be anything, positive or negative)



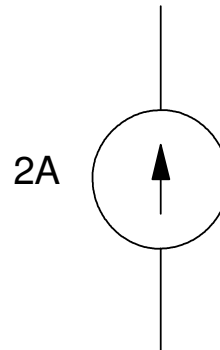
Current Source: LED driver: the current is fixed



---
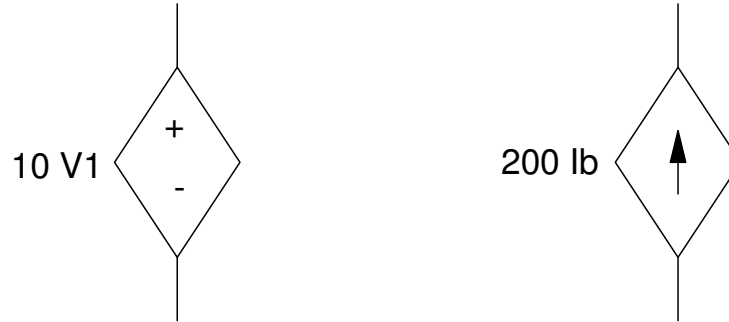
## Dependent Sources

Controlled Current and Voltage Sources: A diamond indicates a controlled voltage source or a controlled current source.



Controlled sources arise from various components covered in ECE 320 Electronics

- Operational Amplifiers (voltage controlled voltage source)
- Transistors (current controlled current source)
- MOSFET (voltage controlled current source)

For this class, just treat them as a device.

---

---

# Ohm's Law

- $V = I R$
- Current goes into the + terminal

Other Forms:

$$I = \frac{V}{R}$$



$$R = \frac{V}{I}$$

Power:

$$P = V I$$

$$P = \frac{V^2}{R}$$

$$P = I^2 R$$

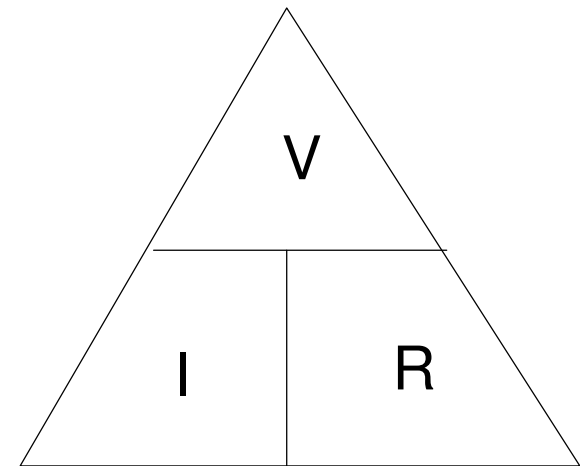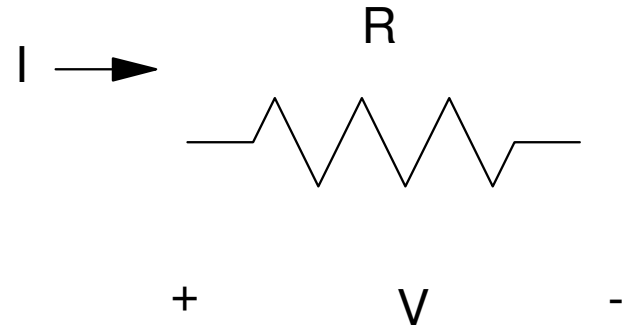

---

# Kirchoff's Laws

Kirchoff's laws simply restate the conservation of voltage and current:

- If you sum the voltages around any closed path, the sum must be zero.
- If you sum the current flowing away from a point, the sum must be zero.




---

## Conservation of Voltage:

Around any closed path, the voltages must add to zero.

- You can use this to find unknown voltages.

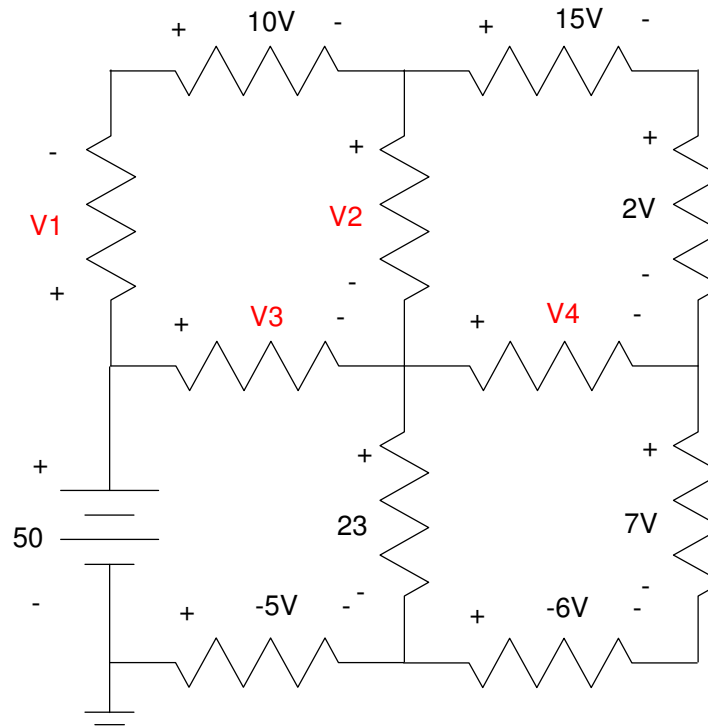Example: determine the voltages  $V1..V4$  for the following circuit:



## Solution:

- Around any closed-path, the voltages must sum to zero.
- Add if you hit the + sign first
- Subtract if you hit the - sign first

Path 1: (Blue)


$$-50 + V_3 + 23 - (-5) = 0$$

$$V_3 = 22V$$

Path 2: (Red)

$$-23 + V_4 + 7 - (-6) = 0$$

$$V_4 = 10V$$

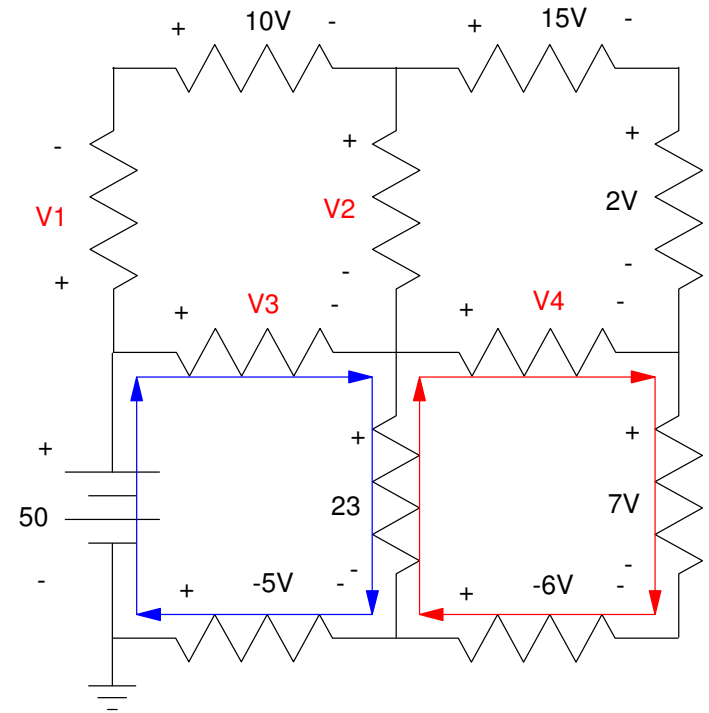

Path 3: (Red)

$$-50 + V_1 + 10 + 15 + 2 - 8 - (-6) - (-5) = 0$$


$$V_1 = 5V$$

Path 4 (Cyan)

$$-23 - V_2 + 15 + 2 + 7 - (-6) = 0$$

$$V_2 = 10V$$


Other paths are also valid

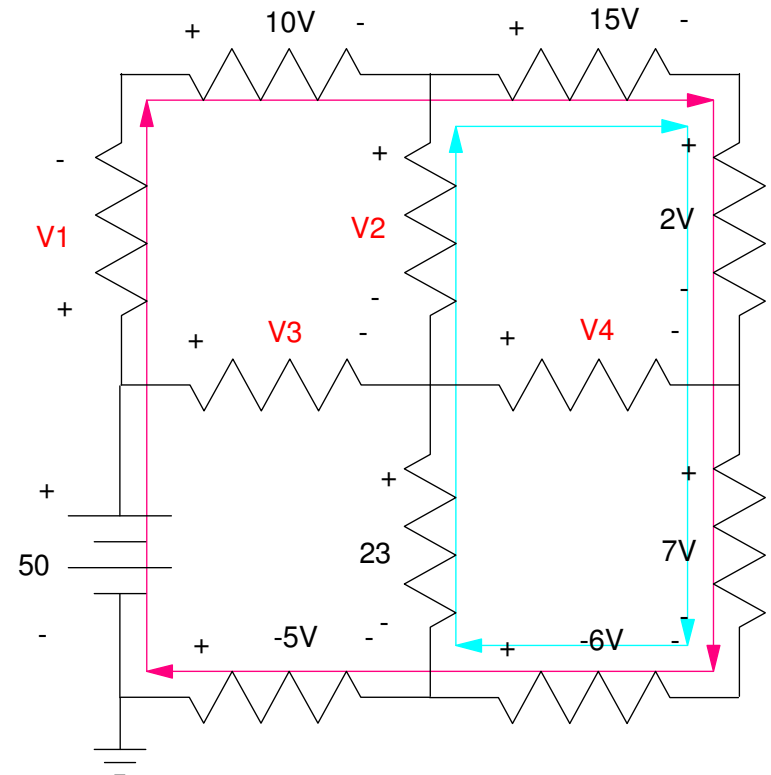

# Conservation of Current

- *Electrons cannot be created or destroyed: they can only be pushed around (Uncle Wally)*
- The current into a node must equal the current out of that node
- The sum of the current from a node must add to zero

Example: Determine  $I_1..I_7$

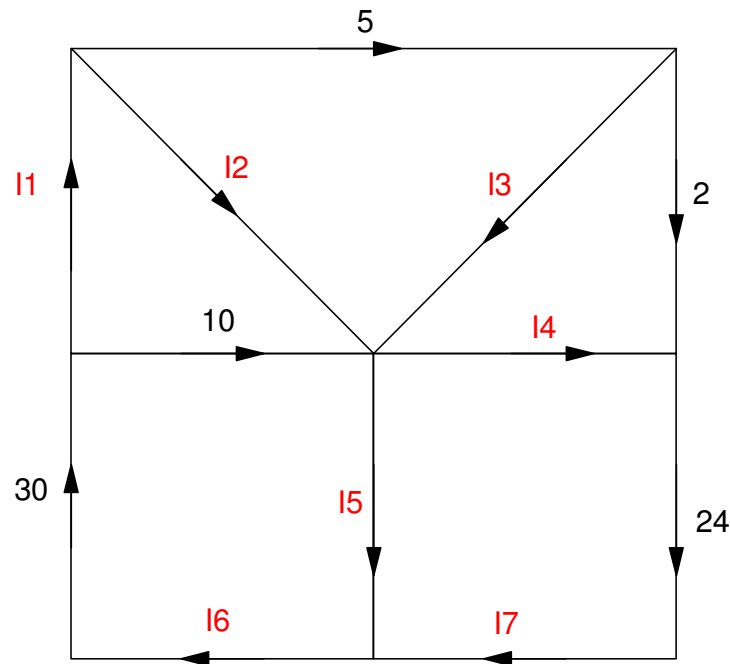

---

A:  $30 = 10 + I1$

$I1 = 20$

B:  $I6 = 30$


C:  $24 = I7$

D:  $5 = I3 + 2$

$I3 = 3$

E:  $2 + I4 = 24$

$I4 = 22$

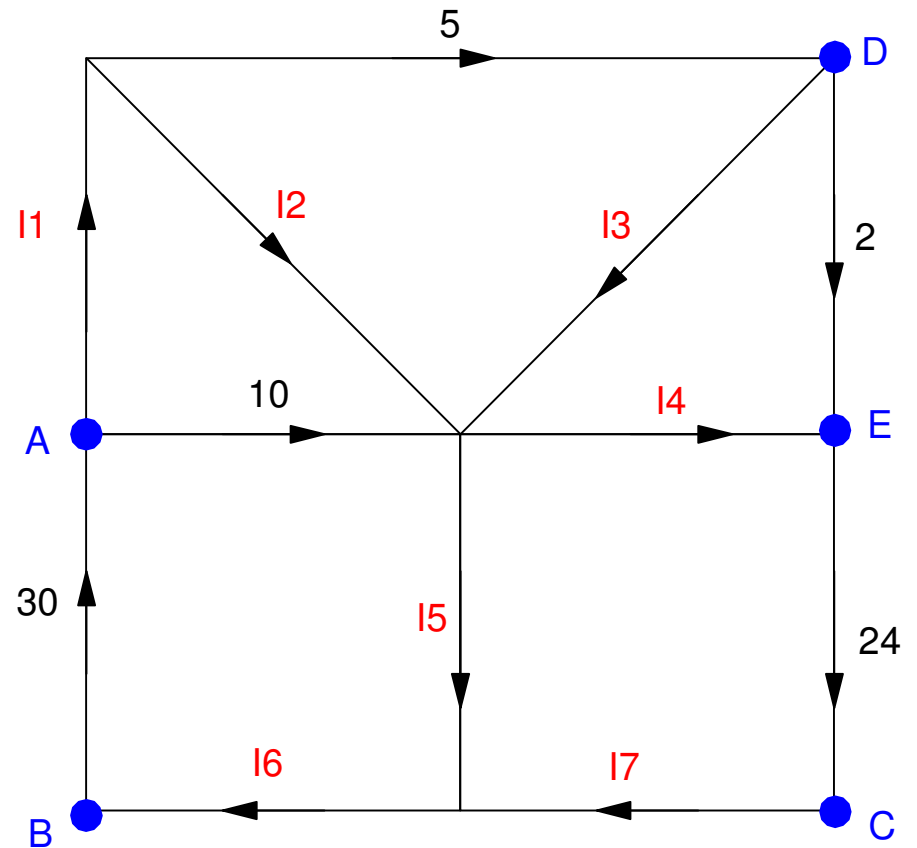

This lets you solve for I2 and I5:

$$F: 20 = I2 + 5$$

$$I2 = 15$$

$$G: I5 + 24 = 30$$

$$I5 = 6$$

