

---

# **Super Loops**

**a.k.a. Super Meshes**

**EE 206 Circuits I**

**Jake Glower - Lecture #8**

Please visit [Bison Academy](#) for corresponding lecture notes, homework sets, and solutions

---

---

# Super-Loops

Current sources cause problems with current loops

- You don't know the voltage across the current source
- You can't sum the voltages to zero

Kirchoff's Voltage Law: The sum of the voltages around any closed path must sum to zero.

- Pick a different closed path to complete N equations for N unknowns
- If this path includes several current loops, the path is called a *SuperLoop*

note: There are usually multiple ways to do this

---

---

## Example: Find $I_1$ .. $I_4$

- 4 windows
- Write 4 equations for 4 unknowns

Easy one: ( current source )

$$I_1 - I_3 = 6$$

Loop  $I_2$  and  $I_4$

$$-12 + 2I_2 + 10(I_2 - I_3) = 0$$

$$12(I_4 - I_3) + 8(I_4 - I_1) + 14(I_4) = 0$$


4th equation???

---

SuperLoop:

Option 1:


$$10(I_3 - I_2) + 4(I_1) + 14(I_4) = 0$$

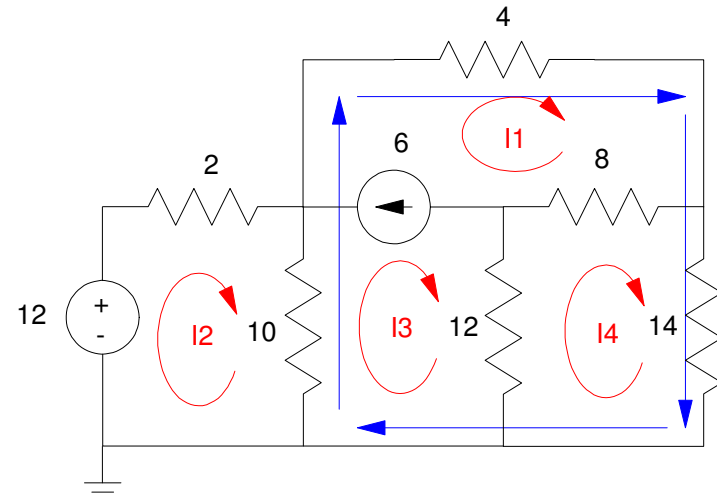

Option 2:

$$10(I_3 - I_2) + 4(I_1) + 8(I_1 - I_4) + 12(I_3 - I_4) = 0$$

Both are valid

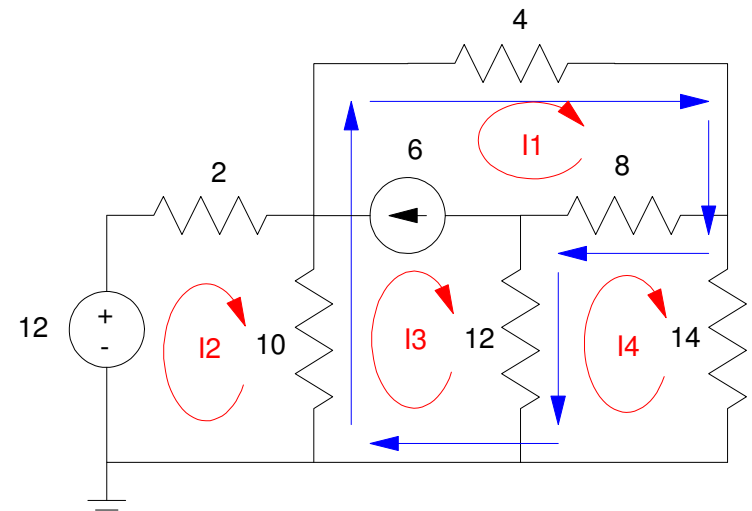

---

Solving: Group terms

$$12I_2 - 10I_3 = 12$$

$$-8I_1 - 12I_3 + 34I_4 = 0$$

$$I_1 - I_3 = 6$$

$$4I_1 - 10I_2 + 10I_3 + 14I_4 = 0$$

Put in matrix form:

$$\begin{bmatrix} 0 & 12 & -10 & 0 \\ -8 & 0 & -12 & 34 \\ 1 & 0 & -1 & 0 \\ 4 & -10 & 10 & 14 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} 12 \\ 0 \\ 6 \\ 0 \end{bmatrix}$$

Throw into MATLAB and solve

---

---

$$A = [0, 12, -10, 0; -8, 0, -12, 34; 1, 0, -1, 0; 4, -10, 10, 14]$$

$$\begin{array}{cccc} 0. & 12. & - 10. & 0. \\ - 8. & 0. & - 12. & 34. \\ 1. & 0. & - 1. & 0. \\ 4. & - 10. & 10. & 14. \end{array}$$

$$B = [12; 0; 6; 0]$$

$$\begin{array}{c} 12. \\ 0. \\ 6. \\ 0. \end{array}$$

$$\text{inv}(A) * B$$

$$\begin{array}{ll} \mathbf{I1} & \mathbf{3.5712271} \\ \mathbf{I2} & \mathbf{-1.0239774} \\ \mathbf{I3} & \mathbf{-2.4287729} \\ \mathbf{I4} & \mathbf{-0.0169252} \end{array}$$

*Current can be negative. It just means the direction we assumed for I1..I4 was wrong.*

---

---

Note: Some superloops don't work that some paths for the 4th equation are not valid. For example, suppose you use this loop:

$$-12 + 2(I_2) + 10(I_2 - I_3) + 12(I_4 - I_3) + 8(I_4 - I_1) + 14(I_4) = 0$$

This shows up in Matlab as an error

- You do not have 4 linearly independent equations
- Your equations miss the 4 Ohm resistor

```
A = [0,12,-10,0; -8,0,-12,34; 1,0,-1,0; -8,12,-22,34];  
B = [12;0;6;12];
```

```
I = inv(A)*B  
      |--error 19  
Problem is singular.
```

---

# Super Loops with Dependent Sources

Dependent sources mean you need extra equations


- One more equation for each dependent source

Example: Find  $I_1..I_4$

Step 1: Define the currents (shown in red)

Step 2: Determine how many equations you need. There are five unknowns ( $I_1, I_2, I_3, I_4, V_x$ ).

- 5 equations for 5 unknowns.

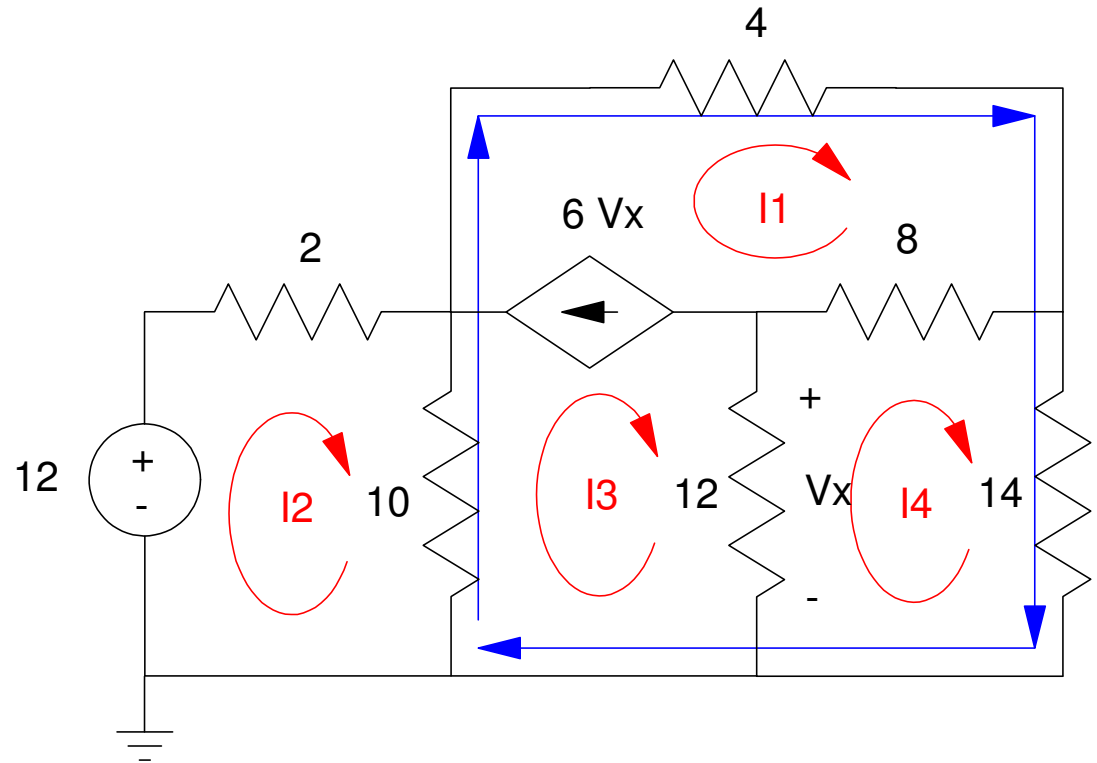



### Step 3: Write the equations

Easy ones:

$$V_x = 12(I_3 - I_4)$$

$$6V_x = I_1 - I_3$$


Loop I2 and I4

$$-12 + 2I_2 + 10(I_2 - I_3) = 0$$

$$12(I_4 - I_3) + 8(I_4 - I_1) + 14(I_4) = 0$$

SuperLoop (shown in blue)

$$10(I_3 - I_2) + 4(I_1) + 14(I_4) = 0$$

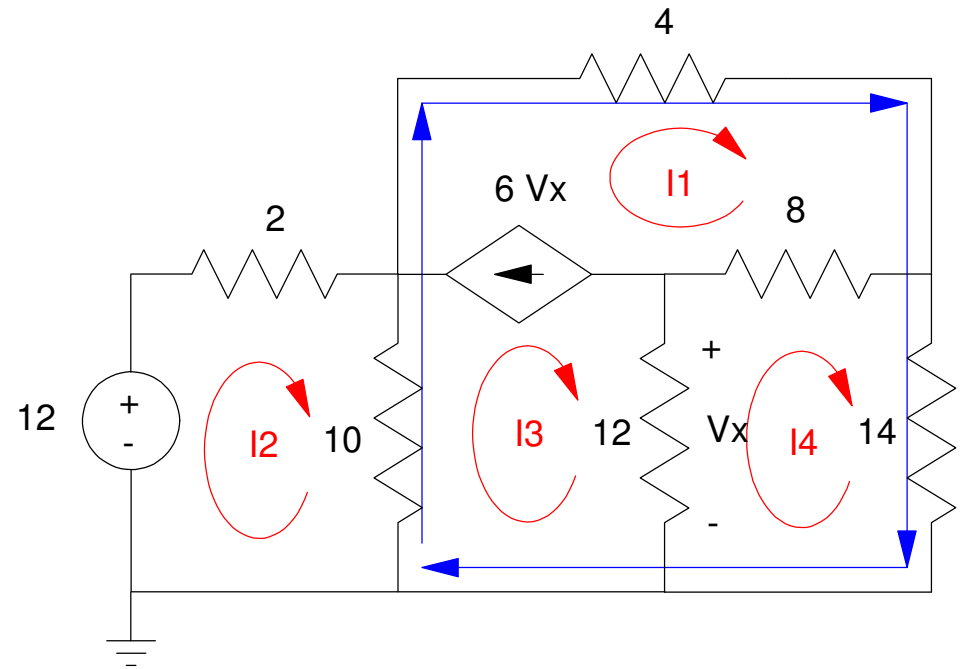

Step 4: Solve. Group terms:

$$12I_3 - 12I_4 - V_x = 0$$

$$I_1 - I_3 - 6V_x = 0$$


$$12I_2 - 10I_3 = 12$$

$$-8I_1 - 12I_3 + 34I_4 = 0$$

$$4I_1 - 10I_2 + 10I_3 + 14I_4 = 0$$

Write these in matrix form
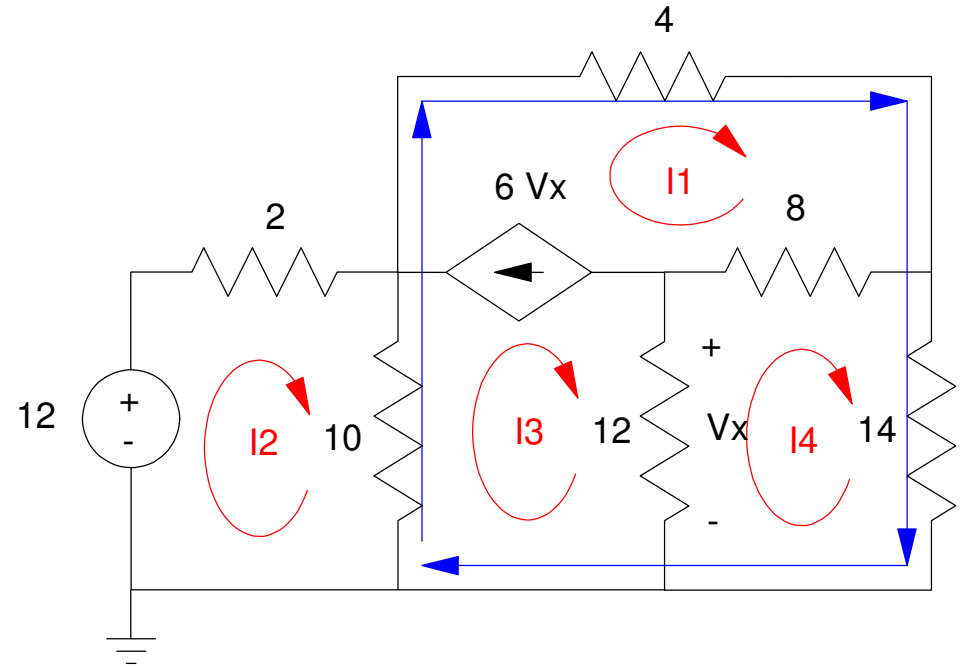
$$\begin{bmatrix} 0 & 0 & 12 & -12 & -1 \\ 1 & 0 & -1 & 0 & -6 \\ 0 & 12 & -10 & 0 & 0 \\ -8 & 0 & -12 & 34 & 0 \\ 4 & -10 & 10 & 14 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \\ V_x \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 12 \\ 0 \\ 0 \end{bmatrix}$$



Throwing these equations into MATLAB and solve:

```
A = [0, 0, 12, -12, -1 ; 1, 0, -1, 0, -6 ; 0, 12, -10, 0, 0];  
A = [A ; -8, 0, -12, 34, 0 ; 4, -10, 10, 14, 0]
```

```
0.    0.    12.   -12.   -1.  
1.    0.    -1.    0.    -6.  
0.    12.   -10.    0.    0.  
-8.    0.   -12.   34.    0.  
4.   -10.    10.   14.    0.
```

```
B = [0; 0; 12; 0; 0];
```

```
I = inv(A) * B
```

```
I1    1.0219378  
I2    1.3210662  
I3    0.3852794  
I4    0.3764369  
Vx    0.1061097
```

