

---

# **Thevenin Equivalents & Max Power Transfer**

**EE 206 Circuits I**

**Jake Glower - Lecture #11**

Please visit [Bison Academy](#) for corresponding  
lecture notes, homework sets, and solutions




## Thevenin and Norton Equivalents (take 2)

Sometimes, the Thevenin resistance isn't obvious.

- If so, apply a test voltage and compute the current draw
- The Thevenin resistance looking in is  $V_{in} / I_{in}$

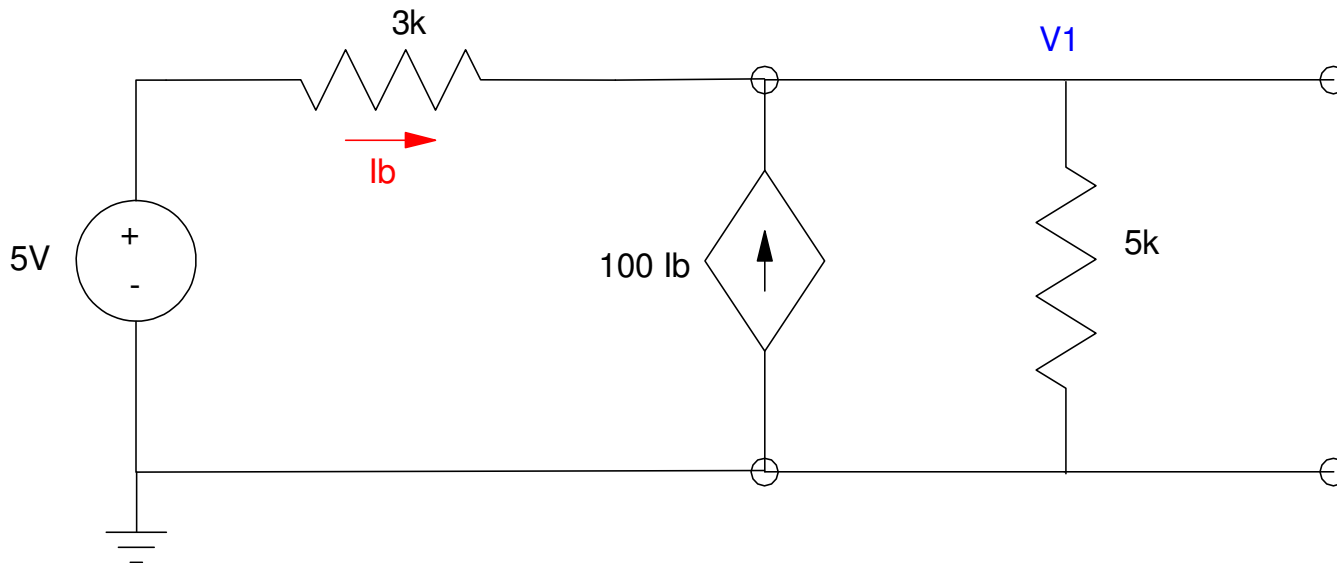**Example 1:** Determine the Thevenin equivalent for the following circuit



---

$V_{th}$ : Determine the open-circuit voltage. Write the voltage node equation at V1


$$I_b = \left( \frac{5 - V_1}{3k} \right)$$

$$\left( \frac{V_1 - 5}{3k} \right) - 100I_b + \left( \frac{V_1}{5k} \right) = 0$$

Substitute and solve

$$V_1 = \left( \frac{\left( \frac{101}{3k} \right)}{\left( \frac{101}{3k} \right) + \left( \frac{1}{5k} \right)} \right) 5V = 4.9705V$$

This is  $V_{th}$ .

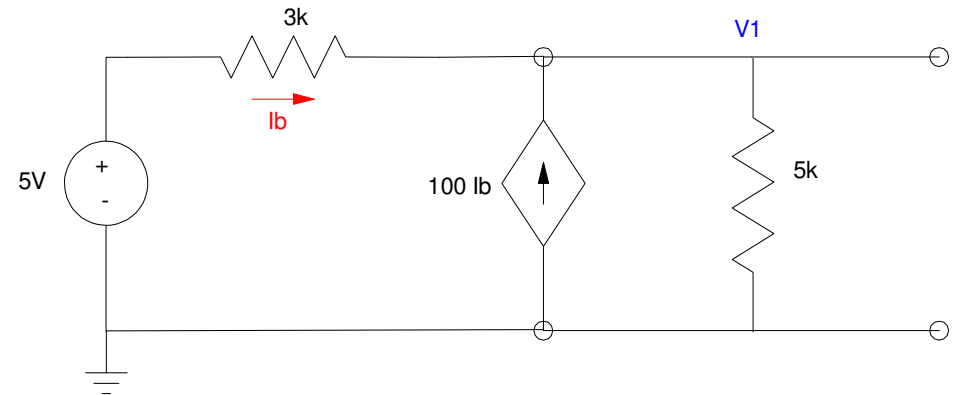

$R_{th}$ :

- Turn off the voltage source
- Measure the resistance

This isn't obvious. So

- Apply a 1V test voltage
- Compute the current drwa ( $I_{in}$ )



$$I_b = \left( \frac{0V - 1V}{3k} \right)$$

$$I_{in} = \left( \frac{1V - 0V}{3k} \right) - 100I_b + \left( \frac{1V}{5k} \right)$$

$$I_{in} = 33.87mA$$

So
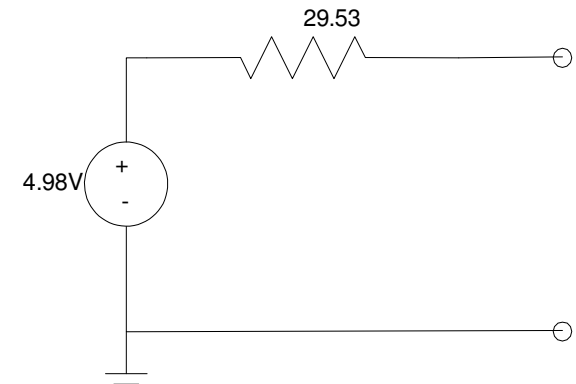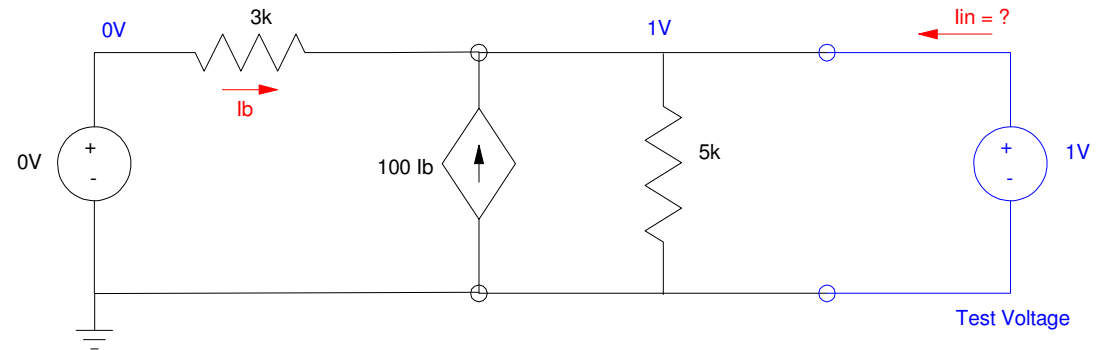
$$R_{th} = \frac{V_{in}}{I_{in}} = \frac{1V}{33.87mA} = 29.53\Omega$$



## Example 2: Determine the Thevenin equivalent

$V_{th}$ : Find  $V_3$  (open circuit voltage)

$$V_2 = -1000V_1$$

$$\left(\frac{V_1-1}{1k}\right) + \left(\frac{V_1-V_3}{10k}\right) = 0$$

$$\left(\frac{V_3-V_1}{10k}\right) + \left(\frac{V_3-V_2}{100}\right) = 0$$

Solve ( time passes.... )

$$A = [1000, 1, 0; 11, 0, -1; -1, -100, 101];$$


$$B = [0; 10; 0];$$

$$V = \text{inv}(A) * B$$

$$V_1 = 0.0100$$

$$V_2 = -9.9891$$

$$V_3 = -9.8901 = V_{th}$$

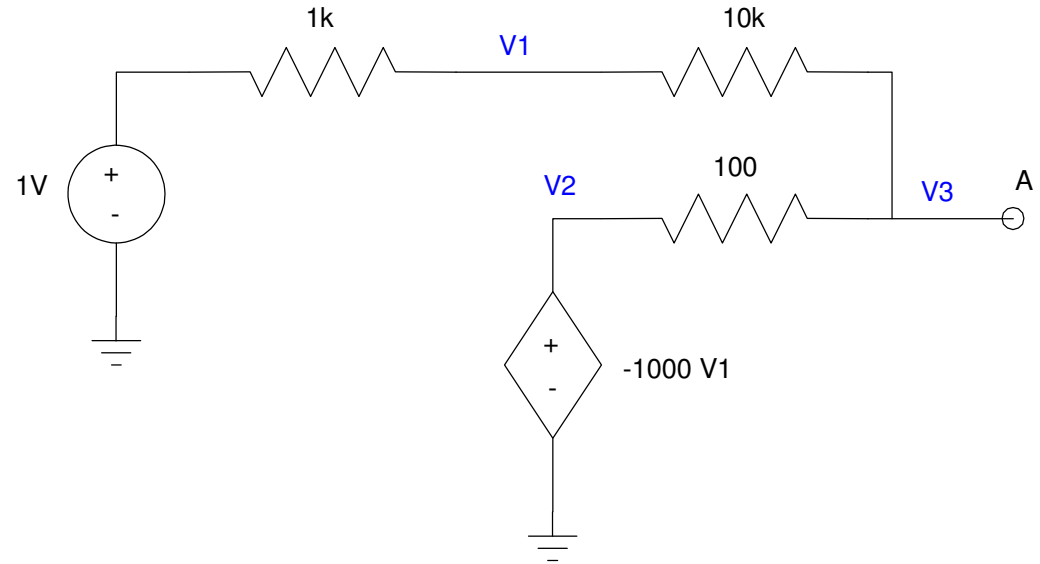

$R_{th}$ :


- Turn off voltage sources and measure the resistance
- Since this isn't obvious, apply a 1V test voltage

$$V_1 = \left( \frac{1k}{1k+10k} \right) \cdot 1V = 90.91mV$$


$$V_2 = -1000V_1 = -90.91V$$

$$I_{in} = \left( \frac{1V}{11k} \right) + \left( \frac{1V - (-90.91V)}{100} \right) = 919.2mA$$
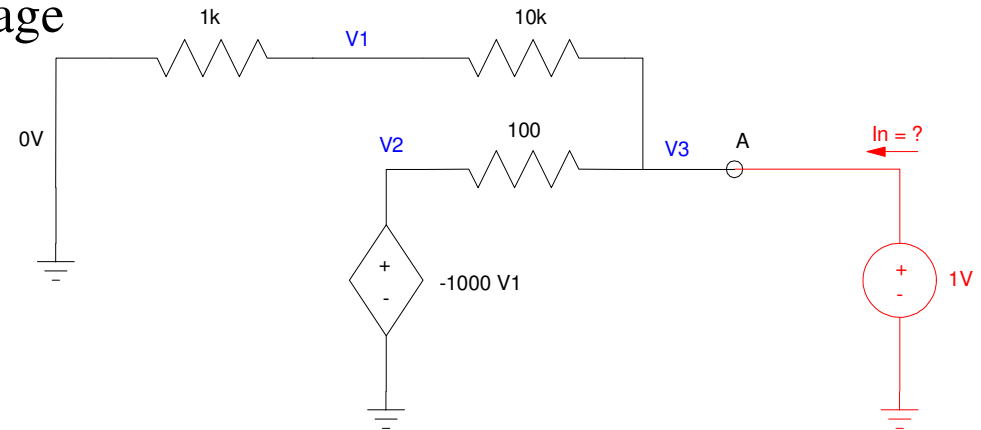
$$R_{in} = \frac{V_{in}}{I_{in}} = \frac{1V}{919.2mA} = 1.088\Omega$$



So, the Thevenin equivalent is...

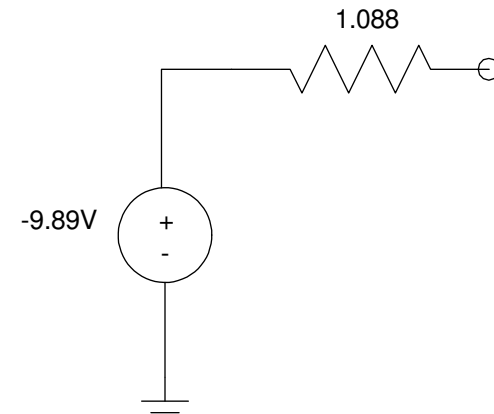


---
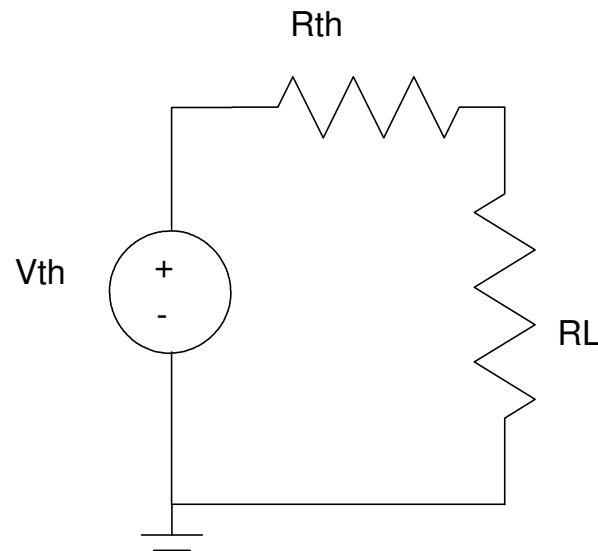
# Max Power Transfer

What resistance ( $R_L$ ) maximizes the power to the load?

- ( $V_{th}$ ,  $R_{th}$ ) models a solar panel. What load maximizes the power the solar cell produces?
- ( $V_{th}$ ,  $R_{th}$ ) models a stereo. What speaker ( $R_L$ ) maximizes the output power?



---

**Case 1:**  $R_{th}$  is fixed. Find  $R_L$  to maximize the power to the load.

Note that there is a maximum point:

- If  $R_L = 0$ , the power to the load is zero
- If  $R_L = \text{infinity}$ ,  $I = 0$  and the power to the load is again zero.

Somewhere between  $R_L = 0$  and  $R_L = \text{infinity}$  is a maximum power transfer.

$$I = \left( \frac{V_{th}}{R_{th} + R_L} \right)$$

$$P = I^2 R_L$$


$$P = \left( \frac{R_L}{(R_{th} + R_L)^2} \right) V_{th}^2$$

$$\frac{d}{dR_L} \left( \frac{R_L}{(R_{th} + R_L)^2} \right) = 0$$

$$(R_L + R_{th})(R_{th} - R_L) = 0$$

$$R_L = R_{th} \quad \text{maximum}$$

$$R_L = -R_{th} \quad \text{minimum}$$

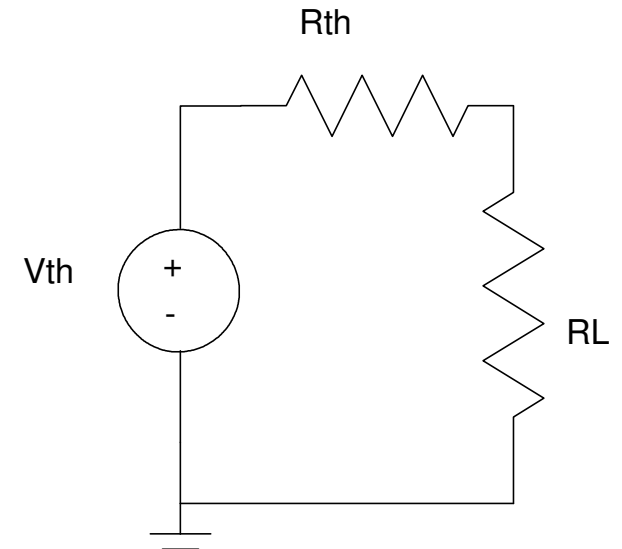




---

Assume for instance that  $V_{th} = 12V$  and  $R_{th} = 2 \text{ Ohms}$ :

```
Vin = 12;  
Rth = 2;  
RL = [0:0.01:10]';  
I = Vin ./ (Rth + RL);  
P = (I .^ 2) .* RL;
```

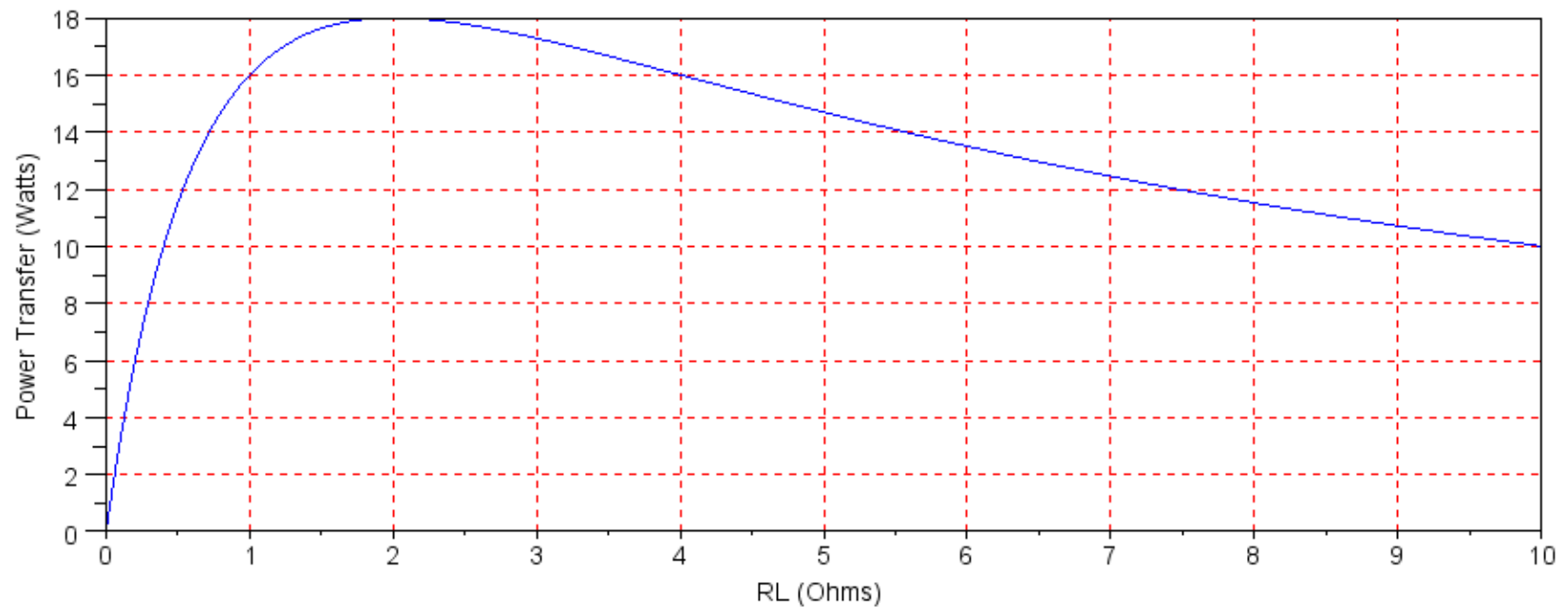Note that at maximum power transfer, you are 50% efficient




---

**Case 2:**  $R_L$  is fixed. Find  $R_{th}$  to maximize the power to the load.

The solution in this case is *not*  $R_{th} = R_L$

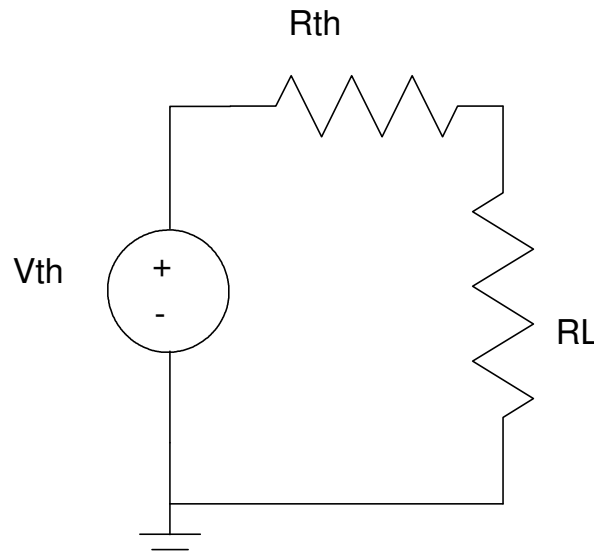
- Maximum is when  $R_{th} = -R_L$
- Closest you can get is  $R_{th} = 0$



---

$V_{th} = 12V$  and  $R_L = 2 \text{ Ohms}$
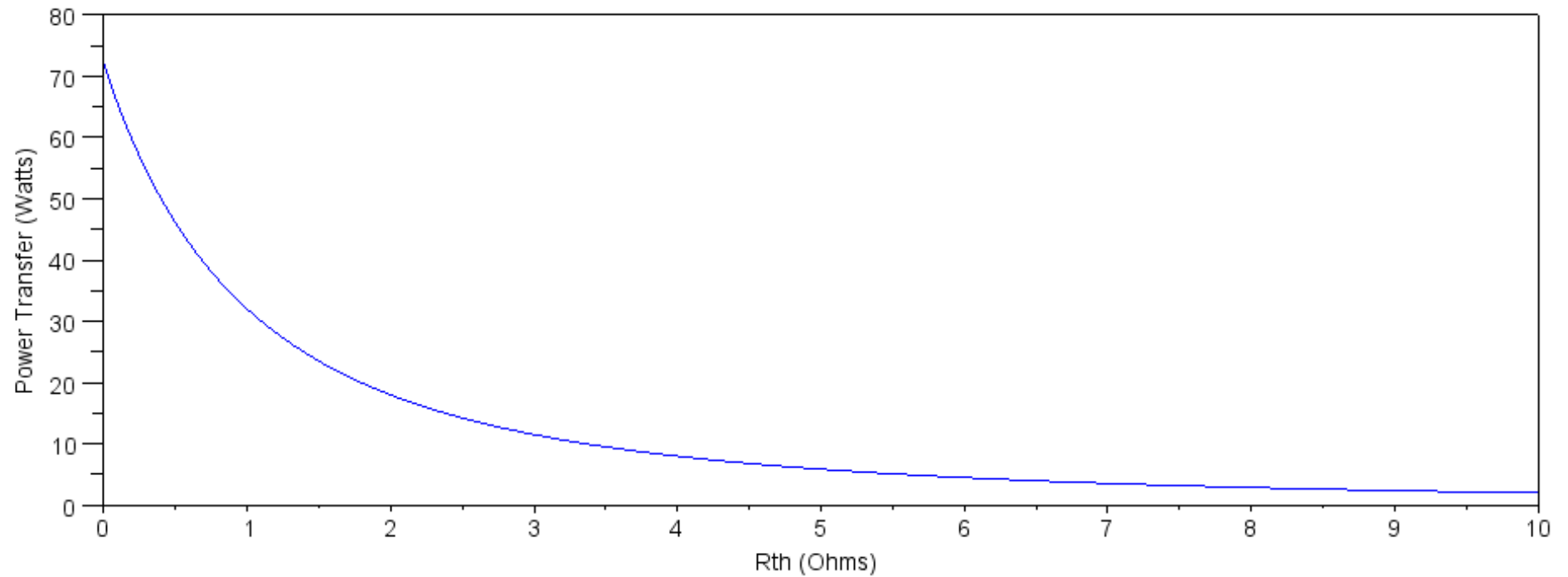
```
Vth = 12;  
RL = 2;  
Rth = [0:0.01:10]';  
I = Vth ./ (RL + Rth);  
P = ( I .^ 2 ) .* RL;  
plot(Rth, P);
```



---

**Case 3:** Find  $R_L$  to maximize the efficiency of the system.

Efficiency is the power to the load divided by the total power dissipated.

$$eff = \left( \frac{P_{Load}}{P_{total}} \right)$$

or

$$eff = \frac{I^2 R_L}{I^2 (R_{th} + R_L)} = \left( \frac{R_L}{R_L + R_{th}} \right)$$

Max efficiency is

- $R_L = \text{infinity}$
- Power = 0

That's one of the problems of delivering power to a load

- For high efficiency, you want  $R_L \gg R_{th}$
- For maximum power, you want  $R_L = R_{th}$

