

---

# **Superposition**

## **EE 206 Circuits I**

### **Jake Glower - Lecture #12**

Please visit [Bison Academy](#) for corresponding  
lecture notes, homework sets, and solutions



---

# Superposition

- A circuit composed of resistors, inductors, capacitors, voltage sources, current sources, and dependent sources is a linear system.
- Linear systems have the property

$$f(a + b) = f(a) + f(b)$$

Meaning....

- If a circuit has two or more inputs,
- You treat this as two separate circuits, each with just one of the inputs.
- The net voltages (and currents) will be the sum of the separate problems

This is called *superposition*

---

## Example 1:

$$V_0 = 10$$


$$\left(\frac{V_1 - V_0}{10}\right) + \left(\frac{V_1}{100}\right) + \left(\frac{V_1 - V_2}{20}\right) = 0$$

$$\left(\frac{V_2 - V_1}{20}\right) + \left(\frac{V_2}{200}\right) + \left(\frac{V_2 - V_3}{30}\right) = 0$$

$$\left(\frac{V_3 - V_2}{30}\right) + \left(\frac{V_3}{300}\right) + \left(\frac{V_3 - V_4}{40}\right) = 0$$

$$\left(\frac{V_4 - V_3}{40}\right) + \left(\frac{V_4}{400}\right) = 0$$

$$V_4 = 5$$

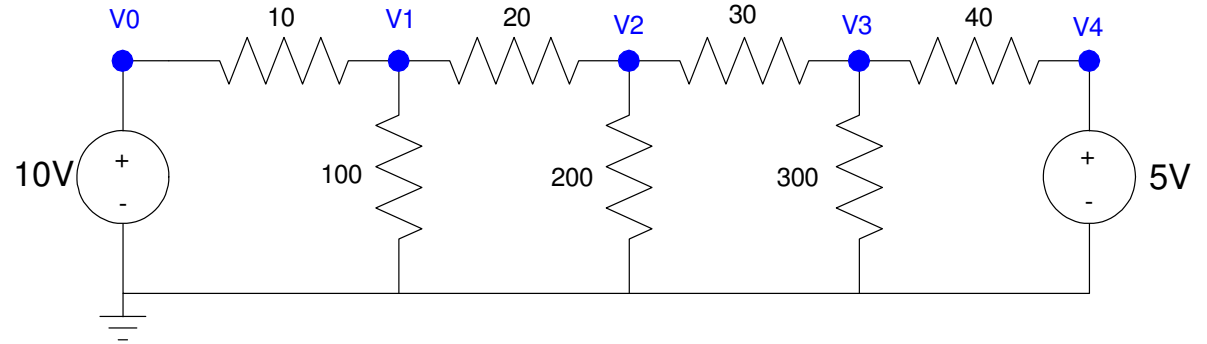


## Result

	V0	V1	V2	V3	V4
V0 = 10V V4 = 5V	10.00 V	8.42 V	6.95 V	5.78 V	5.00 V

## Superposition (take 1):

- $V_0 = \text{on}$
- $V_4 = \text{off}$


	$V_0$	$V_1$	$V_2$	$V_3$	$V_4$
$V_0 = 10\text{V}$ $V_4 = 0\text{V}$	10.00V	8.04 V	5.71 V	3.09 V	0.00 V

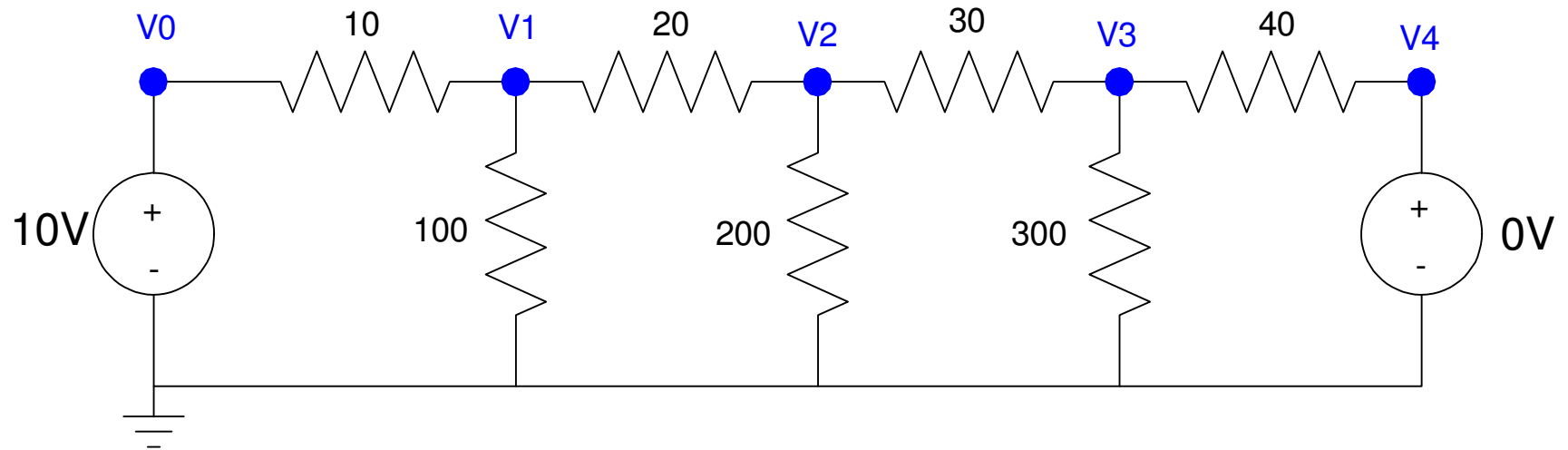

## Superpositon (take 2)

- $V_0 = \text{off}$
- $V_4 = \text{on}$

	$V_0$	$V_1$	$V_2$	$V_3$	$V_4$
$V_0 = 0V$ $V_4 = 5V$	0.00 V	0.386 V	1.24 V	2.69 V	5.00 V

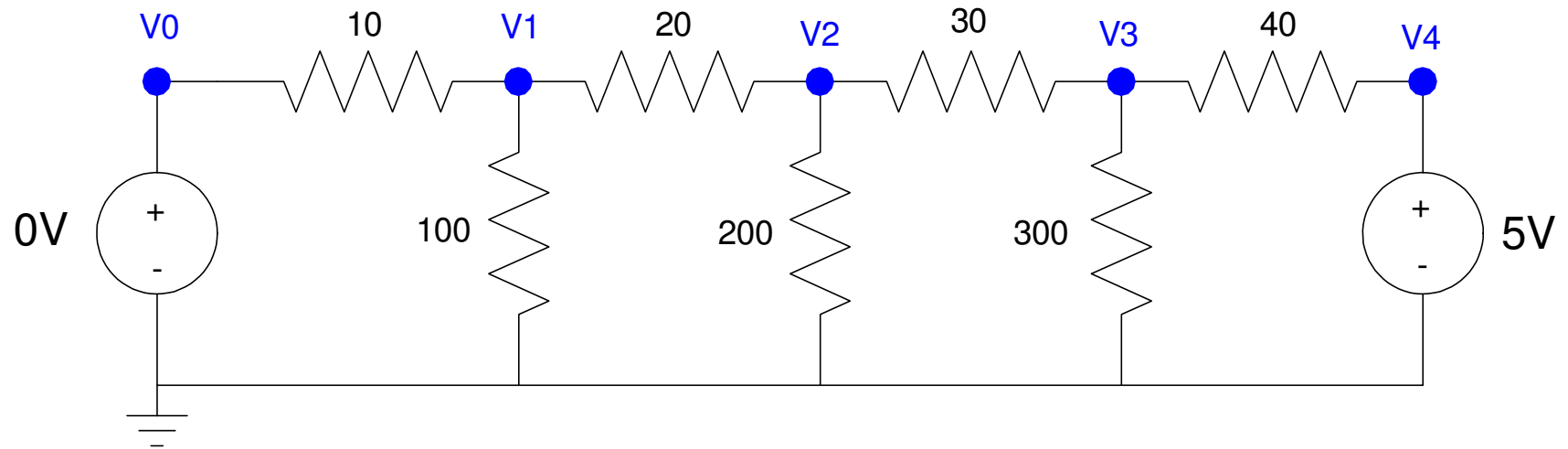

---

## Superposition (take 3)

Note that the voltages add up

	V0	V1	V2	V3	V4
V0 = 10V, V4 = 0V	10.00V	8.04 V	5.71 V	3.09 V	0.00 V
V0 = 0V V4 = 5V	0.00 V	0.386 V	1.24 V	2.69 V	5.00 V
V0 = 10V V4 = 5V	10.00 V	8.42 V	6.95 V	5.78 V	5.00 V


---

## Example 2: R-2R Ladder.

Determine  $Y$  as a function of  $A$ ,  $B$ ,  $C$ , and  $D$

By superposition, we know that


$$Y = aA + bB + cC + dD$$

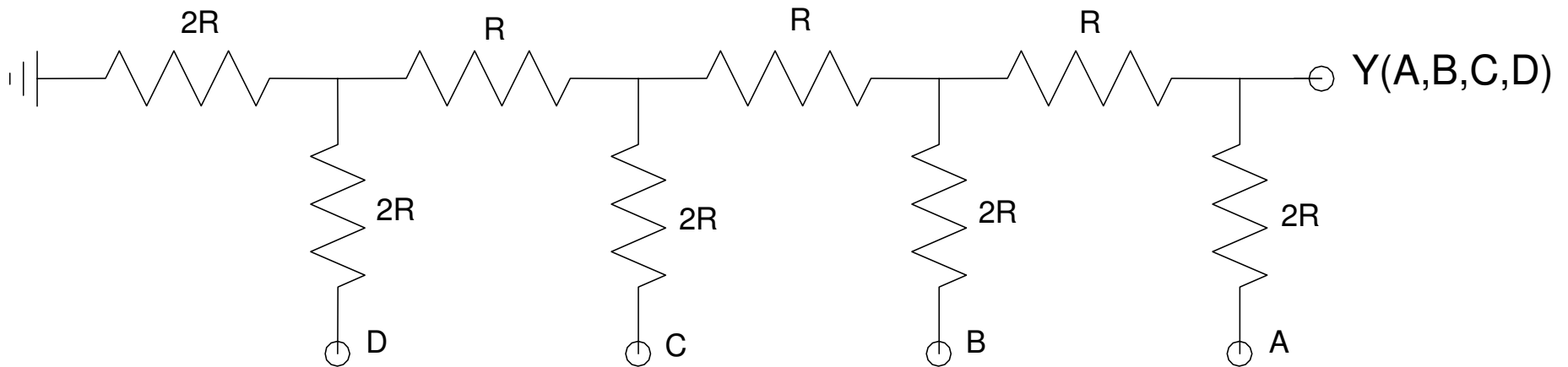

Case 1:  $A = 1, B = C = D = 0$ .

- Take the Thevenin equivalent of the circuit looking left at x. All you see is  $2R \parallel 2R = R$  to ground.
- Repeat at y. All you see is  $2R \parallel 2R = R$  to ground.
- Repeat at z. All you see is  $2R \parallel 2R = R$  to ground.
- By voltage division,  $Y = 1/2$  volt.


$$a = 1/2$$

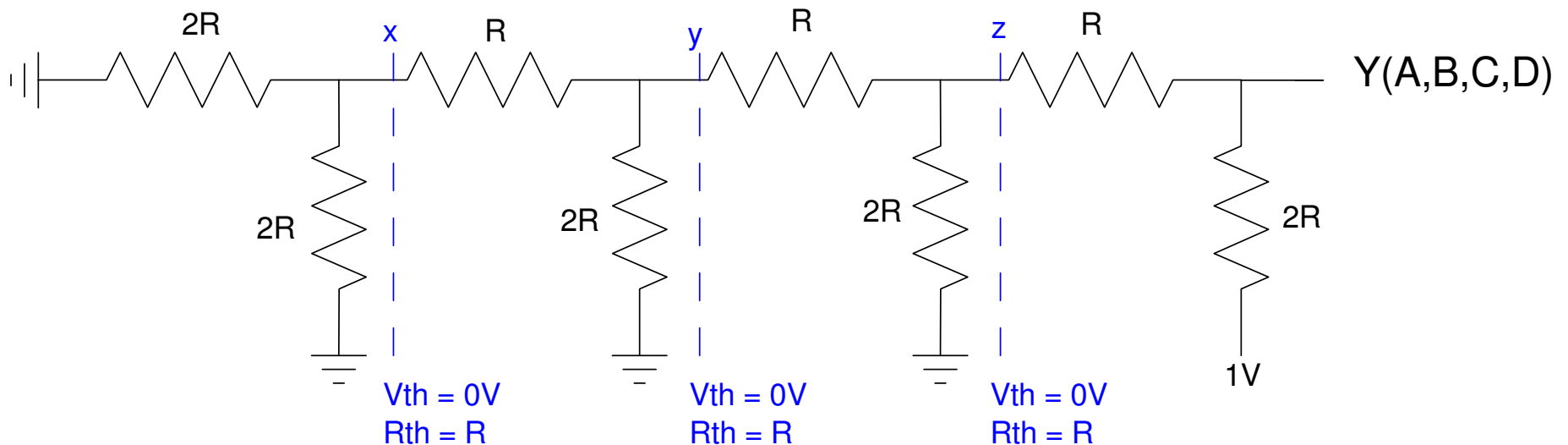

Case 2:  $A = 0$ ,  $B = 1$ ,  $C = D = 0$ .

- At w looking left, all you see is  $2R \parallel 2R = R$
- At x looking left, all you see is  $2R \parallel 2R = R$
- At y looking left, all you get
  - $R_{th} = 2R \parallel 2R = R$        $V_{th} = 1/2 \text{ V}$
- At z looking left, you get
  - $R_{th} = 2R \parallel 2R = R$        $V_{th} = 1/2 * 1/2 = 1/4$


$b = 1/4$

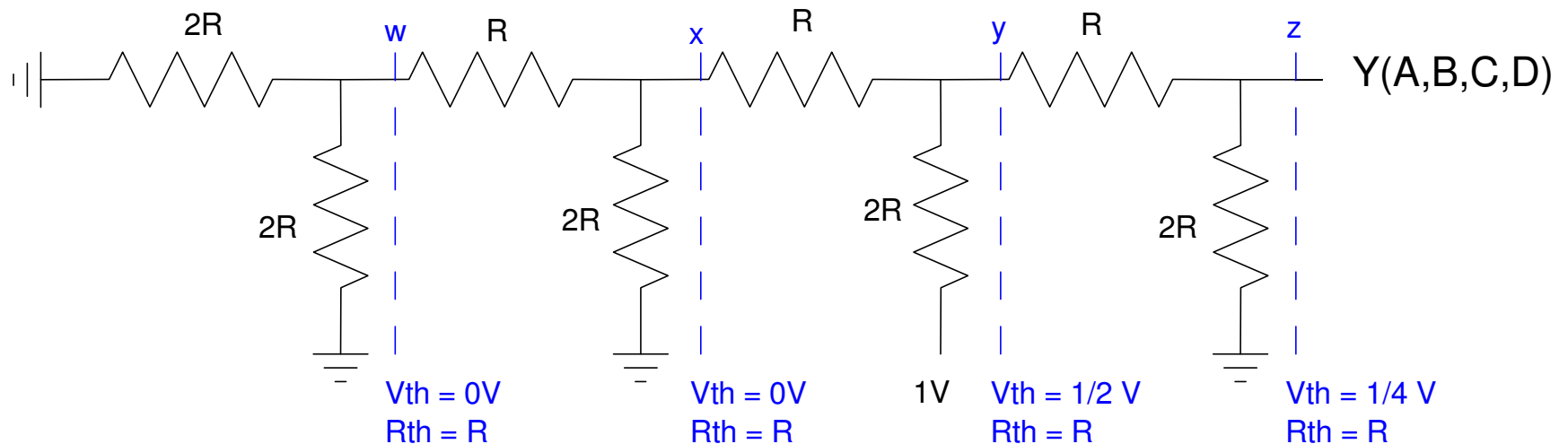

Case 3:  $A = B = D = 0$ .  $C = 1$ .

- Taking the Thevenin equivalents looking left, you wind up with

- $Y = 1/8 \text{ V} \quad (c = 1/8)$

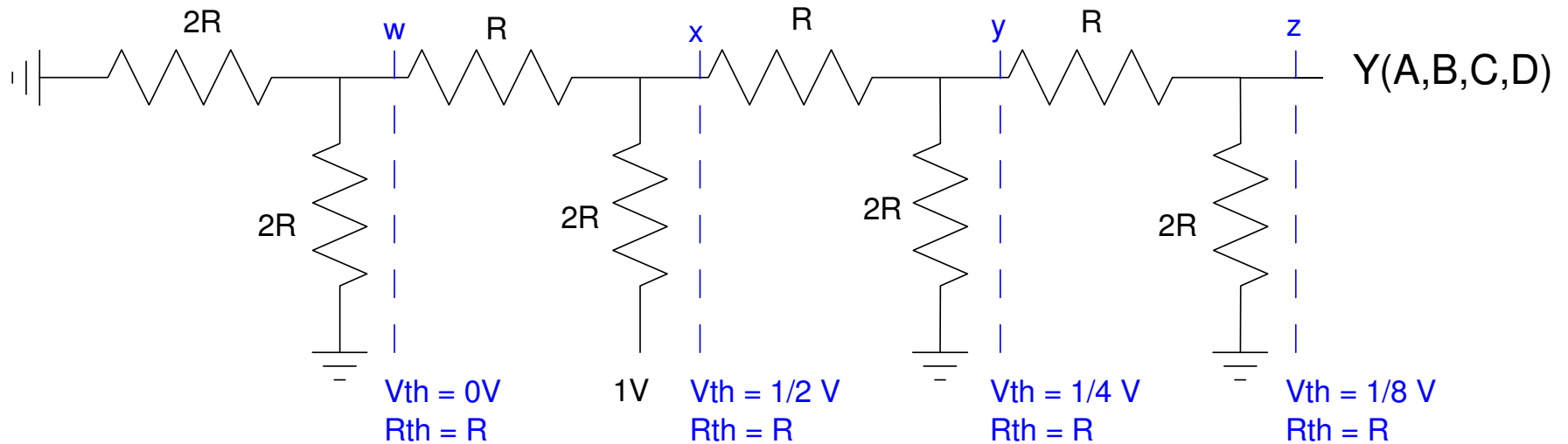


---

The net result is

$$Y = \left(\frac{1}{2}\right)A + \left(\frac{1}{4}\right)B + \left(\frac{1}{8}\right)C + \left(\frac{1}{16}\right)D$$

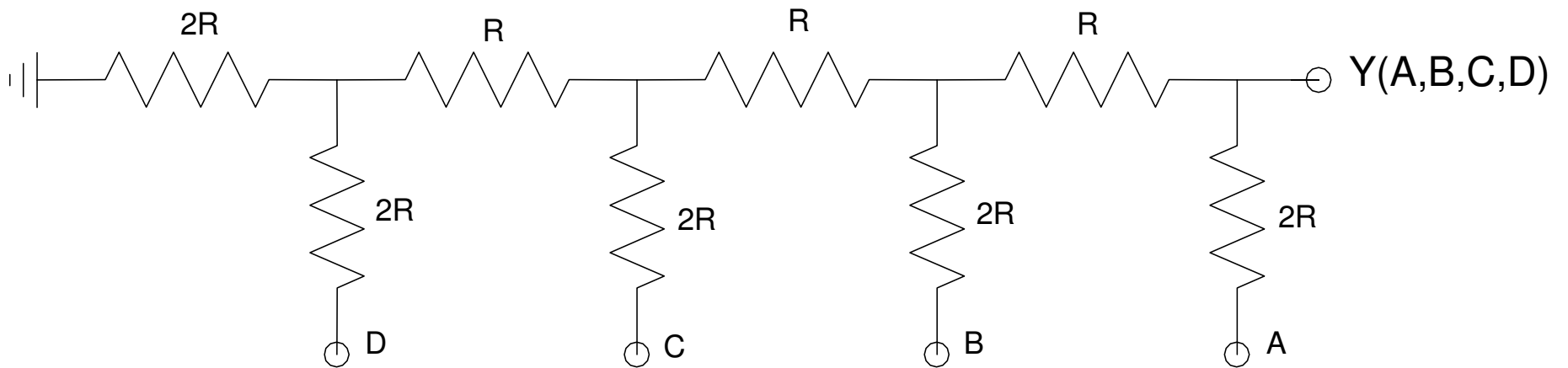- This circuit converts a binary number into an analog voltage



---

## Example 3: Weighted Average

Case 1: Design a circuit so that  $Y$  is the average of  $\{ A, B, C \}$


$$Y = \left( \frac{A+B+C}{3} \right)$$

By symmetry, use three resistors:

$$\left( \frac{Y-A}{R} \right) + \left( \frac{Y-B}{R} \right) + \left( \frac{Y-C}{R} \right) = 0$$

$$3Y = A + B + C$$

$$Y = \left( \frac{A+B+C}{3} \right)$$

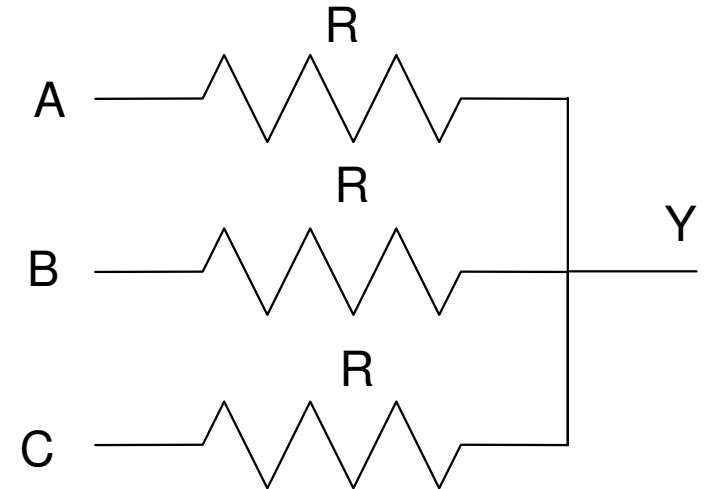


---

Case 2: Design a circuit so that Y is the weighted average:

$$Y = \left( \frac{2A+B+C}{4} \right)$$

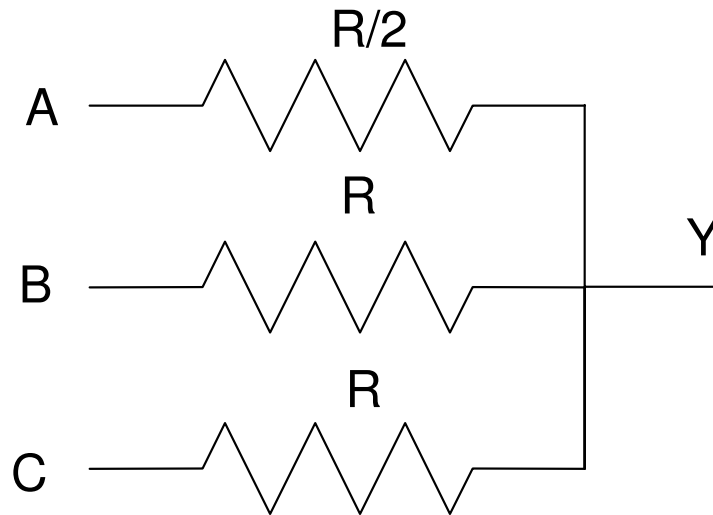Solution: Add A twice. This is equivalent to reducing R by 2:




---

Case 3: Design a circuit to implement

$$Y = \left( \frac{aA + bB + cC}{a + b + c} \right)$$

Solution:

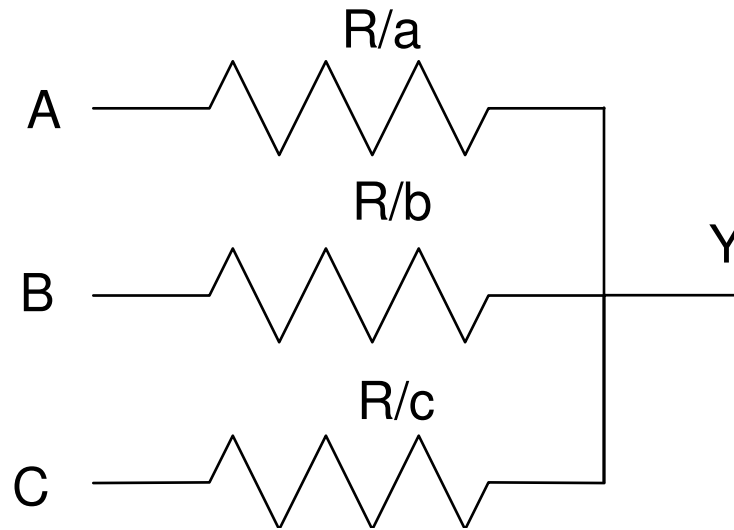

Y is the weighted average of A, B, C

---

## Example: Level Shifting

- Let A be an analog signal in the range of ( -10V, +10V )

Design a circuit to shift this voltage to the range of 0..5V.

Solution: Y is related to A as

$$Y = \frac{1}{4}A + 2.5$$

Rewrite as

$$Y = \frac{1}{4}A + \frac{1}{2}(5V) + \frac{1}{4}(0V)$$

$$Y = \left( \frac{1 \cdot (A) + 2 \cdot (5V) + 1 \cdot (0V)}{4} \right)$$

