

---

# **Comparitors and Schmitt Triggers**

## **EE 206 Circuits I**

### **Jake Glower - Lecture #16**




Please visit Bison Academy for corresponding  
lecture notes, homework sets, and solutions

---
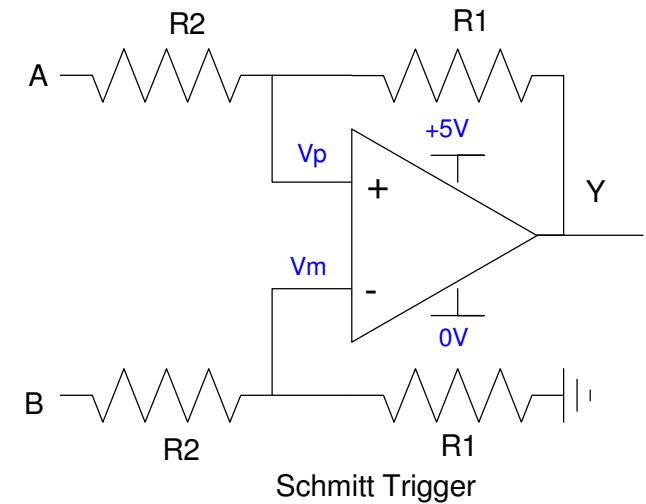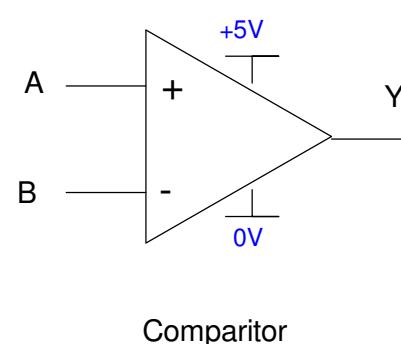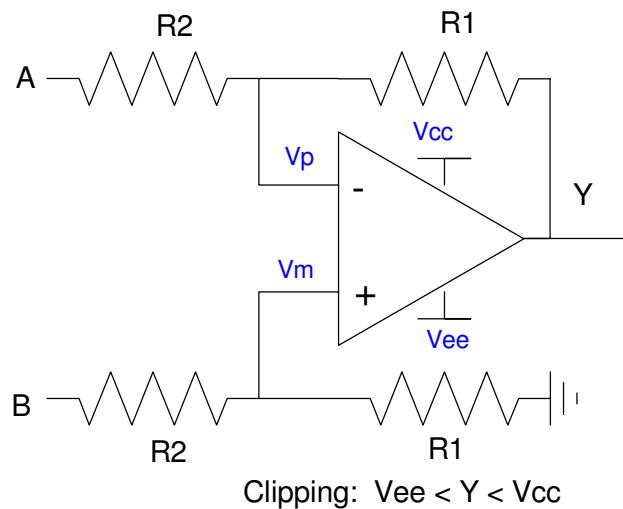
# Comparitors and Schmitt Triggers

$V_p = V_m$  does not *always* hold


- Clipping (if you try to output  $Y > V_{cc}$ ,  $Y$  clips at  $V_{cc}$ )
- A comparitor circuit (no feedback), or
- A Schmitt trigger (positive feedback).



# Clipping

- If you are using negative feedback  $V_p = V_m$
- Unless you try to output a voltage that exceeds your power supplies


Example:  $y = 7.00x$

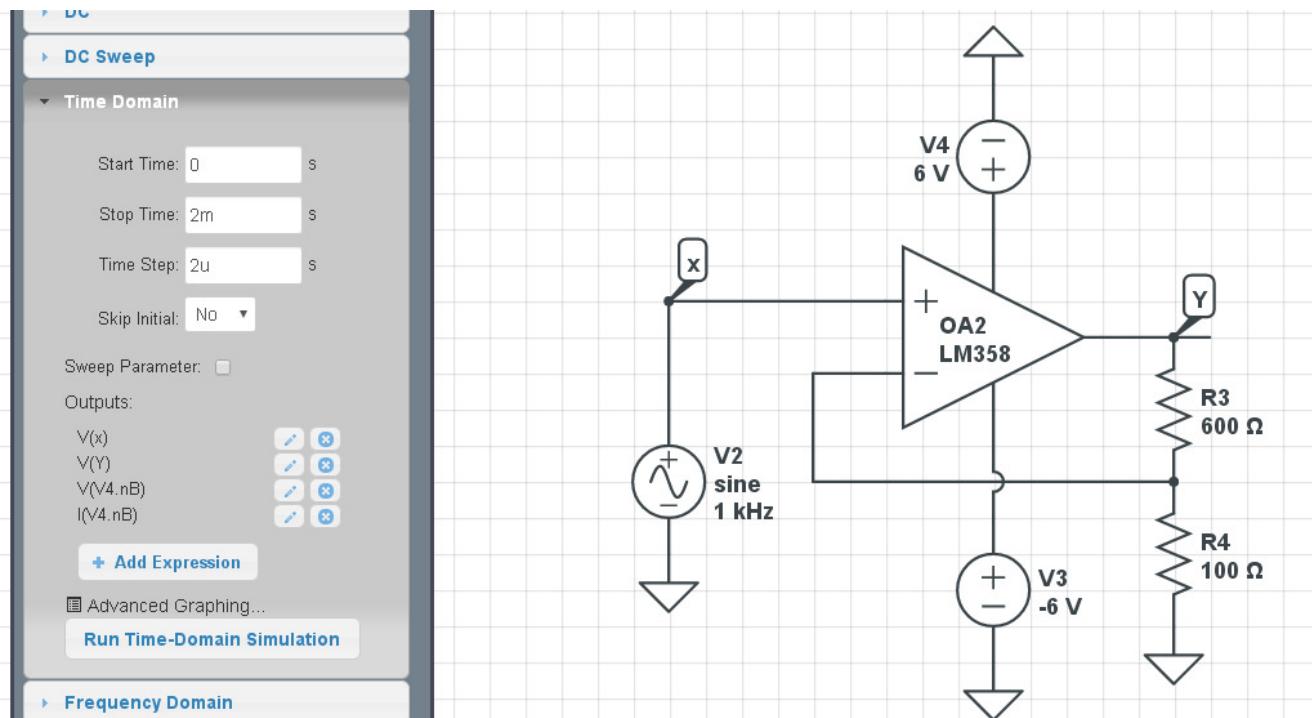

---

With a +6V and -6V power supply

- $Y = 7X$
- limited to  $-6V < Y < +6V$

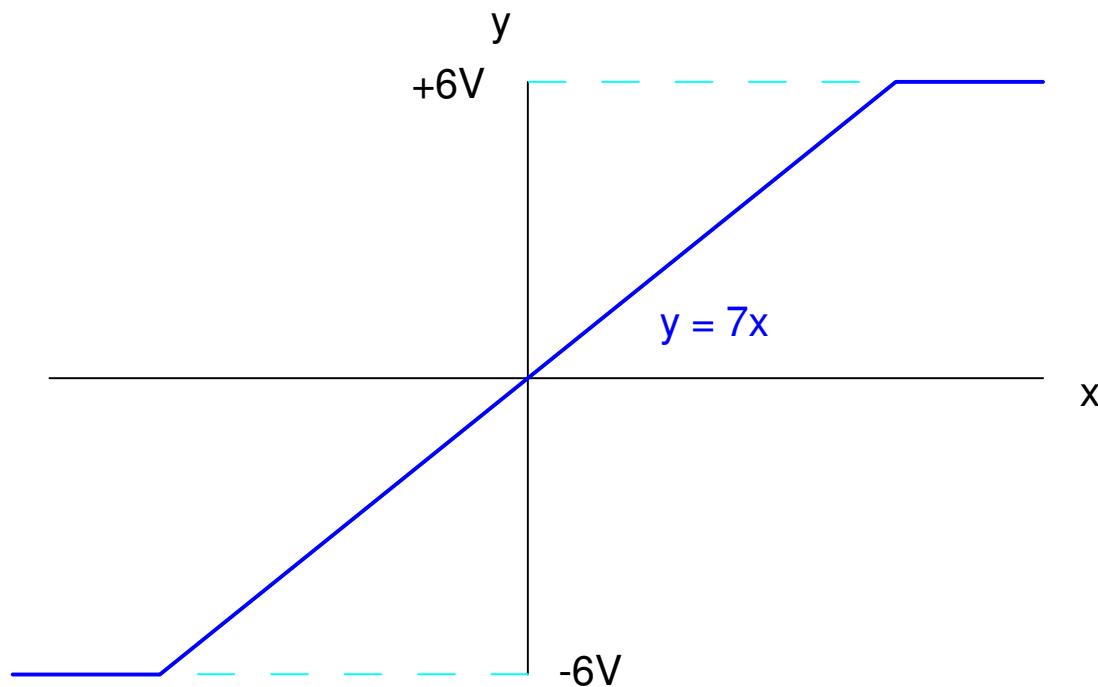


With +/- 6V power supplies, the output ( $y$ ) is limited to +6V and -6V

---

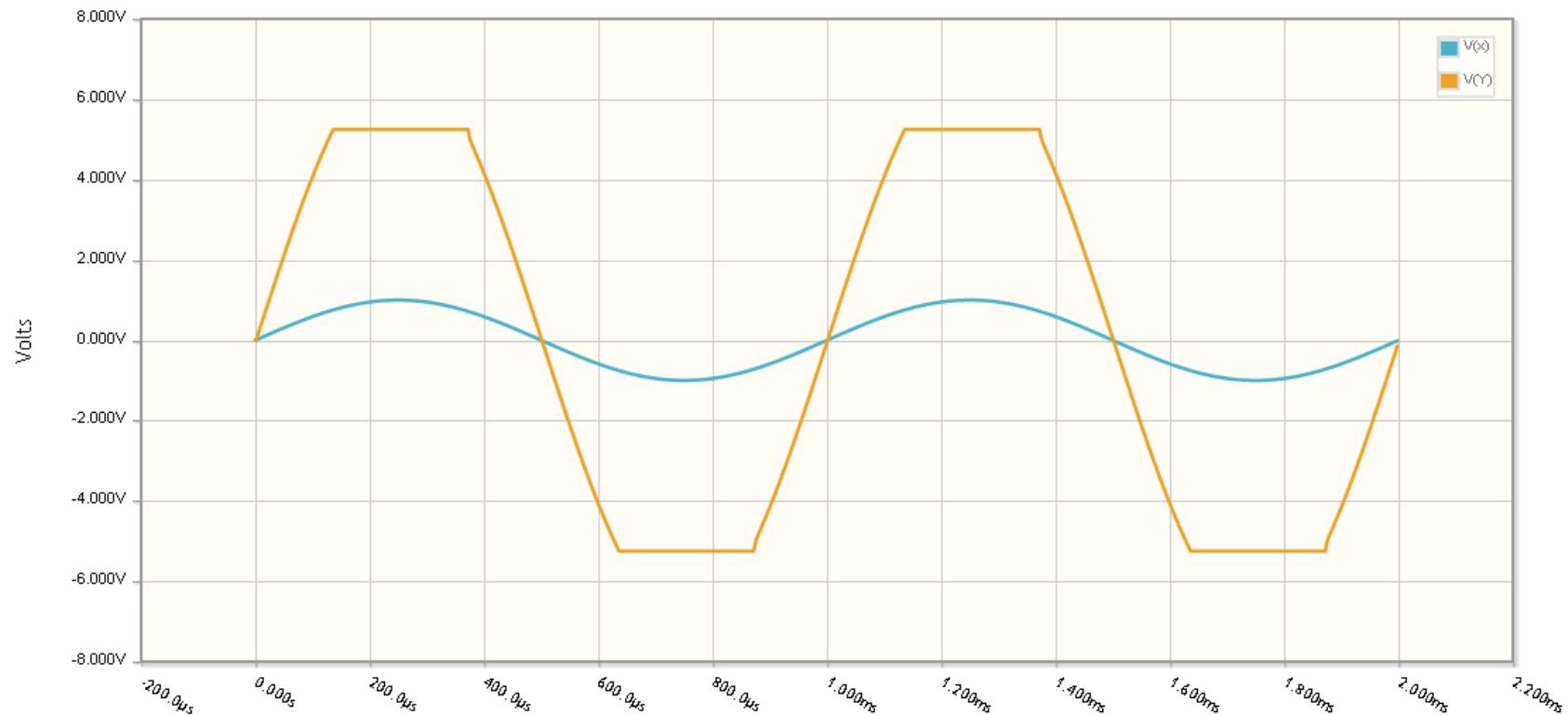
## Example:

- $V1 = 1\text{Vp}$ , 1kHz sine wave
- $V2 = 7\text{Vp}$ , 1kHz sine wave
- Clipped at  $\pm 6\text{V}$



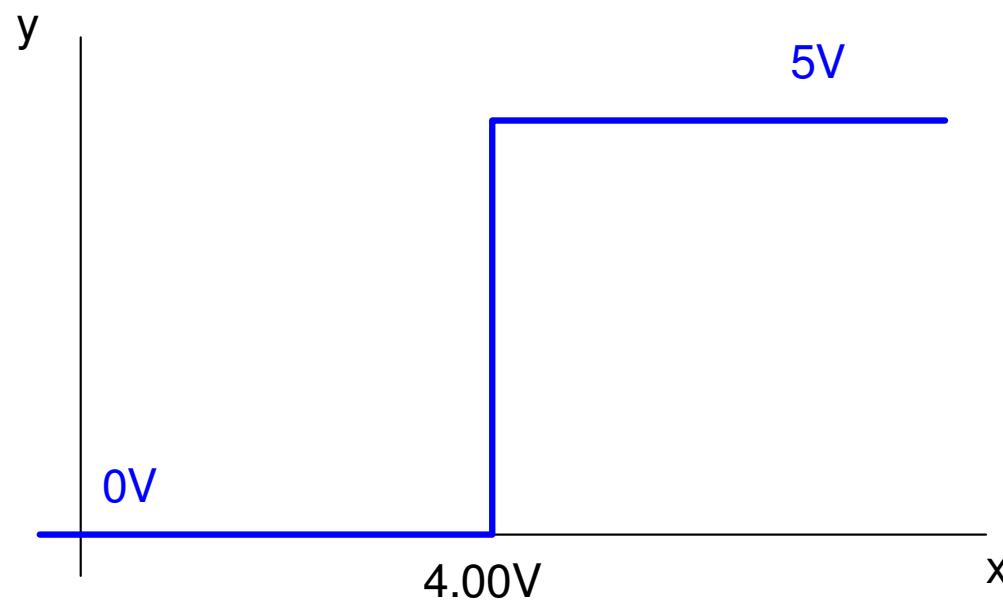
## Comparitors:

- Outputs a binary signal (0V, 5V typical)
- Turn a motor on (5V) or off (0V)
- Turn a light on (5V) or off (0V)




For example, design a circuit which outputs

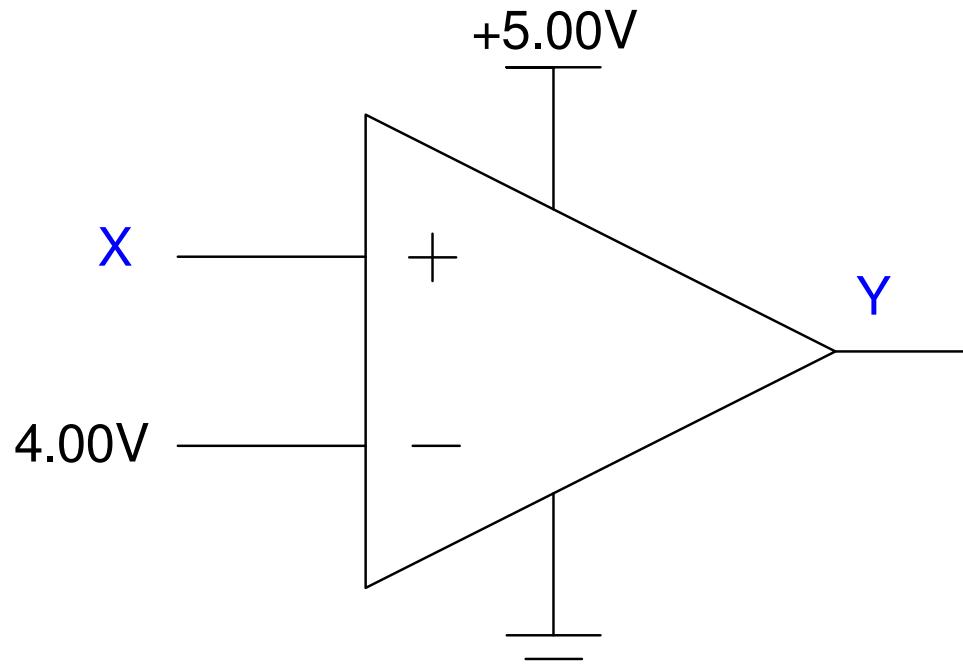- +5V when the input is more than 4.0V
- 0V when the input is less than 4.0V


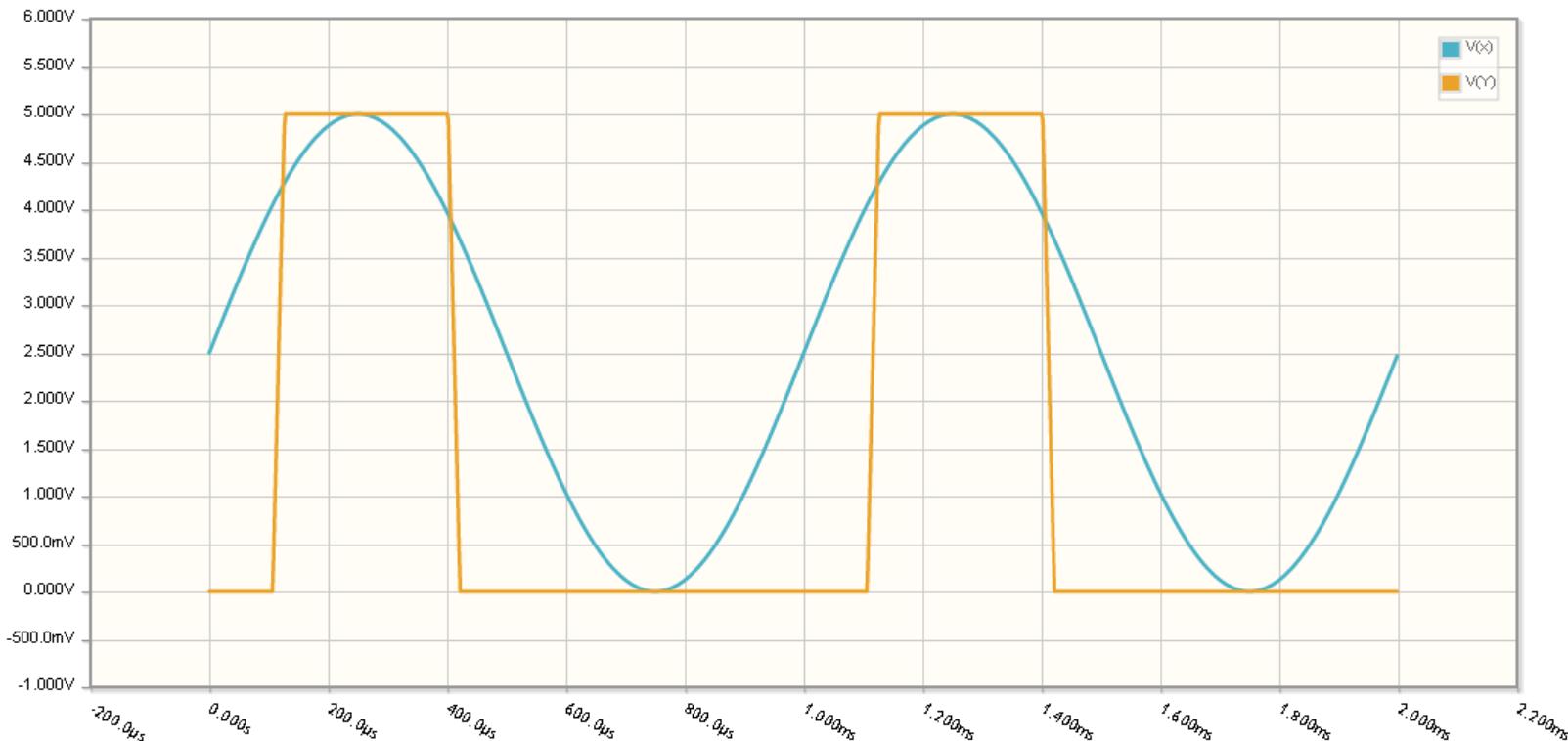
## CircuitLab Example:

- $X = 1\text{Vp}, 1\text{kHz}$  sine wave
- $y(t) = \begin{cases} 5\text{V} & x > 4.0\text{V} \\ 0\text{V} & otherwise \end{cases}$



## Temperature Sensor: Output

- +5V when the temperature is above +20C
- 0V when the temperature is below +20C

Use a thermistor where

$$R = 1000 \exp\left(\frac{3905}{T+273} - \frac{3905}{298}\right) \Omega$$


Solution: Use a voltage divider

- R = 1250.59 Ohms
- X = 2.7784V

As temperature goes up

- R goes down
- X goes down, and
- Y goes up (to +5V)


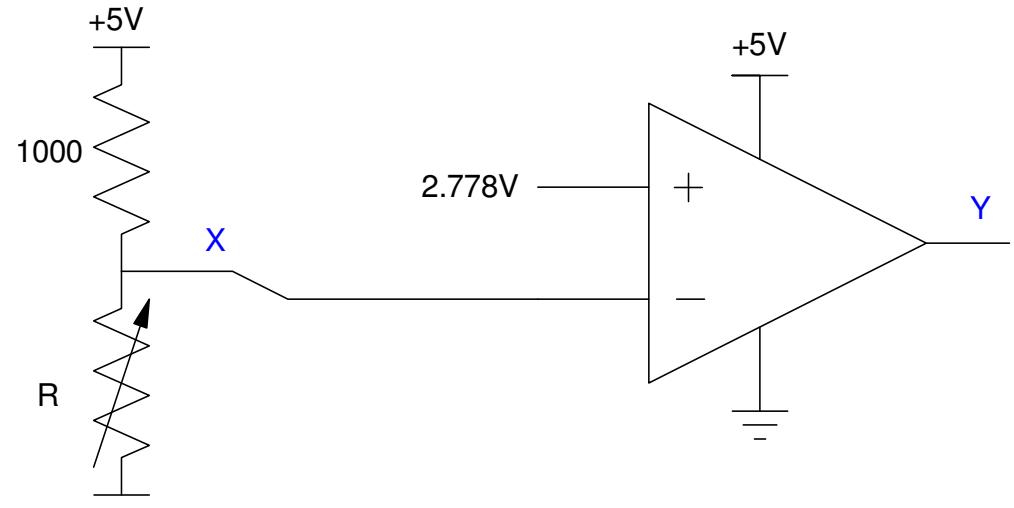
Connect the voltage divider to the negative input.


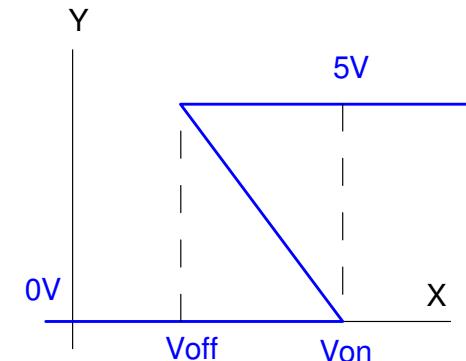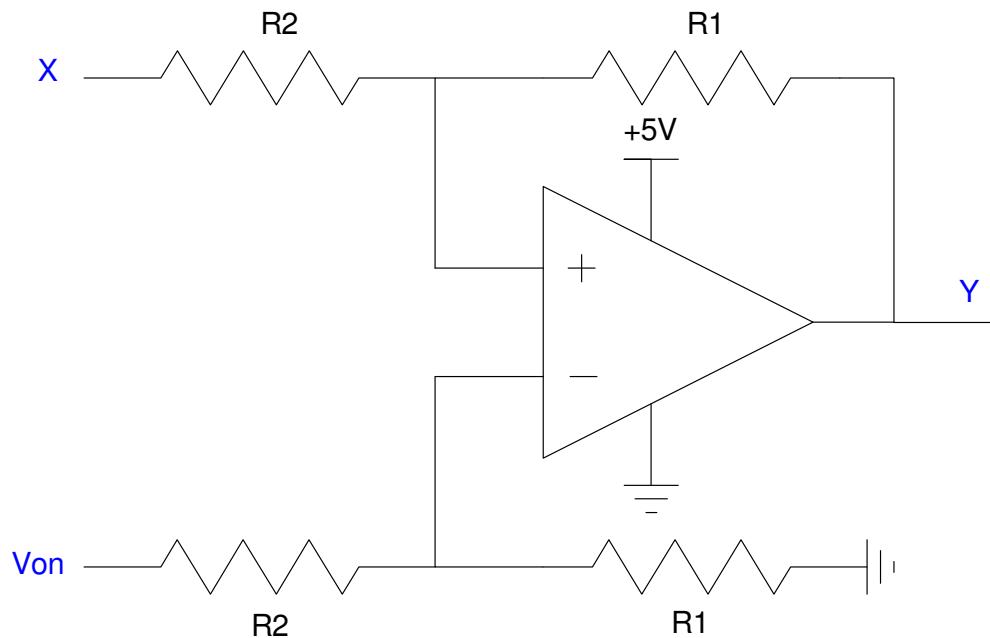
# Schmitt Trigger



- Comparitors chatter when  $V_p = V_m$
- To avoid this chatter, add hysteresis

$$Y = \begin{cases} 5V & X > V_{on} \\ 0V & X < V_{off} \\ \text{no change} & V_{off} < X < V_{on} \end{cases}$$



Flip inputs to get opposite relationship (Y = off when X is large)
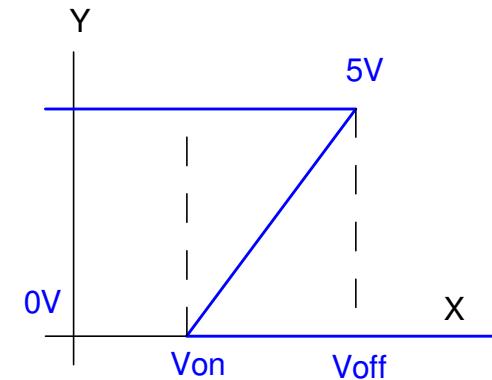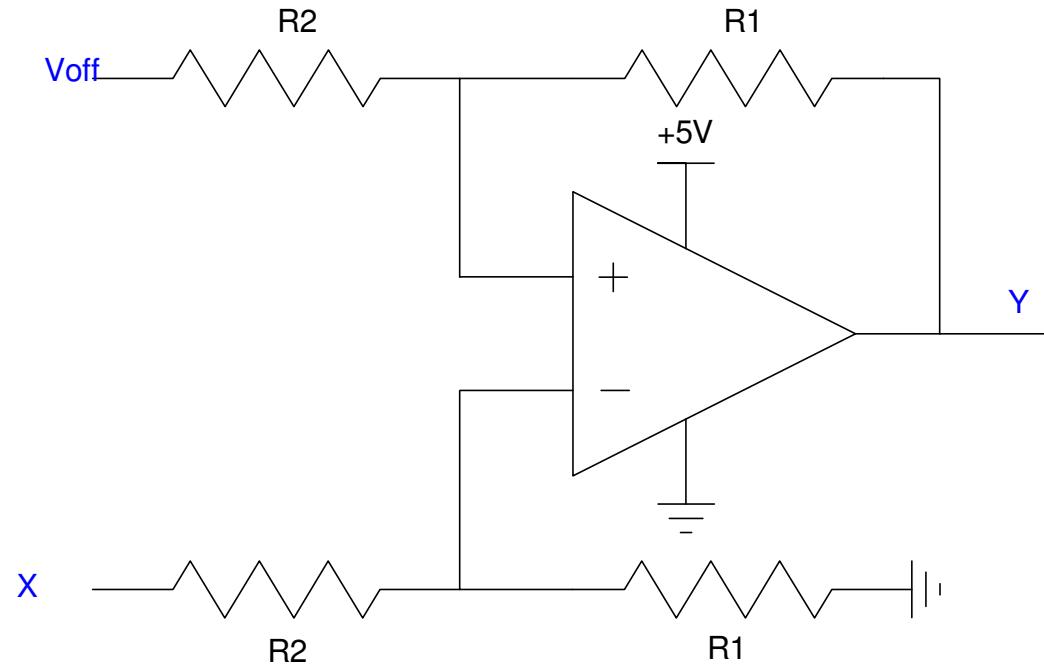
$$gain = \left( \frac{5V - 0V}{V_{off} - V_{on}} \right) = \left( \frac{R_1}{R_2} \right)$$



---

Example: Design a circuit which outputs

- 5V for temperatures more than 20C
- 0V for temperatures below 15C, and
- No change of 15C < T < 20C

Solution: Use a Schmitt Trigger. First, convert temperature to resistance and voltage. Assume a thermistor where

$$R = 1000 \exp\left(\frac{3905}{T+273} - \frac{3905}{298}\right) \Omega$$

along with a voltage divider with a 1k resistor.


---

At 20C (on)

- $R = 1250.59$  Ohms
- $X = 2.7784V$
- $Y = 5.00V$

At 15C (off)

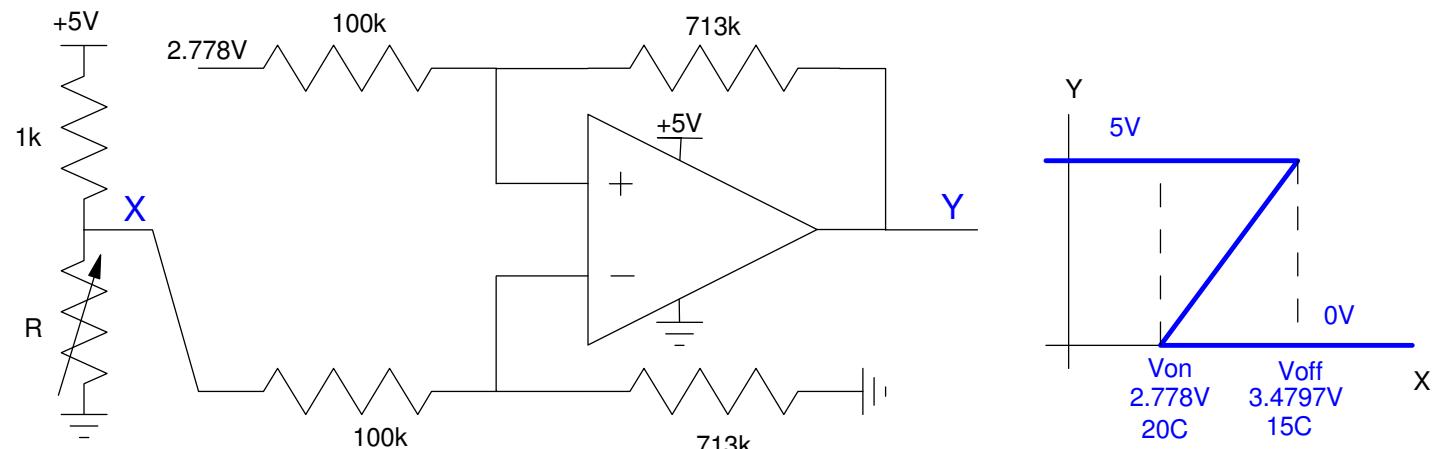- $R = 1576.17$  Ohms
- $X = 3.0591 V$
- $Y = 0.00V$



As X goes up, Y goes down. Connect to the minus input.

Y turns on at 2.7784V. Make the offset 2.7784V.


The gain required is

$$gain = \left( \frac{5V - 0V}{3.4797V - 2.7784V} \right) = 7.1296$$

Pick R1 and R2 in a 7.1296 : 1 ratio

Validation in CircuitLab

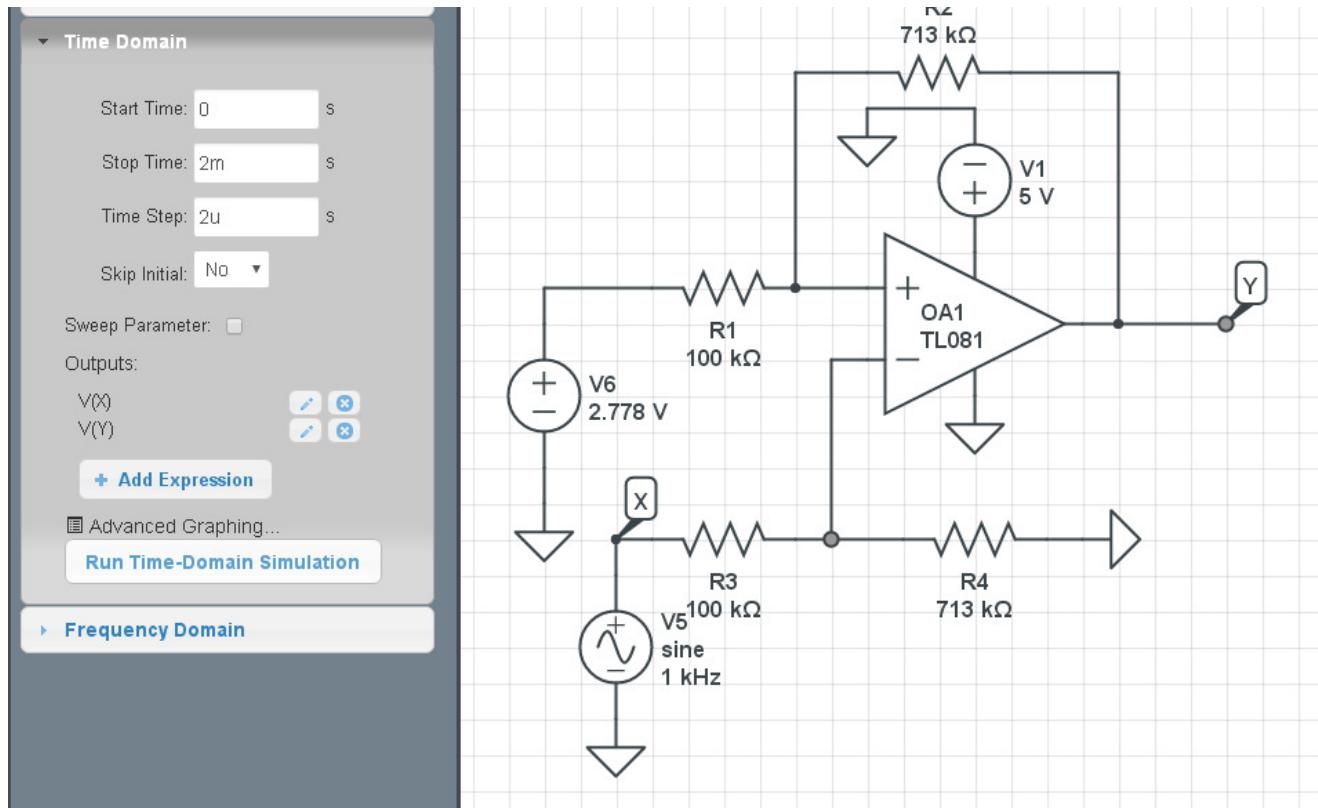- Sweep temperature and verify that Y switches at 20C and 15C, or
- Sweep R and verify that Y switches at 1250 Ohms and 1576 Ohms, or
- Sweep the voltage at X and verify that Y switches at 2.778V and 3.4797V



X = blue

$Y = \text{orange}$

- $V_{on} = 2.760V$
- $V_{off} = 3.514V$

