

---

# **Op-Amp Circuits with Phasors**

## **EE 206 Circuits I**

**Jake Glower**

**03/19/20**


Please visit Bison Academy for corresponding  
lecture notes, homework sets, and solutions

---

# Single-Pole Low-Pass Filter

Find the voltage,  $y(t)$ , for

$$x(t) = 3 \sin(50t)$$

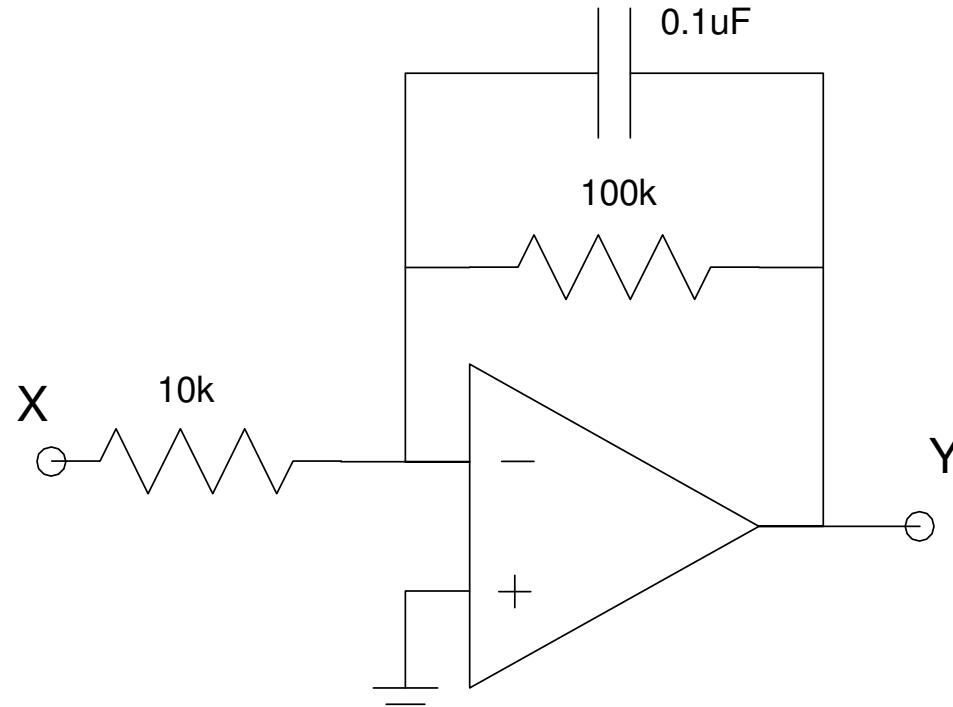


## Step 1:

- Define ground (already done)
- Define the voltage nodes
- Convert to the phasor domain

$$x(t) = 3 \sin(50t) \rightarrow X = 0 - j3$$
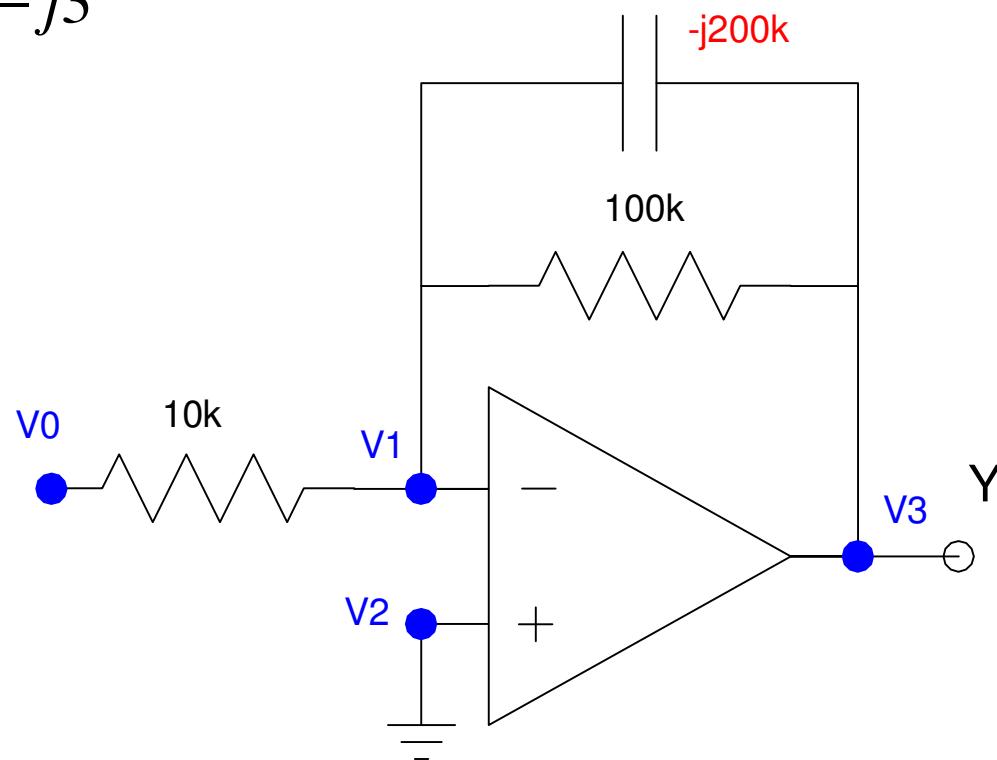
$$0.1\mu F \rightarrow \frac{1}{j\omega C} = -j200k$$



---


## Step 2: Write the voltage node equations

$$V_0 = -j3$$

$$V_1 = V_2$$

$$V_2 = 0$$
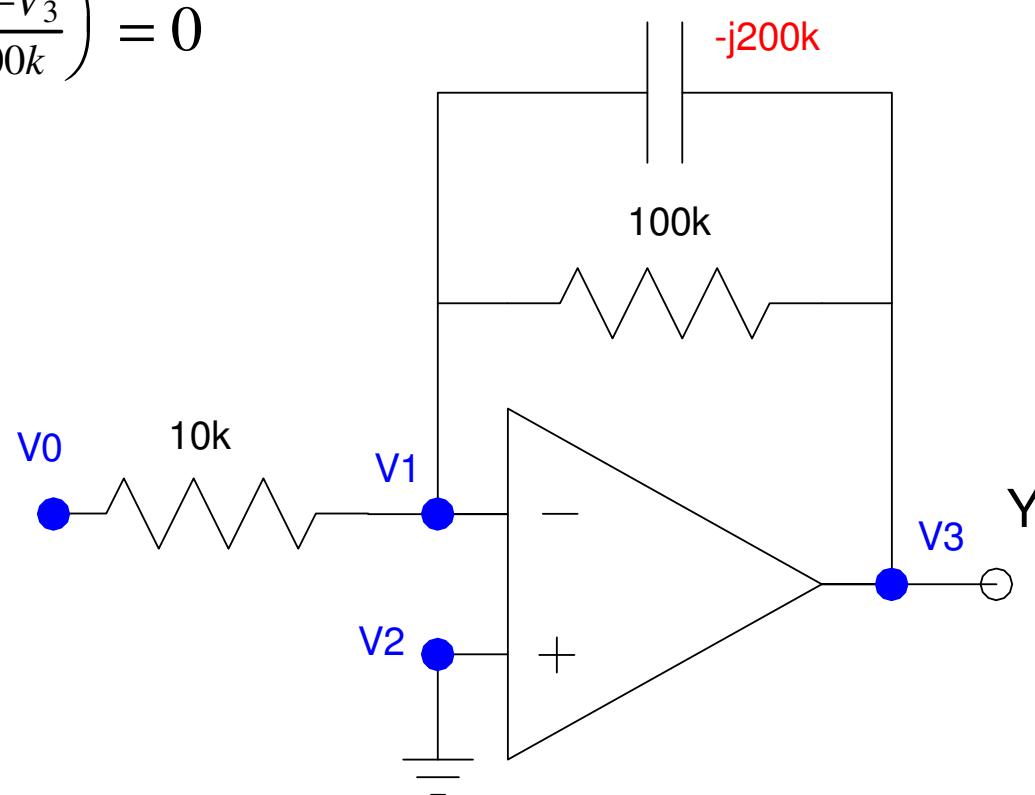
$$\left(\frac{V_1 - V_0}{10k}\right) + \left(\frac{V_1 - V_3}{-j200k}\right) + \left(\frac{V_1 - V_3}{100k}\right) = 0$$



---

Solve

$$V_3 = 12 + j24 = 26.8 \angle 63^\circ$$


meaning


$$v_3(t) = 12 \cos(50t) - 24 \sin(50t)$$

$$v_3(t) = 26.8 \cos(50t + 63^\circ)$$

Checking in CircuitLab: The input is
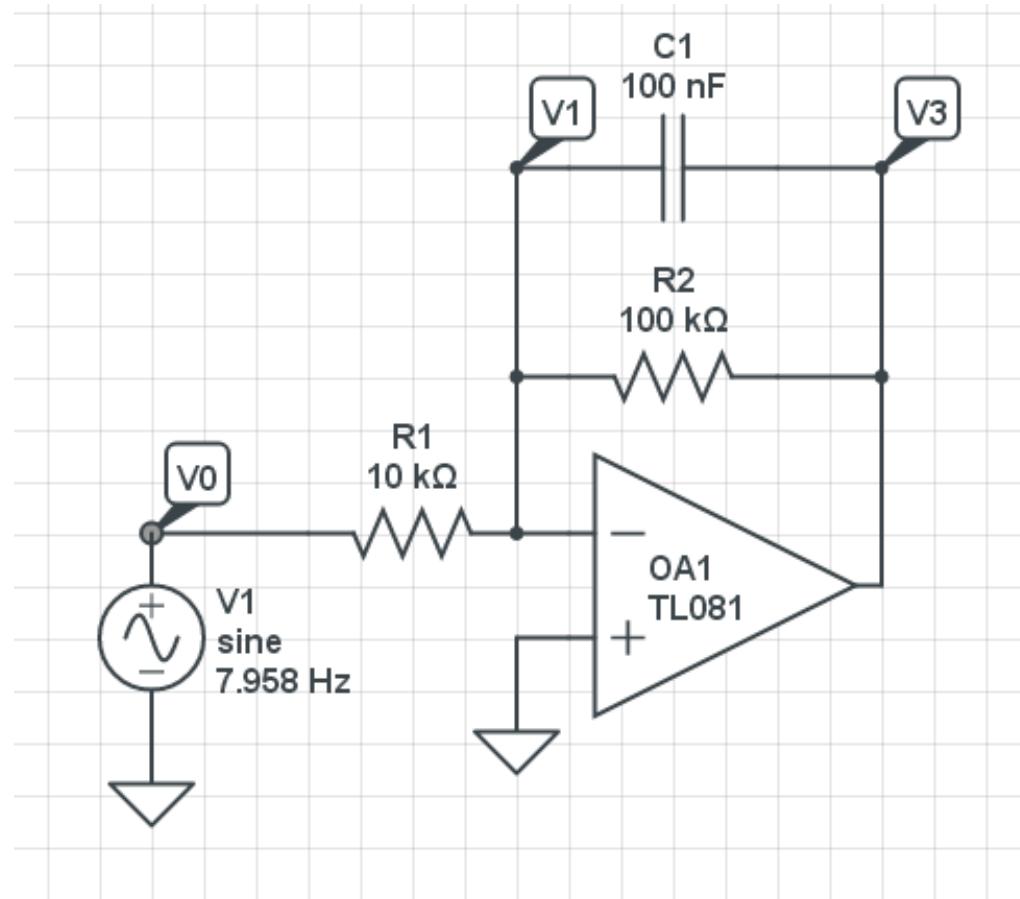
$$H_z = \frac{\omega}{2\pi} = \frac{50 \text{ rad/sec}}{2\pi} = 7.958 \text{ Hz}$$



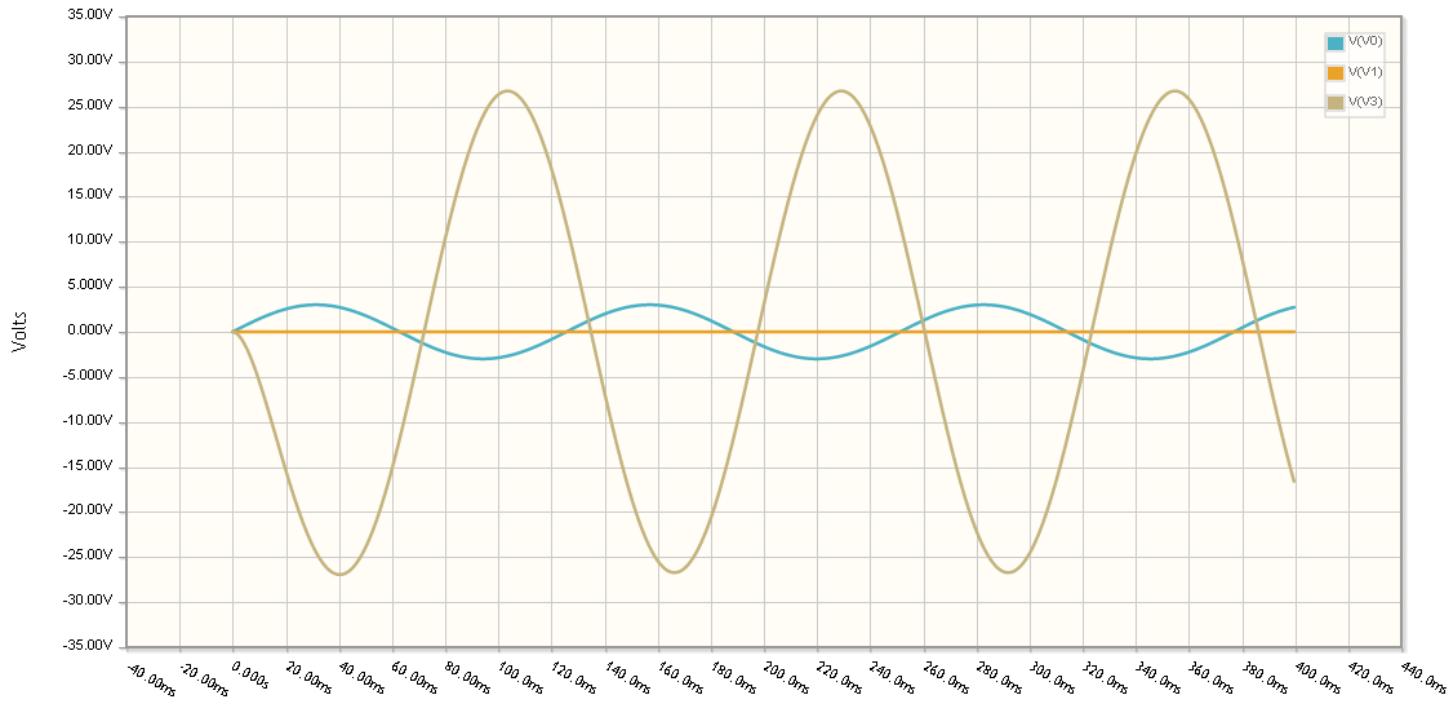


- The period is 126ms ( $7.958\text{Hz} = 50 \text{ rad/sec}$ )
- The peak is 26.825V ( vs. 26.8V calculated )
- The peak of  $V_3$  is at  $t = 104.6\text{ms}$  (delay = -297 degrees)

This matches our calculations

## Example 2: Two-Pole Op-Amp Circuit

Find  $y(t)$  for

$$x(t) = 3 \cos(40t)$$

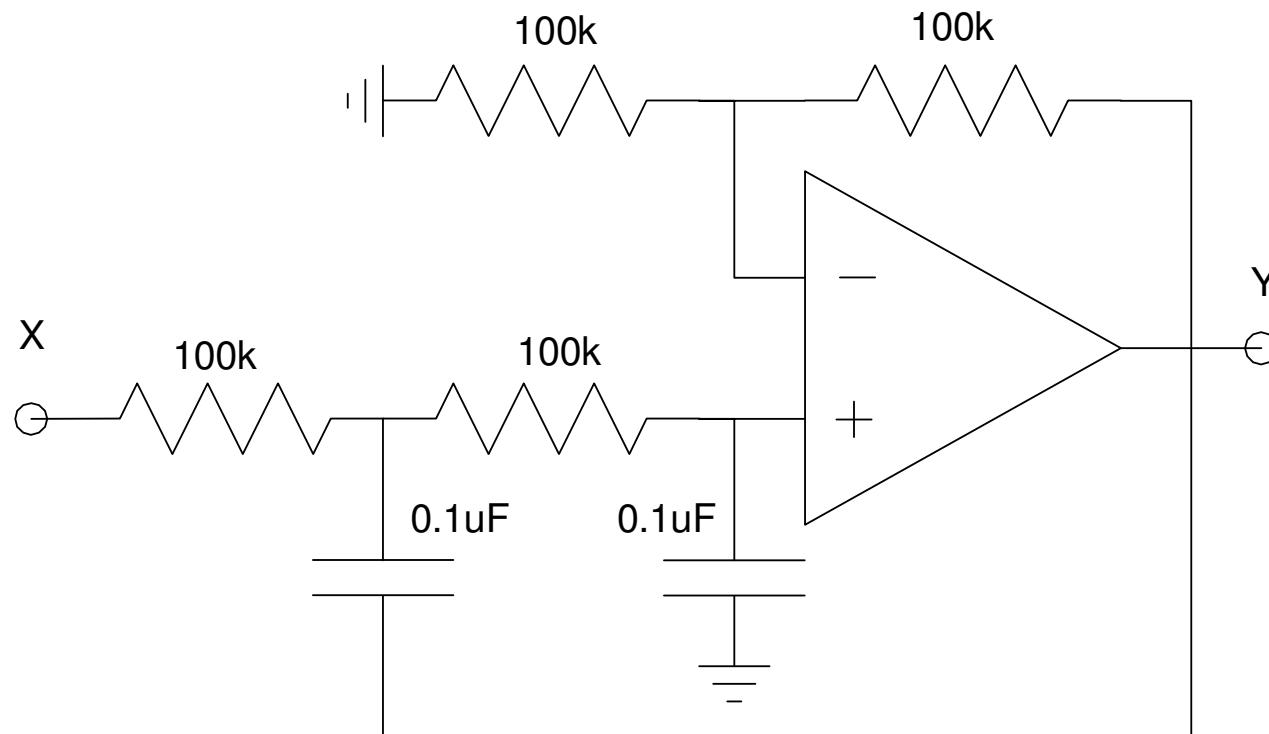


## Step 1:

- Define circuit ground (already done)
- Define the voltage nodes
- Convert to phasors

$$3 \cos(40t) \rightarrow 3 + j0$$
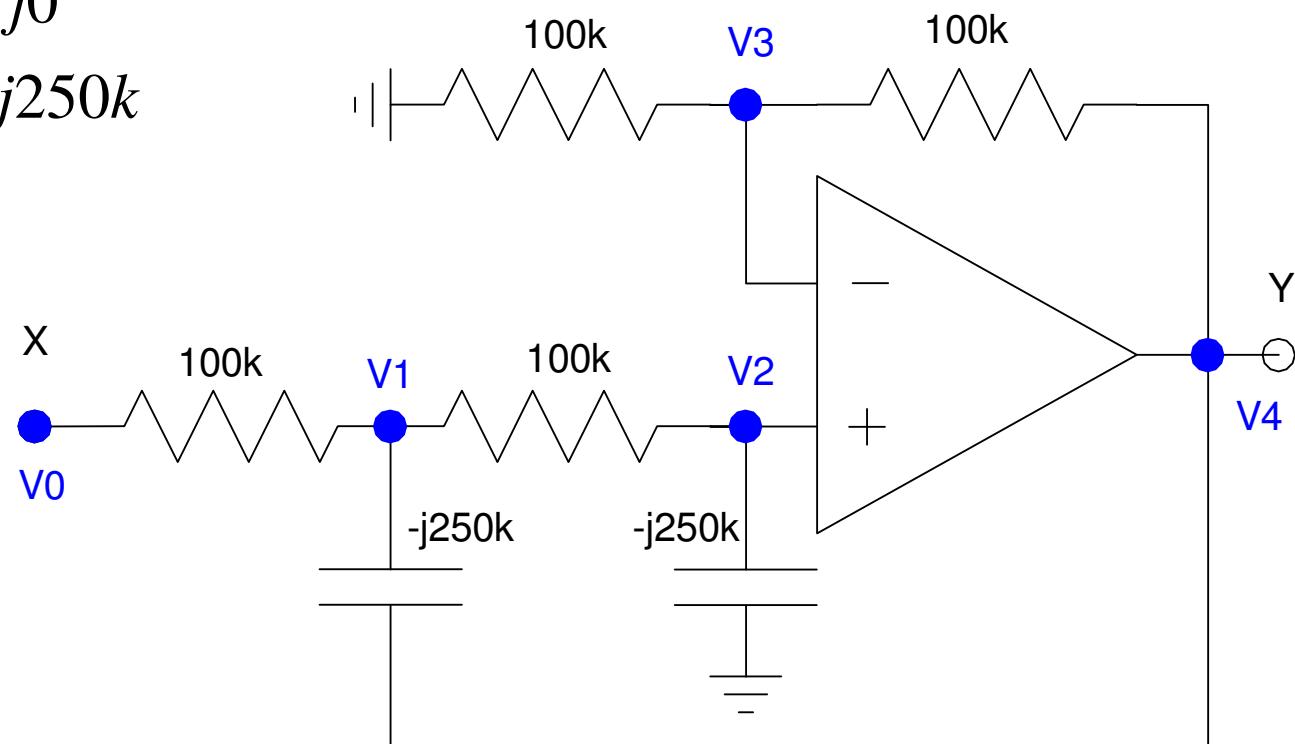
$$0.1 \mu F \rightarrow \frac{1}{j\omega C} = -j250k$$



## Step 2: Write the voltage node equations.


$$V_0 = 3 + j0$$

$$V_2 = V_3$$

$$\left(\frac{V_1 - V_0}{100k}\right) + \left(\frac{V_1 - V_4}{-j250k}\right) + \left(\frac{V_1 - V_2}{100k}\right) = 0$$

$$\left(\frac{V_2 - V_1}{100k}\right) + \left(\frac{V_2 - 0}{-j250k}\right) = 0$$
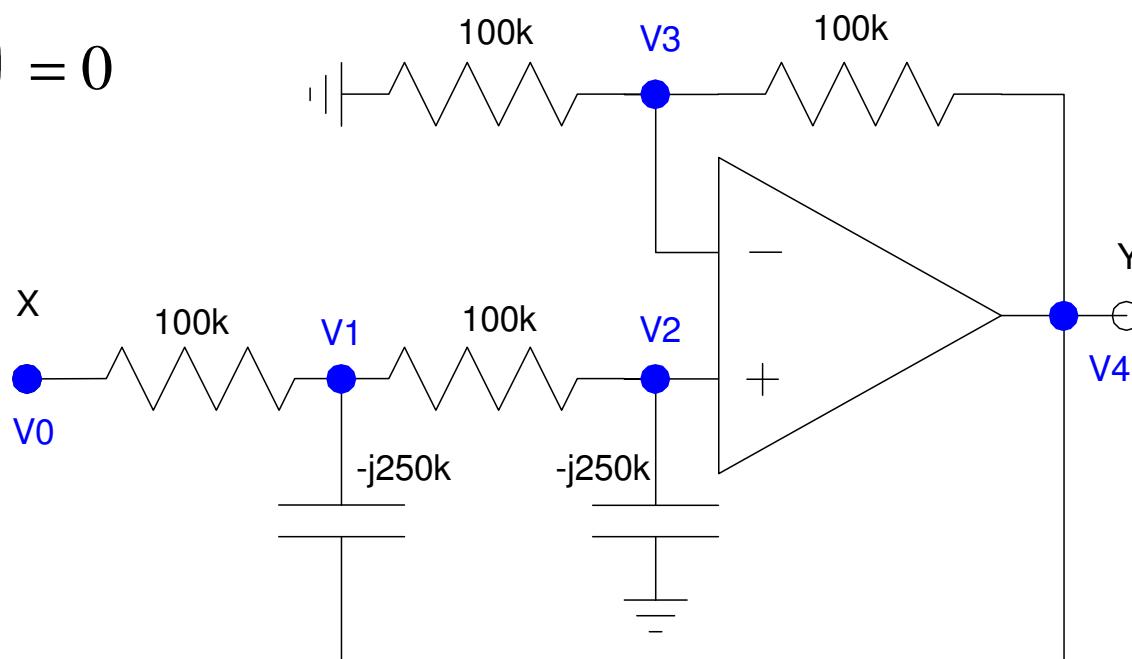
$$\left(\frac{V_3 - 0}{100k}\right) + \left(\frac{V_3 - V_4}{100k}\right) = 0$$



---

## Step 3: Solve

Group terms

$$V_0 = 3$$

$$V_2 - V_3 = 0$$

$$\left(\frac{-1}{100k}\right)V_0 + \left(\frac{1}{100k} + \frac{1}{-j250k} + \frac{1}{100k}\right)V_1 + \left(\frac{-1}{100k}\right)V_2 + \left(\frac{-1}{100k}\right)V_4 = 0$$

$$\left(\frac{-1}{100k}\right)V_1 + \left(\frac{1}{100k} + \frac{1}{-j250k}\right)V_2 = 0$$

$$\left(\frac{1}{100k} + \frac{1}{100k}\right)V_3 + \left(\frac{-1}{100k}\right)V_4 = 0$$


V1	3.4658041	-	0.2218115i
V2	2.9112754	-	1.3863216i
V3	2.9112754	-	1.3863216i
V4	5.8225508	-	2.7726433i

= Y

---

$$v_4(t) = 5.822 \cos(40t) + 2.77 \sin(40t)$$

## Checking in CircuitLab:

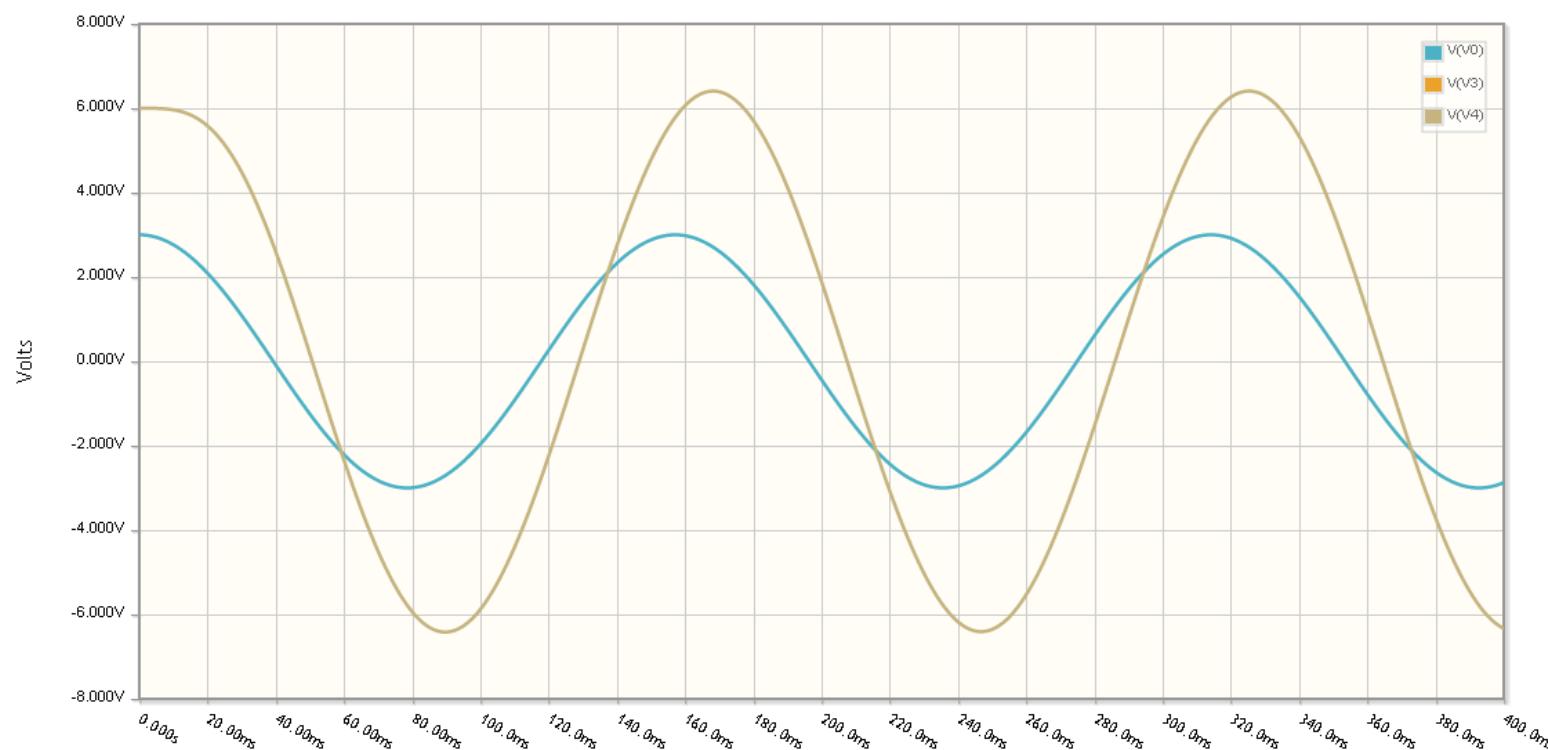

The output peak is 6.447V ( vs. 6.447V computed )

$$\phi = \left( \frac{9.9\text{ms delay}}{157\text{ms period}} \right) \cdot 360^\circ = 22.7^\circ \text{ delay ( vs. 25 degrees computed )}$$

