

---

# **Superposition with Phasors**

## **EE 206 Circuits I**

**Jake Glower**

**03/19/20**

Please visit [Bison Academy](#) for corresponding  
lecture notes, homework sets, and solutions

---


# Superposition with Phasors

Op-Amp circuits with RLC components are linear circuits. *Linear* means

$$f(ax + by) = af(x) + bf(y)$$

In English, this means that

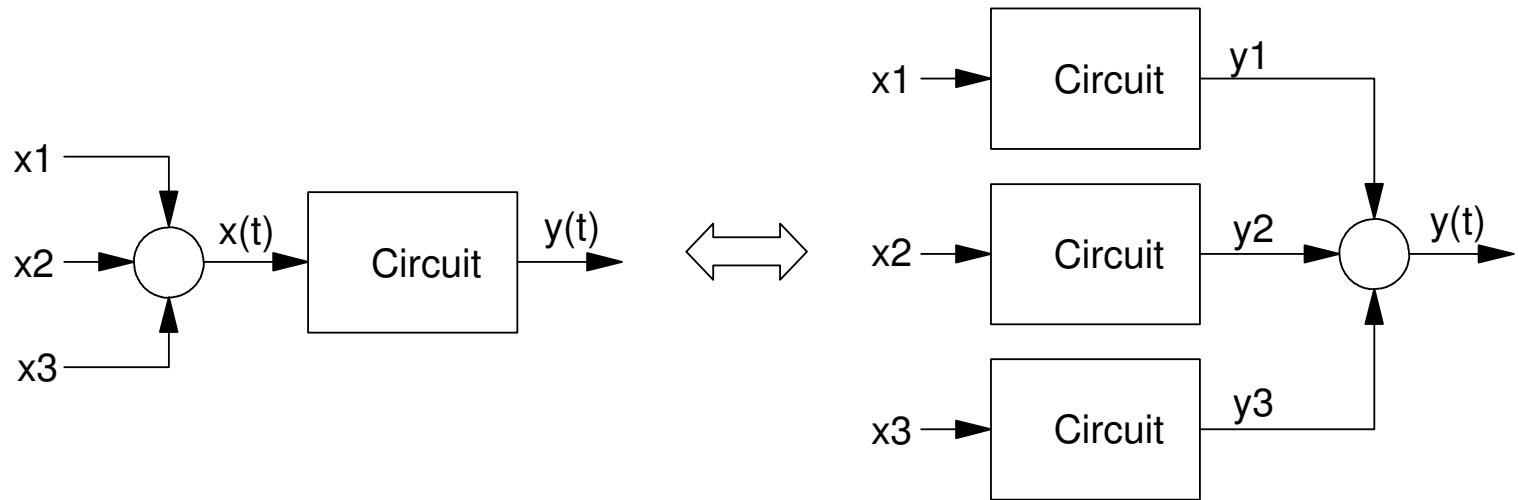
- If the input has N terms,
- You can treat this as N separate problems.


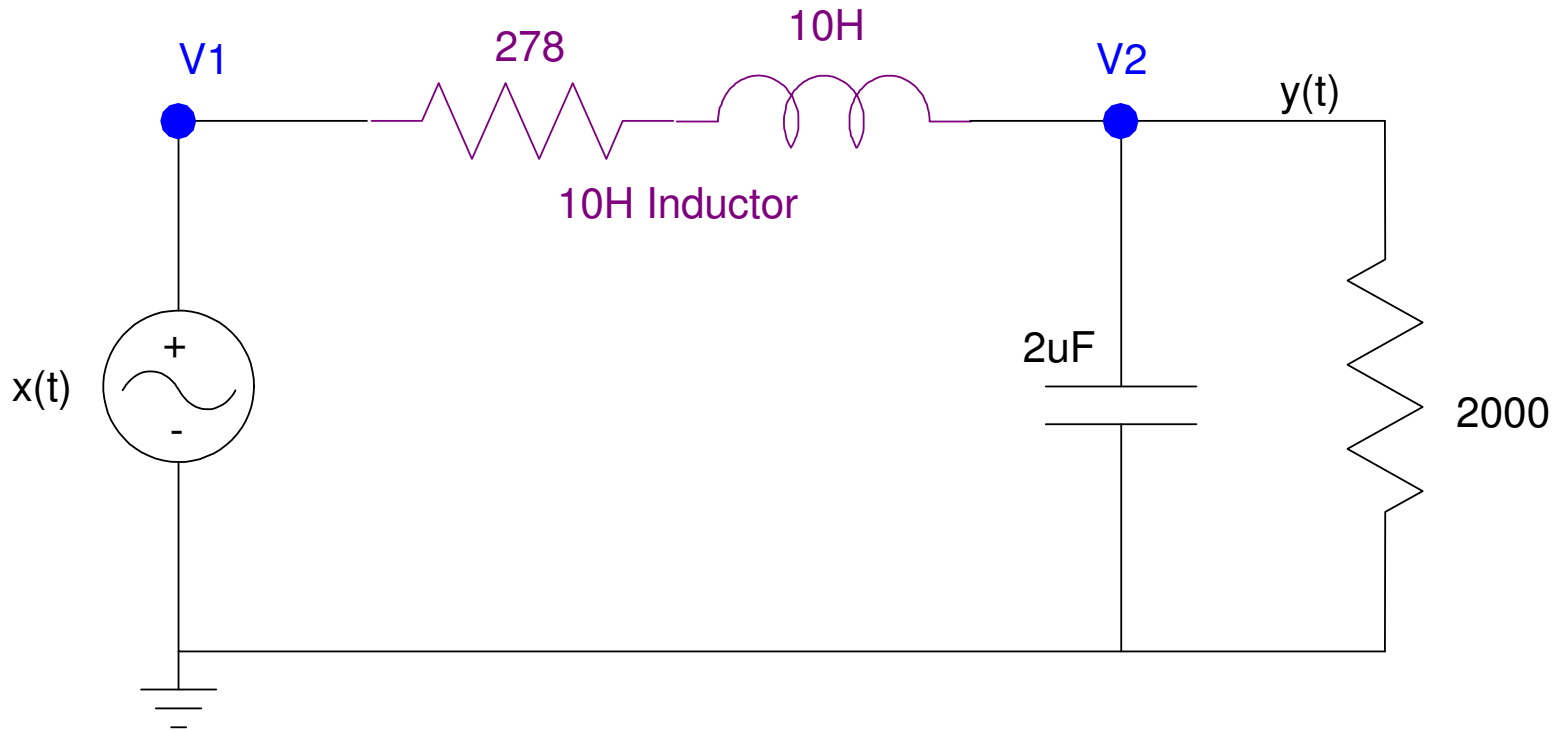
## Example: RLC Filter

Determining  $y(t)$  for the following circuit assuming

$$x(t) = 10 + 9 \sin(100t) + 8 \cos(200t)$$



Solution: Use superposition and treat this as three separate problems.


## Analyze at $\omega = 0$ (DC)

$$x_1(t) = 10$$

Analyze the circuit for this input.

$$\omega = 0 \qquad L \rightarrow j\omega L = 0 \qquad C \rightarrow \frac{1}{j\omega C} = \infty$$
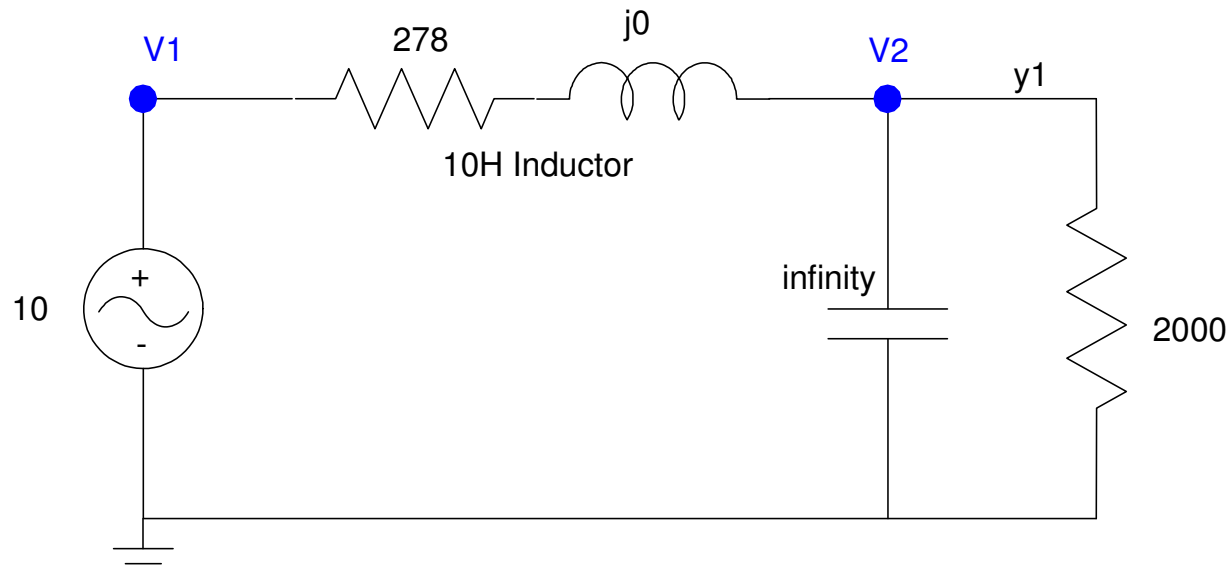
$$Y_1 = \left( \frac{2000}{2000+278} \right) \cdot 10 = 8.7796$$



## Analyze at $\omega = 100$ rad/sec

$$x_2(t) = 9 \sin(100t)$$


$$\omega = 100$$

$$X = 0 - j9$$

$$L \rightarrow j\omega L = j1000$$

$$C \rightarrow \frac{1}{j\omega C} = -j5000$$
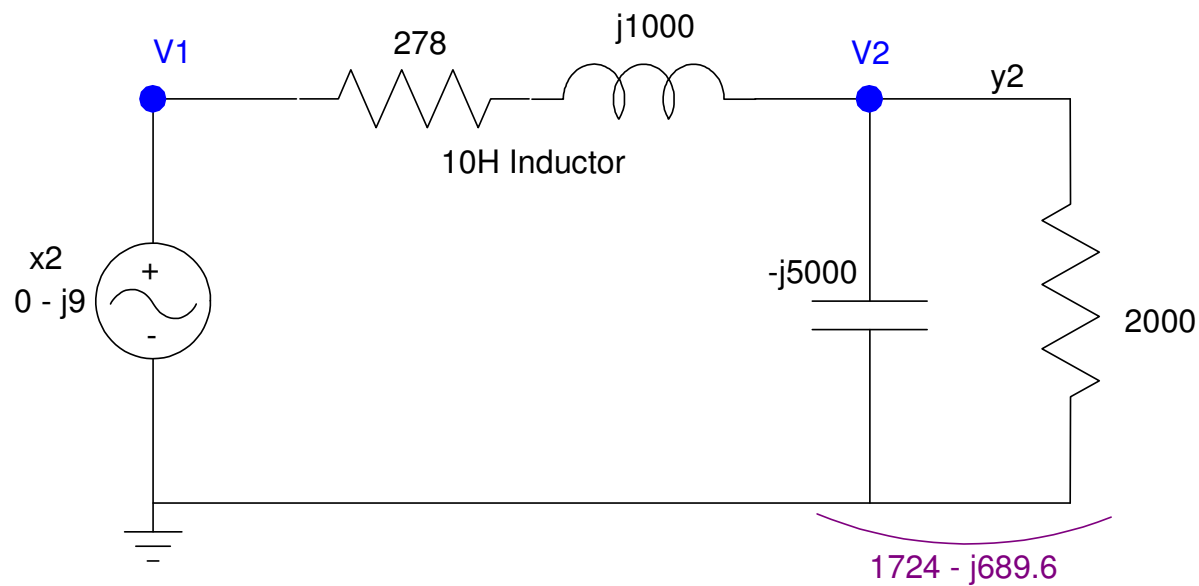
$$Y_2 = \left( \frac{(1724 - j689.6)}{(1724 - j689.6) + (278 + j1000)} \right) \cdot (0 - j9) = -4.201 - j7.099$$



## Analyze at $\omega = 200$ rad/sec


$$x_3(t) = 8 \cos(200t)$$

$$X = 8 + j0$$

$$L \rightarrow j\omega L = j2000$$

$$\omega = 200$$

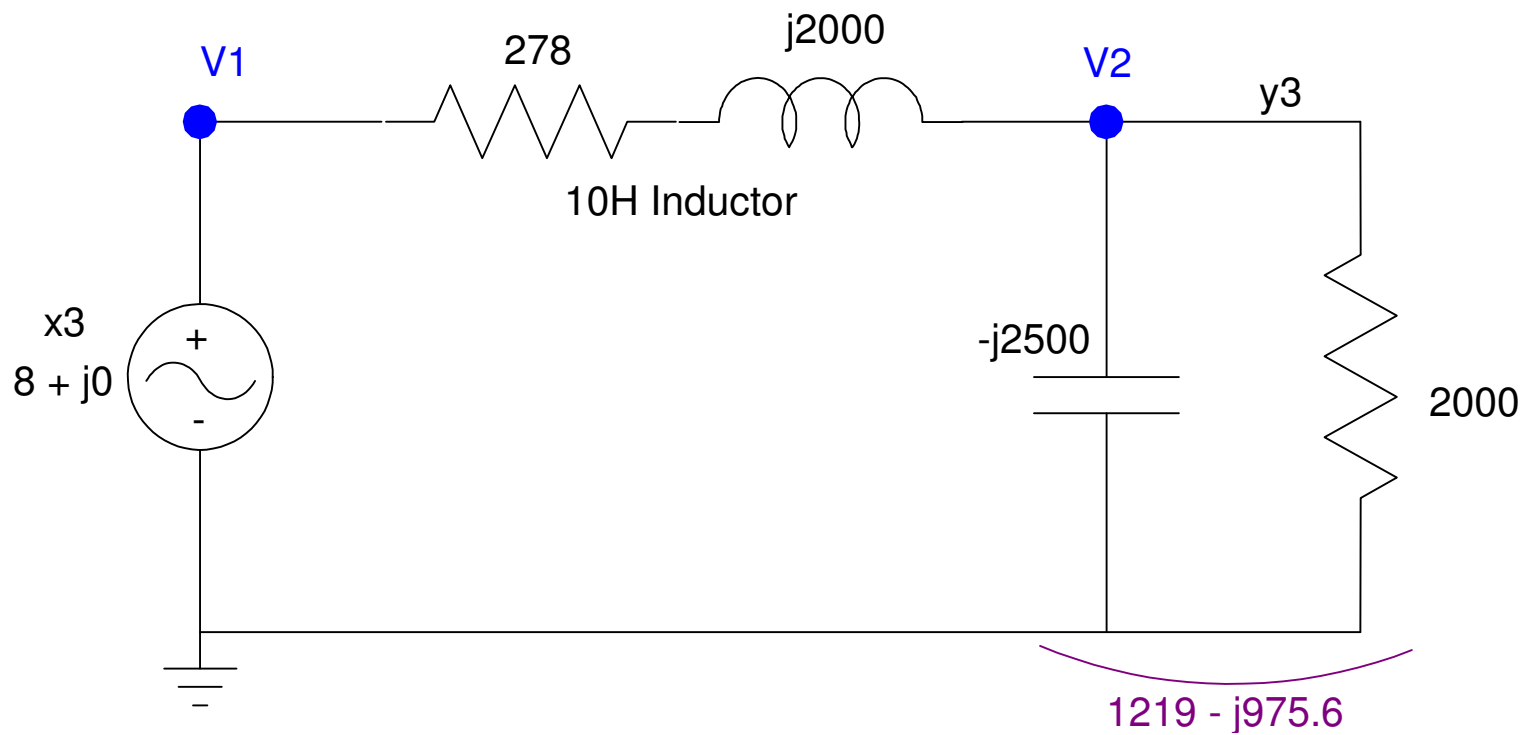
$$C \rightarrow \frac{1}{j\omega C} = -j2500$$



$$\left( \frac{1}{2000} + \frac{1}{-j2500} \right)^{-1} = 1219 - j975.6$$

$$Y = \left( \frac{1219 - j975.6}{(1219 - j975.6) + (278 - j2000)} \right) \cdot (8 + j0)$$

$$Y = 2.009 - j6.586$$

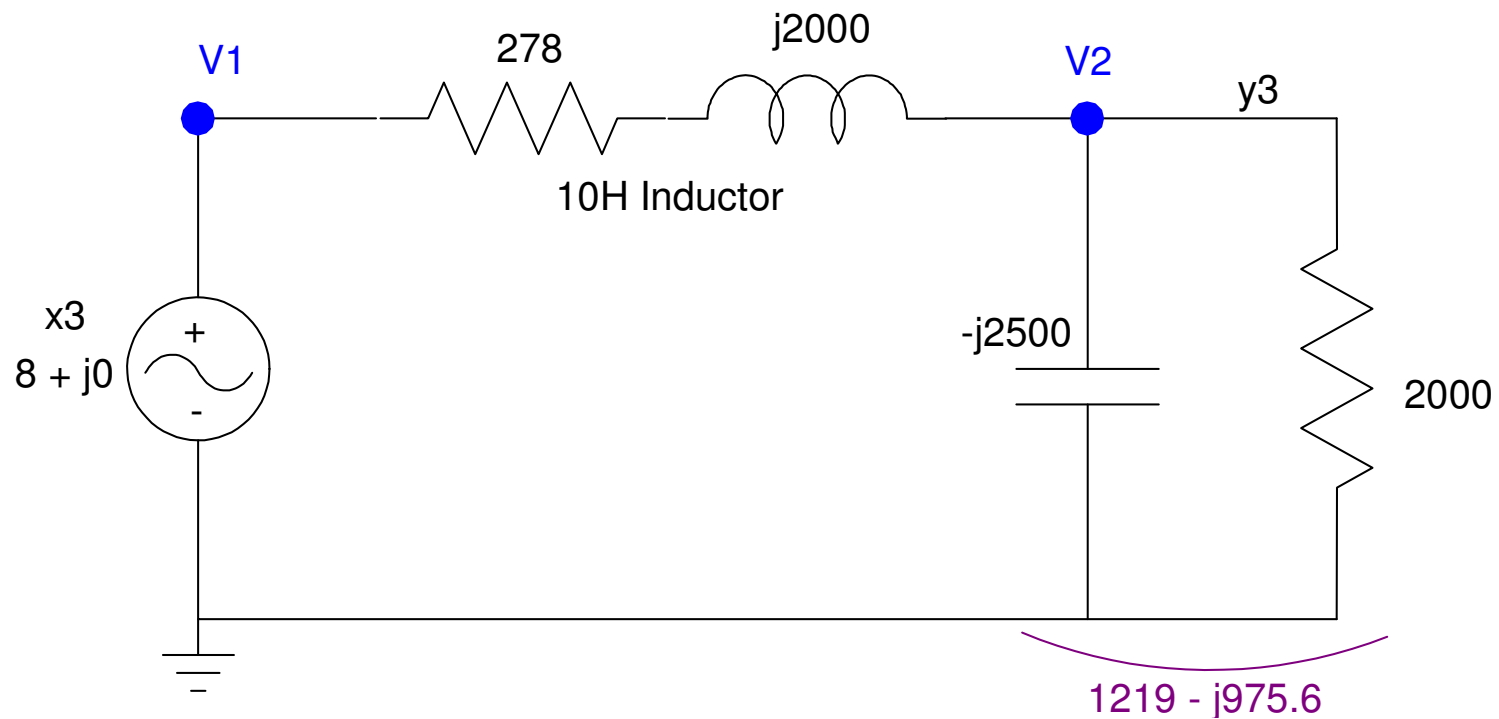

---

The total answer is the sum of the three parts

$$y(t) = y_1 + y_2 + y_3$$

$$\omega = 0 \quad Y_1 = 8.7796$$

$$\omega = 100 \quad Y_2 = -4.201 - j7.099$$

$$\omega = 200 \quad Y_3 = 2.009 - j6.596$$

$$y(t) = 8.7796 \\ -4.201 \cos(100t) + 7.099 \sin(100t) \\ +2.009 \cos(200t) + 6.596 \sin(200t)$$

---