

# ECE 311 - Homework #5

## Complex Power

1) Determine the voltage, current, impedance, and power for the following

	Voltage	Current	Impedance	Power
a)	$10 + j20$	$30 + j40$		
b)	$10 + j20$		$30 + j30$	
c)	$10 + j20$			$30 + j40$
d)			$10 + j20$	$30 + j40$

2) Determine the voltage, current, impedance, and power for the following

	Voltage	Current	Impedance	Power
a)	$10\angle 20^\circ$	$30\angle 40^\circ$		
b)	$10\angle 20^\circ$		$30\angle 40^\circ$	
c)	$10\angle 20^\circ$			$30\angle 40^\circ$
d)			$10\angle 20^\circ$	$30\angle 40^\circ$