

ECE 311 - Homework #3

Phasors (review)

1) Find Y as a complex number

$$Y = \left(\frac{50s+3}{(s+2)(s+5)} \right)_{s=-1+j2}$$

Using Matlab (overkill - your calculator should also work. Especially on midterms...)

```
>> s = -1 + j*2;  
>> Y = (50*s + 3) / ( (s+2)*(s+5) )
```

Y =

10.0000 + 4.7000i

2) Find Y as a complex number

$$Y = \left(\frac{200}{s^3+6s^2+8s+50} \right)_{s=-3+j4}$$

```
>> s = -3 + j*4;  
>> Y = 200 / ( s^3 + 6*s^2 + 8*s + 50)
```

Y =

1.3626 + 0.9174i

3) Express y(t) in phasor form

real = cosine(), -imag = sine()

a) $y(t) = 3 \cos(10t) + 7 \sin(10t)$

$$Y = 3 - j7$$

b) $y(t) = -2 \cos(50t) + 200 \sin(50t)$

$$Y = -2 - j200$$

c) $y(t) = 20 \sin(30t)$

$$Y = 0 - j20$$

4) Determine the phasor impedance of the following

a) 10mH inductor operating at 100Hz

$$100 \text{ Hz} = 377 \text{ rad/sec}$$

$$\omega = 2\pi f = 2\pi \cdot 100\text{Hz}$$

The impedance of an inductor is

$$Z = j\omega L = j \cdot 628 \cdot 10\text{mH}$$

$$Z = j6.28\Omega$$

b) 10mH inductor operating at 1000 Hz

$$\omega = 2\pi f = 6283$$

$$Z = j\omega L = j \cdot 6283 \cdot 10\text{mH}$$

$$Z = j62.8\Omega$$

for inductors, the impedance goes up with frequency

c) 0.1uF capacitor operating at 100Hz

$$Z = \frac{1}{j\omega C} = \frac{1}{j \cdot 628 \cdot 0.1\mu\text{F}}$$

$$Z = -j15,915\Omega$$

d) 0.1uF capacitor operating at 1000Hz

$$Z = \frac{1}{j\omega C} = \frac{1}{j \cdot 6283 \cdot 0.1\mu\text{F}}$$

$$Z = -j1,591\Omega$$

for capacitors, impedance goes down as frequency goes up

5) Assume V_{in} contains a DC and 16Hz (100 rad/sec) signal:

$$V_{in} = 10 + 3 \sin(100t)$$

a) Determine the impedances of the inductor, capacitor, and resistor at DC and 100 rad/sec

DC (blue)

AC (red)

$$\omega = 0$$


$$\omega = 100$$

$$L \rightarrow j\omega L = 0$$

$$L \rightarrow j\omega L = j10$$

$$C \rightarrow \frac{1}{j\omega C} = \infty$$
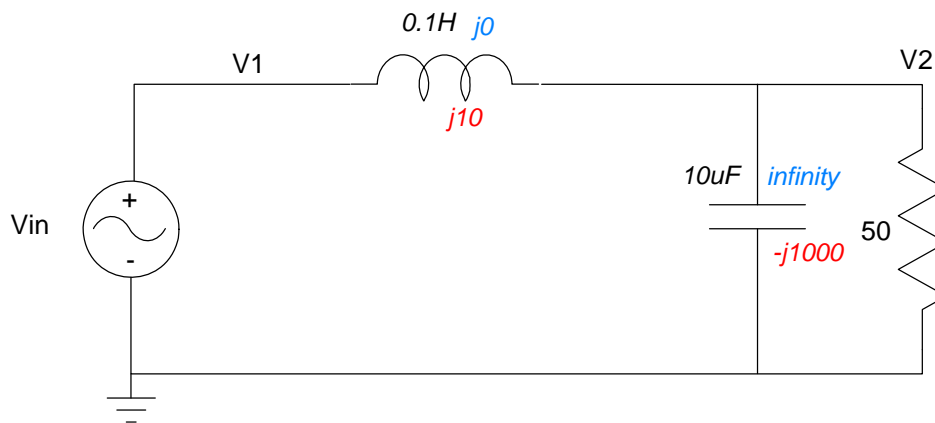
$$C \rightarrow \frac{1}{j\omega C} = -j1000$$



b) Determine the voltage, V_2 , using phasor analysis

Voltage node equation

DC

AC

$$V_{in} = 5$$

$$V_{in} = -j3 \quad (3 \sin(100t) \Rightarrow 0 - j3)$$

$$V_2 = V_{in} = 5$$

$$\left(\frac{V_2 - V_{in}}{j10} \right) + \left(\frac{V_2}{-j1000} \right) + \left(\frac{V_2}{50} \right) = 0$$

$$V_2 = 2.97 \angle -101^\circ \quad \text{polar form}$$

$$v_2(t) = 2.97 \cos(100t - 101^\circ)$$

$$V_2 = -0.567 - j2.915 \quad \text{rectangular form}$$

$$v_2(t) = -5.67 \cos(100t) + 2.915 \sin(100t)$$

Total Answer:

$$v_2(t) = 10 + 2.97 \cos(100t - 101^\circ) \quad \text{polar form}$$


$$v_2(t) = 5 - 5.67 \cos(100t) + 2.915 \sin(100t) \quad \text{rectangular form}$$

Either answer is correct.

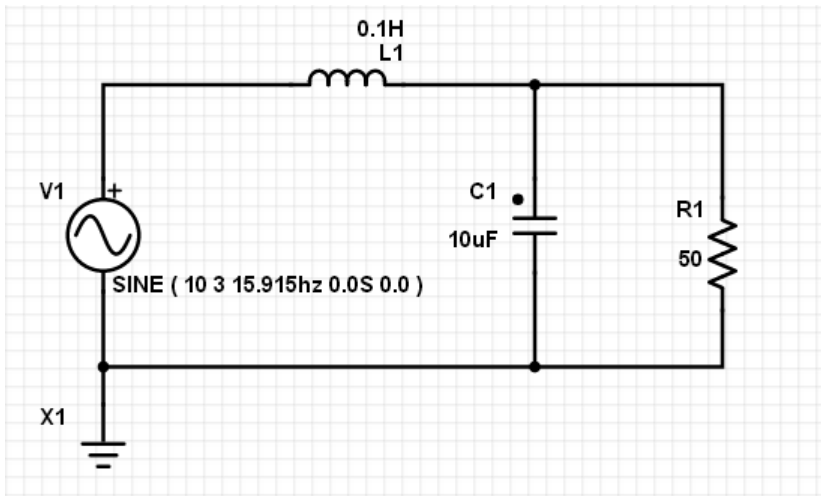
c) Check your answer using PartSim (or similar program)

Input the circuit in PartSim. Use a transient input (sinusoid) with a

- 10V DC offset
- 3V AC amplitude
- 15.915Hz (100 rad/sec)



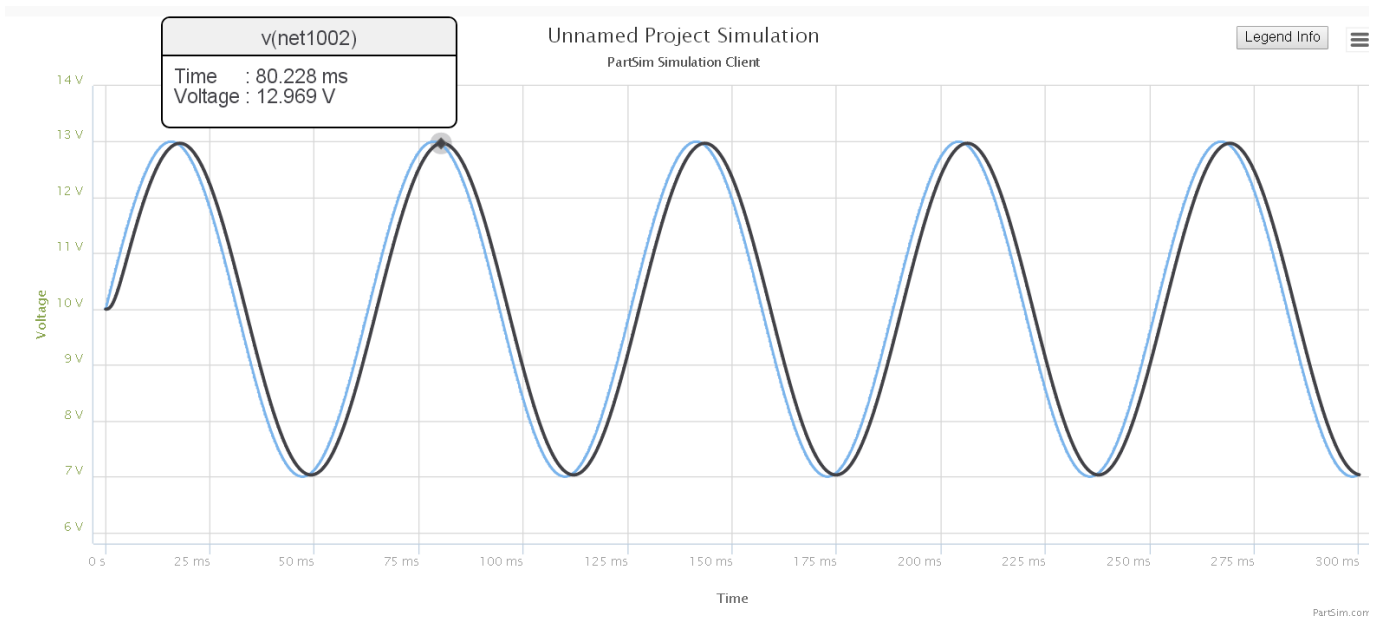Run a transient simulation for several cycles



The DC signal at the output (black) is 10V

The AC signal is 2.969Vp (vs. 2.97Vp computed)

The AC signal has a small delay (-10 degrees computed)

6) Assume V_{in} contains a DC and 160Hz signal:

$$V_{in} = 5 + 3 \sin(1000t)$$

a) Determine the impedances of the inductor, capacitor, and resistor at DC and 1000 rad/sec

DC

AC (1000 rad/sec)

no change

$$\omega = 1000$$


$$L = 0$$

$$L \rightarrow j\omega L = j100$$

$C = \text{infinity}$

$$C \rightarrow \frac{1}{j\omega C} = -j100$$

$$V_{in} = -j3$$

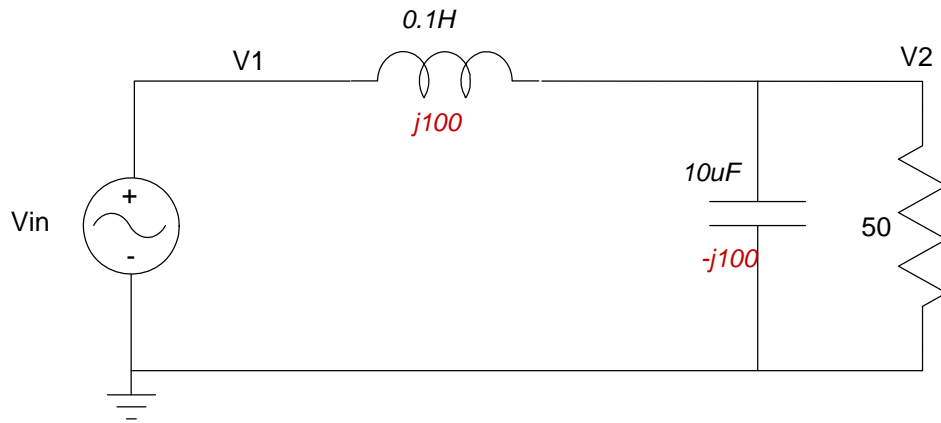

b) Determine the voltage, V_2 , using phasor analysis

DC

AC

$$V_2 = V_1 = 5$$

$$50 \parallel -j100 = 40 - j20$$

$$V_2 = \left(\frac{40 - j20}{(40 - j20) + (j100)} \right) (0 - j3)$$

$$V_2 = 1.5 \angle 180^\circ$$

$$v_2(t) = 1.5 \cos(1000t + 180^\circ)$$

Total answer: DC + AC

$$v_2(t) = 5 + 1.5 \cos(1000t + 180^\circ)$$

Checking in PartSim (not required)

