


ECE 311 - Homework #6

Balanced 3-Phase Circuits

For each problem, let


- $V_a = 120\angle 0^\circ$
- $V_b = 120\angle -120^\circ$
- $V_c = 120\angle -240^\circ$

1) Find V_1 , V_2 , V_3 , and the power delivered to each resistor

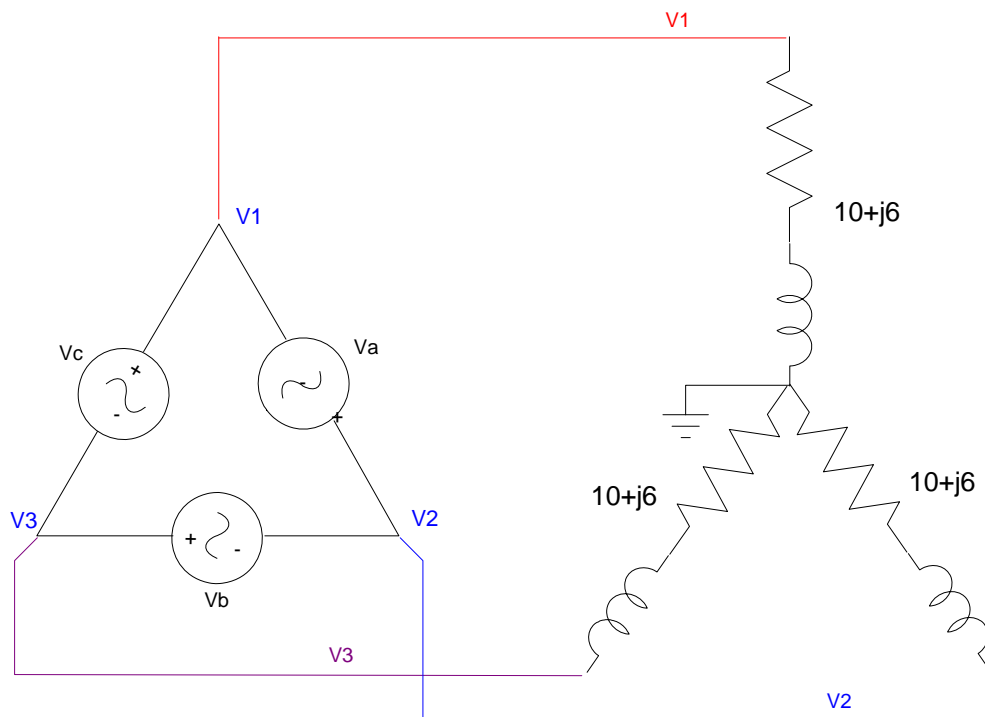

Problem 1: Y-Delta Connection

Start with a Y-Delta conversion

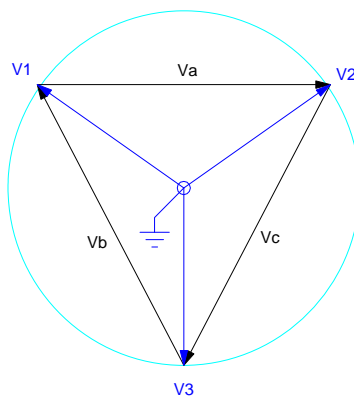

$$V_1 = \frac{120}{\sqrt{3}}\angle 150^\circ \quad V_2 = \frac{120}{\sqrt{3}}\angle 30^\circ \quad V_3 = \frac{120}{\sqrt{3}}\angle -90^\circ$$

Power is the same for all three phases:


$$V = I \cdot Z$$

$$P = V \cdot I^* = \frac{|V|^2}{Z^*} = |I|^2 \cdot Z$$

$$P = \frac{\left(\frac{120}{\sqrt{3}}\right)^2}{10-j3}$$

$$P = 440 + j132$$

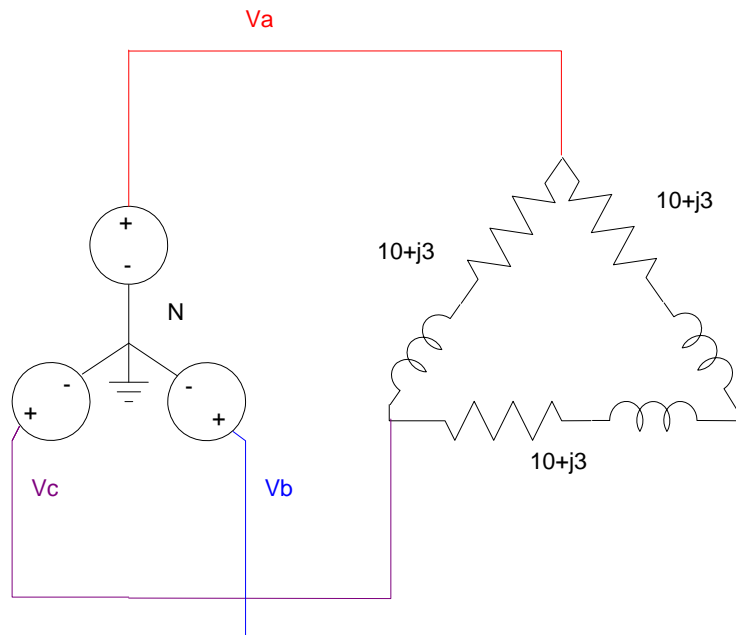2) Find the power delivered to each resistor



Y-Delta Connection

$$V_{ab} = V_a - V_b = (120 \angle 0^\circ) - (120 \angle -120^\circ) = 120\sqrt{3} \angle 30^\circ$$

$$P = \frac{|V|^2}{Z^*} = \frac{(120\sqrt{3})^2}{10-j3}$$

$$P = 3963 + j1189$$