

ECE 311 - Homework #15


L and C in the LaPlace Domain

Find the LaPlace impedance from A to B for the following circuits. Assume zero initial conditions:


$$R \rightarrow R$$

$$L \rightarrow Ls$$

$$C \rightarrow \frac{1}{Cs}$$

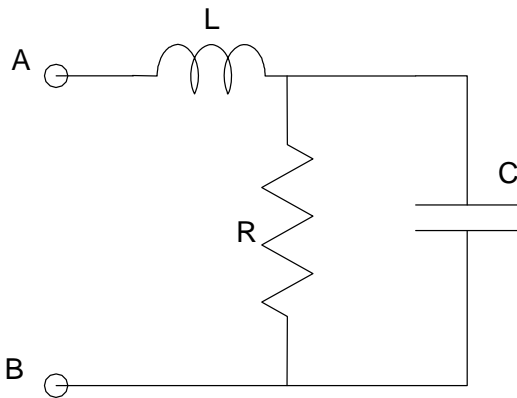

Problem 1

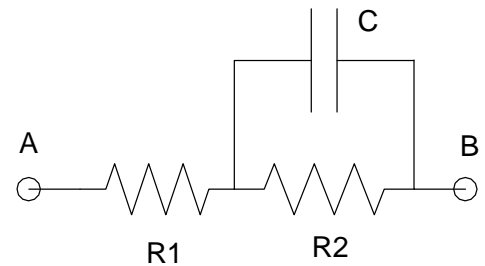

Problem 2

Problem 1) Add the resistor and capacitor in parallel

$$Z_1 = Ls + \left(\frac{1}{R} + \frac{1}{1/Cs} \right)^{-1}$$

$$Z_1 = Ls + \left(\frac{1}{R} + Cs \right)^{-1}$$

$$Z_1 = Ls + \left(\frac{R}{1+RCs} \right)$$

$$Z_1 = \left(\frac{Ls(1+RCs)}{1+RCs} \right) + \left(\frac{R}{1+RCs} \right)$$

$$Z_1 = \left(\frac{R+Ls(1+RCs)}{1+RCs} \right)$$

$$Z_1 = \left(\frac{RLCs^2 + Ls + R}{1+RCs} \right)$$


Problem 2) Same but use R1 instead of Ls

$$Z_2 = R_1 + \left(\frac{1}{R_2} + Cs \right)^{-1}$$


$$Z_2 = R_1 + \left(\frac{R_2}{1+R_2Cs} \right)$$

$$Z_2 = \left(\frac{R_1(1+R_2Cs) + R_2}{1+R_2Cs} \right)$$

$$Z_2 = \left(\frac{R_1R_2Cs + R_1 + R_2}{1+R_2Cs} \right)$$

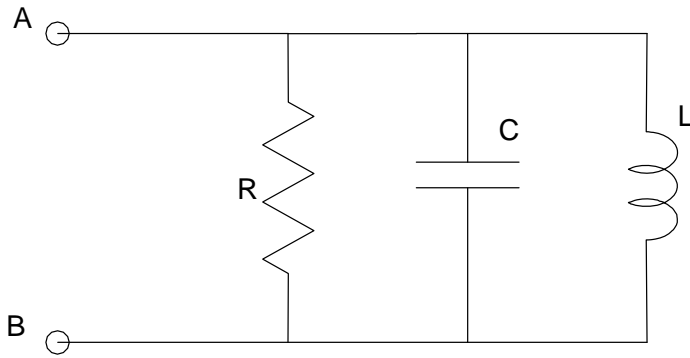

Problem 3

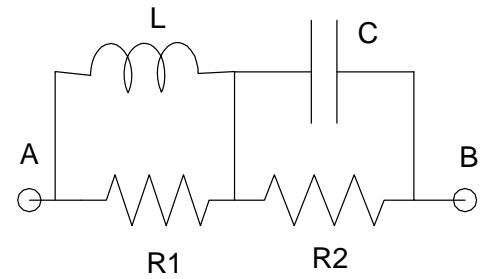

Problem 4

Problem 3:

$$Z_3 = \left(\frac{1}{R} + \frac{1}{1/Cs} + \frac{1}{Ls} \right)^{-1}$$

$$Z_3 = \left(\frac{1}{\frac{1}{R} + Cs + \frac{1}{Ls}} \right)$$

$$Z_3 = \left(\frac{1}{\frac{1}{R} + Cs + \frac{1}{Ls}} \right) \left(\frac{RLs}{RLs} \right)$$

$$Z_3 = \left(\frac{RLs}{RLCs^2 + Ls + R} \right)$$

Problem 4:

$$Z_4 = \left(\frac{1}{\frac{1}{Ls} + \frac{1}{R_1}} \right) + \left(\frac{1}{\frac{1}{Cs} + \frac{1}{R_2}} \right)$$

$$Z_4 = \left(\frac{1}{\frac{1}{Ls} + \frac{1}{R_1}} \right) + \left(\frac{1}{Cs + \frac{1}{R_2}} \right)$$

$$Z_4 = \left(\frac{1}{\frac{1}{Ls} + \frac{1}{R_1}} \right) \left(\frac{R_1 Ls}{R_1 Ls} \right) + \left(\frac{1}{Cs + \frac{1}{R_2}} \right) \left(\frac{R_2}{R_2} \right)$$

$$Z_4 = \left(\frac{R_1 Ls}{R_1 + Ls} \right) + \left(\frac{R_2}{R_2 Cs + 1} \right)$$

$$Z_4 = \left(\frac{R_1 Ls}{R_1 + Ls} \right) \left(\frac{R_2 Cs + 1}{R_2 Cs + 1} \right) + \left(\frac{R_2}{R_2 Cs + 1} \right) \left(\frac{R_1 + Ls}{R_1 + Ls} \right)$$

$$Z_4 = \left(\frac{R_1 Ls (R_2 Cs + 1) + R_2 (R_1 + Ls)}{(R_1 + Ls) (R_2 Cs + 1)} \right)$$

$$Z_4 = \left(\frac{R_1 R_2 L C s^2 + (R_1 + R_2) L s + R_1 R_2}{(R_1 + Ls) (R_2 Cs + 1)} \right)$$