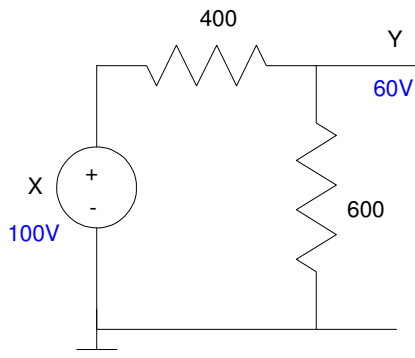


Phasors and Complex Numbers

Introduction

If you have a DC signal feeding a circuit, a single number can be used to describe the circuit. For example, consider the following circuit:



Voltage Divider: $Y = 0.6X$

From before, the output by voltage division is


$$Y = \left(\frac{R_1}{R_1 + R_2} \right) X$$

$$Y = \left(\frac{600}{600 + 400} \right) X$$

$$Y = 0.6 \cdot X$$

A good way to describe this circuit is to say it has a gain of 0.6: the output is 0.6 of the input.

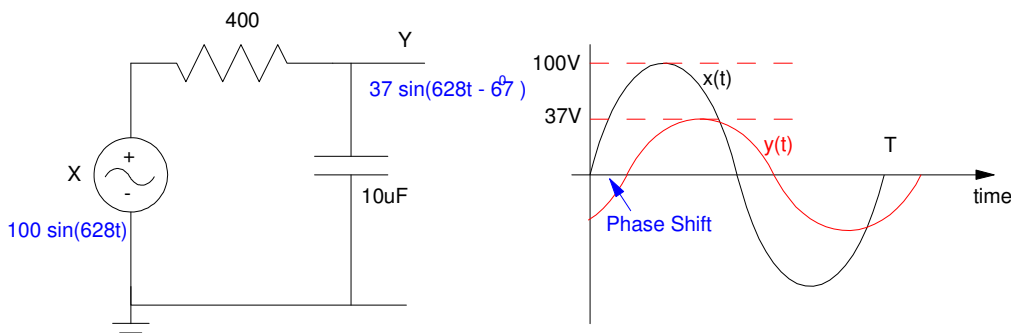If you change the circuit to be a capacitor and $X(t)$ to be a sinusoid, however, the input / output relationship becomes a little more complicated



If the input is a 628 rad/sec sine wave, it is also a 100Hz sine wave

$$\omega = 2\pi f$$

$$f = \frac{\omega}{2\pi} = \frac{628}{2\pi} = 100\text{Hz}$$

The period is 10ms

$$T = \frac{1}{f} = \frac{1}{100\text{Hz}} = 0.01 \text{ sec}$$

If the input is sine wave, starting at $t=0$, with an amplitude of 100V, then

$$x(t) = 100 \sin(628t)$$

The output, however, is different than the input by both amplitude as well as a phase shift.

$$y(t) = 37 \sin(628t - 67^\circ)$$

You likewise need two numbers to describe this circuit

- An amplitude which tells you how much the signal is amplified, and
- An angle which tells you the phase shift of this circuit.

Complex numbers are a way to determine both of these with a single number.

Complex Numbers

Let


$$j = \sqrt{-1}$$

Any given number can then have a real and a complex part

$$x = a + jb$$

You can express this number in rectangular form ($a + jb$) or polar form

$$x = c\angle\theta$$

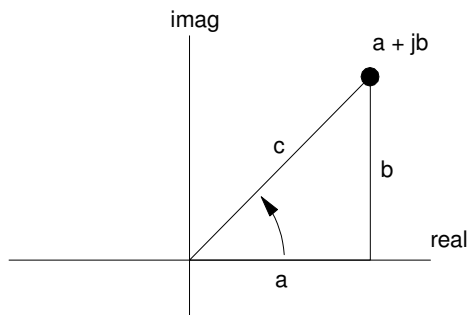

Complex Number ($a + jb$) can also be expressed as ($c\angle\theta$)

When you add complex numbers, the rectangular form is more convenient: the real part adds and the complex part adds.

$$(a_1 + jb_1) + (a_2 + jb_2) = (a_1 + a_2) + j(b_1 + b_2)$$

When you multiply complex numbers, polar form is more convenient: the amplitudes multiply, the angles add:

$$(c_1 \angle \theta_1)(c_2 \angle \theta_2) = c_1 c_2 \angle (\theta_1 + \theta_2)$$

Complex numbers let you express sine and cosine with a single number as well. The complex exponential is

$$e^{j\omega t} = \cos(\omega t) + j \sin(\omega t)$$

If you multiply by a complex number

$$\begin{aligned} (a + jb) \cdot e^{j\omega t} &= (a + jb) \cdot (\cos(\omega t) + j \sin(\omega t)) \\ &= (a \cos(\omega t) - b \sin(\omega t)) + j(-) \end{aligned}$$

Taking the real part you get

$$a + jb \Rightarrow a \cos(\omega t) - b \sin(\omega t)$$

The complex number $a + jb$ represents a sine wave:

- **The real part is the cosine term**
- **The complex part is the -sine term**

With complex exponential, you can represent both sine and cosine with a single (complex) number.

Complex Impedance's

The impedance is the relationship between current and voltage. For a resistor

$$V = IR$$

The impedance of a resistor is R.

The impedance of a capacitor and inductor is a little trickier. First, assume all functions are of the form

$$x(t) = a \cdot e^{j\omega t}$$

where 'a' could be complex. The VI characteristics for a capacitor is

$$I = C \frac{dV}{dt}$$

If

$$V(t) = v_0 e^{j\omega t}$$

then

$$\frac{dV}{dt} = j\omega \cdot v_0 e^{j\omega t}$$

$$\frac{dV}{dt} = j\omega \cdot V$$

Then

$$I = C \cdot j\omega \cdot V$$

$$V = \left(\frac{1}{j\omega C}\right) I$$

The complex impedance of a capacitor is $\left(\frac{1}{j\omega C}\right)$

The impedance of an inductor is from

$$V = L \frac{dI}{dt}$$

Assuming current is of the form

$$I = i_0 \cdot e^{j\omega t}$$

then


$$V = L \cdot j\omega \cdot I$$

The complex impedance of an inductor is $j\omega L$

This lets you analyze any RLC circuit the same way you analyzed a resistor circuit - only the impedance's will be complex numbers.

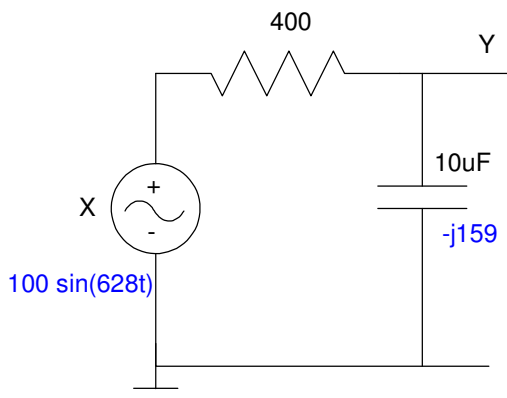Example 1: RC Circuit

Determine $y(t)$ for the following circuit:



Step 1: Replace the capacitor with its complex impedance. Since the input is 628 rad/sec, that's the frequency you care about

$$\omega = 628 \text{ rad/sec}$$

$$Z_c = \frac{1}{j\omega C} = -j159\Omega$$

Step 2: Solve just like you did with a DC circuit, only with complex numbers

$$Y = \left(\frac{-j159}{-j159+400} \right) X$$

$$Y = (0.37 \angle -68^\circ) \cdot 100 \sin(628t)$$

$$y(t) = 37 \sin(100t - 68^\circ)$$

In MATLAB:

```
>> C = 10e-6;
>> w = 628;
>> Zc = 1 / (j*w*C)

      0 -159.24i
>> Gain = Zc / (400 + Zc)

      0.1368 - 0.3436i

>> X = 0 - j*100;    // x(t) = 100 sin(628t)
>> Y = Gain * X

-34.3632 -13.6796i
```

meaning

$$y(t) = -34.3632 \cos(628t) + 13.6796 \sin(628t)$$

which is the rectangular form of $y(t)$.

If you prefer polar form:

```
>> abs(Y)


      36.9860
>> angle(Y)*180/pi

-158.2930
```

$$y(t) = 36.986 \cos(628t - 158^\circ)$$

In PartSim (www.PartSim.com)

Input the circuit using drag and drop

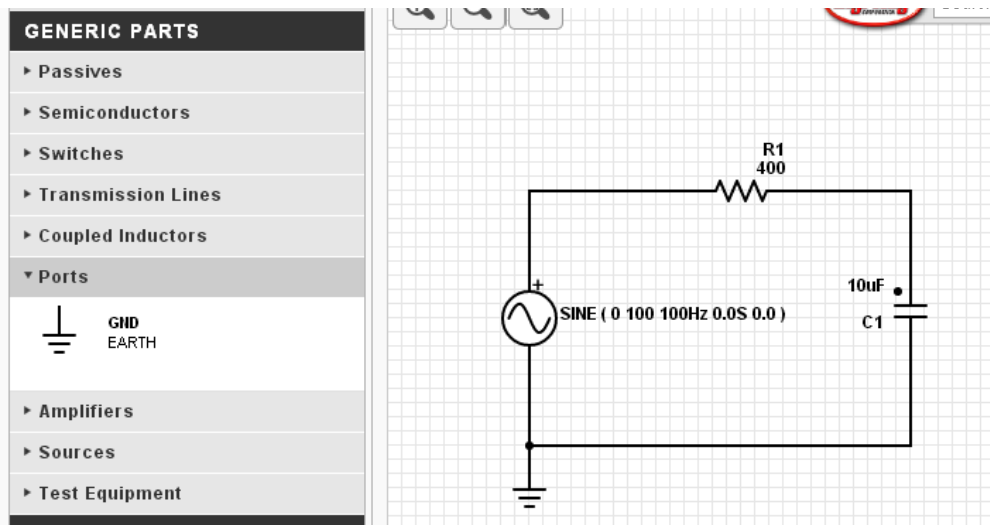


Make the input a sine wave with

- no DC offset
- 100V amplitude
- 100Hz


Enable DC Voltage	<input type="checkbox"/>
DC Voltage	<input type="text" value="1.0"/>
Enable AC:	<input type="checkbox"/>
AC Magnitude:	<input type="text" value="1.0"/>
AC Phase:	<input type="text" value="0"/>
Transient Source:	
<input type="radio"/> None <input checked="" type="radio"/> Sine <input type="radio"/> Pulse <input type="radio"/> Exponential <input type="radio"/> FM <input type="radio"/> AM <input type="radio"/> Noise	
Offset:	<input type="text" value="0"/>
Amplitude:	<input type="text" value="100"/>
Frequency:	<input type="text" value="100Hz"/>
Delay:	<input type="text" value="0.0S"/>
Damping Factor:	<input type="text" value="0.0"/>

Run a transient response for

- 30ms (3 cycles)
- 10us step size

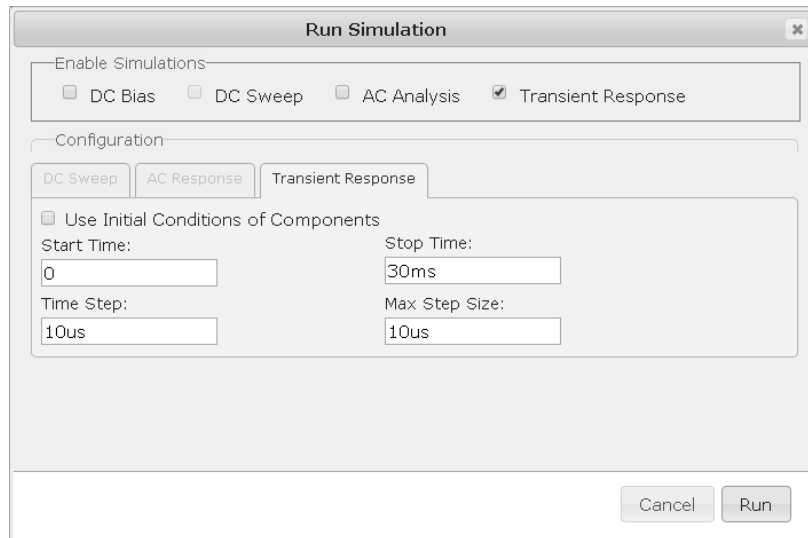

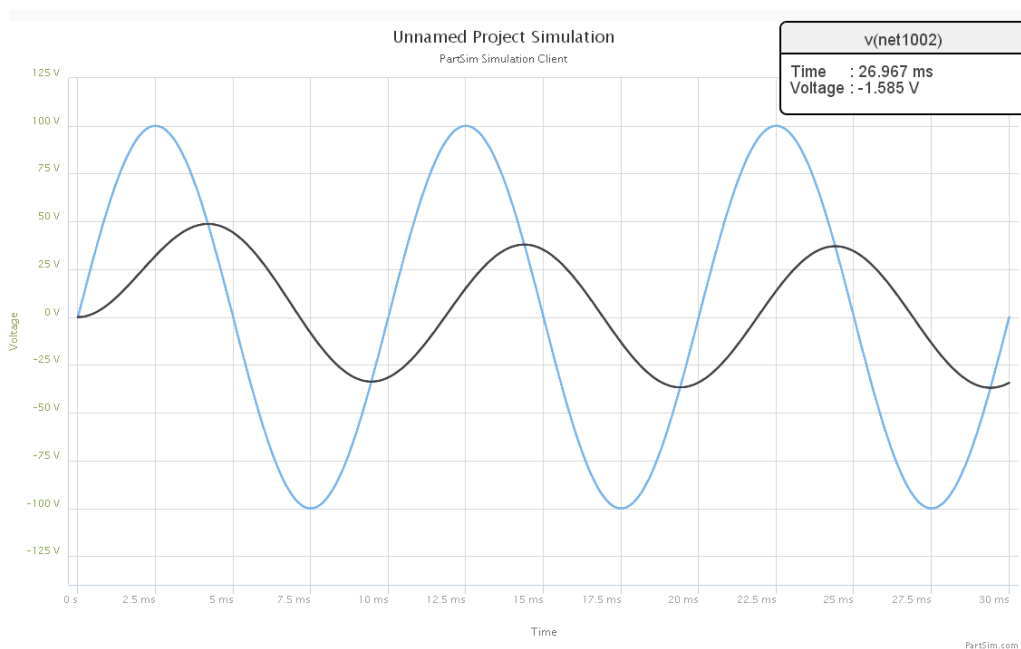This results in a simulated input and output waveform:



Input (blue) and Output (black)

Note from the PartSim plot, the output after a short transient is

- 39Vp (as calculated)
- Delayed by 68 degrees from the input (as calculated)

To calculate the delay, use the following procedure:

- One cycle is 360 degrees or four divisions
- The output has zero crossings delayed by 0.8 divisions.

The phase shift is thus


$$\left(\frac{0.8\text{div}}{4\text{div}}\right) 360^\circ = 72^\circ \quad (\text{actually } 68 \text{ degrees but it's hard to read a graph that accurately})$$

Negative phase shift is a delay.

Example 2: 3-Stage RC Circuit

Find the voltages for the following circuit when the input is

$$x(t) = 100 \cos(2t)$$

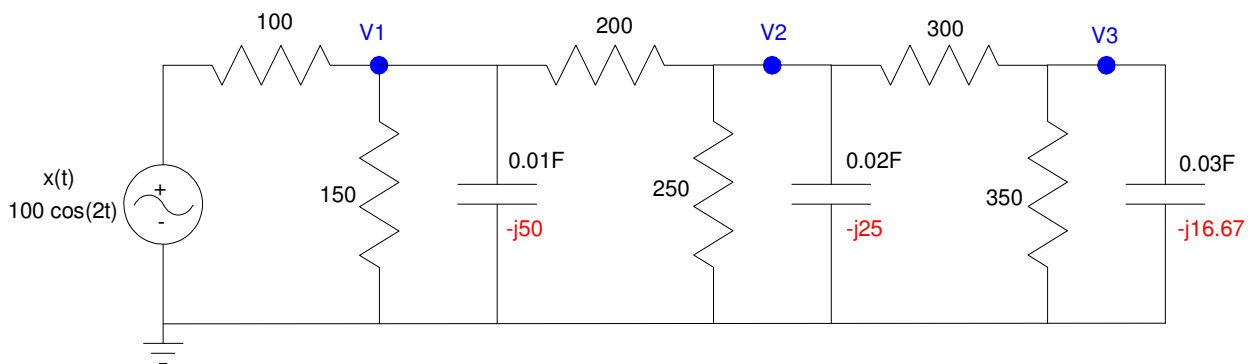

Step 1: Change the capacitors to their complex impedance (shown in red)

$$\omega = 2$$

$$0.01\text{F}: Z_c = \frac{1}{j\omega C} = -j50\Omega$$

$$0.02\text{F}: Z_c = \frac{1}{j\omega C} = -j25\Omega$$

$$0.03\text{F}: Z_c = \frac{1}{j\omega C} = -j16.67\Omega$$

Step 2: Write N equations for N unknowns

$$V1: \left(\frac{V_1 - X}{100}\right) + \left(\frac{V_1}{150}\right) + \left(\frac{V_1}{-j50}\right) + \left(\frac{V_1 - V_2}{200}\right) = 0$$

$$V2: \left(\frac{V_2 - V_1}{200}\right) + \left(\frac{V_2}{250}\right) + \left(\frac{V_2}{-j25}\right) + \left(\frac{V_2 - V_3}{300}\right) = 0$$

$$V3: \left(\frac{V_3 - V_2}{300}\right) + \left(\frac{V_3}{350}\right) + \left(\frac{V_3}{-j16.67}\right) = 0$$

Step 3: Solve.

First, group terms

$$\left(\frac{1}{100} + \frac{1}{150} + \frac{1}{-j50} + \frac{1}{200}\right)V_1 + \left(\frac{-1}{200}\right)V_2 = \left(\frac{1}{100}\right)X$$

$$\left(\frac{-1}{200}\right)V_1 + \left(\frac{1}{200} + \frac{1}{250} + \frac{1}{-j25} + \frac{1}{300}\right)V_2 + \left(\frac{-1}{300}\right)V_3 = 0$$

$$\left(\frac{-1}{300}\right)V_2 + \left(\frac{1}{300} + \frac{1}{350} + \frac{1}{-j16.67}\right)V_3 = 0$$

Place in matrix form

$$\begin{bmatrix} \left(\frac{1}{100} + \frac{1}{150} + \frac{1}{-j50} + \frac{1}{200}\right) & \left(\frac{-1}{200}\right) & 0 \\ \left(\frac{-1}{200}\right) & \left(\frac{1}{200} + \frac{1}{250} + \frac{1}{-j25} + \frac{1}{300}\right) & \left(\frac{-1}{300}\right) \\ 0 & \left(\frac{-1}{300}\right) & \left(\frac{1}{300} + \frac{1}{350} + \frac{1}{-j16.67}\right) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} \left(\frac{1}{100}\right) \\ 0 \\ 0 \end{bmatrix} X$$

Put into MATLAB and solve

```
>> a11 = 1/100 + 1/150 - 1/(j*50) + 1/200;
>> a12 = -1/200;
>> a13 = 0;
>> a21 = -1/200;
>> a22 = 1/200 + 1/250 - 1/(j*25) + 1/300;
>> a23 = -1/300;
>> a31 = 0;
>> a32 = -1/300;
>> a33 = 1/300+1/350-1/(j*16.67);
>> A = [a11, a12, a13; a21, a22, a23; a31, a32, a33]

    0.0217 + 0.0200i   -0.0050                   0
   -0.0050           0.0123 + 0.0400i   -0.0033
    0                -0.0033           0.0062 + 0.0600i

>> B = [1/100; 0; 0]

    0.0100
    0
    0

>> V = inv(A)*B*X

    24.2853 -23.2416i
   -1.7971 - 3.5726i
   -0.2066 + 0.0785i
```

meaning

$$V_1(t) = 24.28 \cos(2t) + 23.24 \sin(2t)$$

$$V_2(t) = -1.79 \cos(2t) + 3.57 \sin(2t)$$

$$V_3(t) = 0.21 \cos(2t) + 0.08 \sin(2t)$$

If you prefer polar representation:

```
>>abs (V)
```

```
33.6147
 3.9991
 0.2210
```

```
>> angle (V) *180/pi
```

```
-43.7420
-116.7040
159.1878
```


meaning


$$V_1(t) = 33.61 \cos(2t - 43.7^\circ)$$

$$V_2(t) = 3.999 \cos(2t - 116.7^\circ)$$

$$V_3(t) = 0.22 \cos(2t + 159.2^\circ)$$

PartSim Simulation

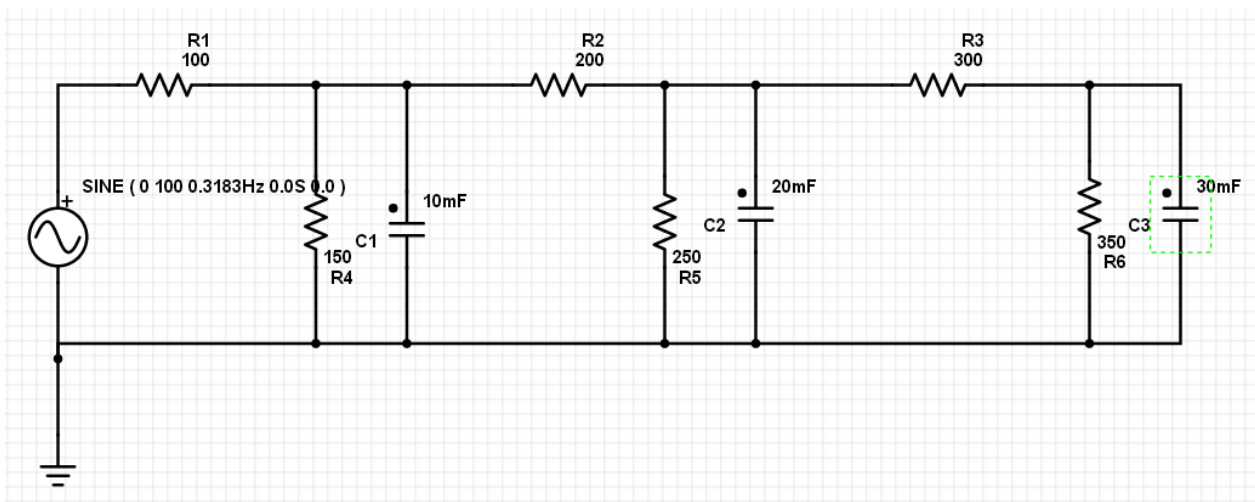

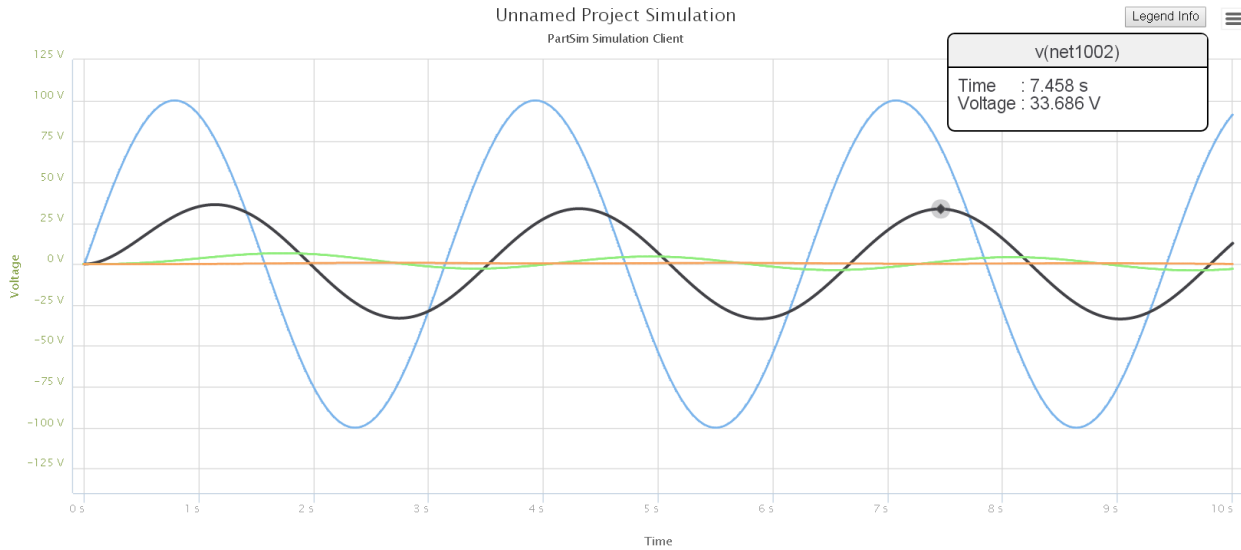

Transient Response of V_{in} (blue), V_1 (black), V_2 (green), and V_3 (orange)

Note that V_1 has

- A peak of 33.686V (vs. 33.61V computed)
- A delay of $\left(\frac{0.4 \text{ div}}{3.2 \text{ div}}\right) 360^\circ = 45^\circ$ (vs. 43.7 degrees computed)

Likewise, V_2 and V_3 match our calculations

	V_{in}	V_1	V_2	V_3
Calculated	100V	33.61V	3.999V	220mV
PartSim	100V	33.678V	4.233V	592 mV