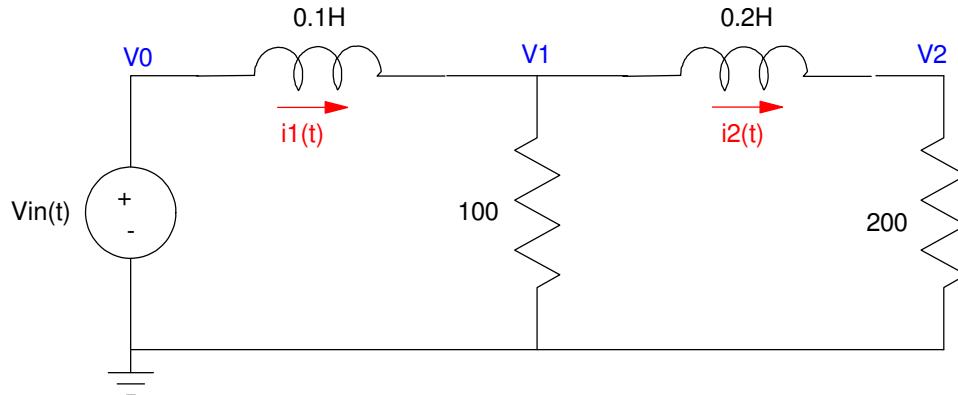


Voltage Nodes in the LaPlace Domain

Note: The parallel model for inductors and capacitors work better when writing voltage node equations.

Example 1: Find $V_2(t)$ for the following circuit. Assume

$$v_{in}(t) = \begin{cases} 5V & t < 0 \\ 0V & t > 0 \end{cases}$$




From before, the current at $t=0$ is

$$i_1(0) = 75mA$$

$$i_2(0) = 25mA$$

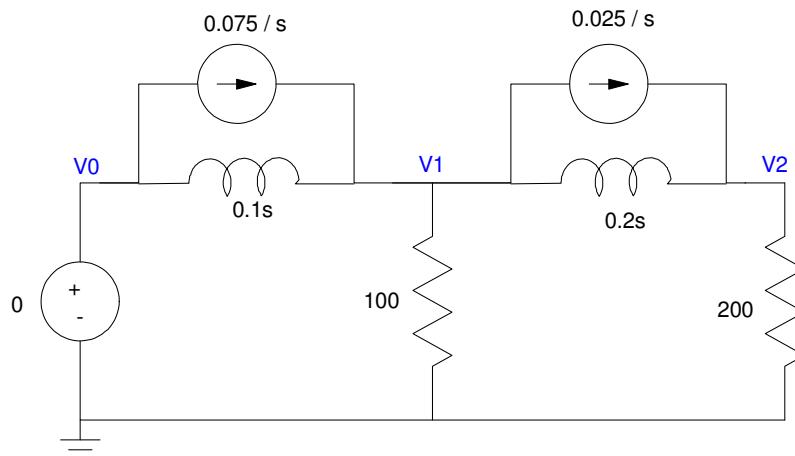The parallel model (for voltage nodes) would be



with the voltage node equations being

$$\left(\frac{V_1}{0.1s}\right) - \left(\frac{0.075}{s}\right) + \left(\frac{V_1}{100}\right) + \left(\frac{0.025}{s}\right) + \left(\frac{V_1-V_2}{0.2s}\right) = 0$$

$$\left(\frac{V_2-V_1}{0.2s}\right) + \left(\frac{V_2}{200}\right) - \left(\frac{0.025}{s}\right) = 0$$

Grouping terms to solve for V2(s)

$$\left(\frac{1}{0.1s} + \frac{1}{100} + \frac{1}{0.2s}\right)V_1 - \left(\frac{1}{0.2s}\right)V_2 = \left(\frac{0.05}{s}\right) \quad (1)$$

$$-\left(\frac{1}{0.2s}\right)V_1 + \left(\frac{1}{0.2s} + \frac{1}{200}\right)V_2 = \left(\frac{0.025}{s}\right) \quad (2)$$

Solve: Method #1: Gauss elimination

$$aV_1 - bV_2 = c \quad * b$$

$$-bV_1 + dV_2 = e \quad * a$$

$$(-b^2 + ad)V_2 = bc + ae$$

$$V_2 = \left(\frac{bc+ae}{ad-b^2} \right)$$

Plugging back in the values of (a, b, c, d, e)

$$V_2 = \left(\frac{\left(\frac{1}{0.2s}\right)\left(\frac{0.05}{s}\right) + \left(\frac{1}{0.1s} + \frac{1}{100} + \frac{1}{0.2s}\right)\left(\frac{0.025}{s}\right)}{\left(\frac{1}{0.1s} + \frac{1}{100} + \frac{1}{0.2s}\right)\left(\frac{1}{0.2s} + \frac{1}{200}\right) - \left(\frac{1}{0.2s}\right)^2} \right)$$

Simplify (30 minutes later....)

$$V_2 = \left(\frac{5(s+2500)}{(s+500)(s+2000)} \right)$$

Method #2: State Space. Place the system in the form of

$$sX = AX + BU$$

$$Y = CX + DU$$

Rewrite equations (1) and (2)

$$(0.01s + 15)V_1 - (5)V_2 = (0.05) \quad (1)$$

$$-(5)V_1 + (0.005s + 5)V_2 = (0.025) \quad (2)$$

Solve for the highest derivative

$$sV_1 = -1500V_1 + 500V_2 + 5 \quad (1)$$

$$sV_2 = 1000V_1 - 1000V_2 + 5 \quad (2)$$

Place in matrix form (note: $U(s) = 1$, meaning the input is a delta function for this circuit)

$$\begin{bmatrix} sV_1 \\ sV_2 \end{bmatrix} = \begin{bmatrix} -1500 & 500 \\ 1000 & -1000 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} + \begin{bmatrix} 5 \\ 5 \end{bmatrix}$$

$$Y = V_2 = \begin{bmatrix} 0 & 1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} + [0]$$

Place in Matlab

```
A = [-1500, 500; 1000, -1000]
B = [5; 5]
C = [0, 1]
D = 0;
G = ss(A, B, C, D);
zpk(G)
```


$$V2(s) = \frac{5(s+2500)}{(s+2000)(s+500)}$$

To find $v_2(t)$, take the inverse-LaPlace transform


$$V_2 = \left(\frac{5(s+2500)}{(s+500)(s+2000)} \right) = \left(\frac{6.667}{s+500} \right) + \left(\frac{-1.667}{s+2000} \right)$$

$$v_2(t) = (6.667e^{-500t} - 1.667e^{-2000t})u(t)$$

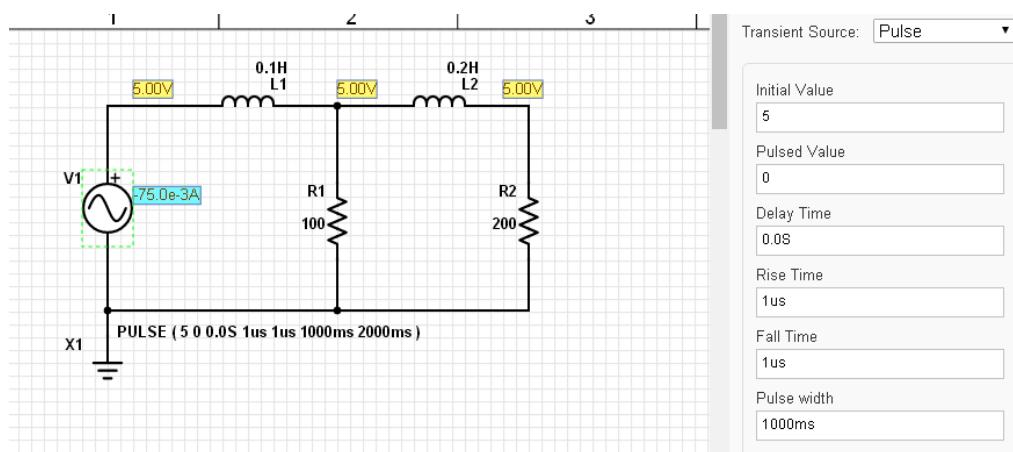Checking in PartSim: Input the circuit with the input being a pulse source




Run a transient simulation:

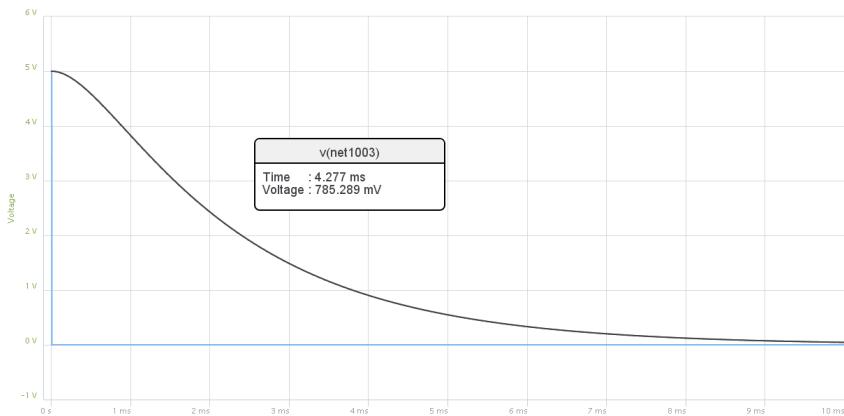

This matches up with the Matlab solution

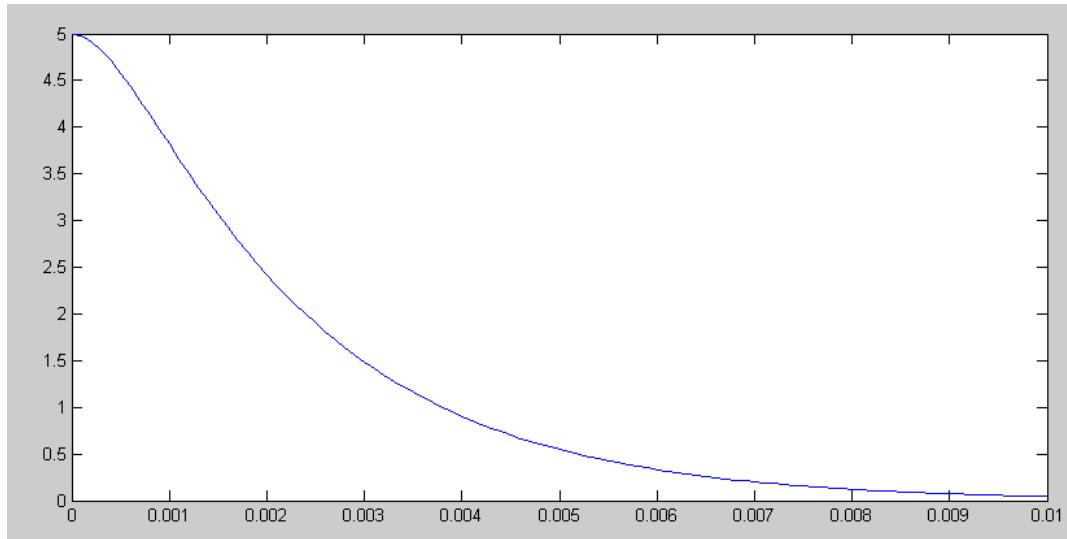
```
t = [0:0.0001:0.01]';  
y = impulse(G, t);  
plot(t,y);
```



Voltage Nodes with Capacitors

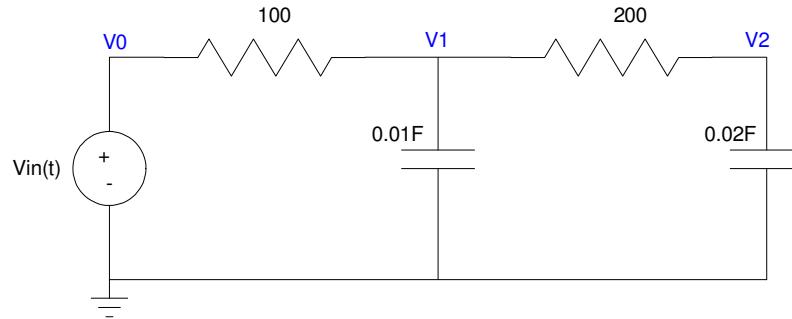Example 2: Find $v_2(t)$ assuming


$$v_{in}(t) = \begin{cases} 5V & t < 0 \\ 0V & t > 0 \end{cases}$$



Solution: Find the initial conditions. Capacitors are open circuits at DC, resulting in

$$v_1(0) = v_2(0) = 5V$$

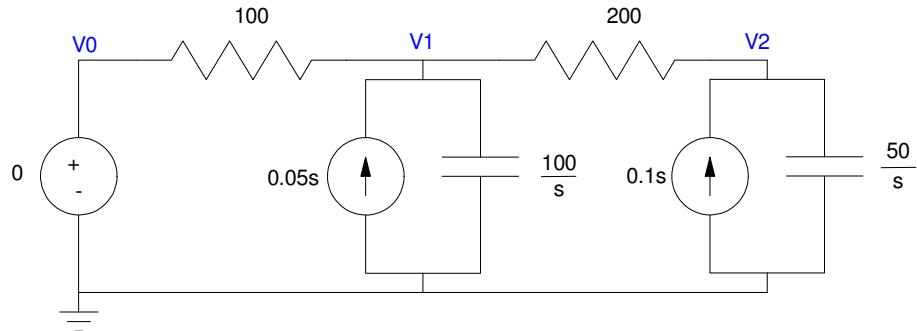Convert to LaPlace using the parallel model



Write the voltage node equations

$$\left(\frac{V_1}{100}\right) - 0.05s + \left(\frac{V_1}{100/s}\right) + \left(\frac{V_1 - V_2}{200}\right) = 0 \quad (1)$$

$$\left(\frac{V_2 - V_1}{200}\right) - 0.01s + \left(\frac{V_2}{50/s}\right) = 0 \quad (2)$$

Simplify and group terms

$$(0.01s + 0.015)V_1 - (0.005)V_2 = 0.05s$$

$$(-0.005)V_1 + (0.02s + 0.005)V_2 = 0.1s$$

Solve: Method #1: Gauss Elimination. Express this as

$$aV_1 - bV_2 = c \quad * \text{ b}$$

$$-bV_1 + dV_2 = e \quad * \text{ a}$$

add the two equations

$$(-b^2 + ad)V_2 = bc + ae$$

$$V_2 = \left(\frac{bc+ae}{ad-b^2} \right)$$

Substituting in for (a, b, c, d, e)

$$V_2 = \left(\frac{(0.005)(0.05s) + (0.01s + 0.015)(0.1s)}{(0.01s + 0.015)(0.02s + 0.005) - (0.005)^2} \right)$$

Method #2: State Space. Rewrite (1) and (2) as

$$sV_1 = -15V_1 + 0.5V_2 + 5s$$

$$sV_2 = 0.25V_1 - 0.25V_2 + 5s$$

Place in matrix form

$$\begin{bmatrix} sV_1 \\ sV_2 \end{bmatrix} = \begin{bmatrix} -15 & 0.5 \\ 0.25 & -0.25 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} + \begin{bmatrix} 5 \\ 5 \end{bmatrix} s$$

$$Y = V_2 = \begin{bmatrix} 0 & 1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} + [0]$$

Place in Matlab

```
A = [-15, 0.5 ; 0.25, -0.25];
B = [5; 5];
C = [0, 1];
D = 0;
G = ss(A, B, C, D);
zpk(G)
```

$$G = \frac{5(s+15.25)}{(s+15.01)(s+0.2415)}$$

This is the impulse response ($U(s) = 1$). We want $U(s) = s$, so multiply by 's'

$$v2 = \frac{5s(s+15.25)}{(s+15.01)(s+0.2415)}$$

Capacitors

From before, the VI characteristics for a capacitor is

$$i(t) = C \frac{dv}{dt}$$

Taking the LaPlace transform

$$I(s) = C \cdot (sV - v(0))$$


$$I(s) = CsV - Cv(0)$$

Solving for V

$$V = \left(\frac{1}{Cs} \right) I + v(0)$$

This gives the series (Thevenin) model for a capacitor. The parallel model has
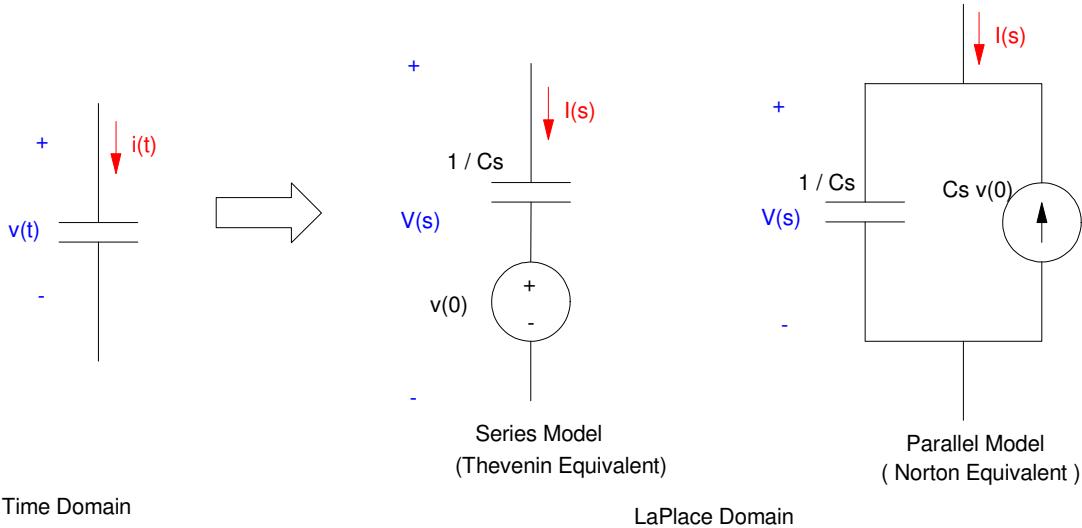
$$I_{short} = \frac{V_{th}}{R_{th}} = \frac{v(0)}{1/Cs} = Csv(0)$$




Note that

- The series model is more useful when writing current loop equations
- The parallel model is more useful when writing voltage node equations.

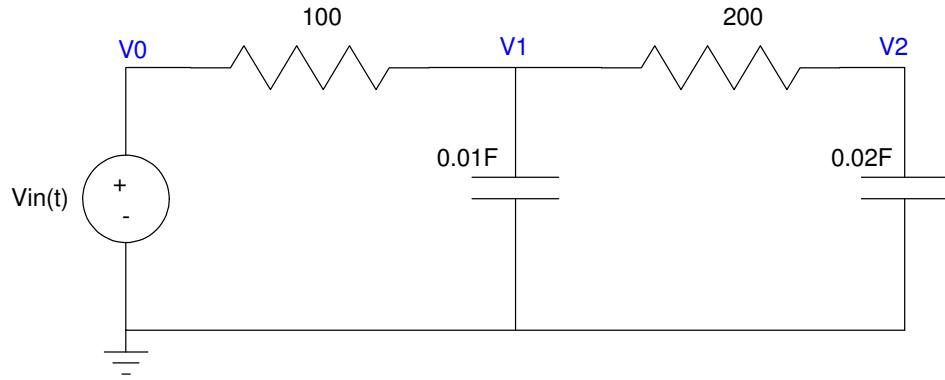Example: Convert the following circuit to the LaPlace domain and write the voltage node and current loop equations.

$$v_{in}(t) = \begin{cases} 5V & t < 0 \\ 10V & t > 0 \end{cases}$$



Solution: First find the initial conditions. For $t < 0$, the voltage is a constant (5V). Using phasor analysis,

$$C \rightarrow \frac{1}{j\omega C} = \infty$$

$$V_1 = V_2 = 5V$$


For the series (Thevenin) model, you have a voltage source with

$$V_{th} = v(0) = 5$$

For the parallel (Norton) model, you have a current source with

$$I_N = \frac{V_{th}}{R_{th}} = \frac{v(0)}{1/C_s} = C \cdot v(0) \cdot s$$


Series Model for $t > 0$:

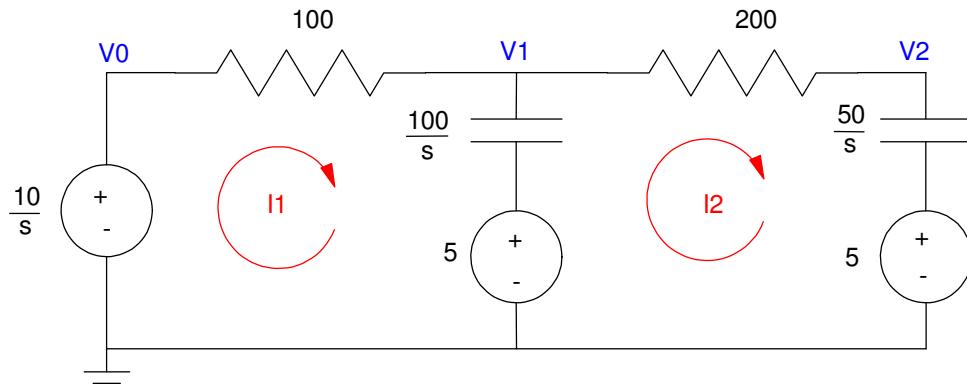

The current loop equations are then:

$$\begin{aligned} -\frac{10}{s} + 100I_1 + \left(\frac{100}{s}\right)(I_1 - I_2) + 5 &= 0 \\ -5 + \left(\frac{100}{s}\right)(I_2 - I_1) + 200I_2 + \left(\frac{50}{s}\right)I_2 + 5 &= 0 \end{aligned}$$

Parallel Model for $t > 0$:

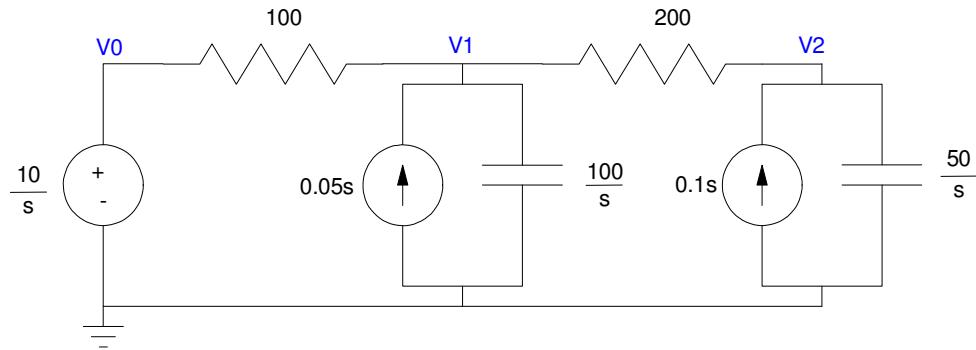

the voltage node equations become

$$\begin{aligned} V_0 &= \frac{10}{s} \\ \left(\frac{V_1 - V_0}{100}\right) - 0.05s + \left(\frac{V_1}{100/s}\right) + \left(\frac{V_1 - V_2}{200}\right) &= 0 \\ \left(\frac{V_2 - V_1}{200}\right) - 0.1s + \left(\frac{V_2}{50/s}\right) &= 0 \end{aligned}$$