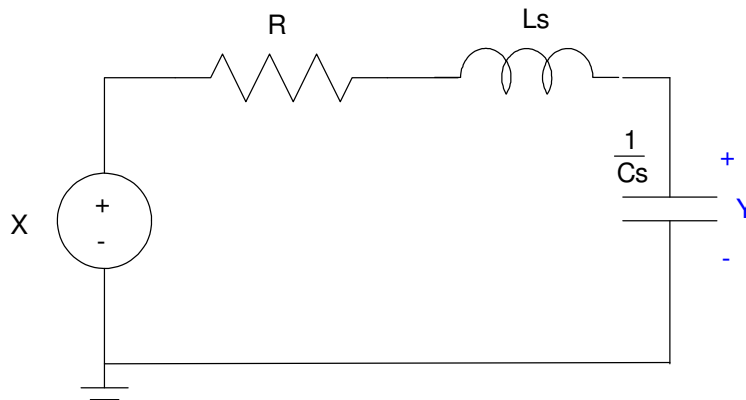


Passive RLC Filters

With RC and RL filters, you're stuck with real poles. With RLC filters, you can have both real and complex poles. You can also build

- Low pass filters (block high-frequency signals),
- High-pass filters (block DC terms), and
- Band-pass filters (block both high and low frequencies, only pass a select range of frequencies)

Low Pass RLC Filter



Assume ideal components. The transfer function for the following RLC filter is

$$Y = \left(\frac{\frac{1}{Cs}}{R + Ls + \frac{1}{Cs}} \right) X$$

$$Y = \left(\frac{1}{LCs^2 + RCs + 1} \right) X$$

Note that

- At DC ($s = 0$), the gain is one. This passes DC
- At high frequencies, the gain is proportional to $\frac{1}{s^2}$. This blocks high frequencies.
- Unlike an RC filter, the poles can be real or complex.

The poles of an RLC filter are the solutions to

$$LCs^2 + RCs + 1 = 0$$

or

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

If the roots are complex,

$$s = -a \angle \pm \theta$$

then

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = (s + a\angle\theta)(s + a\angle -\theta)$$

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = s^2 + (2a \cos \theta)s + a^2$$


Matching terms

$$\frac{R}{L} = 2a \cos \theta$$

$$\frac{1}{LC} = a^2$$

With a Bode plot

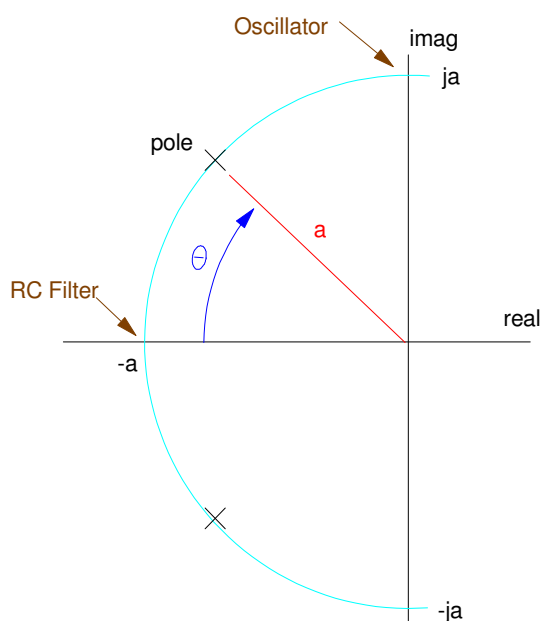- The amplitude of the poles tells you the corner frequency (in rad/sec),
- The angle of the poles tells you the damping ratio.




With an RLC filter, you can place the poles anywhere you want: real or complex.

The damping ratio determines the gain at the corner and how you go from one asymptote to another.

$$\zeta = \cos \theta$$

The damping ratio (and hence the angle) determines the gain at the corner
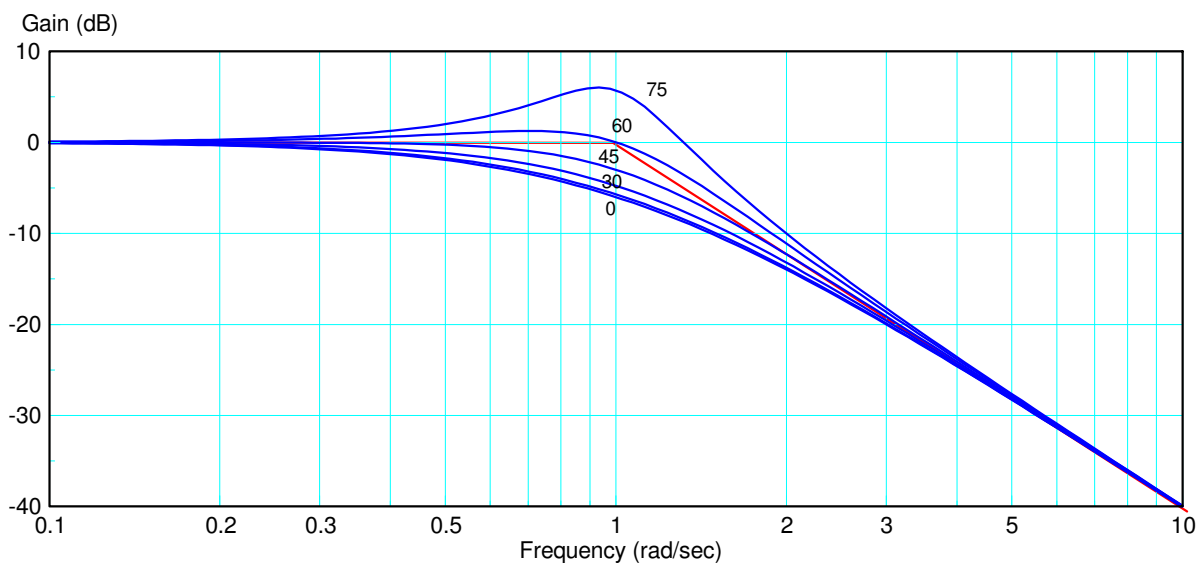
$$G(s = ja) = \left(\frac{a^2}{s^2 + 2\zeta as + a^2} \right)_{s=ja} = \left(\frac{a^2}{-a^2 + 2j\zeta a^2 + a^2} \right) = \left(\frac{1}{j2\zeta} \right)$$



Gain vs. Frequency for poles at $s = 1$ and angles of $\{0, 15, 30, 45, 60, 75\}$ degrees

Note that by allowing the poles to be complex, you can build a better low-pass filter.

Example: Specify R , L , and C so that the filter has the transfer function of

$$Y = \left(\frac{100^2}{s^2 + 140s + 100^2} \right) X = \left(\frac{100^2}{(s + 100 \angle 45^\circ)(s + 100 \angle -45^\circ)} \right) X$$

The transfer function of the RLC filter is

$$Y = \left(\frac{1}{LCs^2 + RCs + 1} \right) X = \left(\frac{\frac{1}{LC}}{s^2 + \frac{R}{L}s + \frac{1}{LC}} \right) X = \left(\frac{100^2}{s^2 + 140s + 100^2} \right) X$$

With 3 degrees of freedom and two constraints, something is arbitrary. Let

$$R = 100$$

Then

$$\frac{R}{L} = 140$$

$$L = 0.7143H$$

$$\frac{1}{LC} = 100^2$$

$$C = 140\mu F$$

High-Pass RLC Filter

If the output is the voltage across the inductor, the gain becomes

$$Y = \left(\frac{Ls}{Ls + R + \frac{1}{Cs}} \right) X$$

$$Y = \left(\frac{LCs^2}{LCs^2 + RCs + 1} \right) X$$

For this filter

- The high frequency gain is one, and
- The DC gain is zero

Band-Pass RLC Filter

If the output is the voltage across the resistor, the gain becomes

$$Y = \left(\frac{R}{Ls + R + \frac{1}{Cs}} \right) X$$

$$Y = \left(\frac{RCs}{LCs^2 + RCs + 1} \right) X$$

For this filter

- The DC gain is zero
- The high-frequency gain is zero
- At $\omega = \frac{1}{\sqrt{LC}}$, the gain is one