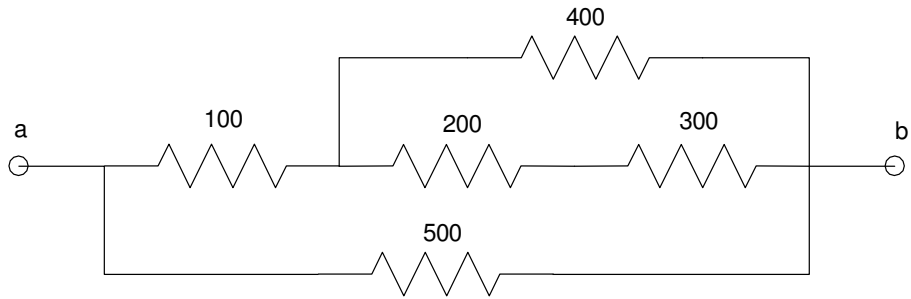


# ECE 320: Handout #1


## Circuits I Review

1) Find the resistance from a to b




2) Write the voltage node equations

3) Write the current loop equations

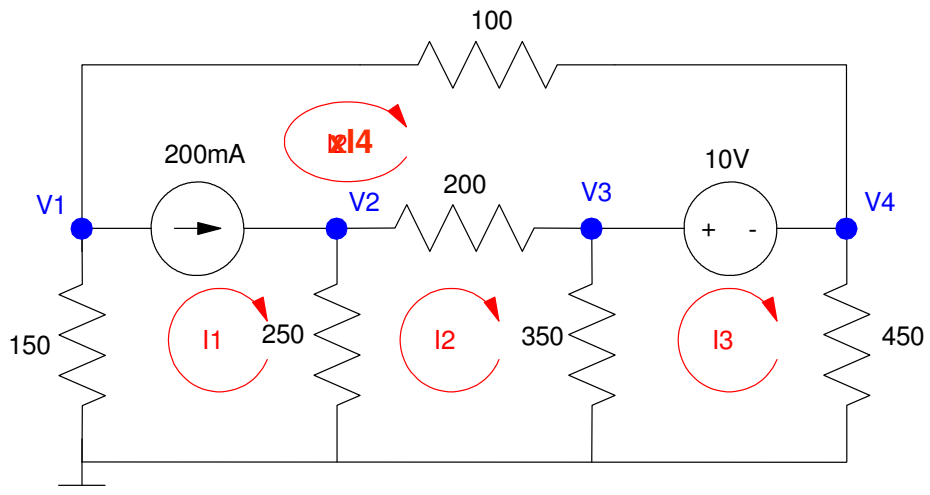

# Solutions

1) Find the resistance from a to b

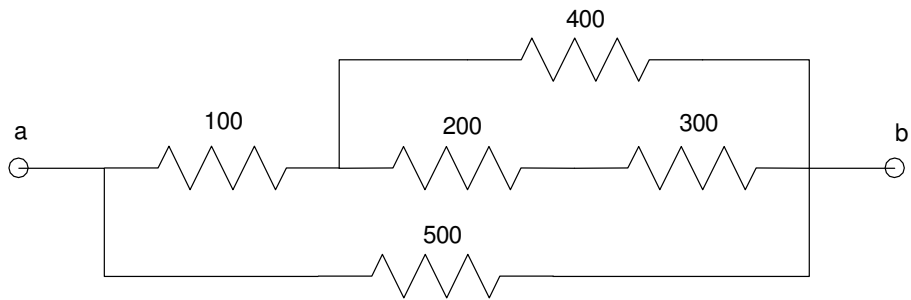

$$200 + 300 = 500$$


$$500 \parallel 400 = 222.22$$

$$222.22 + 100 = 322.22$$

$$322.22 \parallel 500 = 195.95$$

**answer: 195.95 Ohms**

2) Write the voltage node equations

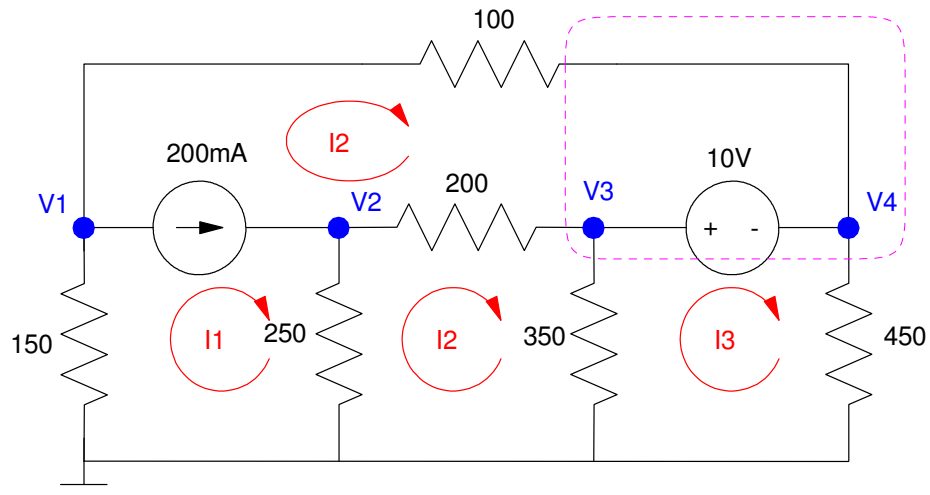

Four nodes means you need 4 equations for 4 unknowns

Start with the easy one

$$V_3 - V_4 = 10$$

Node equations (the sum of the current flowing from the node must be zero)


$$V_1: \left( \frac{V_1}{150} \right) + 200mA + \left( \frac{V_1 - V_4}{100} \right) = 0$$

$$V_2: -200mA + \left( \frac{V_2}{250} \right) + \left( \frac{V_2 - V_3}{350} \right) = 0$$

SuperNode (shown in pink): Other super nodes also work

$$\left( \frac{V_4 - V_1}{100} \right) + \left( \frac{V_3 - V_2}{200} \right) + \left( \frac{V_3}{350} \right) + \left( \frac{V_4}{450} \right) = 0$$

3) Write the current loop equations

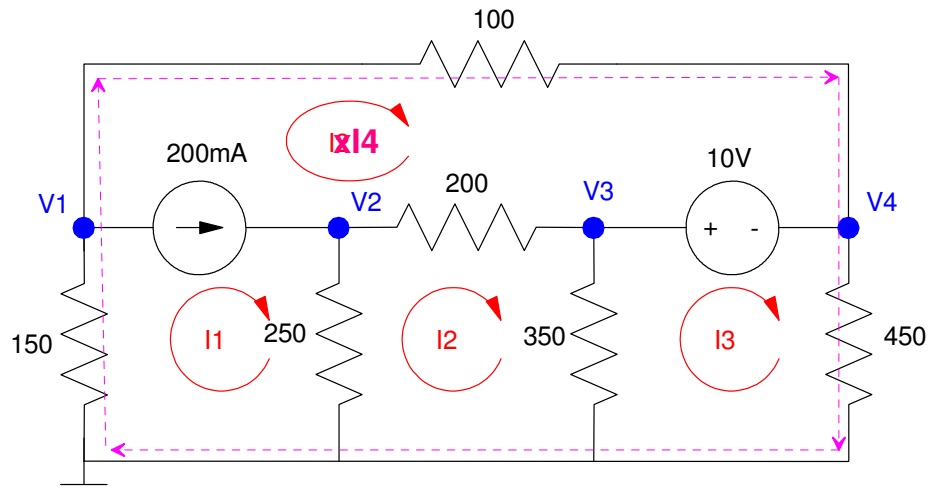

Four unknown current loops. Write 4 equations for 4 unknowns.

Start with the easy one

$$I_1 - I_4 = 200mA$$

Loop Equations: The sum of the voltage drops around any closed path must be zero.

Loop I2

$$250(I_2 - I_1) + 200(I_2 - I_4) + 350(I_2 - I_3) = 0$$

Loop I3

$$350(I_3 - I_2) + 10 + 450I_3 = 0$$

SuperLoop

$$150I_1 + 100I_4 + 450I_3 = 0$$