

# ECE 320: Handout #23


## MOSFET Switch

The specifications for an IRF530 MOSFET (default MOSFET for CircuitLab) is

- $\max(I_c) = 14A$  continuous, 49A instantaneous
- $\max(V_{ds}) = 100V$
- $160m\Omega @ I_{ds} = 8.4A @ V_{gs} = 10V$
- $V_{gs(th)} = 4.0V$  (max)

Determine

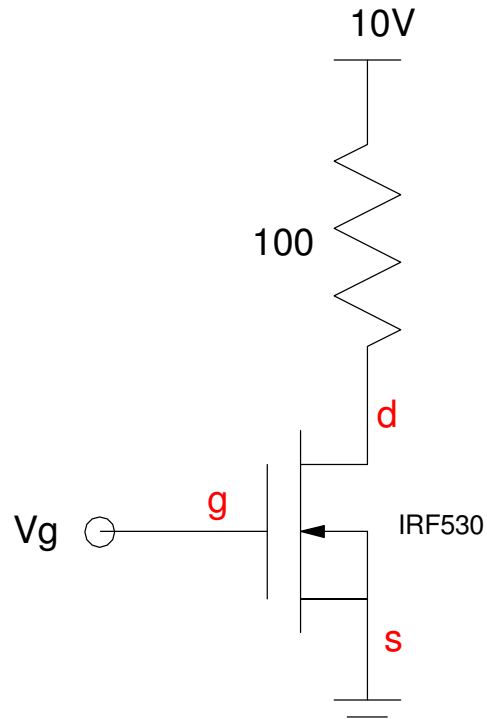- The transconductance gain,  $k_n$ ,
- The Q-point ( $V_{ds}$ ,  $I_{ds}$ ) when  $V_g = 5V$ , and
- The Q-point ( $V_{ds}$ ,  $I_{ds}$ ) when  $V_g = 5V$  and the 100 Ohm resistor is reduced to 10 Ohms



## Solution:

The specifications for an IRF530 MOSFET (default MOSFET for CircuitLab) is

- $\max(I_c) = 14\text{A}$  continuous, 49A instantaneous
- $\max(V_{ds}) = 100\text{V}$
- **160mOhm @  $I_{ds} = 8.4\text{A}$  @  $V_{gs} = 10\text{V}$**
- $V_{gs(th)} = 4.0\text{V}$  (max)

Determine the Q-point ( $V_{ds}$ ,  $I_{ds}$ ) when  $V_g = 10\text{V}$

### Problem 1: Determine $k_n$


The spec is in the ohmic region

$$V_{ds} = (160\text{m}\Omega)(8.4\text{A}) = 1.344\text{V}$$

$$I_d = k_n \left( V_{gs} - V_{th} - \frac{V_{ds}}{2} \right) V_{ds}$$

$$8.4\text{A} = k_n \left( 10\text{V} - 4\text{V} - \frac{1.344\text{V}}{2} \right) 1.344\text{V}$$
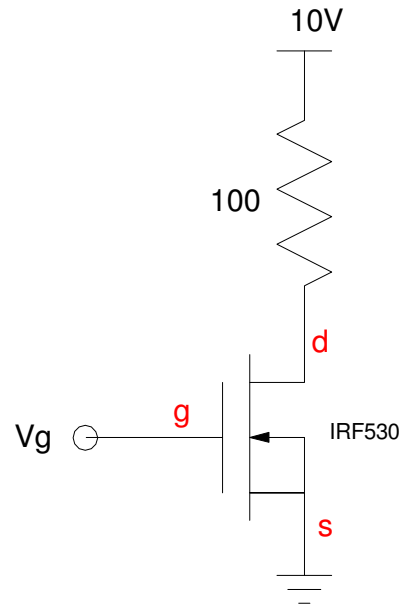
$$k_n = 1.173 \frac{\text{A}}{\text{V}^2}$$



## Problem 2: Determine ( $V_{ds}$ , $I_{ds}$ ) when $V_g = 5V$

Write 2 equations for 2 unknowns.

Assume Ohmic

$$I_d = k_n \left( V_{gs} - V_{th} - \frac{V_{ds}}{2} \right) V_{ds}$$


$$I_d = 1.173 \left( 5V - 4V - \frac{V_{ds}}{2} \right) V_{ds}$$

The load line is

$$100I_d + V_{ds} = 10$$


Turns are two solutions. In Matlab, you can see these
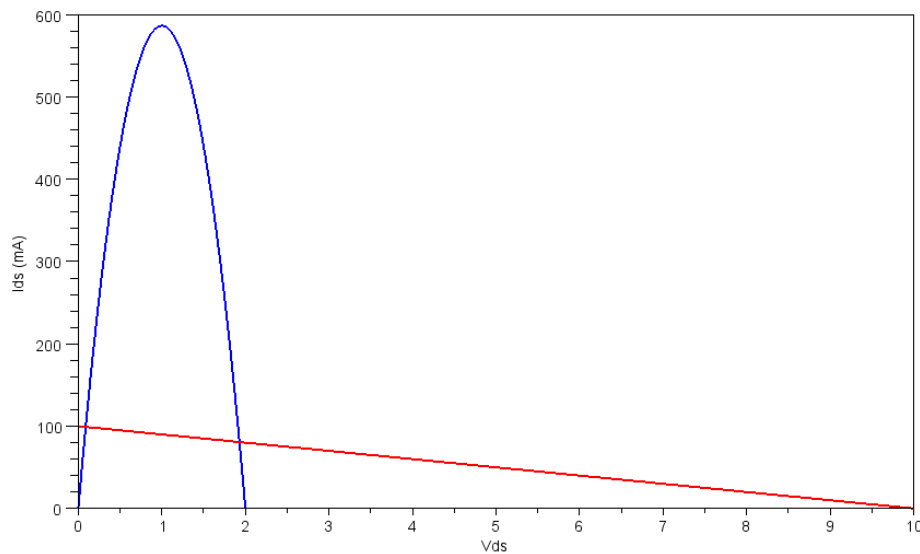
```
-->Vds = [0:0.01:10]';  
-->I1 = 1.173*(5 - 4 - Vds/2).*Vds;  
-->I2 = (10 - Vds) / 100;  
  
-->plot (Vds, I1*1000, Vds, I2*1000);  
-->xlabel('Vds');  
-->ylabel('Ids (mA)')
```



The solution on the left is

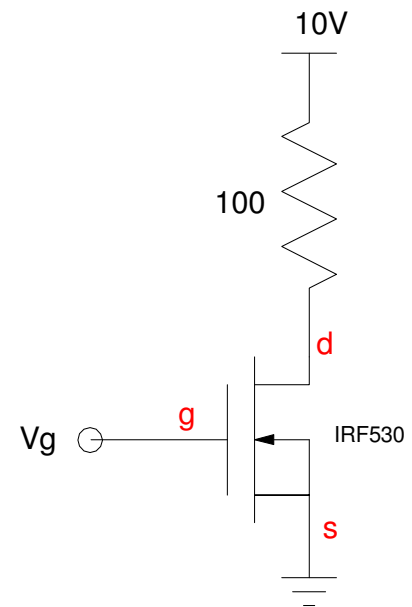- $V_{ds} = 88.33\text{mV}$
- $I_{ds} = 99.1\text{mA}$



### Problem 3: Determine ( $V_{ds}$ , $I_{ds}$ ) when $V_g = 5V$ and $R_d = 10\ \text{Ohms}$

Assume Ohmic again. The MOSFET equation is (no change)

$$I_d = 1.173 \left( 5V - 4V - \frac{V_{ds}}{2} \right) V_{ds}$$

The load line becomes.



$$10I_d + V_{ds} = 10$$

Now there is no solution. This tells you

- The load line does not intersect the Ohmic region equation
- The MOSFET is actually saturated

In Matlab
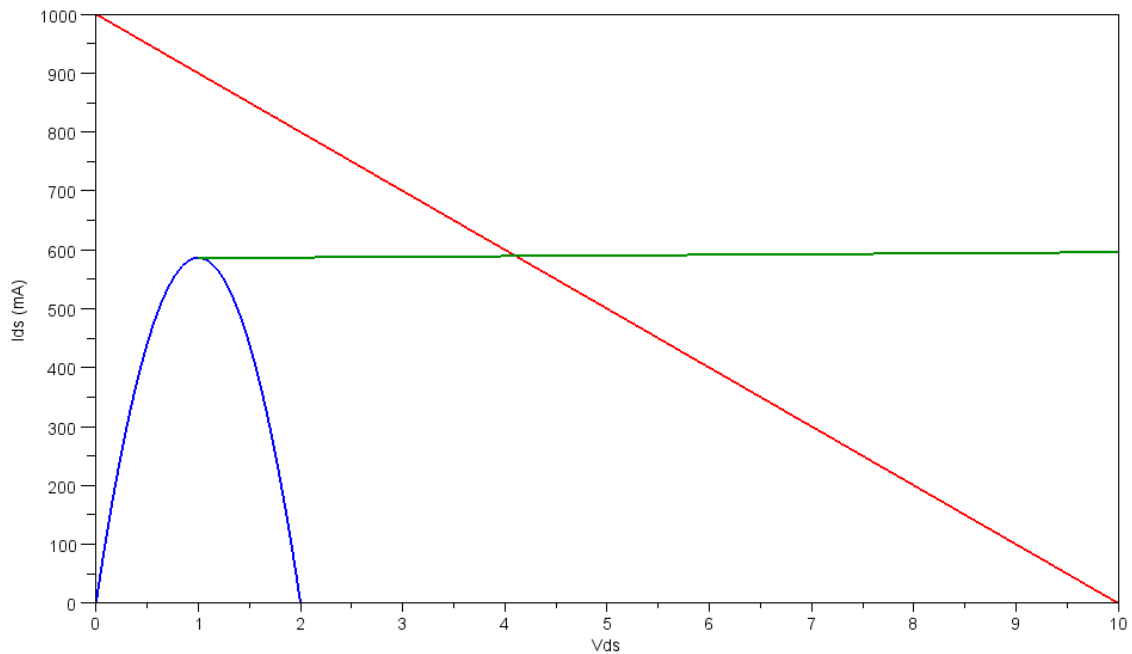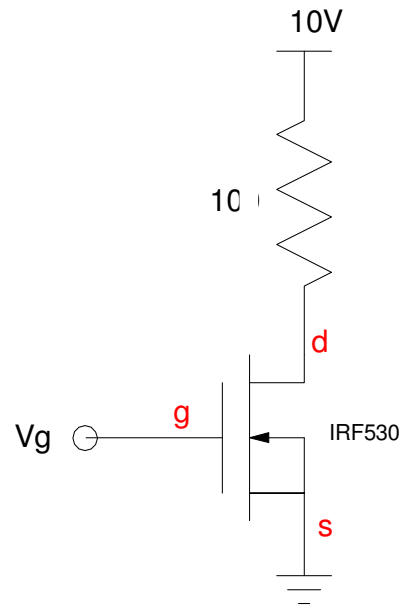
```
-->Vds = [0:0.01:10]';
-->I1 = 1.173*(5 - 4 - Vds/2).*Vds;
-->I2 = (10 - Vds) / 10;
-->plot (Vds, I1*1000, Vds, I2*1000);
-->max (I1) *1000
586.5
-->plot ([1, 10], [586, 596], 'm')
-->xlabel ('Vds');
-->ylabel ('Ids (mA)') 788
```



Load Line (red), Ohmic VI curve (blue), Saturated VI curve (green)

Since we're actually operating in the saturated region, the two equations you need to solve are

$$I_d = \frac{k_n}{2}(V_{gs} - V_{th})^2$$


$$I_d = \frac{1.173}{2}(5V - 4V)^2$$

$$I_d = 586.5mA$$

and the load line

$$10I_d + V_{ds} = 10$$

$$V_{ds} = 4.135V$$

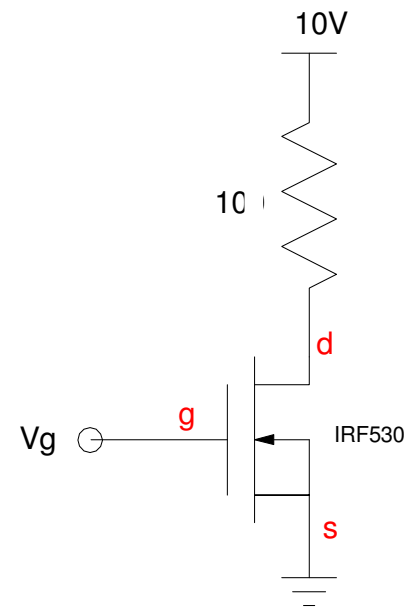

**Problem 2: Determine (Vds, Ids) when Vg = 10V**

Assume saturated state

$$I_d = \left(\frac{k_n}{2}\right)(V_{gs} - V_{th})^2$$

$$I_d = \left(\frac{1.173}{2}\right)(10 - 4)^2 = 21.149A$$

This is more than is possible (10V / 100Ohms = 100mA)

Assume Ohmic. Write 2 equations for 2 unknowns (Id, Vds)

$$I_d = k_n \left( V_{gs} - V_{th} - \frac{V_{ds}}{2} \right) V_{ds}$$

$$I_d = 1.173 \left( 10 - 4 - \frac{V_{ds}}{2} \right) V_{ds}$$

$$V_{ds} + 100I_d = 10$$

Solving

$$\mathbf{V_{ds} = 14.18mV, \quad I_{ds} = 99.7mA}$$

$$\mathbf{R_{ds} = (V_{ds} / I_{ds}) = 142mOhms}$$