


# ECE 320 - Homework #8

TTL Logic, MOSFET theory, MOSFET switch. Due Monday, October 19th

The following circuit implements a function using TTL logic

Assume

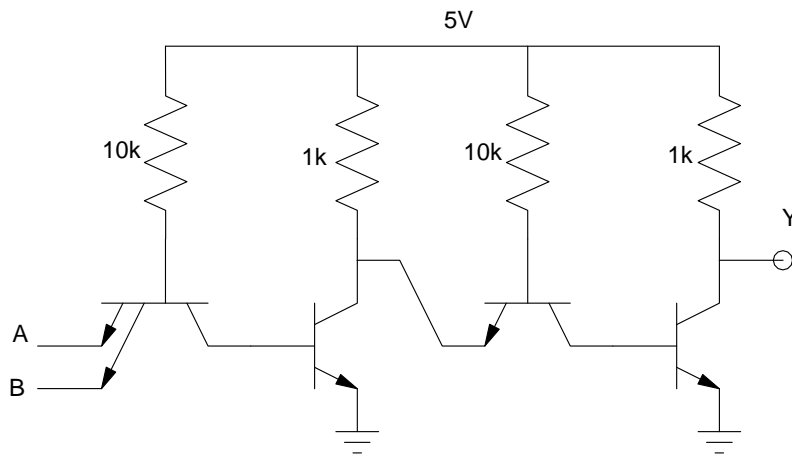
- $\beta = 100$  (NPN used correctly)
- $\beta = 0.1$  (NPN used in reverse)




- 1) What is the logic for this circuit?
- 2) Determine the voltages and currents for  
 $A = B = 5V$
- 3) Determine the voltages and currents for  
 $A = B = 0V$

Assume the VI characteristics for a MOSFET are as follows.

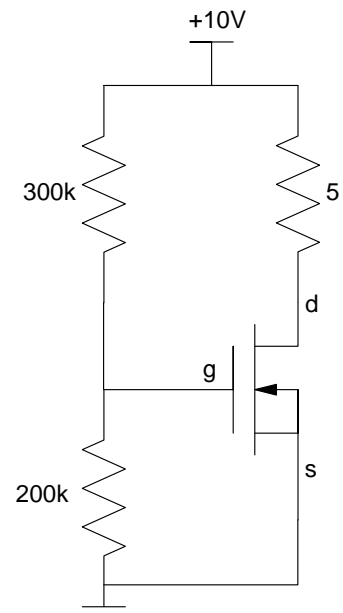- 4) Label the Off / Saturated / Ohmic regions on this figure
- 5) Determine the constant  $k_n$  for this MOSFET
- 6) Draw the load line and determine the operating point if connected as shown to the right:



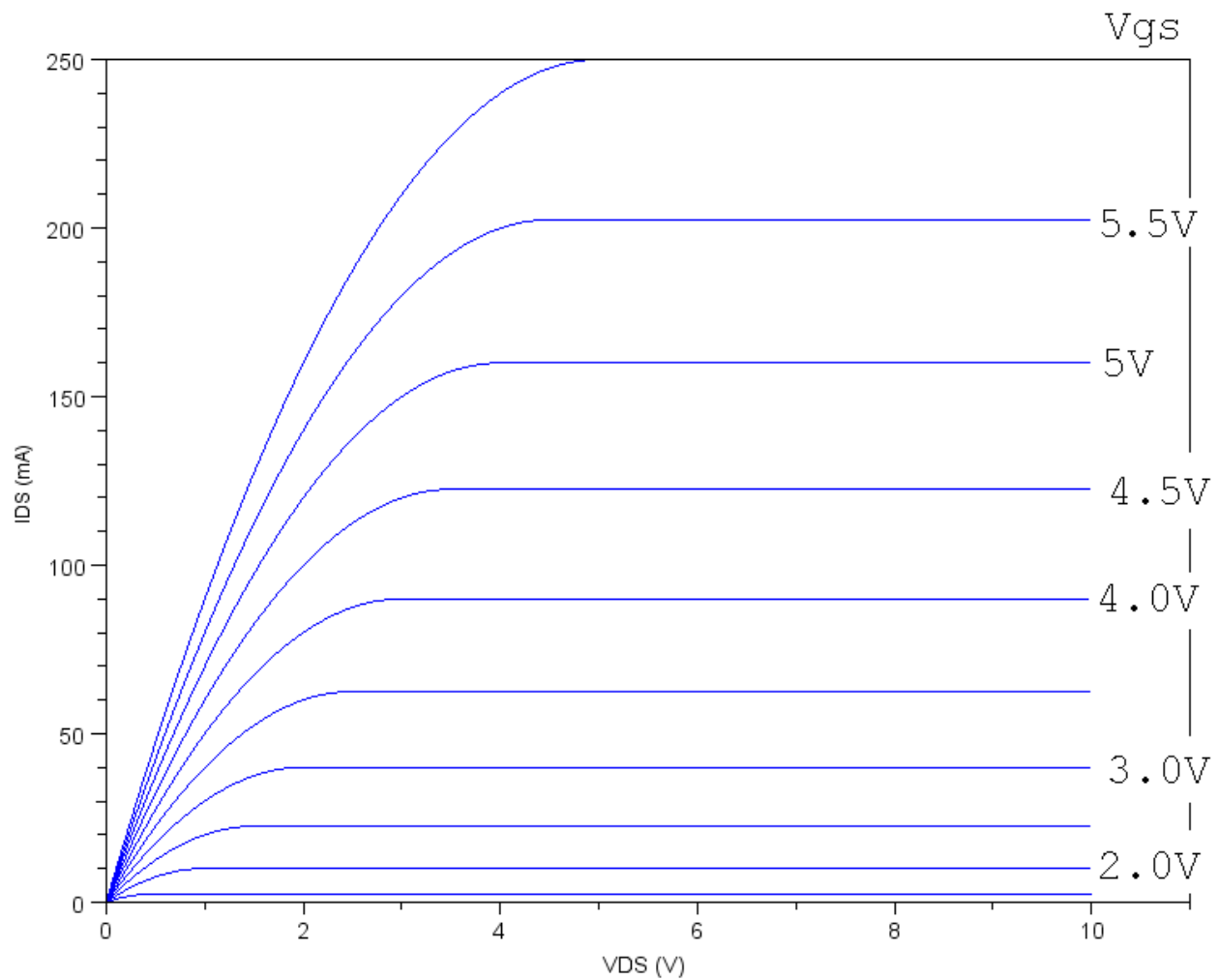

## Lab: (term project)

Take one section of your term project.

7) Requirements: Specify what your circuit is going to do

- Inputs
- Outputs
- Relationship

8) Analysis. Calculations for voltages, currents, resistors, capacitors, etc

9) Test: Check your analysis in simulation.

10) Validation: Build your circuit and check that it meets the requirements.