

ECE 320 - Homework #9

CMOS Logic, Op-Amps, Schmitt Triggers. Due Monday, October 26th

Assume an n-channel MOSFET with the following characteristics:

- $V_t = 2V$
- $R_{ds} = 1 \text{ Ohm @ } V_{gs} = 10V \text{ @ } I_{ds} = 100mA$


and a corresponding p-channel MOSFET with

- $V_t = -2V$
- $R_{ds} = 1 \text{ Ohm @ } V_{gs} = -10V \text{ @ } I_{ds} = 100mA$


- 1) Determine the constant K_n
- 2) Determine the resistance when $V_{gs} = 5V$
- 3) Design a CMOS gate to impliment

$$Y = AB + C$$

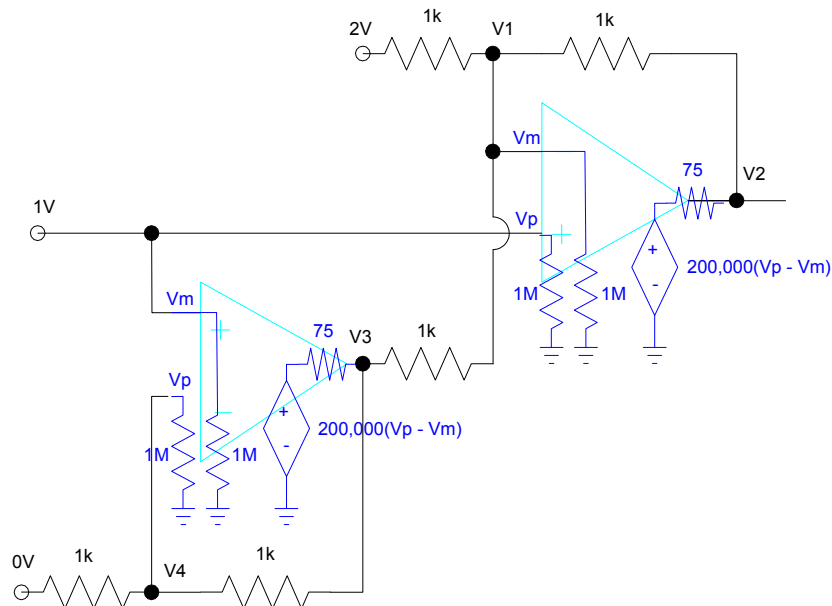- 4) Write the voltage node equations for the following op-amp circuit.



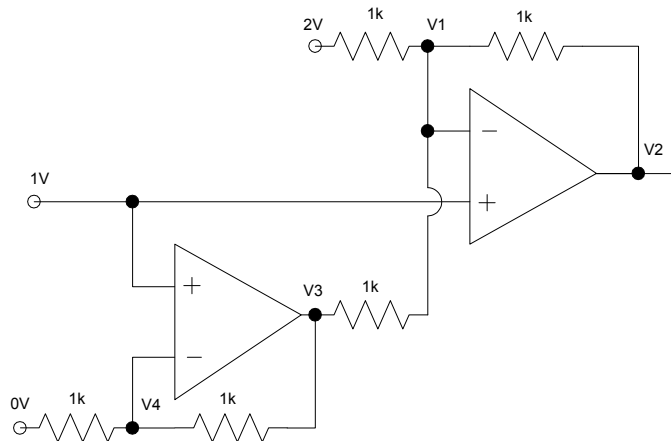5) Assume ideal op-amps. Write the voltage node equations for the following op-amp circuit (same as problem 4 but with ideal op-amps)



6) Comparitor: Design a circuit which outputs

- 10V for $V_{in} < 3V$
- 0V for $V_{in} > 3V$

7) Schmitt Trigger: Design a circuit which outputs

- 10V when $V_{in} > 4V$
- 0V when $V_{in} < 3V$
- No change for $3V < V_{in} < 4V$

8) Schmitt Trigger: Design a circuit for a night-light which outputs

- 0V when the light level is more than 10 Lux and
- 10V when the light level is less than 7 Lux

Assume a light sensor with $R = \frac{100,000}{Lux} \Omega$

Lab: (term project)

Take one section of your term project.

7) Requirements: Specify what your circuit is going to do

- Inputs
- Outputs
- Relationship

8) Analysis. Calculations for voltages, currents, resistors, capacitors, etc

9) Test: Check your analysis in simulation.

10) Validation: Build your circuit and check that it meets the requirements.