


# ECE 320 Quiz 1: Name \_\_\_\_\_

September 3, 2015. EE 206 Review



1) Assume each resistor is 1000 Ohms. Determine the resistance between A and B

$R_{AB} =$


2714  $\Omega$

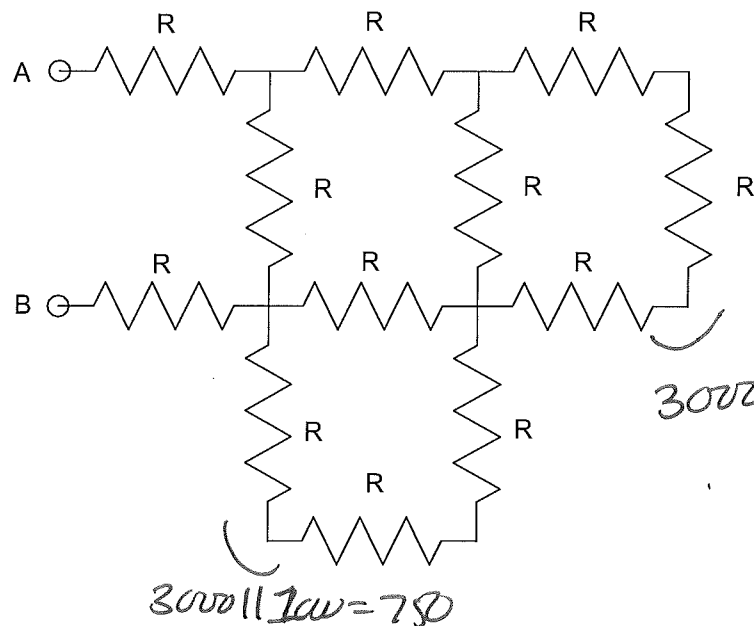

Redraw

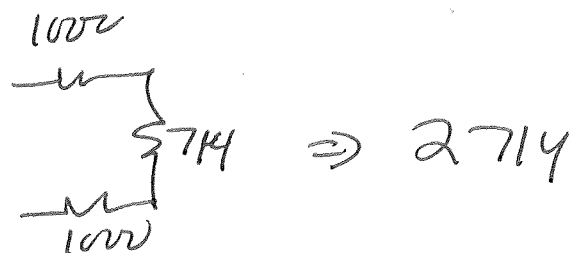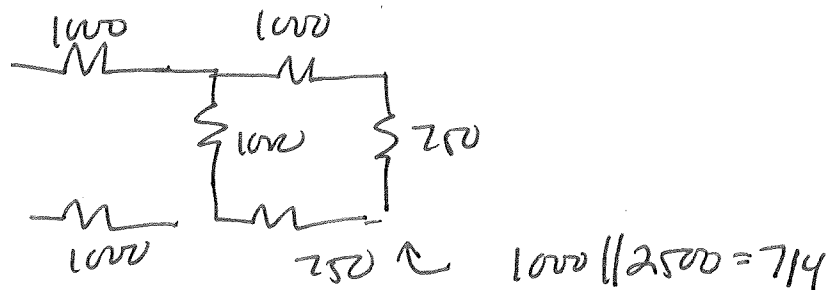

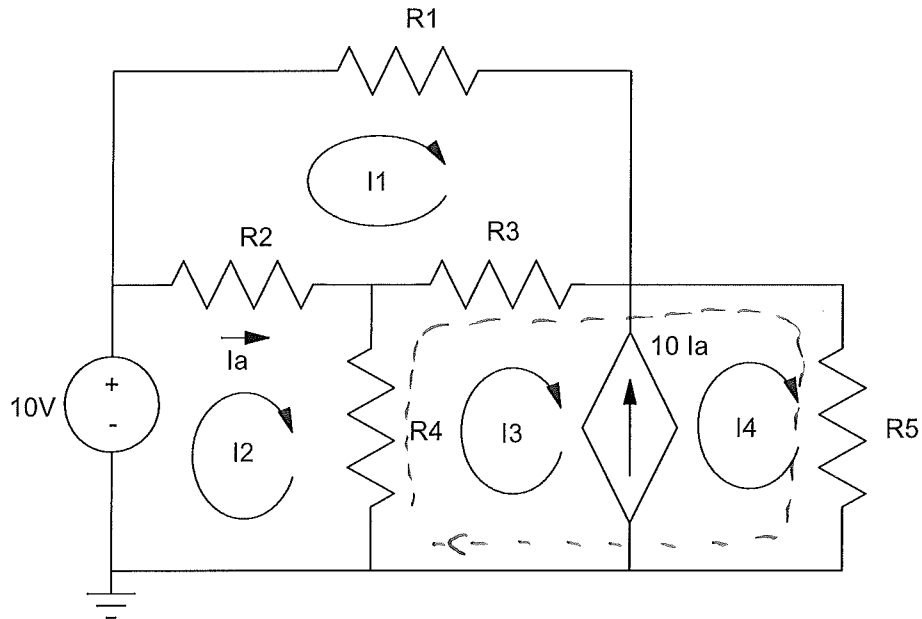2) For the following circuit, use current loops (KCL) to write N equations to solve for N unknowns. You don't need to solve.



Loop Equations:

$$I_1 R_1 + (I_1 - I_3) R_3 + (I_1 - I_2) R_2 = 0$$

$$-10 + (I_2 - I_1) R_2 + (I_2 - I_3) R_4 = 0$$

Superloop


$$(I_3 - I_2) R_4 + (I_3 - I_1) R_3 + I_4 R_5 = 0$$

I source

$$I_4 - I_3 = 10(I_2 - I_1)$$

$I_a$

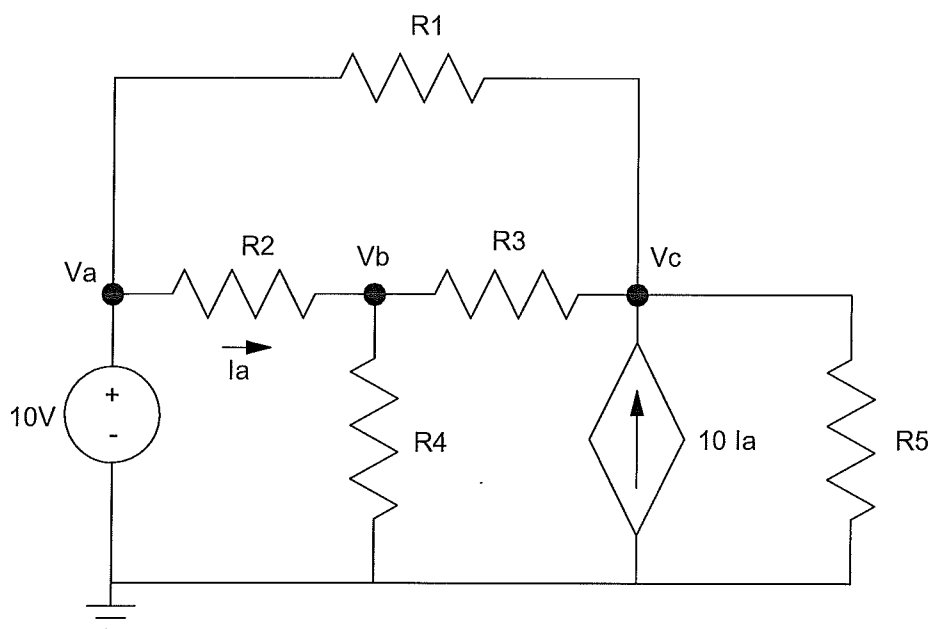3) For the following circuit, use voltage nodes (KVN) to write N equations to solve for N unknowns. You don't need to solve.



Voltage Node Equations:






$$V_a = 10$$

$$\frac{V_b - V_a}{R_2} + \frac{V_b}{R_4} + \frac{V_b - V_c}{R_3} = 0$$

$$\frac{V_c - V_a}{R_1} + \frac{V_c - V_b}{R_3} + \frac{V_c}{R_5} - 10 \left( \frac{V_a - V_b}{R_2} \right) = 0$$

4) Find the Thevenin equivalent for the following circuit.

Vth	Rth
2V	1600 $\Omega$

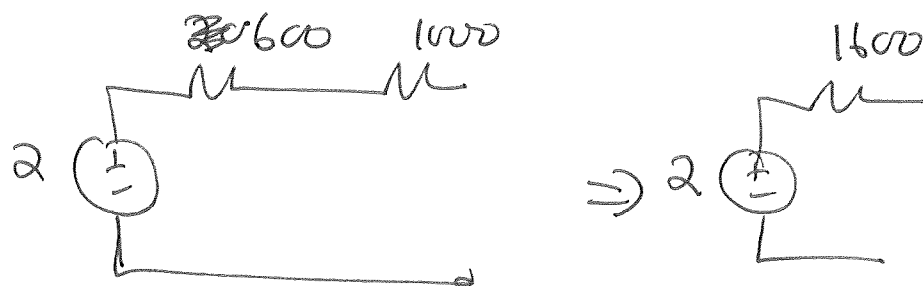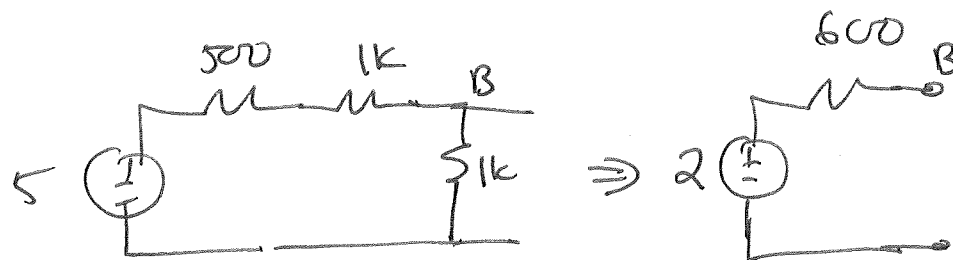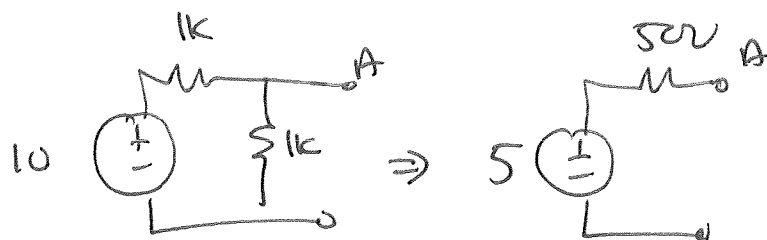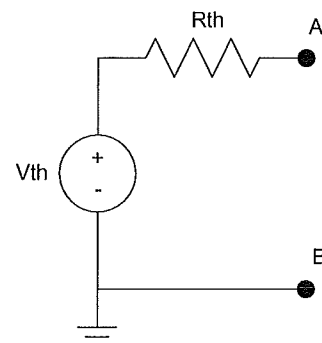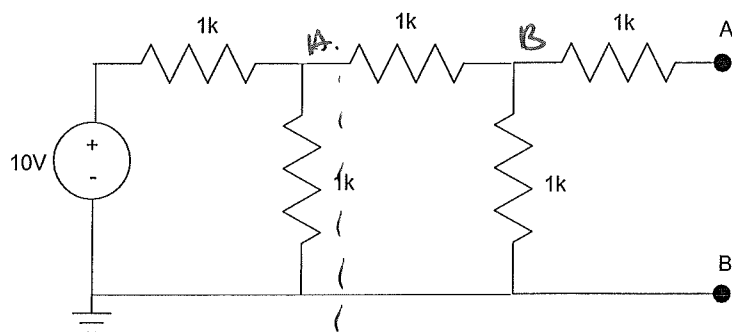


5) The following graph shows the functions

$$y = 3 \sin(x)$$

$$y = 0.04x^2$$

Find all solutions to these two equations

6 solutions  
see graph

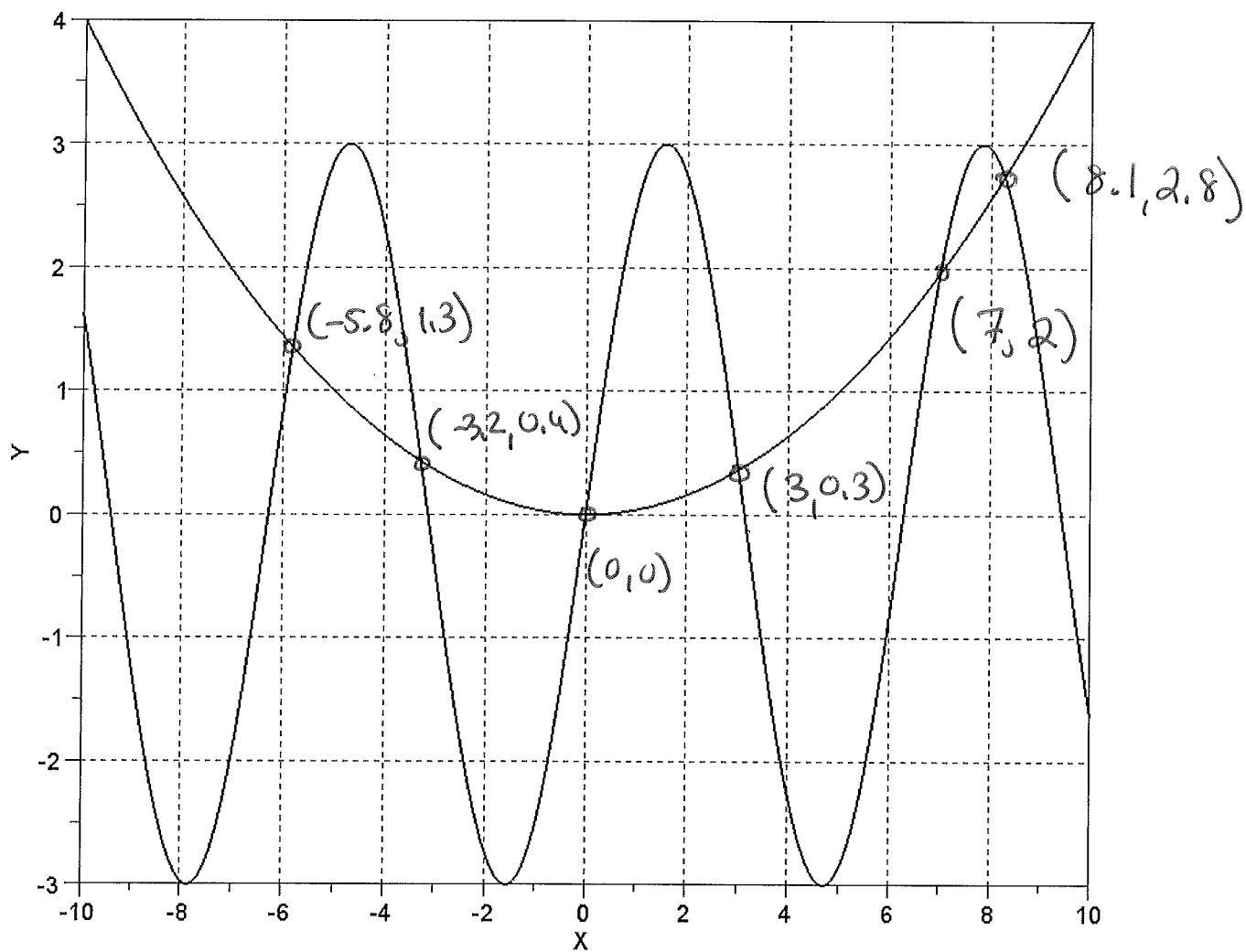



BONUS! Steven Colbert Trivia! Jeb! Bush is one of the first guests on Steven Colbert's Late Show and has already started a controversy. What is it?

- a) The Jeb! Bush campaign started running a fund-raising campaign to see the Colbert Show without asking the Colbert Show.
- b) Insisting that D\*\*\*\*d T\*\*\*p's name not be mentioned on the show.
- c) Insisting that Colbert sign a pledge that he will not run for President as a 3rd party candidate.
- d) The writers for the Colbert Show refused to provide the questions that Colbert will ask Jeb! Bush along with the answers.
- e) The Bush Campaign does not want the interview to be placed on the internet unless they can edit it first.

