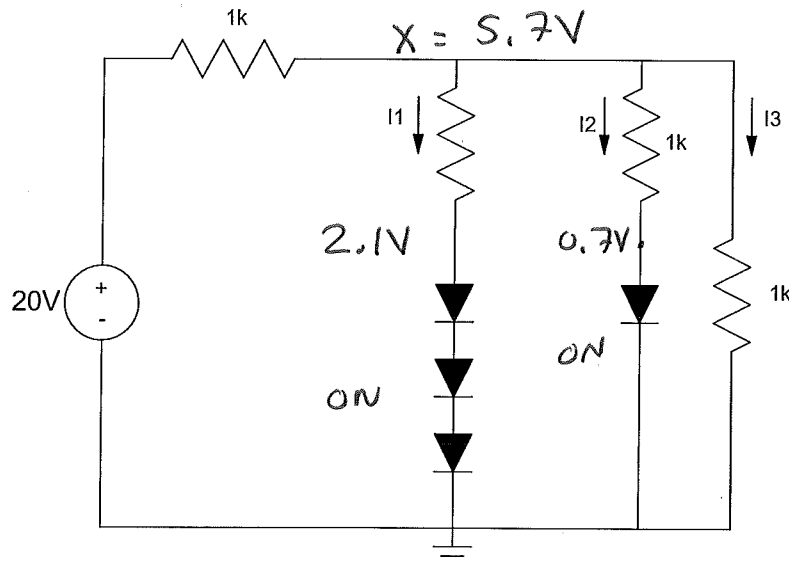


# ECE 320 - Quiz #3 - Name \_\_\_\_\_

Ideal Diode, Light Emitting Diodes. September 17, 2015

1) Assume ideal silicon diodes ( $V_f = 0.7V$ ). Determine the currents  $I_1$ ,  $I_2$ , and  $I_3$

$I_1$	$I_2$	$I_3$
$3.6mA$	$5mA$	$5.7mA$




$$\frac{X-20}{1k} + \frac{X-2.1}{1k} + \frac{X-0.7}{1k} + \frac{X}{1k} = 0$$

$$4X = 22.8$$

$$X = 5.7V$$

2) Assume ideal silicon diodes ( $V_f = 0.7V$ ). Determine the currents  $I_1$ ,  $I_2$ , and  $I_3$

$I_1$	$I_2$	$I_3$
0	$0.2\text{mA}$	$0.9\text{mA}$

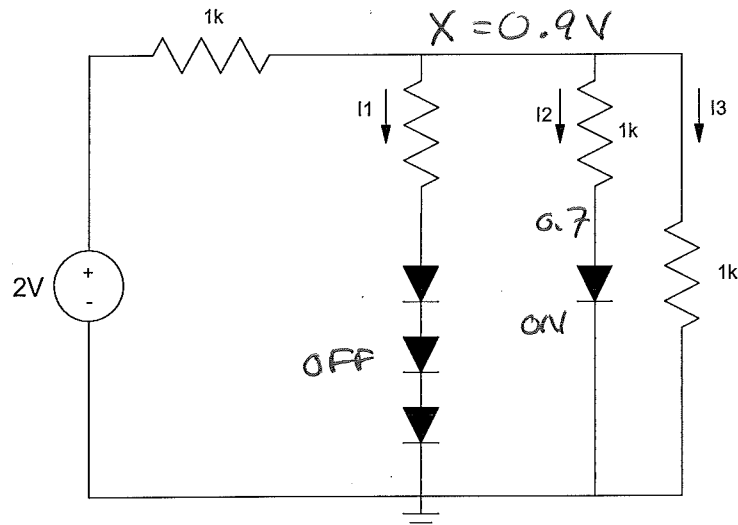


$$\frac{X-2}{1k} + \frac{X-0.7}{1k} + \frac{X}{1k} = 0$$

$$3X = 2.7$$

$$X = 0.9V$$


3) Assume ideal silicon diodes ( $V_f = 0.7V$ ). Determine the voltages  $V_1$ ,  $V_2$ , and  $V_3$

V1	V2	V3
0.5V	0.5V	0.5V

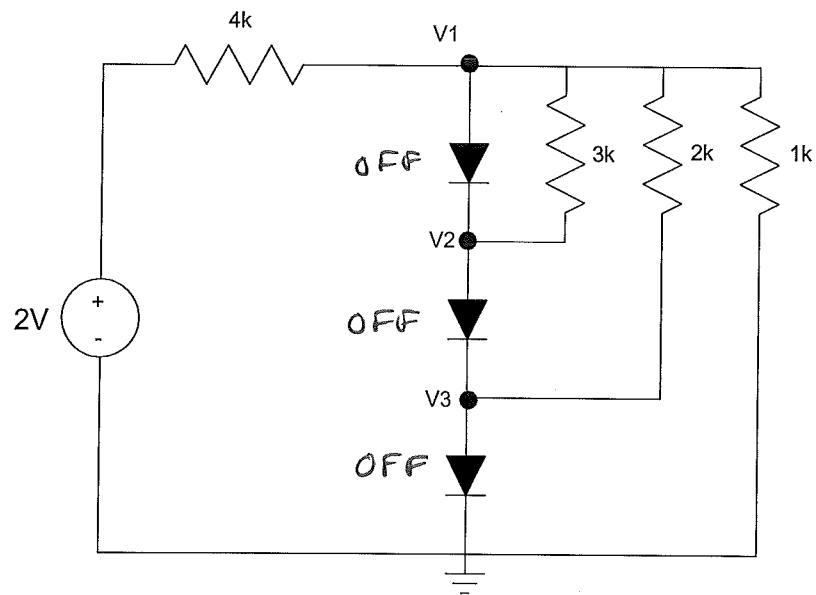

4) Assume ideal silicon diodes ( $V_f = 0.7V$ ). Determine the voltages  $V_1$ ,  $V_2$ , and  $V_3$

$V_1$	$V_2$	$V_3$
0.9143 V	0.9143 V	0.7 V

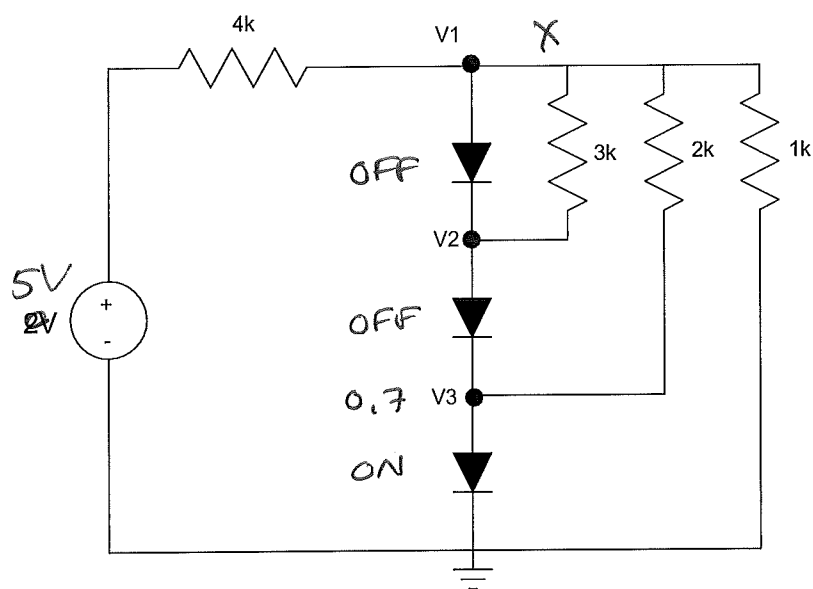

$$\frac{X-5}{4k} + \frac{X-0.7}{2k} + \frac{X}{1k} = 0$$


$$1.75X = 1.6$$

$$X = 0.9143$$

5) Assume ideal diodes with the following specifications:

	red	green	blue
Peak forward current	100mA	100mA	100mA
$V_f @ 20mA$	2.1V	3.6V	3.6V
mcd @ 20mA	8,000	8,000	8,000
dominant wavelength	630nm	520nm	470nm

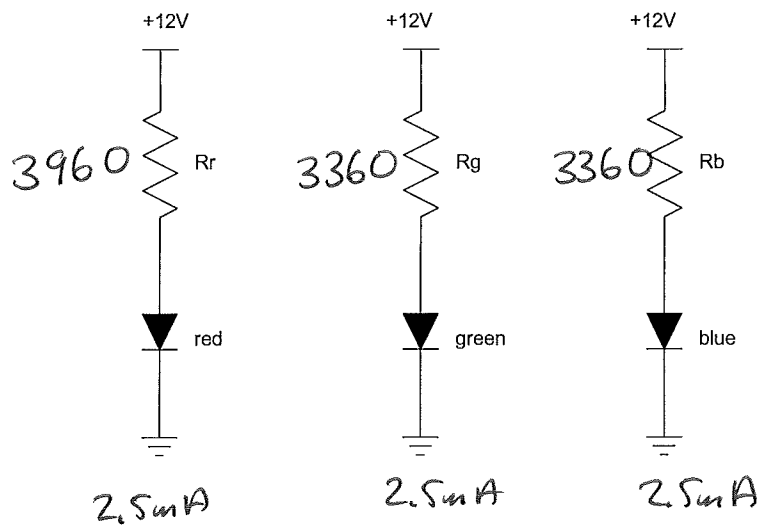Find  $R_r$ ,  $R_g$ , and  $R_b$  so that each LED outputs 1,000 mcd.



$$R_r = \frac{12 - 2.1}{2.5mA} = 3960$$

$$R_b = \frac{12 - 3.6}{2.5mA} = 3360$$

$$R_g = \frac{12 - 3.6}{2.5mA} = 3360$$

Bonus! Cullen Murphy, author of "Are We Rome?" was on the Colbert Show in 2007. Colbert's final question was "United States vs. Rome. Who would win?" What was Cullen Murphy's answer:

- United States: We have nuclear weapons
- United States: Our military-industrial complex is of a scale that Rome could not match.
- Tie: Neither government works all that well.
- Rome: Rome had no scruples and would stop at nothing.
- Rome: Rome could take massive casualties and would never give up.

