
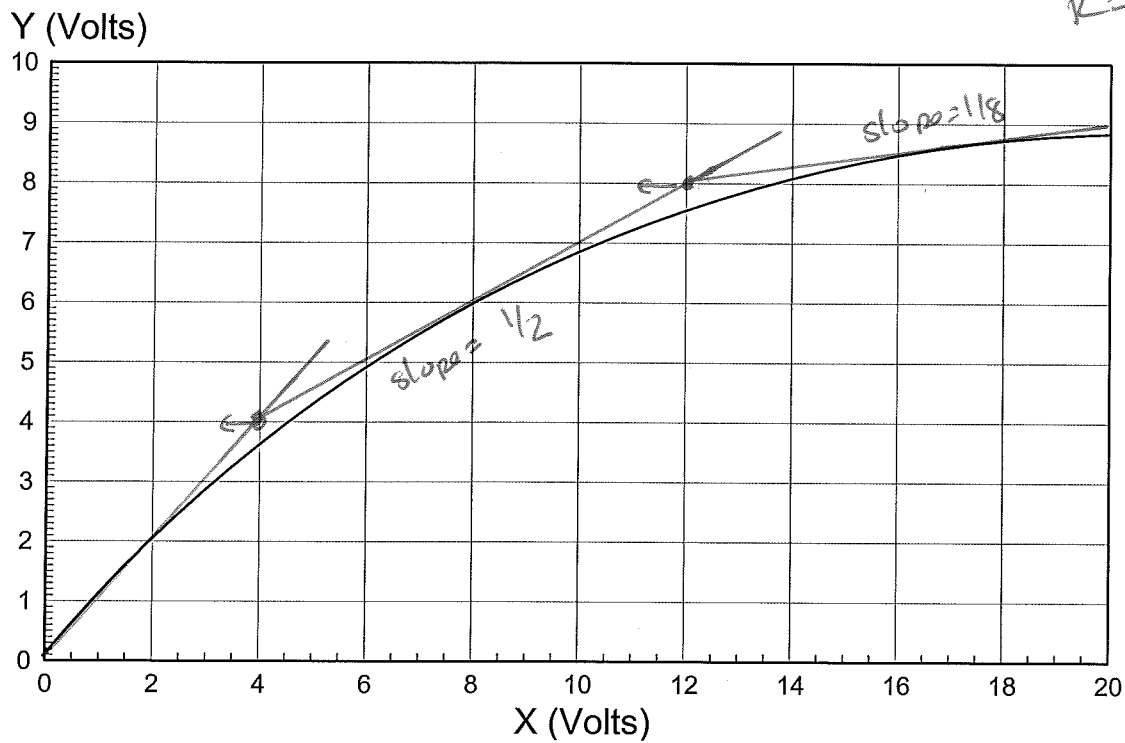


ECE 320 - Quiz #4 - Name _____

Clipper - Max/Min - AC to DC Converters. September 24, 2015

1) Find V_1 , R_1 , V_2 , and R_2 so that the following circuit has approximately the following I/O relationship:

R_1	V_{z1}	R_2	V_{z2}
2000	4V	398	8V

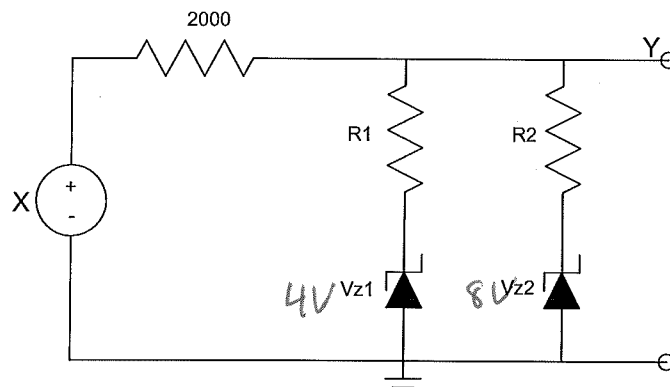



$$\frac{R}{R+2000} = 1/8$$

$$R = 285$$

$$\approx 1000 \parallel R_2$$

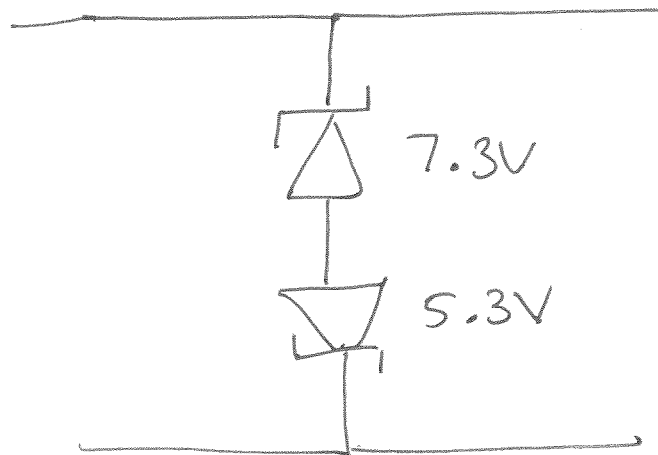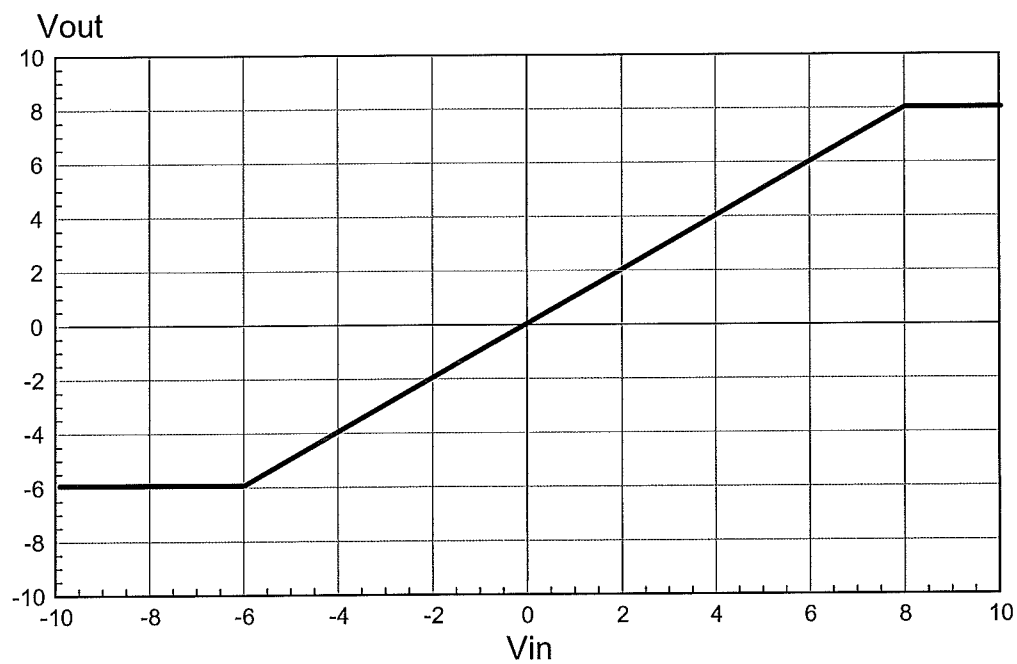2) Design a clipper circuit so that the output is


$$V_{out} = \begin{cases} +8V & V_{in} > 8V \\ V_{in} & -6V < V_{in} < +8V \\ -6V & V_{in} < -6V \end{cases}$$



3) Determine the voltages for the following max/min circuit. Also determine the function is implementing


V1	V2	Y	function: $y=f(A,B,C)$
3.3V	5.3V	4V	$y = \min(\max(A,B), \max(B,C))$

$$y = (A+B)(B+C)$$

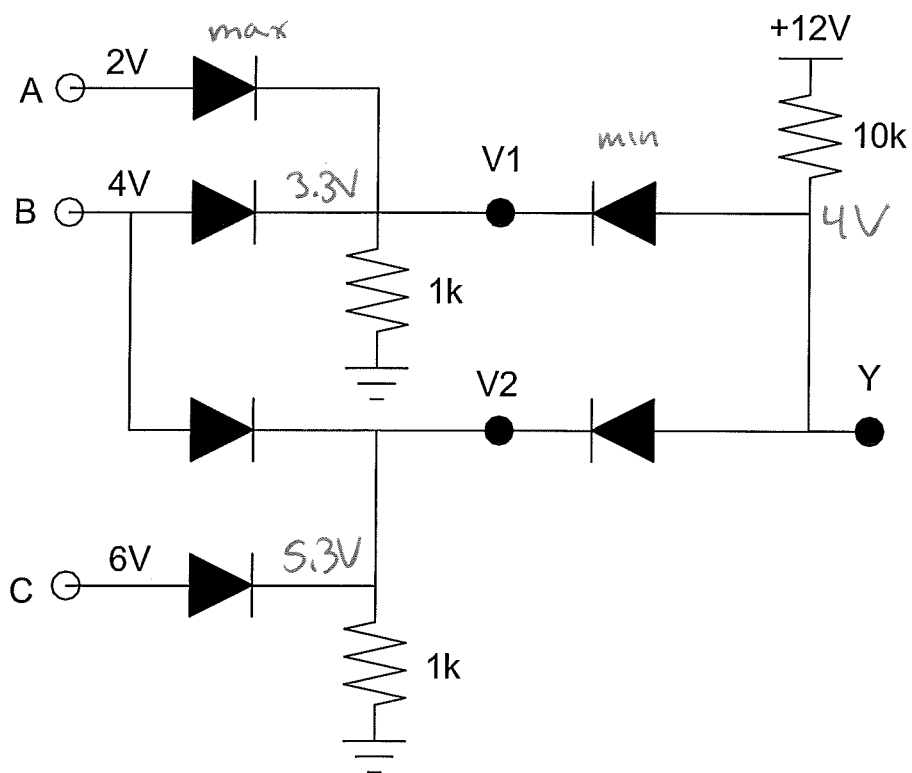

4) Determine the maximum of V_{out} and the peak-to-peak ripple at V_{out}

max(V_{out})	ripple at V_{out} (peak-to-peak)
14.3V	1.797V _{pp}

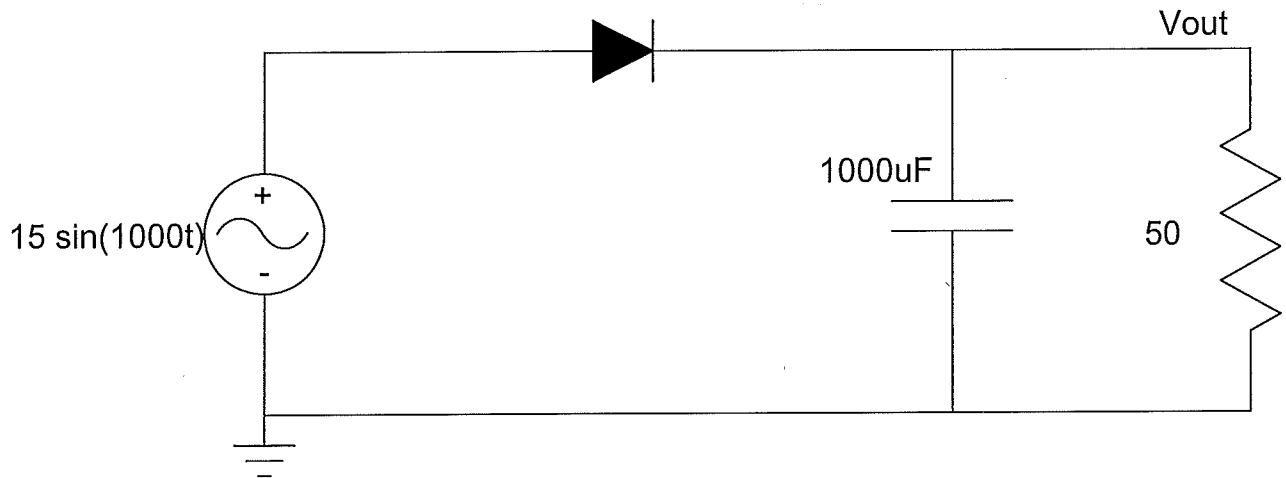

$$f = 159 \text{ Hz}$$

$$dt = 6.3 \text{ ms}$$

$$I = C \frac{dV}{dt}$$

$$I = \frac{14.3}{50} = 286 \mu A$$


$$286 \mu A = 1000 \mu F \cdot \frac{dV}{6.3 \text{ ms}}$$

$$dV = 1.797 \text{ V}$$

5) Determine the voltages at V1 and V2

max(V1)	ripple at V1 (peak-to-peak)	ripple at V2 (peak-to-peak)
13.6V	.8985V _{pp}	.0112V _{pp}

$$15 - 0.7 \times 2$$

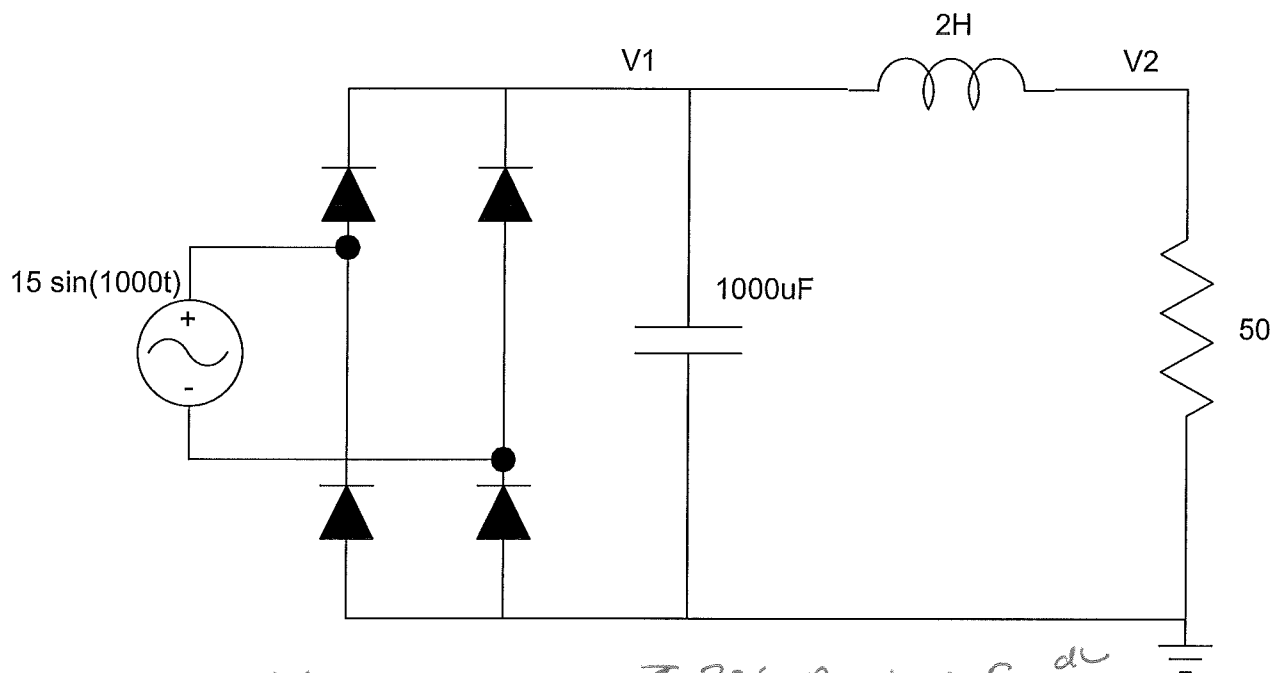

$$I = C \frac{dV}{dt}$$

$$I = \frac{143\text{V}}{50\Omega} = 286\text{mA}$$

$$f = \frac{1000}{2\pi} = 318\text{Hz}$$

$$dt = \frac{1}{f} = 3.1\text{ms}$$

$$\approx 286\text{mA} = 1000\mu\text{F} \cdot \frac{dV}{3.1\text{ms}}$$

$$dV = .8985\text{V}_{pp}$$

$$V_2 = \left(\frac{50}{50 + j\omega L} \right) V_1$$

$$= \left(\frac{50}{50 + j4000} \right) \cdot .8985$$

Colbert Bonus! In 2008, an online vote was taken to name a bridge. Just for fun, Steven Colbert asked his viewers to go online and vote "Colbert". In spite of winning fairly, the bridge was named something else. What was this bridge?

- a) The Megyeri Bridge in Budapest, Hungary
- b) The Ambassador Bridge between Detroit and Windsor, Canada
- c) The Isle of Palms bridge in South Carolina
- d) The Wandsworth Bridge in West London, England
- e) 14th Street Bridge, Washington DC

