

ECE 320 - Quiz 5: Name _____

DC to DC Converters, Transistor Switches. October 1st, 2015


- 1) Design a circuit which converts 20V DC to 5V DC using a transistor, with the output capable of driving 300mA @ 5V. Calculate the efficiency

RL for 300mA	R1	efficiency
16.67 Ω	< 14.3k Let $R_1 = 10k$	24.79%

5V 300mA

$$P_{out} = 300mA \cdot 5V = 1.5W$$
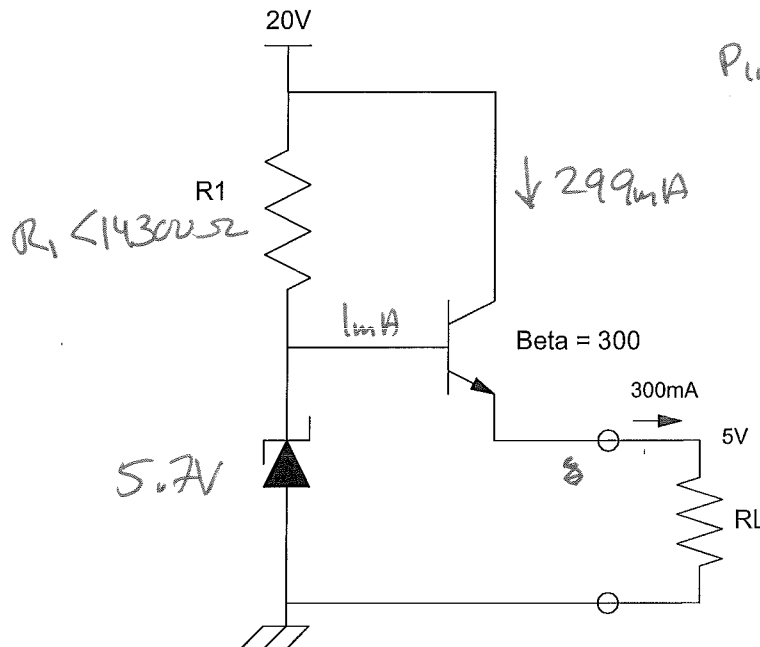
$$P_{in} = (20V \cdot (299mA + \frac{20V - 5V}{R_L})) = 6.66W$$



2) The following Buck converter drops 20V down to 5V DC. Assume


$$L = 1\text{H}$$

$$C = 0$$

$$\text{Switching Frequency} = 1\text{kHz}$$

Determine the following

On/Off Cycle Time for the switch for $V_o = 5\text{V}$	The ripple at the load	efficiency
$\frac{5}{20}$	318 mV_{pp}	90.7%

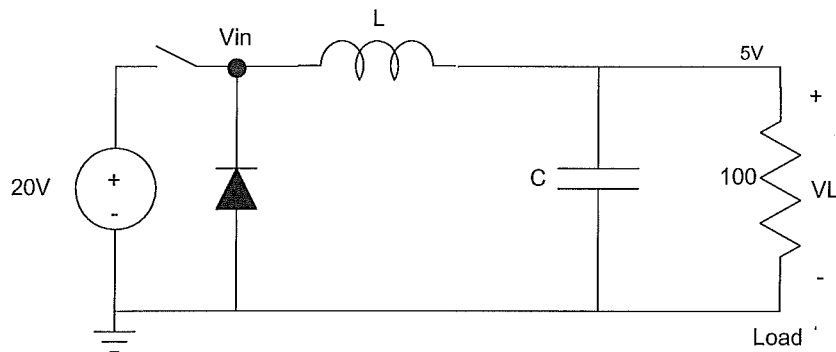

$$\text{ripple} \approx \left(\frac{100}{100 + j\omega L} \right) 20\text{V}_{pp}$$

$$P_{out} = \frac{5^2}{100} = 25\text{mW}$$

$$= 250\text{mW}$$

$$\approx \left(\frac{100}{100 + j6283} \right) 20$$

$$\approx 318\text{V}_{pp}$$

on $P_{loss} = 0$
 $\sum P = 100\text{W}$

off: $\sum P = \frac{5}{5.7} = 87.7\%$

$$\eta = (.25)(100\%) + (.75)(87.7\%)$$

$$\approx 90.7\%$$

3) The following Buck converter drops 20V down to 5V DC. Assume

$$L = 1\text{H}$$


$$C = 10\mu\text{F}$$

$$\text{Switching Frequency} = 1\text{kHz}$$

Determine C so that the ripple is 10mV peak-to-peak

Ripple for $C = 10\mu\text{F}$	C for a ripple of 10mVpp
49.8mV_{pp}	$50\mu\text{F}$

$$(50.66\mu\text{F})$$

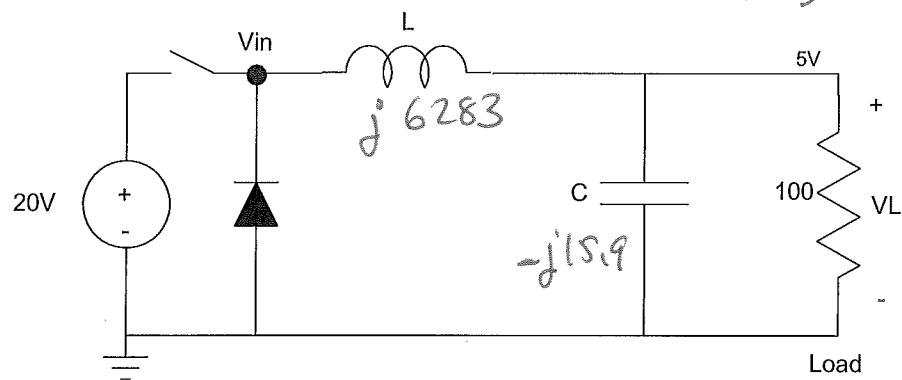

$$V_L \approx \left(\frac{100 \parallel -j15.9}{100 \parallel -j15.9 + j6283} \right) 20V_{pp}$$

$$\approx 0.0498 V_{pp}$$

25x too large


make C 5x ~~smaller~~ bigger

4) For the following circuit, assume the transistor has a current gain of 100 ($\beta = 100$). Determine the following

I_b	I_c	V_{ce}	Transistor State off / active / saturated
2.15mA	215mA	21.85V	active

$(\beta=100)$
 (645mA)
 $(\beta=300)$

17.55V active)

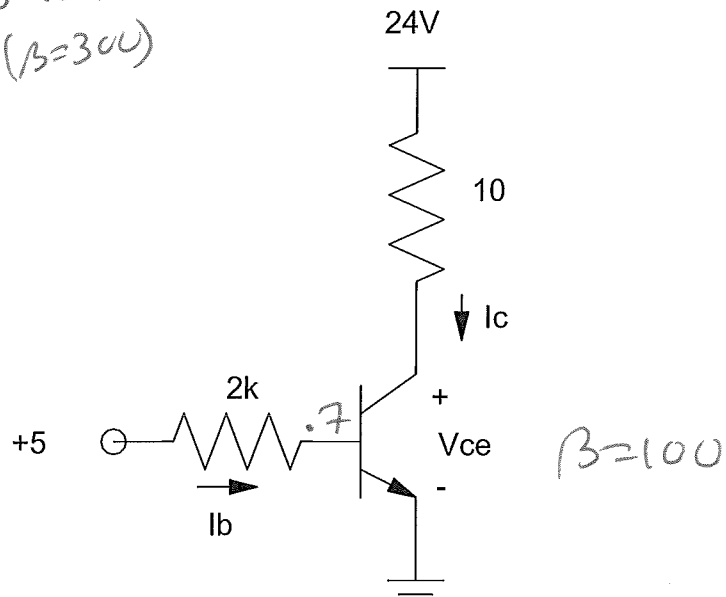


$$\frac{5 - 0.7}{2k} =$$

5) Modify the following circuit so that the

- Current $I_c = 100\text{mA}$
- Current $I_b < 10\text{mA}$
- The transistor is saturated

R_b	R_c	V_{ce}
430..4.3k	238 Ω	0.2V

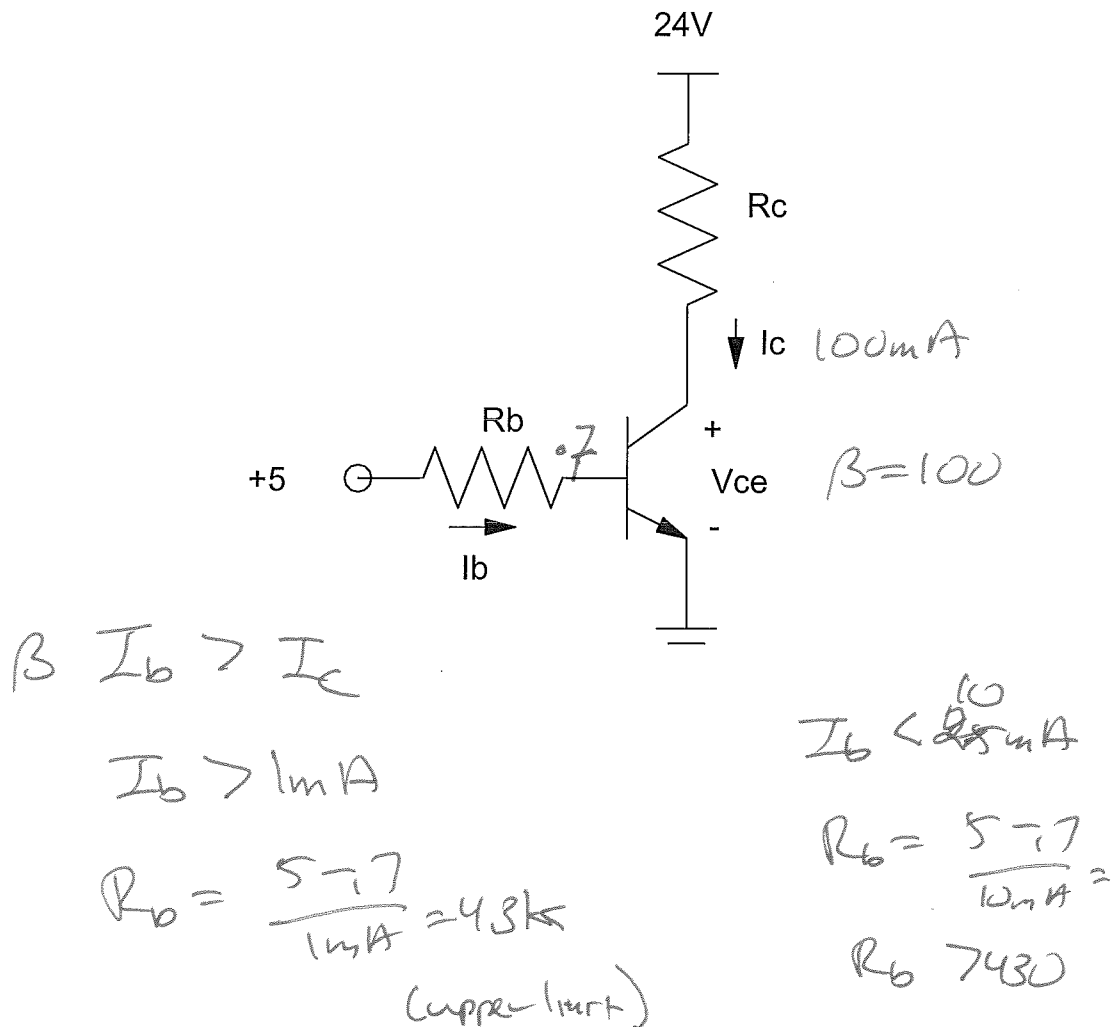

Colbert Trivia! Citizens United was a supreme court decision which opened the doors to Super-PAC's along with their ability to raise unlimited amounts of money from anonymous donors. What happens to the money in a Super-PAC after the election?

- a) The money becomes the property of the candidate
- b) The money becomes the property of the owner of the Super-PAC
- c) Since the donors are anonymous, the money must be given to charity
- d) The money is confiscated by the Federal Election Commission
- e) The money must be transferred to another active Super-PAC

