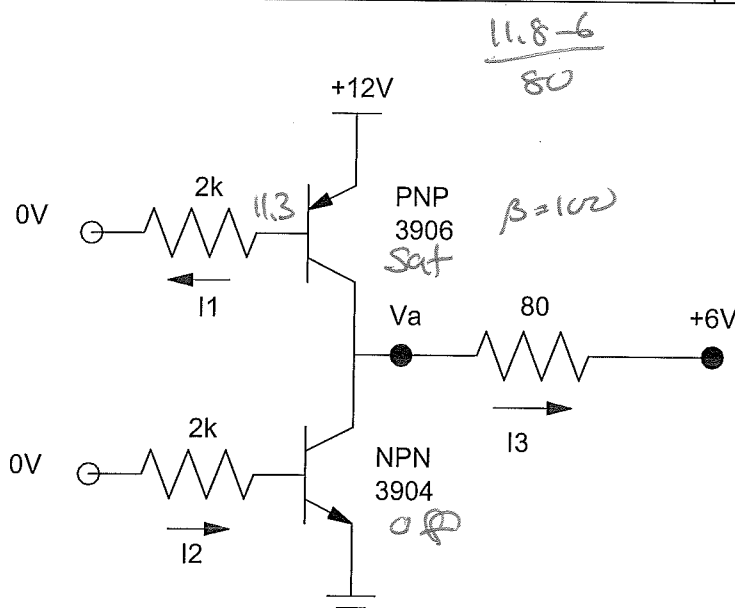


# ECE 320 - Quiz 6: Name \_\_\_\_\_

H-Bridge, SCR Rectifiers. October 8th, 2015

For the following half-H-bridge, determine the voltages and currents. Assume each transistor has a current gain  $\beta = 100$ .

I1	I2	I3	Va
5.65mA	○	72.5mA	11.8V



check:  $\beta I_b > I_c$


$$100 \cdot 5.65 \text{mA} > 72.5 \text{mA}$$

$$565 \text{mA} > 72.5 \text{mA}$$

yes, the PNP is saturated

2) Assume each transistor has a current gain of 100. Determine the voltages and currents.

I1	I2	Va	Vb
1.13mA	-56.5mA	7.28V	11.8V
2	3	3	2
$11.8V - (56mA)80\Omega$			

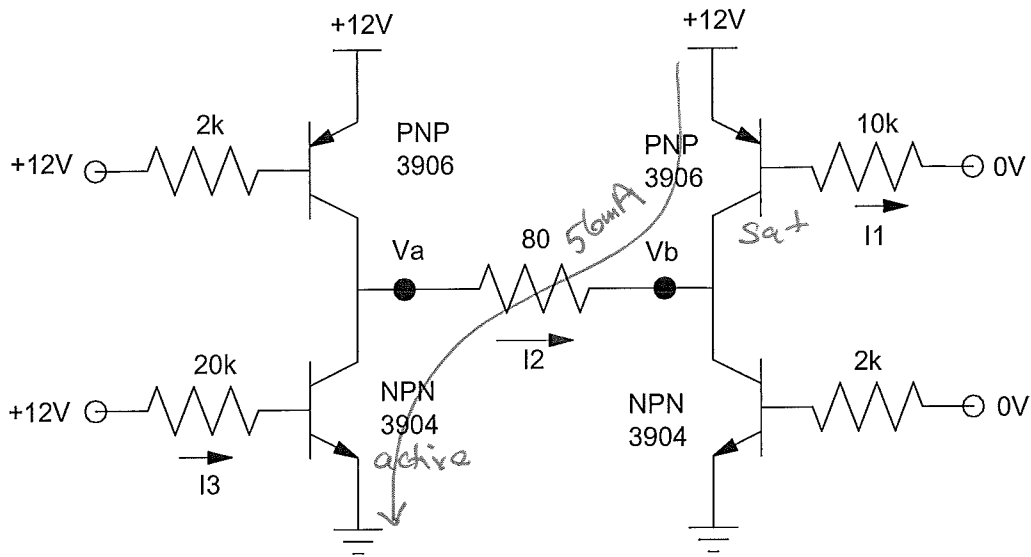

$$I_3 = \frac{12 - 0.7}{20k} = 56.5\mu A$$

$$\beta I_3 = 56.5mA$$

$$I_1 = \frac{11.3 - 0}{10k} = 1.13mA$$

$$\beta I_1 = 113mA$$

$$\frac{12}{80} = 150mA$$

$$I_2 = \text{current} \min(56\mu A, 113mA, 150mA)$$

$$= 56\mu A$$

3) Assume the output of a DC to AC converter is

$$V_{out} = 7 \sin(100t) + 1.5 \sin(200t) + 0.7 \sin(300t)$$

with a load of 1 Ohm. What is the energy in the 1st harmonic (100 rad/sec), the total energy, and the percentage of the energy in the 1st harmonic?

Energy in the 100 rad/sec term	Total Energy	Efficiency: $E(100) / E(\text{total})$
24.5W	25.87W	94.7%

$$P_{100} = \frac{1}{2} \frac{V_p^2}{R} = 24.5W$$

$$P_{200} = \frac{1}{2} \frac{V_p^2}{R} = 1.125W$$

$$P_{300} = \frac{1}{2} \frac{V_p^2}{R} = 0.245W$$

---

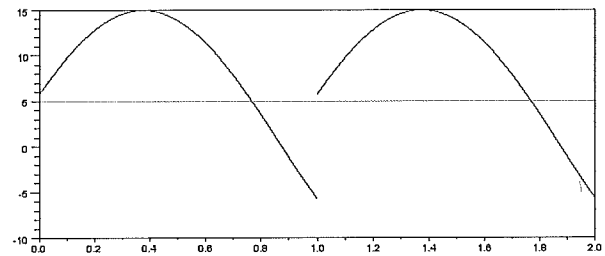

$$P_{total} = 25.87W$$

4a) Assume a SCR with four diodes with the output of the full-wave rectifier being:

$$V_a = 15 \sin(t + \phi) \quad 0 < t < \pi$$

Determine the firing angle,  $\phi$ , so that the DC level is 5.00V

$$\frac{1}{\pi} \int_0^{\pi} 15 \sin(t + \phi) dt = 5$$



Firing Angle =  $58.43^\circ$

$$-\cos(t + \phi) \Big|_0^{\pi} = \frac{5\pi}{15}$$

$$2 \cos(\phi) = \frac{5\pi}{15}$$


$$\phi = 58.43^\circ$$

4b) Assume a SCR with five diodes, with the output of the full-wave rectifier being

$$V_a = \begin{cases} 15 \sin(t) & t > \phi \\ 0 & t < \phi \end{cases}$$

Find the firing angle,  $\phi$ , so that the DC level is 5.00V
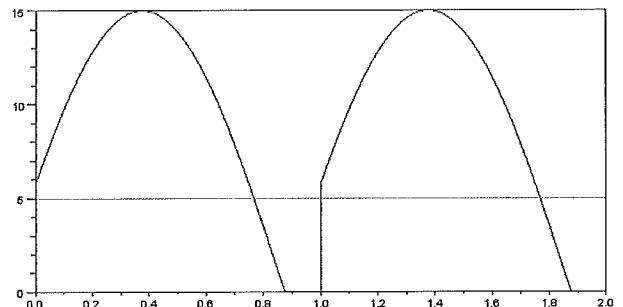
$$\frac{1}{\pi} \int_{\phi}^{\pi} 15 \sin(t) dt = 5$$



Firing Angle =  $87.29^\circ$

$$-\cos(t) \Big|_{\phi}^{\pi} = \frac{5\pi}{15}$$

$$1 + \cos \phi = \frac{5\pi}{15}$$

$$\phi = 87.29^\circ$$

5) Assume a SCR with a firing angle of 45 degrees so that voltage at  $V_a$  is


DC Term: 8.81V

AC: 20.74V<sub>pp</sub> @ 120 Hz

Find R, L, C so that the load has

- A current to the load (R) is 100mA and
- The ripple across the resistor is 100mV<sub>pp</sub>

R	L	C
88.1 $\Omega$	24.23 H 1 H	0 364.8 $\mu$ F

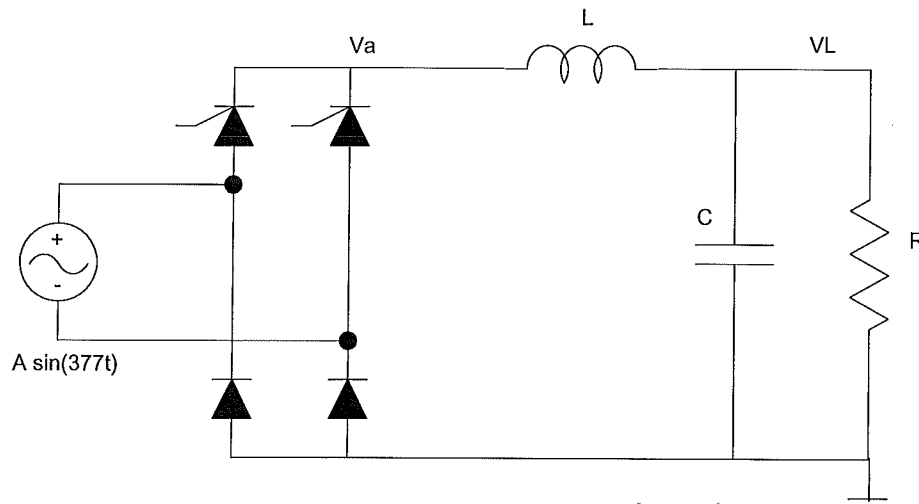

$$\frac{R}{R + j\omega L} 20.74_{pp} = 0.1_{pp}$$

$$\omega L = 18.27 k\Omega$$

$$L = 24.23 H$$

$$C = 0$$

$$L = 1 H$$

$$\frac{1}{\omega^2 LC} = \frac{0.1}{20.74}$$

$$LC = 364.8 \cdot 10^{-6}$$

$$C = 364.8 \mu F$$

Colbert Trivia! What was the slogan for Steven Colbert's presidential campaign in 2012?

- a) Making a better tomorrow tomorrow.
- b) Corporations are people, people are people, cats are people.
- c) We're making cheese great
- d) Vote early, vote often, vote Colbert
- e) Colbert Nation Unite!