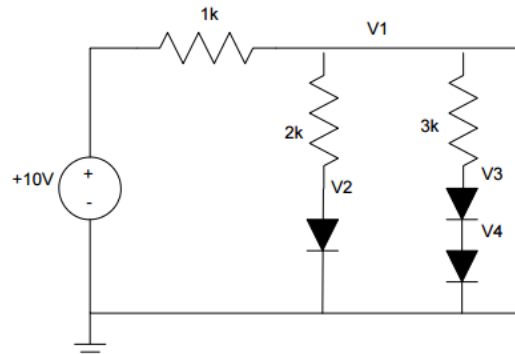


ECE 320 - Solution to Homework #3

Ideal Diode, Light Emitting Diodes. Due monday, September 14th

1) For the following circuit, determine the voltages at each node. Assume ideal silicon diodes.



Assume all diodes on

$$V2 = 0.7V$$

$$V4 = 0.7V$$

$$V3 = 1.4V$$


Use voltage nodes to solve for V1

$$\left(\frac{V_1 - 10}{1k} \right) + \left(\frac{V_1 - 0.7}{2k} \right) + \left(\frac{V_1 - 1.4}{3k} \right) = 0$$

$$V1 = 5.90 V$$


2) Determine the voltages using PartSim (or similar circuit simulator).

3) (Lab) Build this circuit and check your answers.

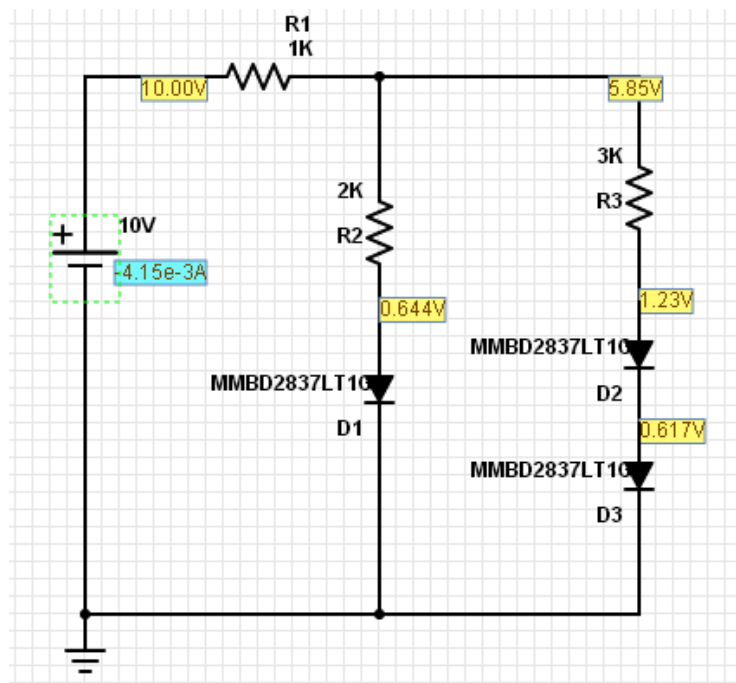

Problem 1-3)

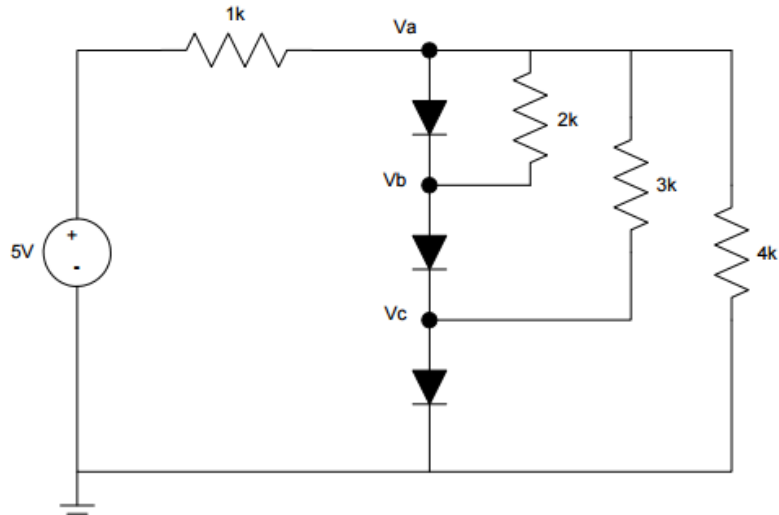4) For the following circuit, determine the voltages at each node. Assume ideal silicon diodes.



Assume the top diode is off, the other two are on

$$V_c = 0.7V$$

$$V_b = 1.4V$$

Solve for V_a

$$\left(\frac{V_a - 5}{1k} \right) + \left(\frac{V_a - 1.4}{2k} \right) + \left(\frac{V_a - 0.7}{3k} \right) + \left(\frac{V_a}{4k} \right) = 0$$

$$V_a = 2.848V$$

Diode 1 is on, so my assumption was off. Try again with all diodes on

$$\mathbf{V_a = 2.1V}$$

$$\mathbf{V_b = 1.4V}$$


$$\mathbf{V_c = 0.7V}$$

Check: the current from V_a to the diode is positive

$$\left(\frac{5 - 2.1}{1k} \right) = I_d + \left(\frac{2.1 - 1.4}{2k} \right) + \left(\frac{2.1 - 0.7}{3k} \right) + \left(\frac{2.1}{4k} \right)$$

$$I_d = 1.558mA > 0mA$$

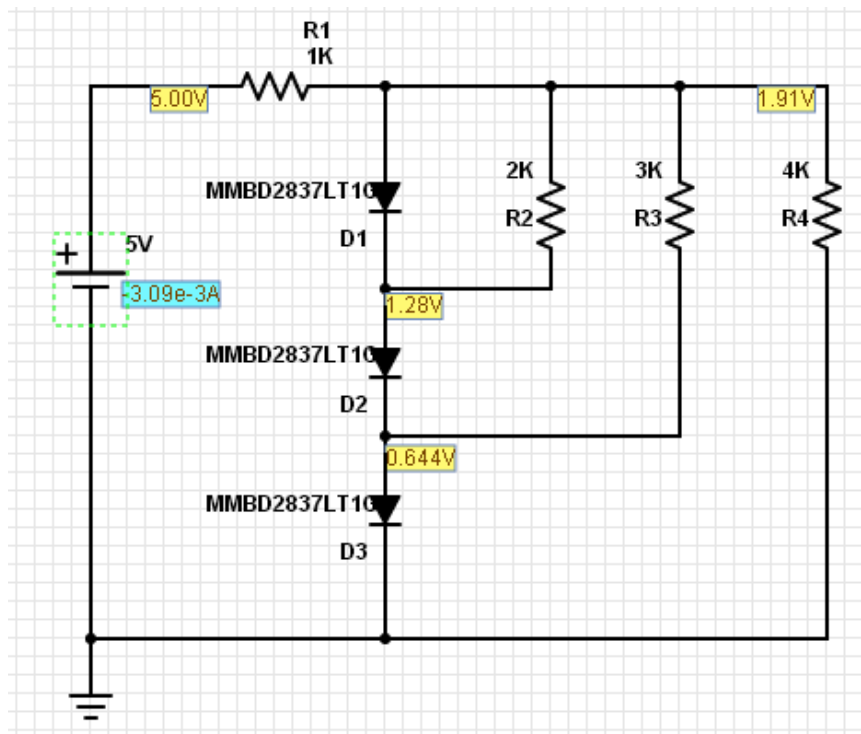5) Determine the voltages using PartSim (or similar circuit simulator).





6) (Lab) Build this circuit and check your answers.

The Piranah RGB LEDs in lab have the followign specifications:

7) Design a circuit to produce yellow light with a 5V source

- Red = 255
- Green = 236
- Blue = 67

	Red	Green	Blue
Vf @ 20mA	2.1	3.6	3.6
mcd @ 20mA	8,000	8,000	8,000
Desired mcd	255	236	67
Desired Current (mA)	0.64	0.59	0.17
R	4,549.02	2,372.88	8,358.21

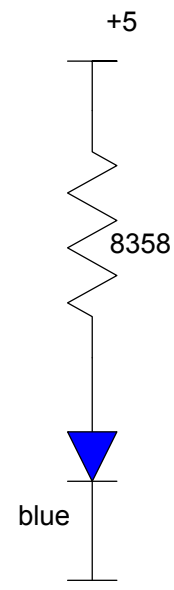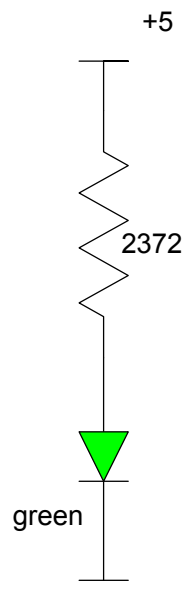

8) Design a circuit to produce NDSU green with a 5V source

- Red = 16
- Green = 64
- Blue = 0

	Red	Green	BlueVf
Vf @ 20mA	2.1	3.6	3.6
mcd @ 20mA	8,000	8,000	8,000
Desired mcd	16	64	0.1
Desired Current (mA)	0.04	0.16	0
R	72,500	8,750	5,600,000

