

# ECE 320 - Homework #6

H-Bridge, DC to AC, SCR. Due Monday, October 5th

1) Design an H-Bridge to drive an 8-Ohms speaker forward and back.

Input:

- 5VDC, capable of driving 3A (i.e. DC power supply on lab bench)
- 0V / 5V TTL signals capable of driving 25mA (i.e. switches on the CADET boards)

Output: 8 Ohm Speaker

Relationship: You should be able to apply +5V, -5V, or 0V across the speaker by adjusting the switches

Note: The transistors in lab are \$0.05 each (vs. \$1.00 for Zetex)

- 3904: NPN,  $\beta > 100$ ,  $I_{cmax} = 200mA$
- 3906: PNP,  $\beta > 100$ ,  $I_{cmax} = 200mA$

Limit the current to 200mA by adding a 0.5W, 20 Ohm resistor in series with the speaker

Calculations:

NPN

$$I_c = \frac{5V}{25\Omega} = 200mA$$

$$\beta I_b > I_c = 200mA$$

$$I_b > 2mA$$

$$R_b < \frac{5V-0.7V}{2mA} = 2150\Omega$$


Let  $R_b = 1k$

PNP: (same as above except)


$$R_b < \frac{4.3V-0V}{2mA} = 2150\Omega$$

Let  $R_b = 1k$

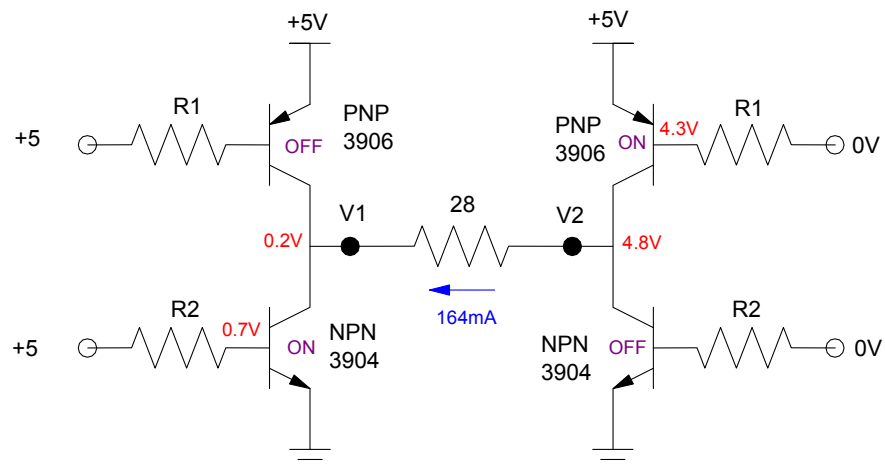
The voltages and currents expected are then as follows:



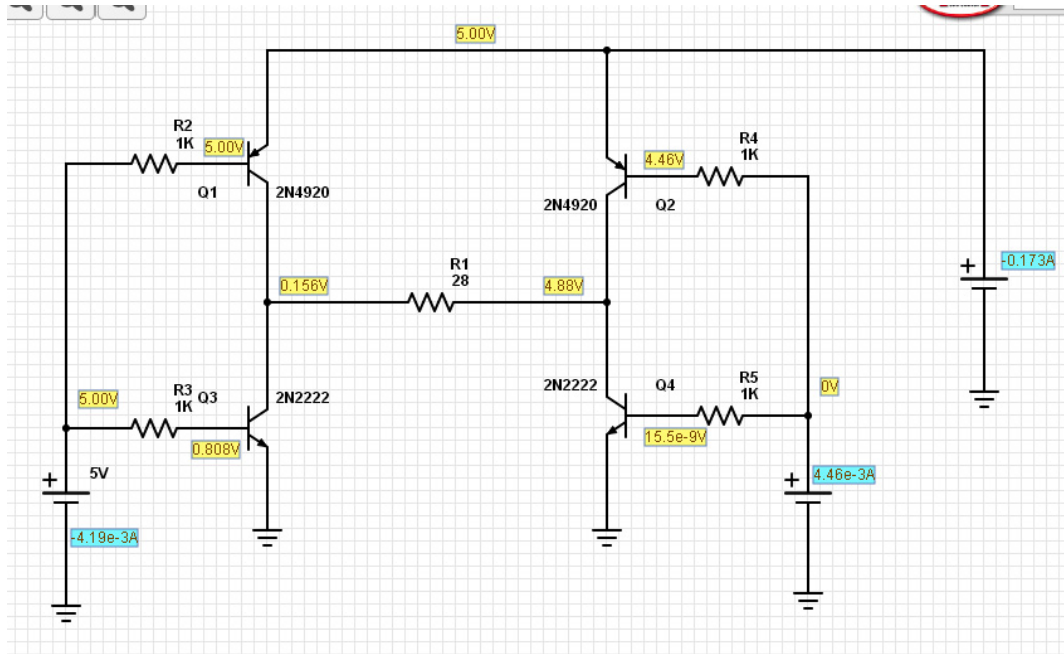2) Check your design in PartSim (three tests: 0V, 5V, -5V)



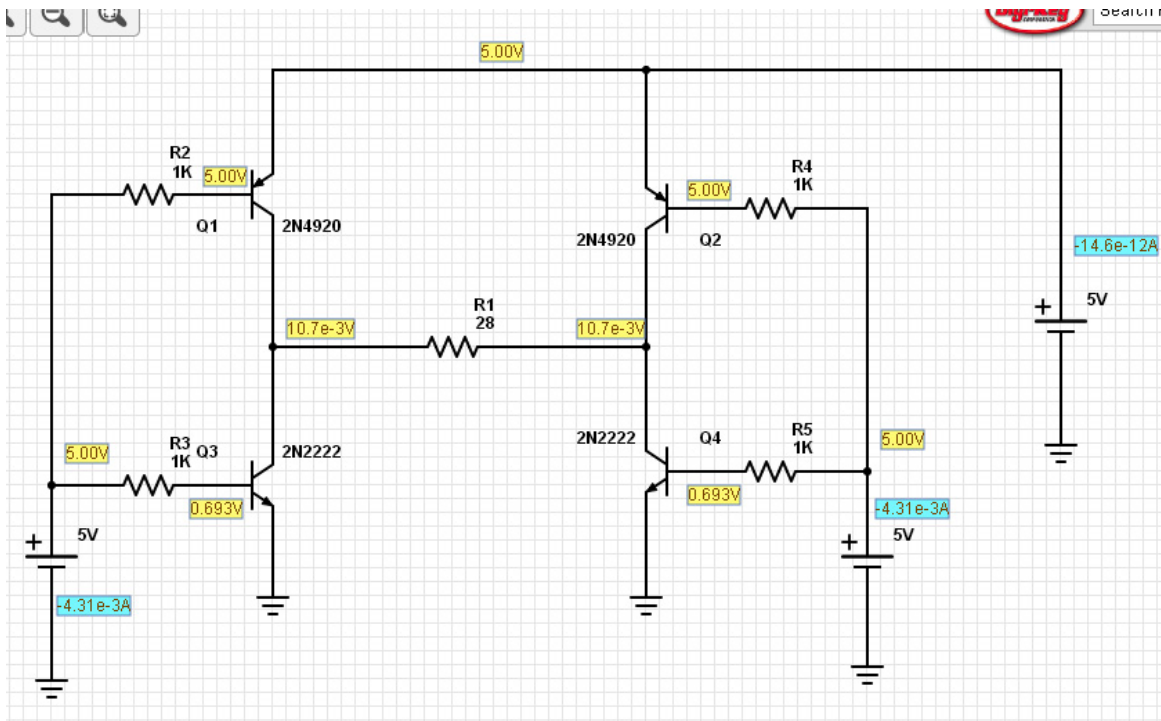Simulated Voltages for +5 (flip left for -5V)




Simulated 0V across speaker

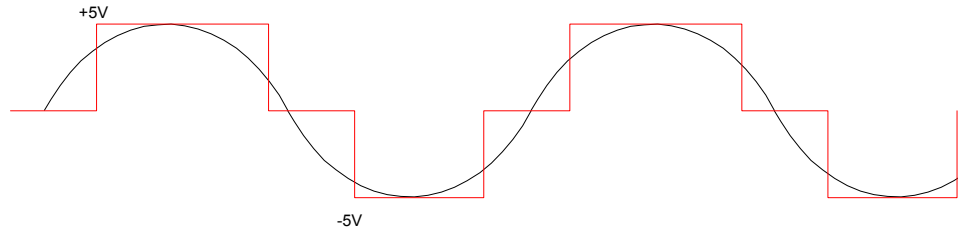3) Assume the H-bridge is to be used to drive an AC motor (BLDC, AC Synchronous, AC Induction motor).

3a) Explain how you convert a DC power supply into an AC voltage


Use an H-Bridge as in problem #1. Switch between +5V and -5V to create an approximate sine wave



3b) Explain how you adjust the speed of the AC motor

Vary the frequency of the sine wave. Frequency = speed

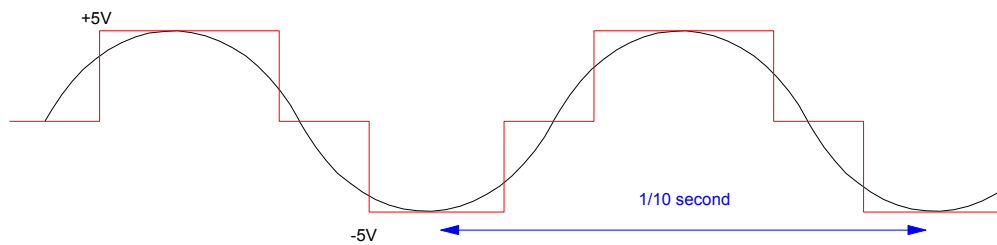3c) Specify the AC waveform you would send to the motor at 10Hz



3d) Calculate the efficiency of your DC to AC converter (MATLAB helps here)

First, input the square wave, Y(t)

```
-->t = [0:0.001:1]';  
-->Y = 5*(t>1/6) .* (t<3/6) - 5*(t>4/6);  
-->plot(t,Y)
```

The DC term is zero:

```
-->DC = mean(Y)  
  
- 0.0049950
```

Compute the 1st harmonic

```
-->w0 = 2*pi;  
  
-->a1 = sum(sin(w0*t) .* Y) / sum( (sin(w0*t)).^2 )  
  
4.7775263  
  
-->b1 = sum(cos(w0*t) .* Y) / sum( (cos(w0*t)).^2 )  
  
- 2.7494819
```

meaning

$$y(t) = 0 + 4.777 \sin(\omega_0 t) - 2.749 \cos(\omega_0 t) + \dots$$

The energy in the total signal vs. the 1st harmonic is:

```
-->y1 = a1*sin(w0*t) + b1*cos(w0*t);  
-->plot(t,y1,'r')
```

```
-->Pin = mean(Y.^2)
```

```
16.658342
```


```
-->Pout = mean(y1.^2)
```

```
15.184579
```

```
-->eff = Pout / Pin
```

```
0.9115301
```

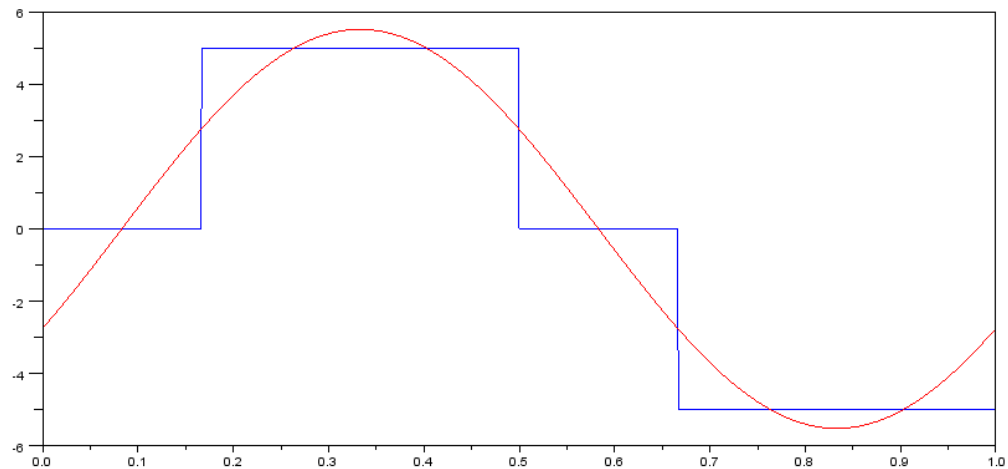The efficiency DC to AC conversion is 91%




Waveform of the signal produced by the H-bridge (blue) and the first term of its Fourier transform

4) Design a full-wave AC to DC converter using diodes and SCRs.

Input: 12V peak, 60Hz, AC signal capable of driving 1A

Output: 4.9V .. 5.1V DC signal, capable of driving 100mA

Tolerance: Output ripple < 200mV @ 100mA

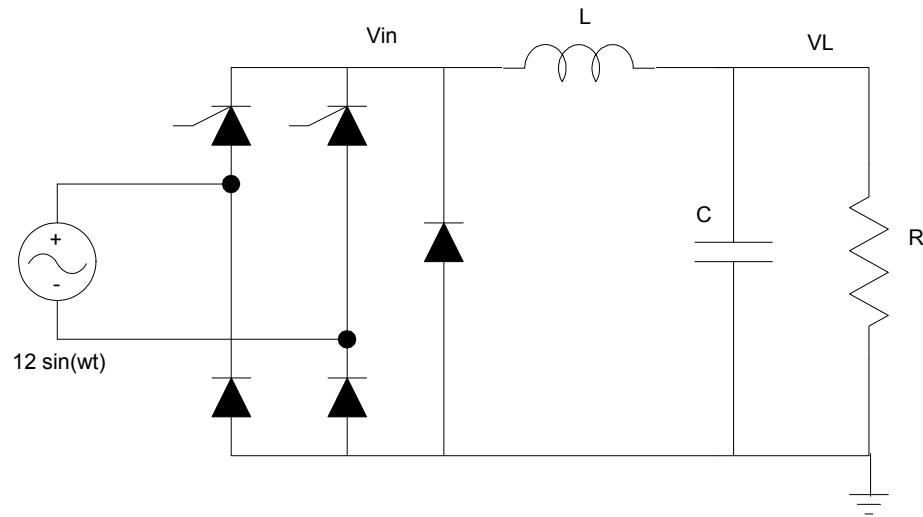

Assume the turn-on time is 'a'. If the AC signal is 10.6V peak and the average is to be 5V, then

$$5 = \frac{1}{\pi} \int_a^{\pi} 10.6 \sin(t) dt$$

$$0.4717 = \frac{1}{\pi} \int_a^{\pi} \sin(t) dt$$

$$1.4819 = -\cos(t) \Big|_a^{\pi}$$

$$1.4819 = 1 + \cos(a)$$

$$a = 61.19^\circ$$


Checking in MATLAB:

```
-->t = [0:0.001:1]';
-->w0 = 2*pi;
-->y = abs(10.6*sin(w0*t));
```

```
-->y1 = y;
-->y1(1:170) = 0;
-->y1(500:670) = 0;
-->mean(y1)
```

4.994485

```
-->plot(t,y1);
```

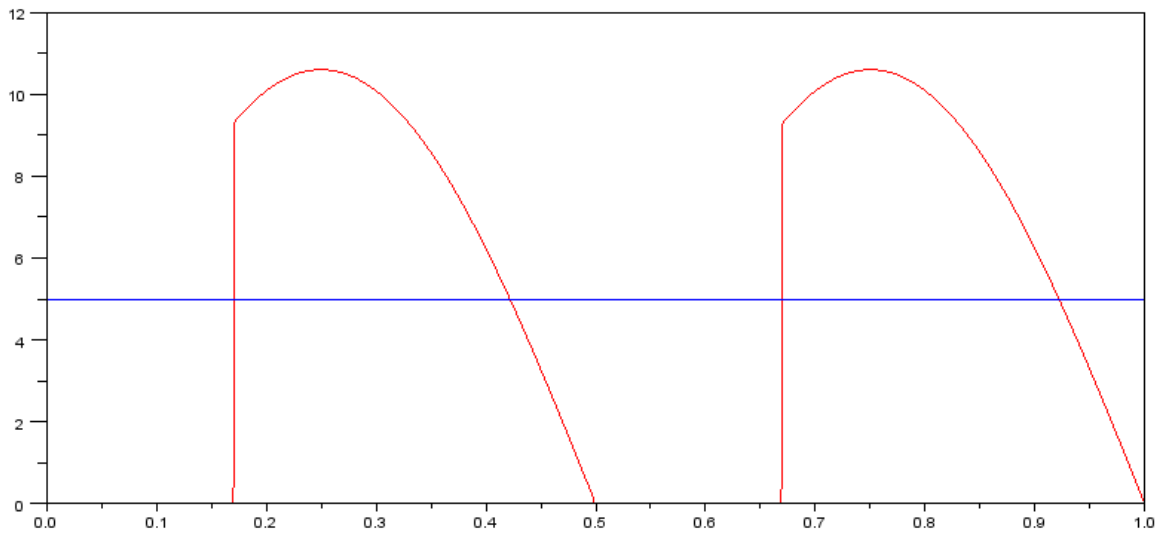

Finding R:

For 100mA at the load

$$R = \frac{5V}{100mA} = 50\Omega$$

To keep the ripple less than 200mVpp

$$V_{in} \approx 5 + 10.6V_{pp}\sin(2\omega_0 t)$$

The DC term goes to the load unchanged (L and C have no effect at DC)

The AC term has an input of 10.6Vpp @ 120Hz

The output by voltage division is

$$V_o = \left( \frac{R \parallel \frac{1}{j\omega C}}{R \parallel \frac{1}{j\omega C} + j\omega L} \right) 10.6V_{pp}$$

If C = 0

$$0.2V_{pp} = \left( \frac{50\Omega}{50\Omega + j\omega L} \right) 10.6V_{pp}$$

$$L = 3.51H$$

If L = 1H

$$C = 93\mu F$$

Checking: In MATLAB, using the code from before for Vin:

```
IL = 0.1;
VC = 5;
```

```

L = 1;
C = 93e-6;
R = 50;

dt = 1/60 / 1000;

for n=1:1000
Vc = Vo(1000);
for i=1:1000

    dIL = (Vin(i) - Vc) / L;
    dVc = (IL - Vc/R) / C;


    IL = IL + dIL*dt;
    Vc = Vc + dVc*dt;

    Vo(i+1) = Vc;

end
end

plot(t,Vo);

```

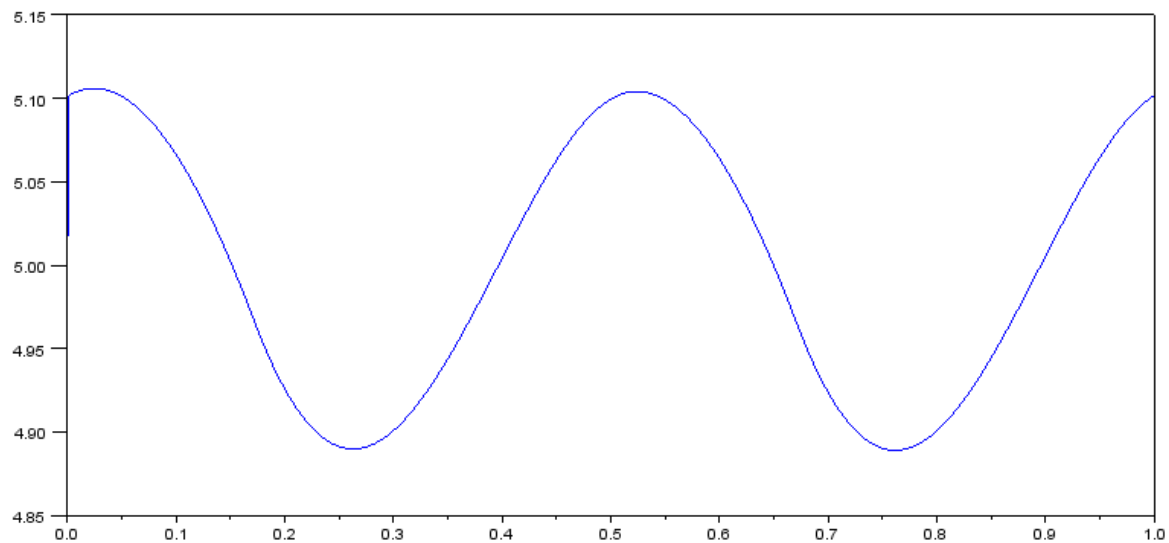

Computed Value of VL with Ideal Diodes after 166 Seconds.  $L = 1H$ ,  $C = 93\mu F$

Lab:

5) Build the H-bridge and verify your computations for problem 1.