

ECE 320 - Homework #8

TTL Logic, MOSFET theory, MOSFET switch. Due Monday, October 19th

The following circuit implements a function using TTL logic

Assume

- $\beta = 100$ (NPN used correctly)
- $\beta = 0.1$ (NPN used in reverse)


1) What is the logic for this circuit?

$$Y = AB$$

The first stage is a NAND gate, the second stage is an inverter.


2) Determine the voltages and currents for

$$A = B = 5V$$

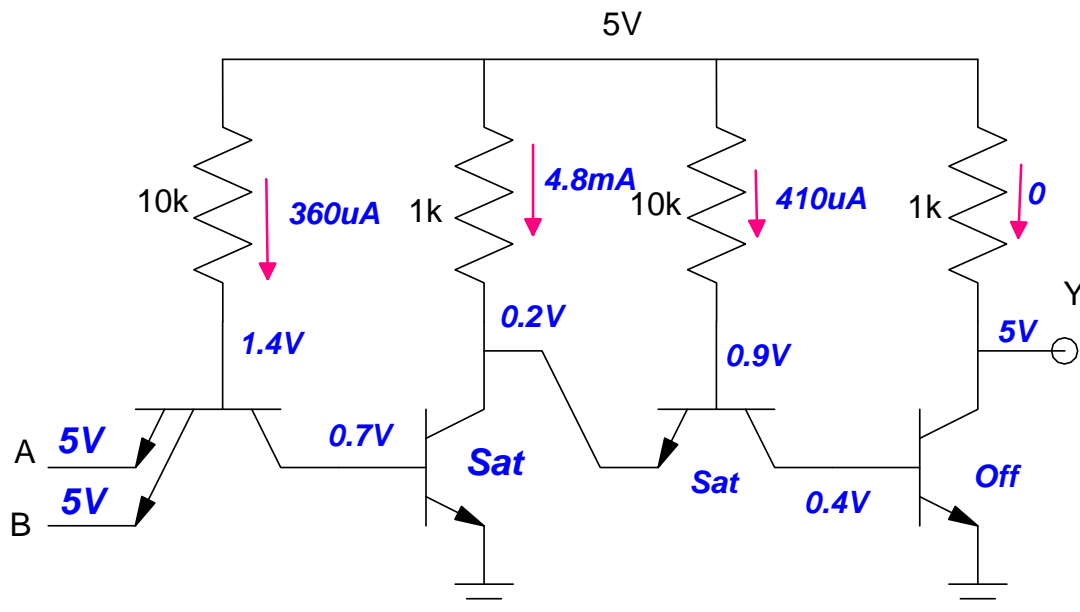

3) Determine the voltages and currents for

$$A = B = 0V$$

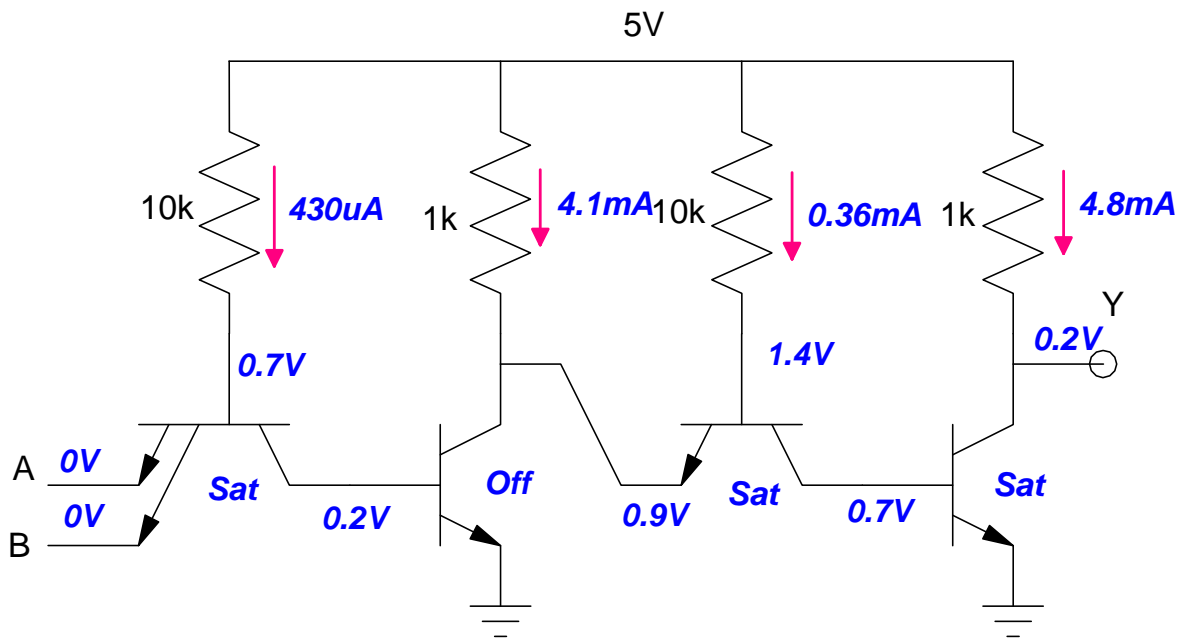

Assume the VI characteristics for a MOSFET are as follows.

4) Label the Off / Saturated / Ohmic regions on this figure

5) Determine the constant k_n for this MOSFET

The current goes to zero at $V_{gs} = 1.0V$


$$V_{tn} = 1.0V$$

Pick a point: $V_{gs} = 5.5V$, $I_{ds} = 200mA$

$$I_{DS} = \frac{k_n}{2}(V_{gs} - V_{tn})^2$$


$$0.2A = \frac{k_n}{2}(5.5V - 1.0V)^2$$

$$k_n = 0.02$$

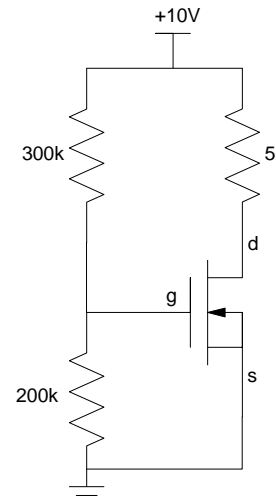

6) Draw the load line and determine the operating point if connected as shown to the right:

$$V_{ds} = 5.5V, I_{ds} = 90mA$$

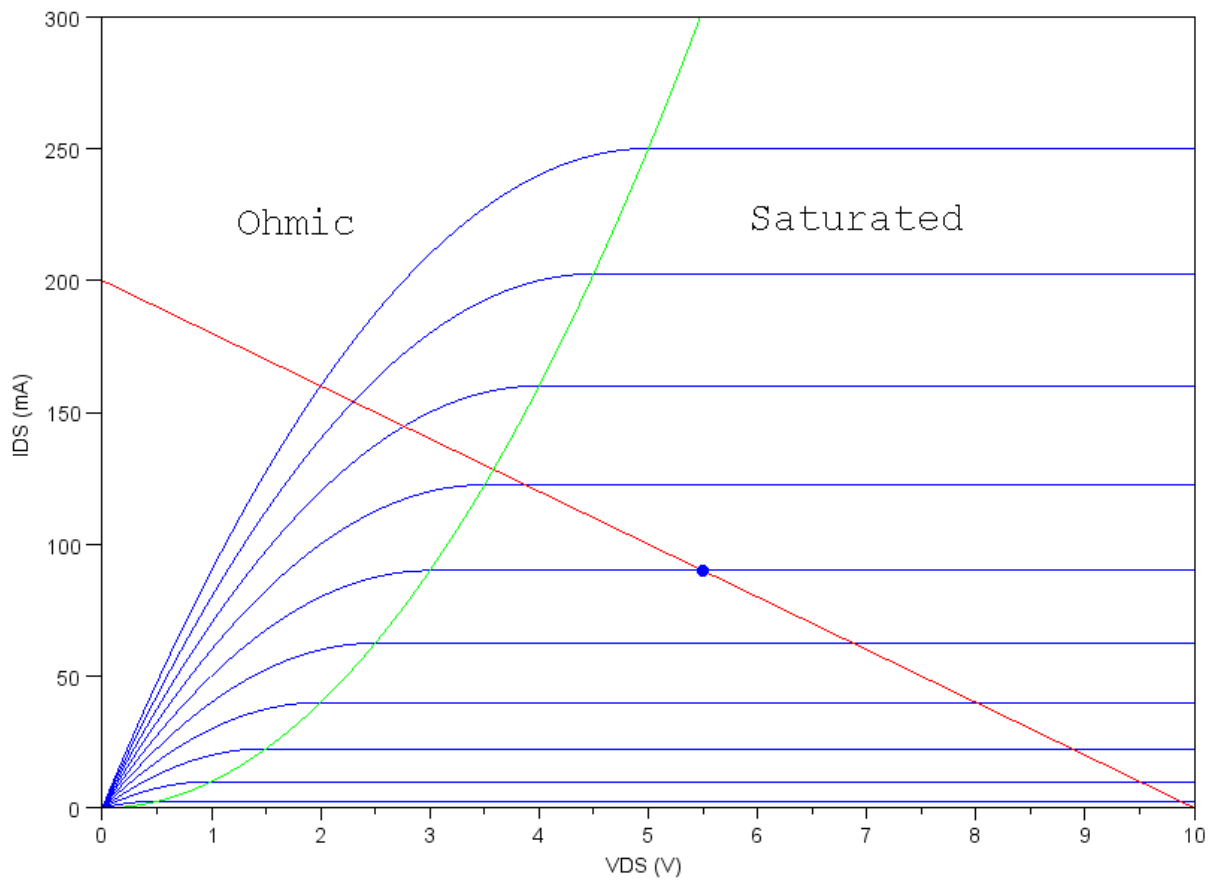

Lab: (term project)

Take one section of your term project.

- 7) Requirements: Specify what your circuit is going to do
 - Inputs
 - Outputs
 - Relationship
- 8) Analysis. Calculations for voltages, currents, resistors, capacitors, etc
- 9) Test: Check your analysis in simulation.
- 10) Validation: Build your circuit and check that it meets the requirements.