

# ECE 320 - Homework #9

CMOS Logic, Op-Amps, Schmitt Triggers. Due Monday, October 26th

Assume an n-channel MOSFET with the following characteristics:

- $V_t = 2V$
- $R_{ds} = 1 \text{ Ohm @ } V_{gs} = 10V \text{ @ } I_{ds} = 100mA$

and a corresponding p-channel MOSFET with

- $V_t = -2V$
- $R_{ds} = 1 \text{ Ohm @ } V_{gs} = -10V \text{ @ } I_{ds} = 100mA$

1) Determine the constant  $K_n$

In the Ohmic region

$$I_{ds} = k_n \left( V_{gs} - V_t - \frac{V_{ds}}{2} \right) V_{ds}$$

Plugging in numbers

$$100mA = k_n \left( 10V - 2V - \frac{(100mA)(1\Omega)}{2} \right) (100mA)(1\Omega)$$

$$k_n = 0.1258$$

2) Determine the resistance when  $V_{gs} = 5V$ . Assume  $I_{ds} = 100mA$  (same as before)

$$100mA = 0.1258 \left( 5V - 2V - \frac{V_{ds}}{2} \right) V_{ds}$$

$$V_{ds} = 0.2778V$$

and the resistance is

$$R_{ds} = \frac{V_{ds}}{I_{ds}} = 2.778\Omega$$

3) Design a CMOS gate to impliment


$$Y = AB + C$$

On the high-side, the output is pulled high if p-channel MOSFET C or A and B are on. Since 0V turns on the MOSFET, feed these with signals A' B' and C'


On the low-side, use DeMorgan's theorem

$$\bar{Y} = \bar{C}(\bar{A} + \bar{B})$$

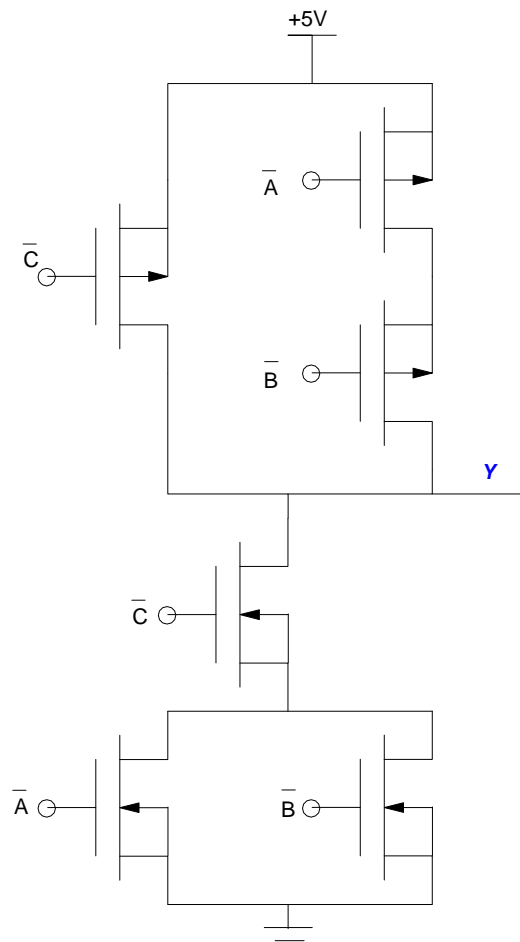The output is pulled low if the n-channel MOSFET is turned on



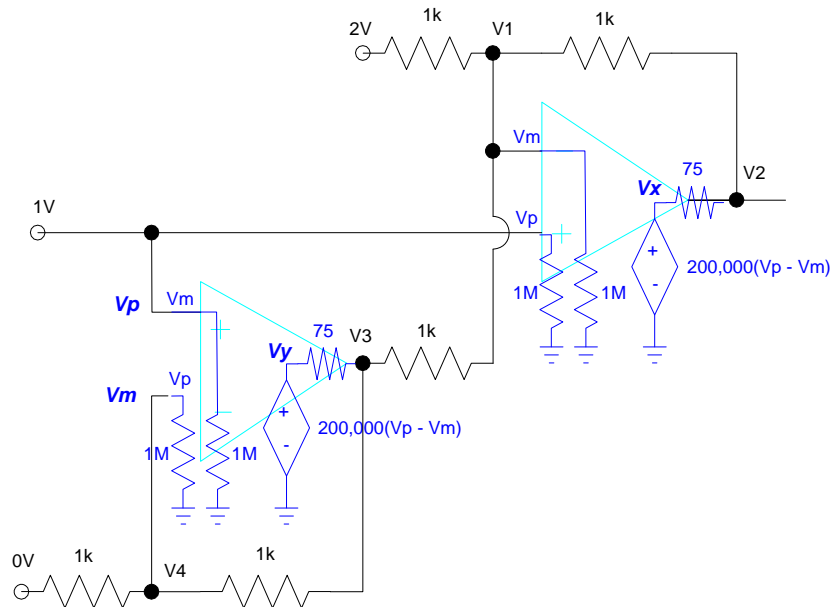4) Write the voltage node equations for the following op-amp circuit.



$$\left( \frac{V_1 - 2V}{1k} \right) + \left( \frac{V_1 - V_2}{1k} \right) + \left( \frac{V_1}{1M} \right) + \left( \frac{V_1 - V_3}{1k} \right) = 0$$

$$\left( \frac{V_2 - V_x}{75} \right) + \left( \frac{V_2 - V_1}{1k} \right) = 0$$


$$V_x = 200,000(1 - V_1)$$

$$\left( \frac{V_3 - V_y}{75} \right) + \left( \frac{V_3 - V_1}{1k} \right) + \left( \frac{V_3 - V_4}{1k} \right) = 0$$

$$V_y = 200,000(1 - V_4)$$

$$\left( \frac{V_4 - 0}{1k} \right) + \left( \frac{V_4}{1M} \right) + \left( \frac{V_4 - V_3}{1k} \right) = 0$$

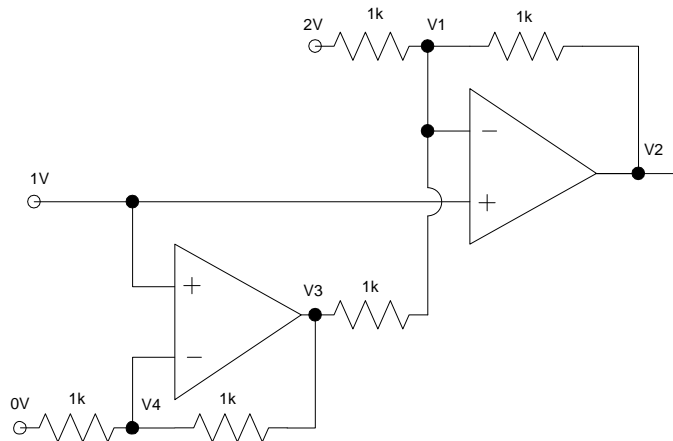5) Assume ideal op-amps. Write the voltage node equations for the following op-amp circuit (same as problem 4 but with ideal op-amps)



Start with the equations at V2 and V4: ( $V_p = V_m$ )

$$V_1 = 1V$$

$$V_4 = 1V$$


Add in two more equations

$$\left(\frac{V_4}{1k}\right) + \left(\frac{V_4 - V_3}{1k}\right) = 0$$

$$\left(\frac{V_1 - 2}{1k}\right) + \left(\frac{V_1 - V_2}{1k}\right) + \left(\frac{V_1 - V_3}{1k}\right) = 0$$


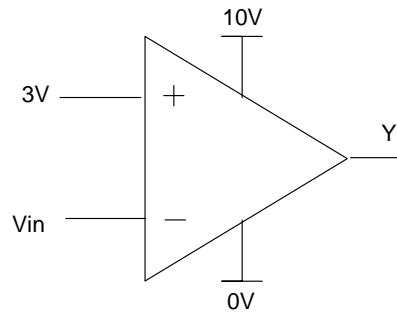
6) Comparitor: Design a circuit which outputs

- 10V for  $V_{in} < 3V$
- 0V for  $V_{in} > 3V$



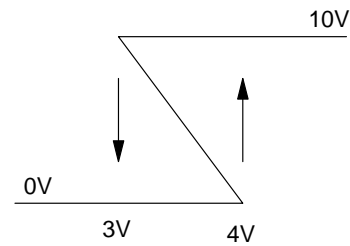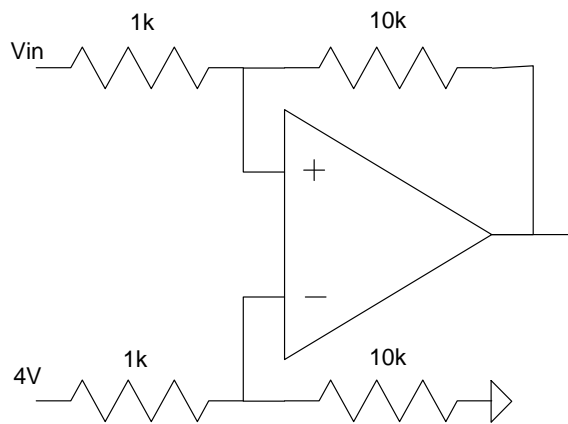7) Schmitt Trigger: Design a circuit which outputs

- 10V when  $V_{in} > 4V$
- 0V when  $V_{in} < 3V$
- No change for  $3V < V_{in} < 4V$



8) Schmitt Trigger: Design a circuit for a night-light which outputs

- 0V when the light level is more than 10 Lux and
- 10V when the light level is less than 7 Lux

Assume a light sensor with  $R = \frac{100,000}{Lux} \Omega$

Assume a 10k resistor for the voltage divider

10 Lux: (0V)

$$R = 10,000 \text{ Ohms}$$

$$V_a = 5V$$



7 Lux: (10V)

$$R = 14,258 \text{ Ohms}$$

$$V_a = 5.8824V$$

Gain
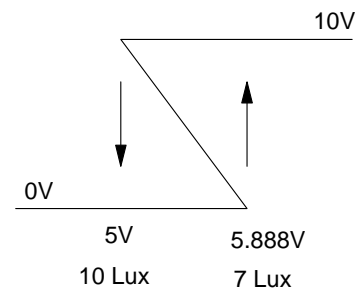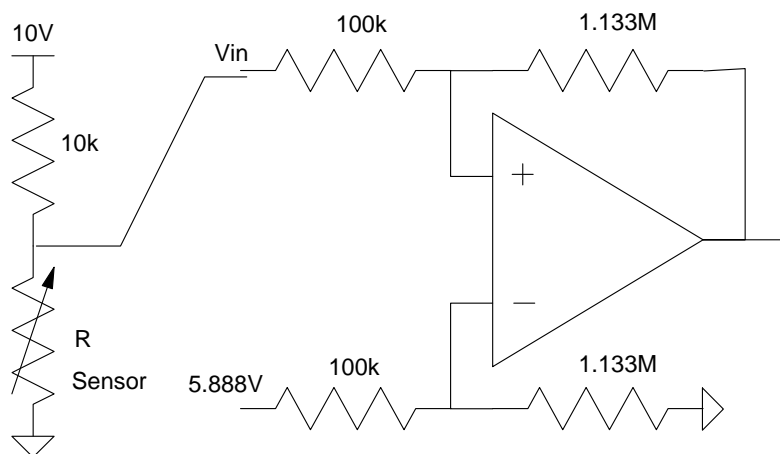
$$Gain = \left( \frac{10V - 0V}{5.8824V - 5V} \right) = 11.33$$



## **Lab: (term project)**

Take one section of your term project.

- 7) Requirements: Specify what your circuit is going to do
  - Inputs
  - Outputs
  - Relationship
- 8) Analysis. Calculations for voltages, currents, resistors, capacitors, etc
- 9) Test: Check your analysis in simulation.
- 10) Validation: Build your circuit and check that it meets the requirements.