

ECE 320: Final - Part 1. Name _____

Semiconductors & Diodes - October 24, 2016

- 1a) Define the following terms:

p-type semiconductor

$$\# \text{holes} \gg \# e^-$$

n-type semiconductor

$$\# e^- \gg \# \text{holes}$$

intrinsic silicon



$$\# e^- \approx \# \text{holes}$$

- 1b) Why does the resistance of silicon decrease as temperature increases?

electrons gain enough energy to break their covalent bonds, creating free e^- and holes.

2) The VI characteristics for an LED is shown below. Draw the load line for the following circuit and determine the operating point.

Load Line	Vd	Id
show on graph	2.2V	65mA

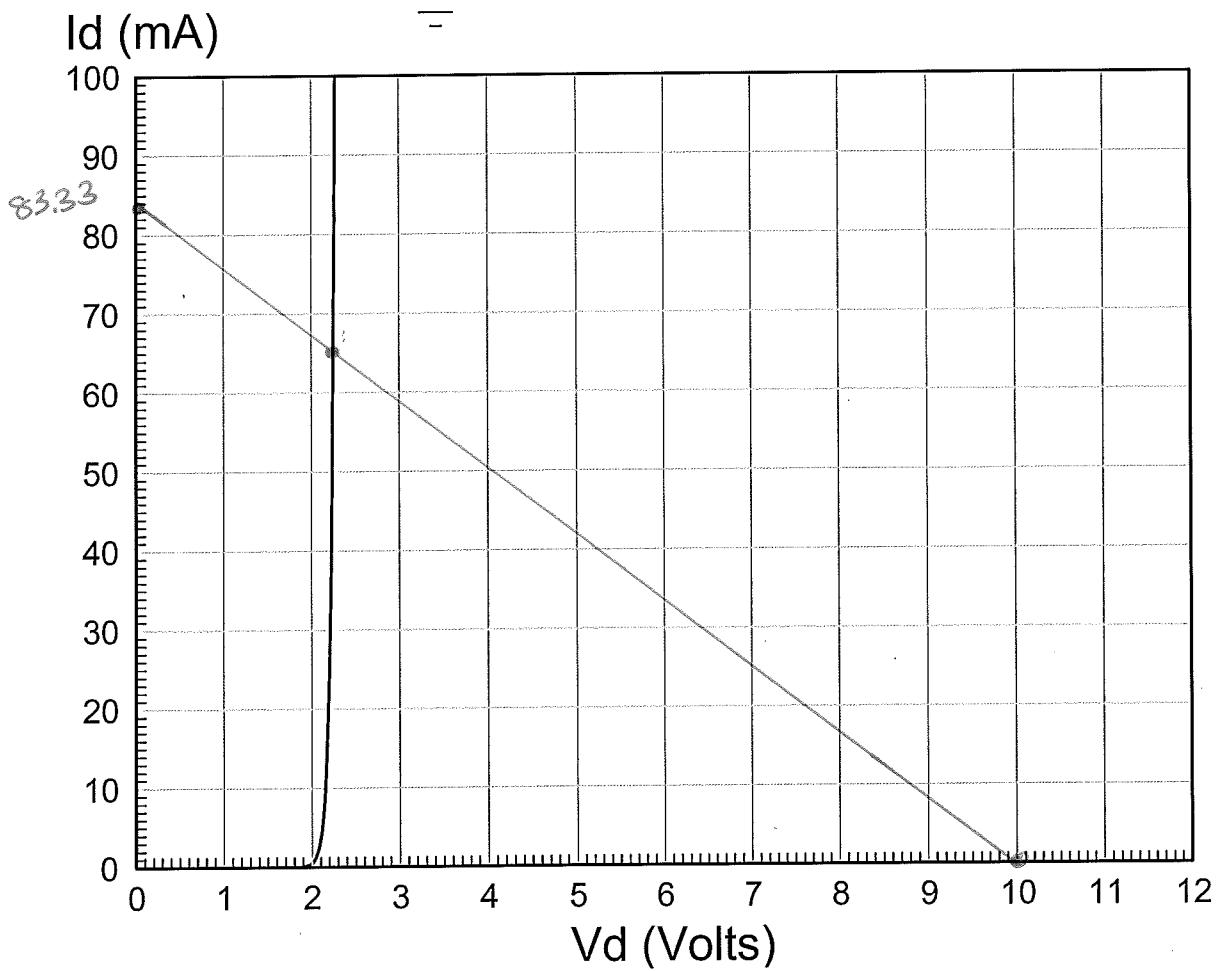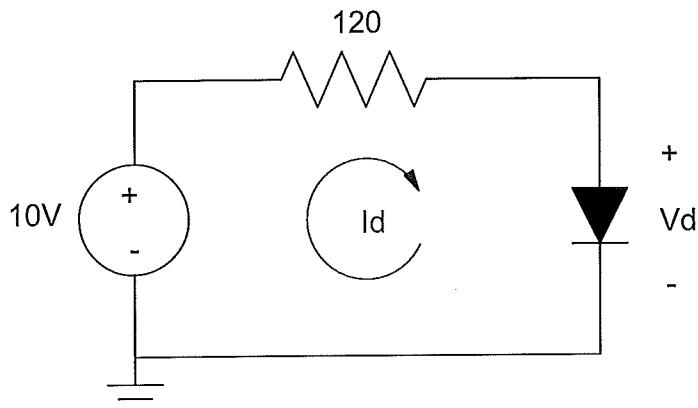

3) Assume ideal silicon diodes ($V_f = 0.7V$). Determine the currents, I1 - I4


I1	I2	I3	I4
20.93 mA	0	4.64 mA	16.29 mA

19.75 mA

-8.25 mA

3.7 mA

21 mA

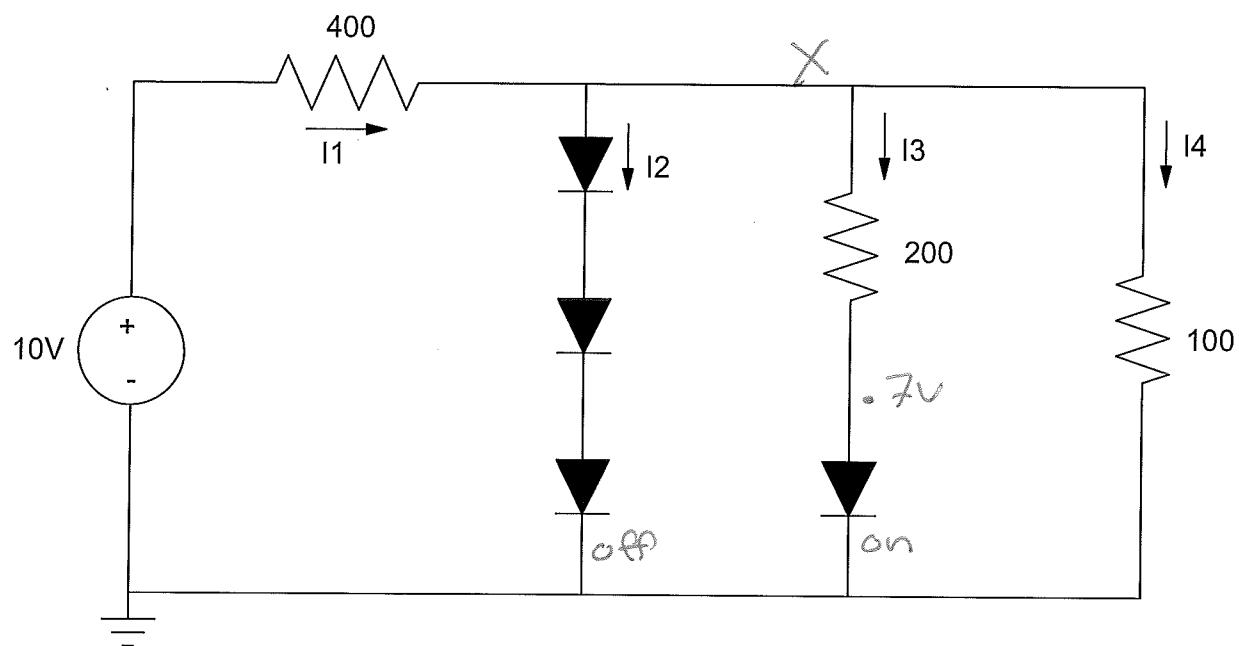


$$\frac{X-10}{400} + \frac{X-0.7}{200} + \frac{X}{100} = 0$$

$$X = 1.6286$$


4) Assume ideal silicon diodes ($V_f = 0.7V$). Determine the currents, I_1 - I_4

I_1	I_2	I_3	I_4
0	4.9mA	$.4\text{mA}$	0

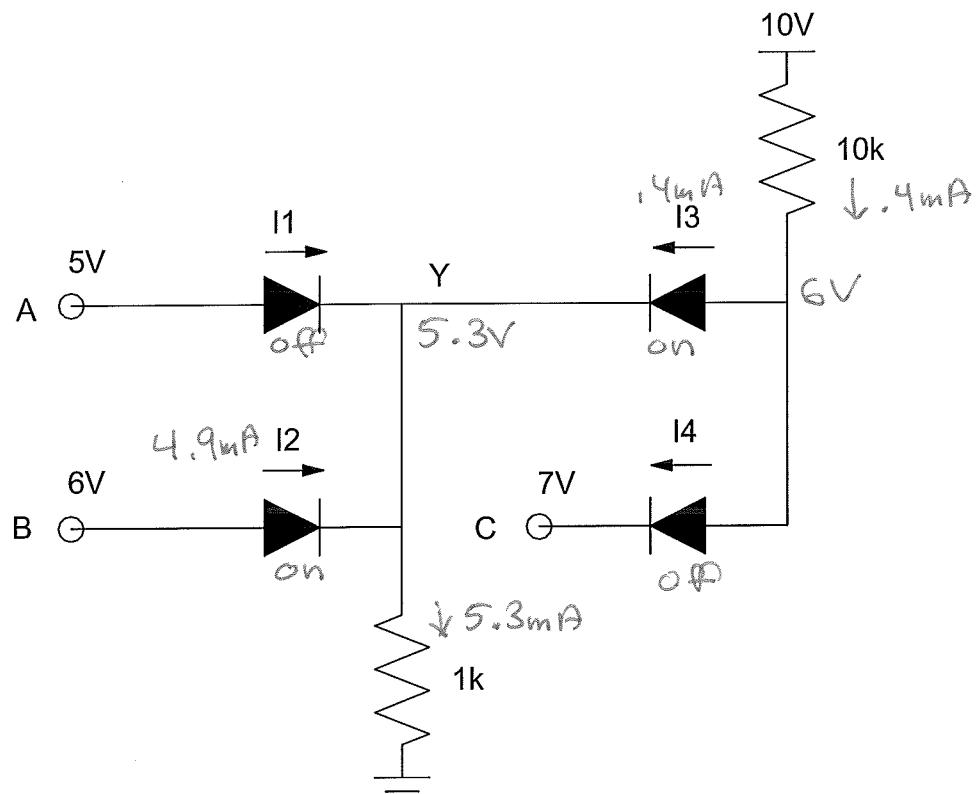

5) For the following AC to DC converter, determine the following

The DC voltage at V_1 $\frac{1}{\pi} \int_0^{\pi} 13.6 \sin(t) \cdot dt$	V_{1pp} The peak-to-peak ripple at V_1 :	V_{2pp} if $C = 0$	V_{2pp} if $C = 50\mu F$
8.658V	13.6V _{pp}	2.58V _{pp}	.683V _{pp}

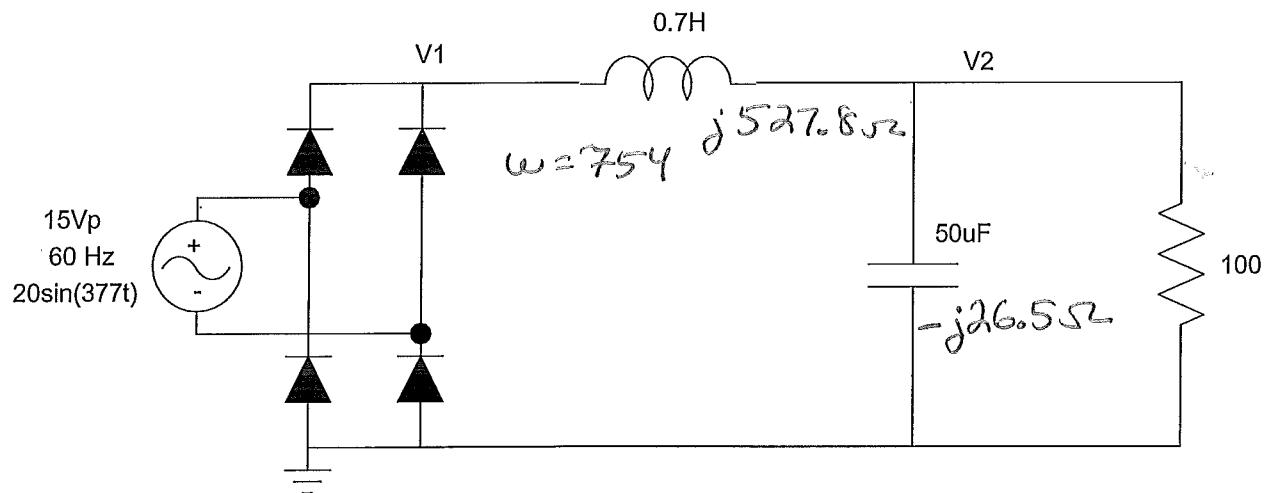


$$\frac{13.6}{\pi} \left(-\cos(t) \right) \Big|_0^\pi = \frac{2}{\pi} \cdot 13.6V = 8.658V$$

$$\left(\frac{10\Omega}{527.8} \right) 13.6 = 2.58$$

$$\left(\frac{26.5}{100} \right) 2.58 = .683$$

Bonus (Part 1): How many people voted in the 2012 Presidential Election in North Dakota?

312,076


 


ECE 320: Final - Part 2. Name Key

BJT Transistors & MOSFET Circuits - October 26, 2016

- 1) Draw the load line for the following circuit. Compute and show on the load line I_b , I_c , and V_{ce} if $\beta = 100$.

Load Line	I_b	I_c	V_{ce}
on graph	565 μA	56.5 μA	3.52 V

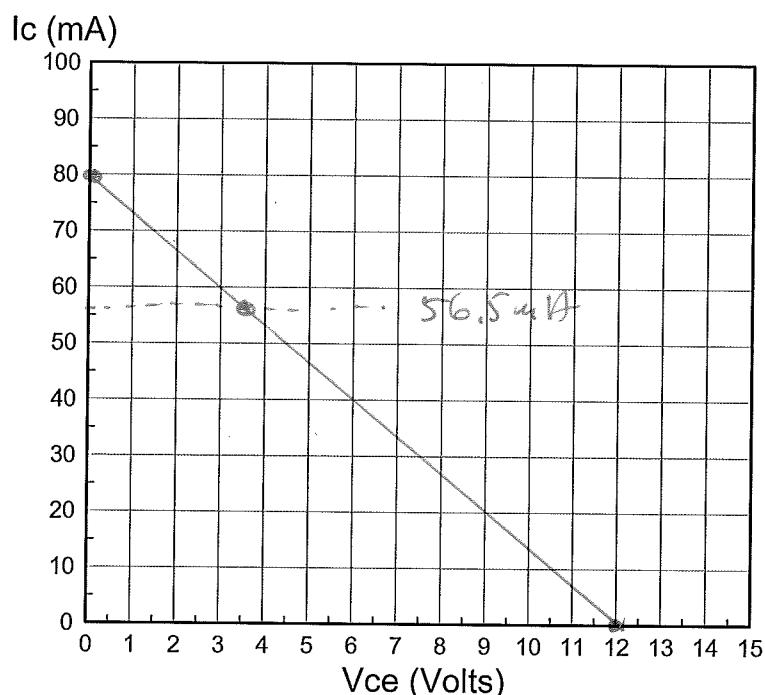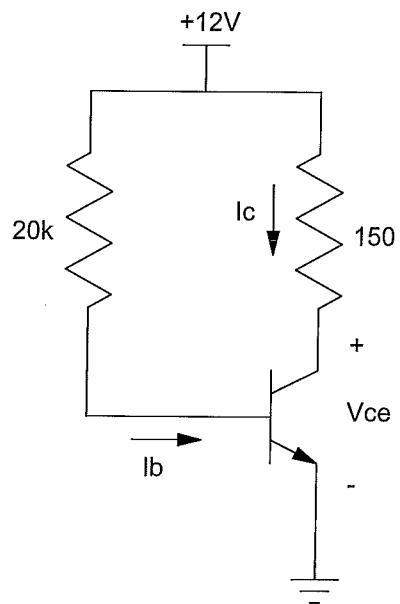


$$I_b = \frac{(R_f - 7)}{20k} = 565 \mu A$$

$$\beta I_b = 56.5 \mu A$$

2) Determine the voltages for the following DTL logic gate. Assume $\beta = 100$

V1	V2	V3	V4
1.4V	0.2V	0.9V	9.09V

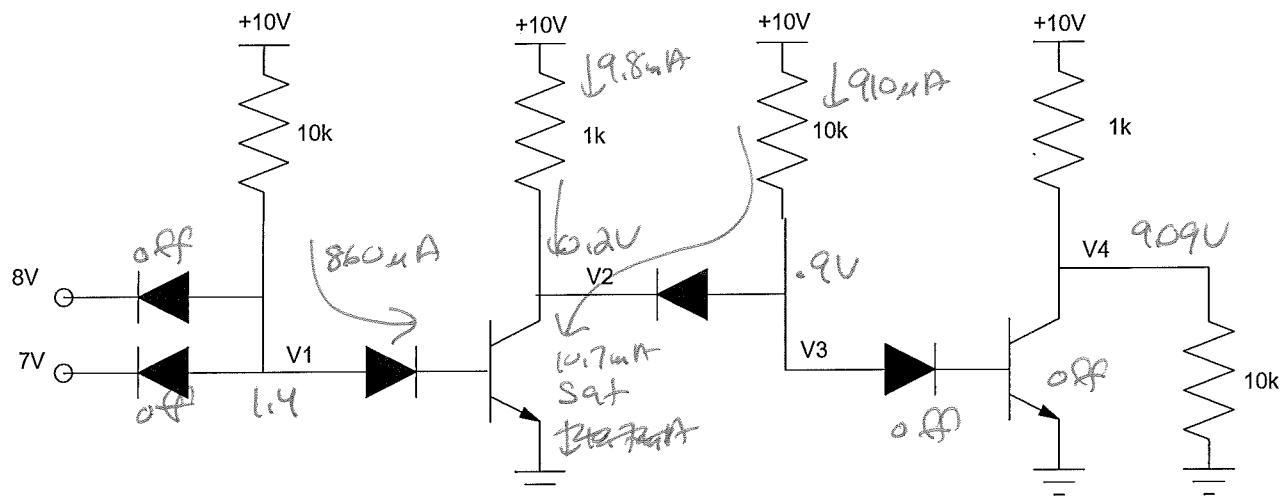

$$\beta I_b = 86 \mu A$$

$$I_c = 10.7 \mu A$$

$$\beta I_b > I_c$$

3) Design a Schmitt Trigger which outputs

- +10V when $R > 6k$ Ohms
- 0V when $R < 4k$ Ohms, and
- Is unchanged for $4k < R < 6k$

