## ECE 320 - Homework #1

Matlab, PartSim, Solving f(x) = 0. Due Monday, August 29th

1) Given 2 equations with 2 unknowns

$$V = 10 - 1000I$$

$$V = 0.052 \cdot \ln{(10^7 \cdot I + 1)}$$

- 1a) Solve in Matlab using graphical methods
- 1b) Solve numerically to find V and I
- 2) Given 2 equations with 2 unknowns

$$V = 10 - 1000I$$

$$I = 0.1 \cdot (V - 2)^2$$

- 2a) Solve in Matlab using graphical methods
- 2b) Solve numerically to find V and I
- 3) Solve using *fminsearch()* in Matlab

$$\left(\frac{V_{1}-10}{100}\right) + \left(\frac{V_{1}-V_{2}}{200}\right) + \left(\frac{V_{1}}{300}\right) + I_{d1} = 0$$
$$I_{d1} + \left(\frac{V_{1}-V_{2}}{200}\right) = I_{d2}$$
$$I_{d1} = 10^{-7} \cdot (e^{20(V_{1}-V_{2})} - 1)$$
$$I_{d2} = 10^{-7} \cdot (e^{20V_{2}} - 1)$$

4) Input this circuit into PartSim to solve for the node votlages

